


# LECTURE #14

- AIM :
- understand number representation,
  - overflow
  - addition/subtraction circuits
  - address ; fast address : carry lookahead adder

## I. Twos Complement numbers :

- the most widely used number system

(for 4-bit numbers  
 $n=4$ )

 

called the "sign bit"

positive/negative number boundary

number wheel

We form two's complement to represent negative numbers as follows:

Ex] +3: 0011

① Take ones complement:

1100

② Add 1: 1

1101

---

Subtraction:

$$+5 - 3 = \underbrace{(+5)}_{0101} + \underbrace{(-3)}_{1101}$$

$$\begin{array}{r} 0101 \\ 1101 \\ \hline \cancel{X}0010 \end{array} \equiv +2 \quad \checkmark$$

↓  
ignore.

① Note that the last stage had a carry-out but this did not indicate overflow!

② Number wheel interpretation: We start at +5, go back 3 steps to arrive at +2,

Overflow <sup>def</sup>  $\equiv$  An overflow occurs in an operation iff the resulting number has no representation in the number system.

• In case of addition and subtraction of two complement n-bit numbers, an overflow occurs iff:


| Operation | A   | B   | Result (n-bit) |
|-----------|-----|-----|----------------|
| A + B     | > 0 | > 0 | < 0            |
| A + B     | < 0 | < 0 | > 0            |
| A - B     | > 0 | < 0 | < 0            |
| A - B     | < 0 | > 0 | > 0            |

- Number wheel interpretation: overflow occurs when you have crossed the boundary shown.

• Detecting overflow: <sup>positive/negative</sup>

- when we build adders, it is good to build overflow detection circuitry to flag us when we have a bogus result.

 
Claim: An overflow in two's complement  $n$ -bit addition/subtraction occurs iff the carry-in of the last stage is  $\neq$  carry-out of the last stage.



PROOF: need to consider only addition (since  $A - B = A + (-B)$ ).

We know that overflow occurs iff

|                  | A  | + | B  | Result: |
|------------------|----|---|----|---------|
| <u>case #1</u> : | >0 |   | >0 | <0, or  |
| <u>case #2</u> : | <0 |   | <0 | >0.     |

 

↑ (negative)  
will get a 1 here iff there is a carry-in to the last stage  
and in this case there will be no carry-out.

case #3:


|   |  |   |
|---|--|---|
| 1 |  | 1 |
| 1 |  | 0 |
| 0 |  |   |

happens iff ∃ no carry-in to the last stage  
(and note that there is no carry-out)


This shows that overflow condition  $\Rightarrow$   
 $\text{carry-in} \neq \text{carry-out}$  in last stage.

- Now, let's show the reverse:

 If  $\text{carry-in} \neq \text{carry-out}$ ; Then:




Hence: need

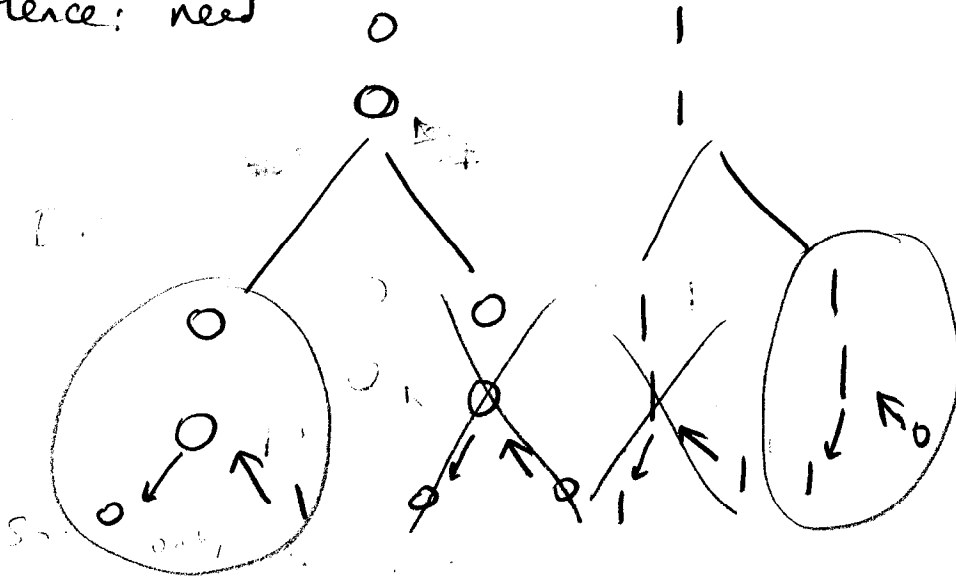

Q.E.D

### Networks for Binary Addition/subtraction


interface  
 schematic:

 



Generate:

 
- At the  $i$ th stage of addition, a carry-out is generated by the  $i$ th stage iff  $A_i = B_i = 1$ .



generates a carry-out of 1 no matter what the carry-in to the  $i$ th stage is.

We write:  $G_i = A_i \cdot B_i$

 - Propagate: The  $i$ th stage will propagate the carry-in iff  $A_i$  and  $B_i$  are different.



We write:  $P_i = A_i \oplus B_i$

---

Now, let's write the sum:  $(S_i)$  and  $C_{i+1}$  (carry-out of stage  $i$ ) in terms of  $P_i, G_i$ 's.

Sum, (st...)

$$S_0 = (A_0 \oplus B_0) \oplus C_0$$

$$= P_0 \oplus C_0$$

$$S_1 = A_1 \oplus B_1 \oplus C_1$$

$$= P_1 \oplus C_1$$

$$S_i = P_i \oplus C_i$$

Carryout:

$$C_1 = A_0 B_0 + C_0 (A_0 \oplus B_0)$$

$$C_{i+1} = A_i B_i + C_i (A_i \oplus B_i)$$

$$C_{i+1} = G_i + C_i P_i$$

∴ The carry out will be 1 iff either a carryout is generated in that stage OR there is a carry-in to that <sup>stage</sup> and it is propagated.



Explicitly, for the first four stages:


$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1(G_0 + P_0 C_0) \\ = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

$$C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 \\ + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

 - The main idea is that the propagate and generate can be computed based on  $A_i, B_i$  with only 1 gate delay. ( $G_i = A_i \cdot B_i$ ,  $P_i = A_i \oplus B_i$ ). So, after a 1-unit gate delay,  $\{P_i, G_i\}$  are all available regardless of the  $n$  (# of stages)



Precompute  $P_i$  and  $G_i$ ; then wait for  $C_i$ .

After  $C_i$  arrives then  $S_i$  will be available 1 gate delay after that.

- The carry's create the critical path.

The 2-stage computation reduces the time to obtain the carryout

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0$$


if up-to fan-in of 5 has delay  $\frac{1}{2}$  unit

$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

$$C_4 = G_3 + P_3 G_2 + \dots + P_3 P_2 P_1 P_0 C_0$$

- But this constant time ( $\textcircled{3}$ ) for carryout cannot be maintained because fan-in is getting larger. ( $\textcircled{4}$  for sum)
- And hardware is getting large

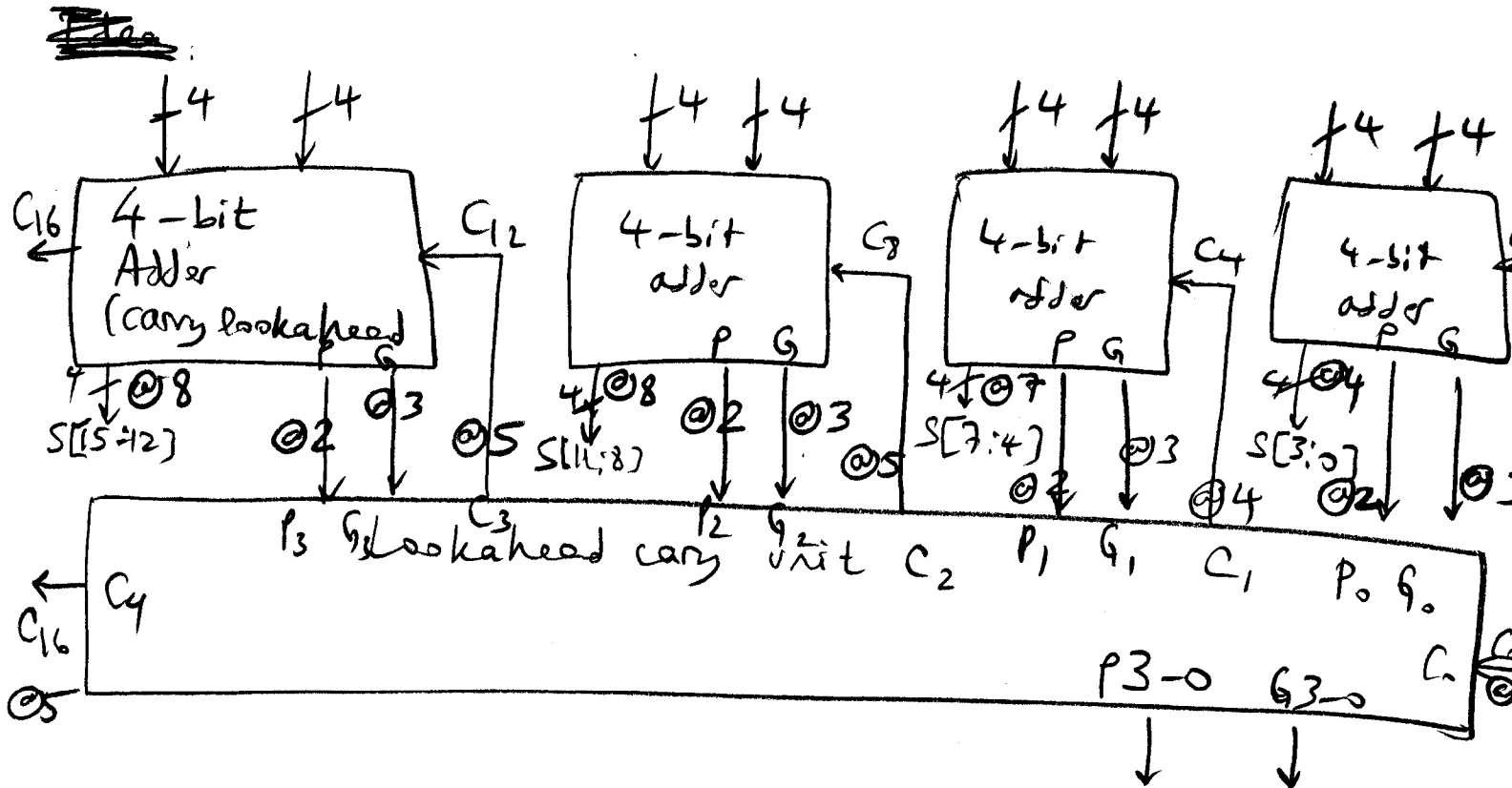How can we scale to larger adders such as 16-bit adder?




Idea: Each 4-bit adder computes its own "group" carry propagate and generate:

- Group propagate:  $P_3 \cdot P_2 \cdot P_1 \cdot P_0$
- Group generate:  $G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0$

- The second-stage circuit computes the lookaheads and the output carries between first-stage 4-bit adders.
- The logic inside this second stage circuit is exactly the same as the one in a 4-bit adder block.
 
# Worst-case Delay Analysis of 16-bit hierarchical CLA Adder:



• Equations for each block.

$\alpha \phi$  : Propagate:  $P_j = A_j \oplus B_j \quad 0 \leq j \leq 3$

generate:  $G_j = A_j \cdot B_j \quad 0 \leq j \leq 3$

carries:

$$C_1 = G_0 + C_0 P_0$$

$$C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

(not needed/used in above design)

$$C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

sum:

$$S_j = P_j \oplus C_j \quad 0 \leq j \leq 3$$

L: THE SCOPE OF ALL VARIABLES HERE IS THIS BLOCK!

group propagate:

$$P = P_3 \cdot P_2 \cdot P_1 \cdot P_0$$

group generate:

$$G = G_3 + P_3 G_2 + P_3 P_2 G_1 + \underbrace{P_3 P_2 P_1 G_0}_{@2}$$

\* Note that all group propagates will be ready @2 line. for  $\alpha_p, \alpha_1, \alpha_2, \alpha_3$ ) and all group generates will be ready @3 (i.e. for  $\alpha_0, \alpha_1, \alpha_2, \alpha_3$ ).

**[B]**: Equations:

$$C_1 = G_0 + \frac{C_0 P_0}{@3}$$

$$C_2 = G_1 + \frac{P_1 G_0}{@4} + \frac{P_1 P_0 C_0}{@3}$$

$$C_3 = G_2 + P_2 G_1 + \frac{P_2 P_1 G_0}{@4} + P_2 P_1 P_0 C_0$$


$$C_4 = G_3 + P_3 G_2 + \frac{P_3 P_2 G_1}{@4} + \frac{P_3 P_2 P_1 G_0}{@3} + \frac{P_3 P_2 P_1 P_0 C_0}{@3}$$

[SCOPE OF ALL THESE VARIABLES IS THIS BLOCK!]

Comments:

- So, the main idea in having the second-stage CLA circuit is to speed up the carries that need to be transferred from one  $\alpha$  block to the next.

 [Exercise: compare the performance of the above adder to:



i.e. a ripple-carry adder on the top-level, and carry-lookahead adder for the  $\alpha$  blocks.]

Going back to the worst-case delay analysis:

Block:  
 $\alpha_i$   
 $1 \leq i \leq 3$

Equations:

Propagate:  $P_j = A_j \oplus B_j \quad 0 \leq j \leq 3$

Generate:  $G_j = A_j \cdot B_j \quad 0 \leq j \leq 3$

carries:

$C_1 = G_0 + \underbrace{C_0}_{\text{assume available @ } x} \cdot P_0 \quad @ (x+1)$

$C_2 = G_1 + P_1 G_0 + \underbrace{P_1 P_0 C_{p_1}}_{@ (x+1)} \quad @ (x+2)$

$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \quad @ (x+2)$

$C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 P_0 C_0 \quad @ (x+2)$

[THE SCOPE OF ALL THESE VARIABLES IS THIS BLOCK!]

[ $C_0$  is the carry-in bit to this block]

Sum: @ (x+3) @ 1 @ (x+2)


$$S_j = P_j \oplus C_j \quad 0 \leq j \leq 3$$

This shows that the sum vector will be ready 3 gate delays after the carry-in to this adder is ready.

Therefore:

| Adder Block | Sum is ready vector |
|-------------|---------------------|
| $\alpha 2$  | @ 7                 |
| $\alpha 3$  | @ 8                 |
| $\alpha 4$  | @ 8                 |

 Finally: The group propagate ( $P_{3-0}$ ) and group generate ( $G_{3-0}$ ) of the  $\beta$  block can be computed (e.g. to build a 64-bit adder:



you can use these 16-bit fast adders as shown above.)

$$\begin{array}{c}
 @3 \\
 P_{3-0} = \underbrace{P_3 \cdot P_2 \cdot P_1 \cdot P_0}_{@3}
 \end{array}$$

[these variables  
are internal to  
the  $\beta$  block.]

$$\begin{array}{c}
 @5 \\
 G_{3-0} = G_3 + P_3 G_2 + P_3 P_2 G_1 + \underbrace{P_3 P_2 P_1 G_0}_{@4}
 \end{array}$$