

LECTURE 5-6

Sequential Circuits:


A circuit is combinational if the output is determined completely by the current set of inputs.

Otherwise, it is sequential.

- Sequential circuits are necessary to implement memory elements (i.e. elements that can remember their state).

* one of the simplest memory elements:

Basic Latch

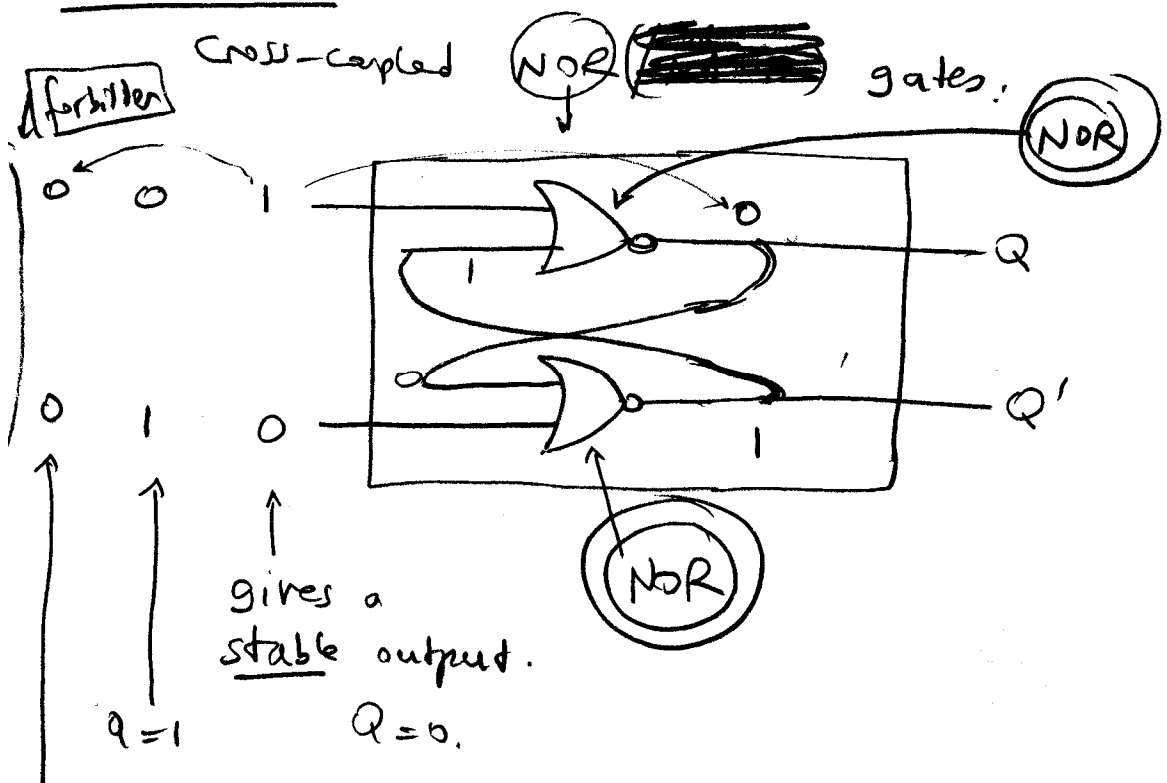

gives a stable output.
 $Q=1$ $Q=0$.

holds the value it had originally



A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

[0 → 1]

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0


[1 → 0]

  From this, we can build a ^(non-clocked) D latch as follows:




interface schematic.

Behavior:

 


 - Q gets D and Q holds the value of D.
- Seems very simple & useless, because if this is all we wanted then




But: useful behavior obtained when clocked

like an
(Enable)
Clocked D-latch :

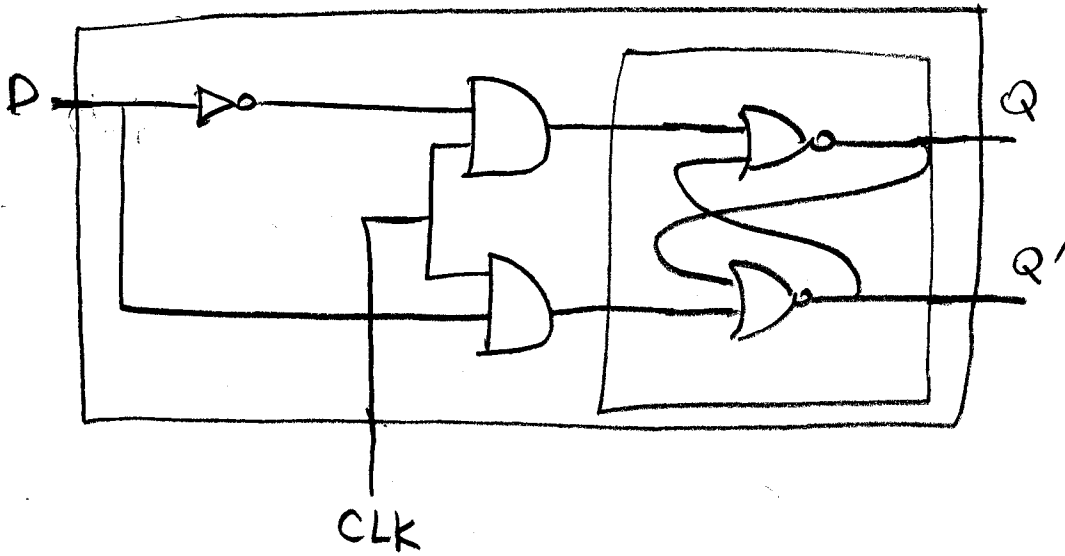

Interface schematic:

 


So, when $CLK = 1$, $Q = D$; and when $CLK = 0$, the basic latch holds the value of Q.

LECTURE # 4

[Reading: Ch 7.1, 7.3]


- Two key memory elements in synchronous design of sequential circuits.

 - clocked D latch
(clocked \overline{D} latch)




- D flip flop

(a) positive edge-triggered

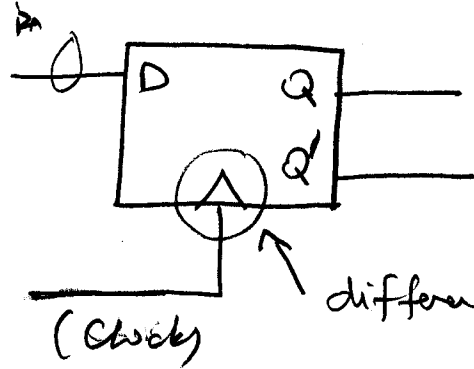


(b) negative edge-triggered

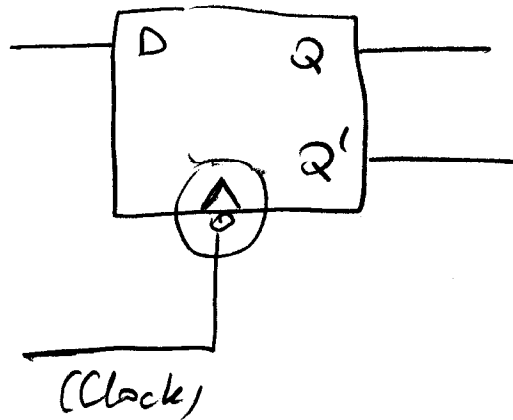

- Each ^{of these} can remember / hold 1 bit.)

- What is the behavior of these memory elements?

 Let's connect a circuit this way for illustration




Latch is transparent to its data input when the CLK is high - otherwise holds its last value

D-FF samples its data input at the rising clock edge (positive) - otherwise holds its last value

D-FF samples its data input at the falling (negative) clock edge - otherwise holds its last value

~~Timing diagram:~~

(Ideal operation)

 


- "Active edge" of the clock :

= { rising edge for a ~~FF~~ PET-FF
 falling edge --- NET-FF.

- Ideal timing diagrams above since ~~are~~ real latch / FF's
show prop. delays & other effects that we will cover later
RESET DISCUSSION → see next page; then come back


- Above, we assumed that "somehow", the latches & ffs were initialized to zero (ie. $Q_{initial} = 0$.)

 - You need an explicit reset input to achieve this:



If $Reset = 1$, then $Q = 0$ (no matter what the D input may be.) This kind of Reset is called asynchronous reset because the change in $Q = 1 \rightarrow Q = 0$ can happen any time. ~~[This is a problem for latches - and we will see why (setup time requirements)]~~ But for now, we will ~~use this kind of reset.~~ (We don't like asynchronous reset because we can see later can cause the circuit to fall into an unstable state.)

Similarly, for ffs:

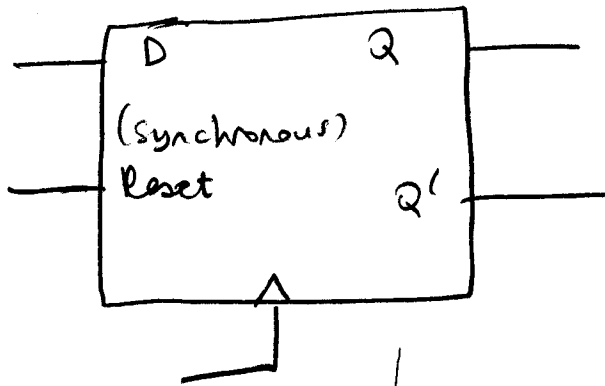

Reset can be asynchronous or synchronous; we prefer



synchronous reset (implemented

as the flip-flop).

Reset on our ffs will always imply synchronous reset.


The ff's reset will be a synchronous reset (we will design it this way.). So: At the active clock edge, if the Reset = 1, then $Q = 0$. Otherwise, $Q = D$.

 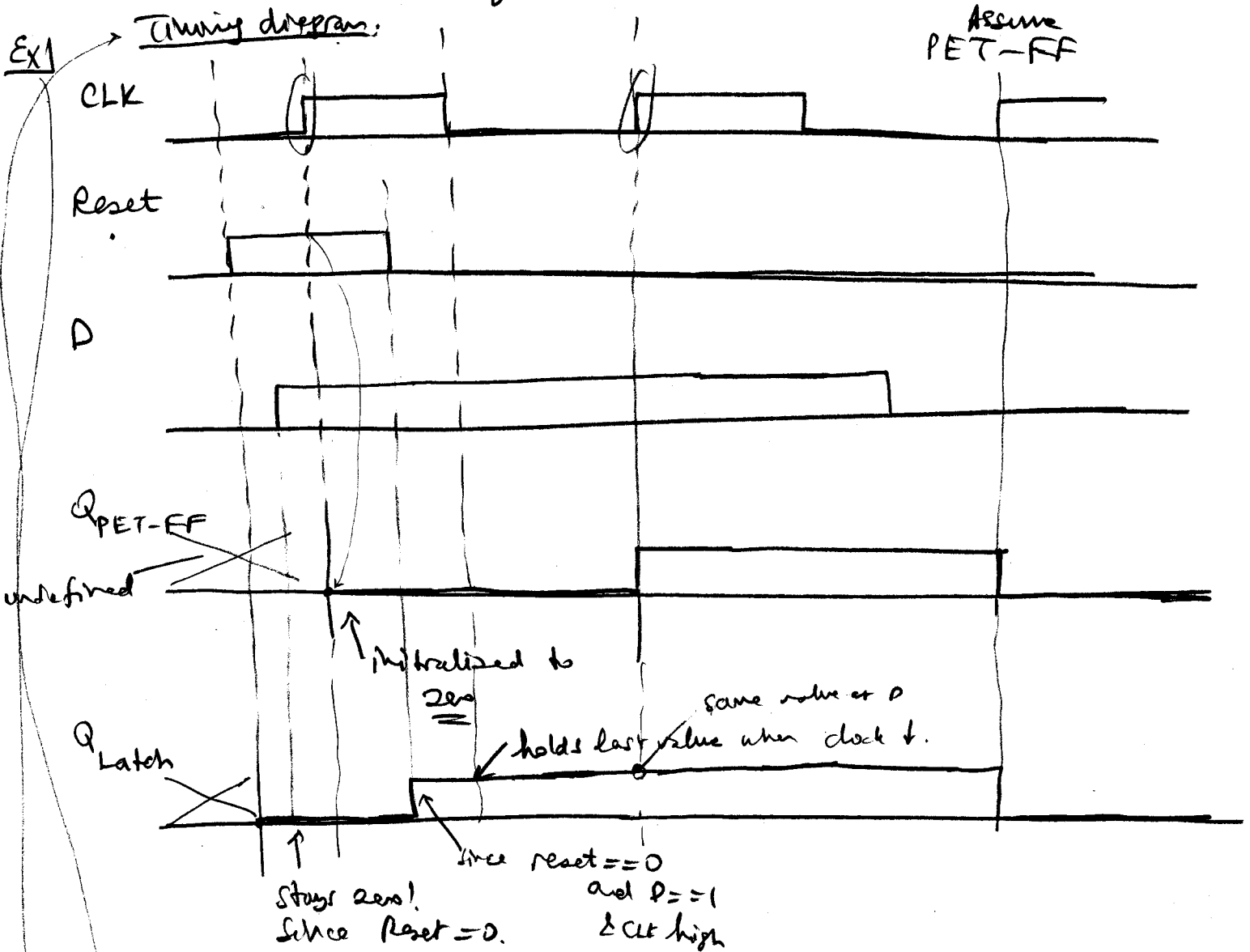- This is the behavior of the FF with ^{synchronous} reset.




NEXT-STATE EQUATION!

① Clocked D latch without Reset input:

 

[Can achieve reset as follows:

 

(do later)
 + will be reset ^{only} when clock goes high.
 - rst must stay high until clk goes low.

Next-state eq'n for a clocked latch (without asynchronous Reset) shows the next value of Q after any change in inputs assuming $CLK = 1$. (does not apply when $CLK = 0$; we know that it holds the value then.)

D	Q	Q^+
0	0	0
0	1	0
1	0	1
1	1	1

"state table"


(Copies D to Q no matter what previous value of Q is.)
 [Memory aspect comes in when $CLK = 0$.]

Next-state equation:

$Q^+ = D$

(clocked D latch without Reset.)

 ② Clocked D latch with asynchronous Reset :



- Next-state eq'n for a clocked D latch with asynchronous Reset must include the CLK input in state table (since we can no longer assume that it "holds" in $CLK = 0$: Reset may happen when $CLK = 0$)


Reset	CLK	D	Q	Q ⁺
1	X	X	X	0
0	0	0	0	0
	0	0	1	1
	0	1	0	0
	0	1	1	1
1	0	0	0	0
	0	0	1	0
	0	1	0	1
	0	1	1	1

} "hold Q"

} "copy D"

Next-state eq'n: $Q^+ = (Reset)' [CLK \cdot D + CLK' \cdot Q]$

③ D flip-flop without Reset:

 

• Next-state eq'n for a D flip-flop shows the next value of Q right after the active clock edge.

• State table:

D	Q	Q ⁺
0	0	0
0	1	0
1	0	1
1	1	1


• Next-state eq'n: $Q^+ = D$

* Same equation as for a clocked D latch without Reset, but very different meaning.

- Latch: Q^+ occurs after any change in inputs.
- FF: Q^+ " at the active clock edge.

(synchronous)
 ④ D flip-flop with Reset :

 - shows the next value of Q right after the active clock edge,



- State table :


Reset	D	Q	Q^+
1	X	X	0
	0	0	0
	0	1	0
	1	0	1
	1	1	1

- Next-state equation :


$$Q^+ = (\text{Reset})' \cdot D$$

R-S latch

Q^+

 

$(Q')^+$

 

Continue here

$$R = \text{Reset} + \text{CLK} \cdot D'$$

$$S = (\text{Reset} + (\text{CLK} \cdot D)')'$$


$$= \text{Reset}' \cdot (\text{CLK} \cdot D)$$

i.e. implement each ON-term by S and each OFF-term by R

③. Implement a D flip-flop without Reset terminal



How do we implement a flip-flop?

 - Here, implement it from 2 latches in cascade



Main idea: Have the first latch be transparent when the CLK is low. Have the second latch be transparent when

  
the CLK is high. This way you get "sampling on the positive CLK edge."



This is called a master-slave D flip-flop. The (refers to the implementation)

first latch (L1) is considered the master and the second latch (L2) is the slave since L2 must follow what L1 (its master) sends it.

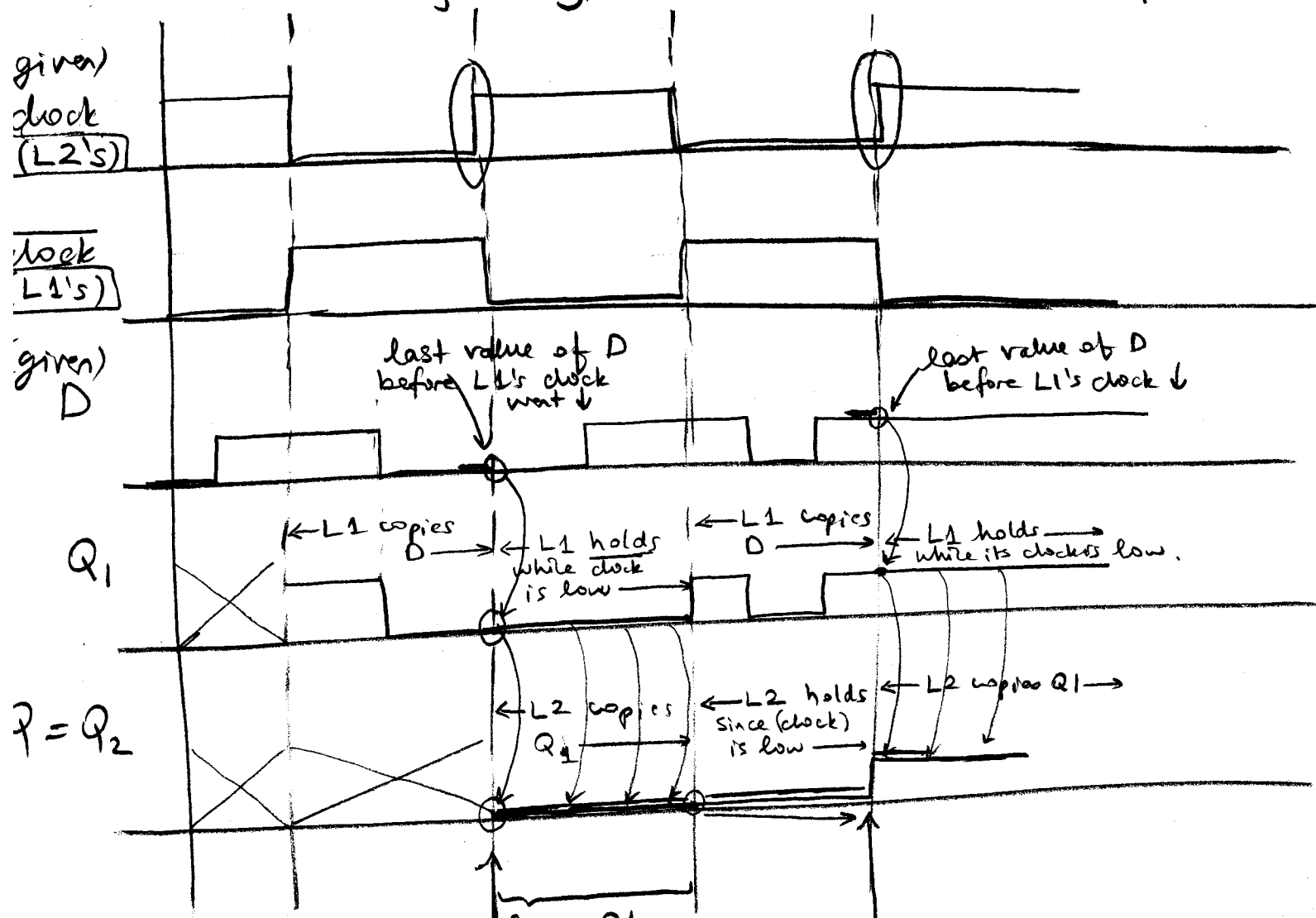- Draw the timing diagram to check its behavior:



Since Q1 is guaranteed to be constant here, Q2 is constant.



Effect: D's value of 0 is sampled at rising clock edge, (and held until next rising edge)

D's value of 1 is sampled at rising clock edge (and held until the next rising edge)

EXERCISE: Build a register with two full bits of 2 latches

Now, we introduce a very useful combinational block:

tristate buffer:

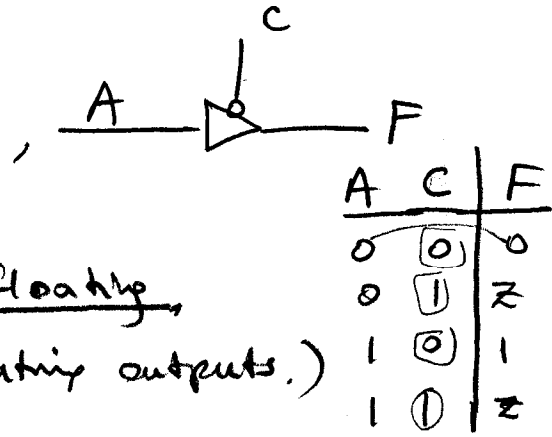 

If $C=1$, $F=A$; otherwise F is floating.
(So far, we had not allowed any floating outputs.)

So:

A	C	F
0	0	Z
0	1	0
1	0	Z
1	1	1

(floating; high impedance)

If we used combinational logic blocks to implement this,

A	C	F
0	0	X
0	1	0
1	0	X
1	1	1

← don't care

$$F = C \cdot A \quad (\text{min SOP form})$$




(produces 0 when $C=0$)

But tristate buffers can be used in ways that combinational ^{well defined}

cannot:

Ex

 

$$F = A \cdot C + B \cdot C'$$

(implements a 2:1 mux)

requires much less hardware than the AND-OR gate implementation.

note how F is left floating at each end of the...

In computer architecture, we need to hold > 1 bit.


~~Read~~
~~Write~~

e.g. Let's say I want to perform operations on bytes.

1 byte = 8 bits. You need to hold those 8 bits together

somewhere, perform an operation and perhaps write the ^{resulting} byte somewhere

e.g.

 



] a "register" holds this

Ex) Design an 8-bit register using flip-flops. The

circuit will have ~~the following inputs:~~ a 1-bit control input Read and 1-bit control input Write.


When $Read = 1$, we read the register contents to output. When $Write = 1$, we write the register with new content.

(Draw measure)

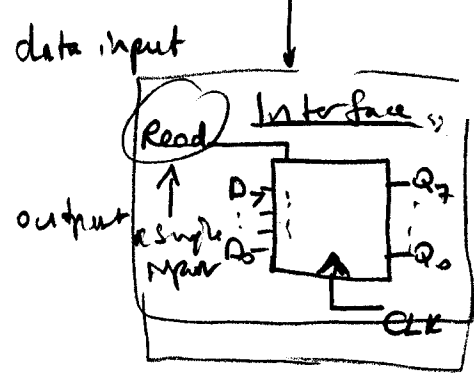 

[Ask class] how to do this.

 
Since all operations will be ~~identical~~ ^{identical} on each bit, let's focus on 1 bit only.



control circuitry must make sure that Read and Write not asserted at same time.

Replicate this cell 8 times to get the design.

Two cells drawn here.

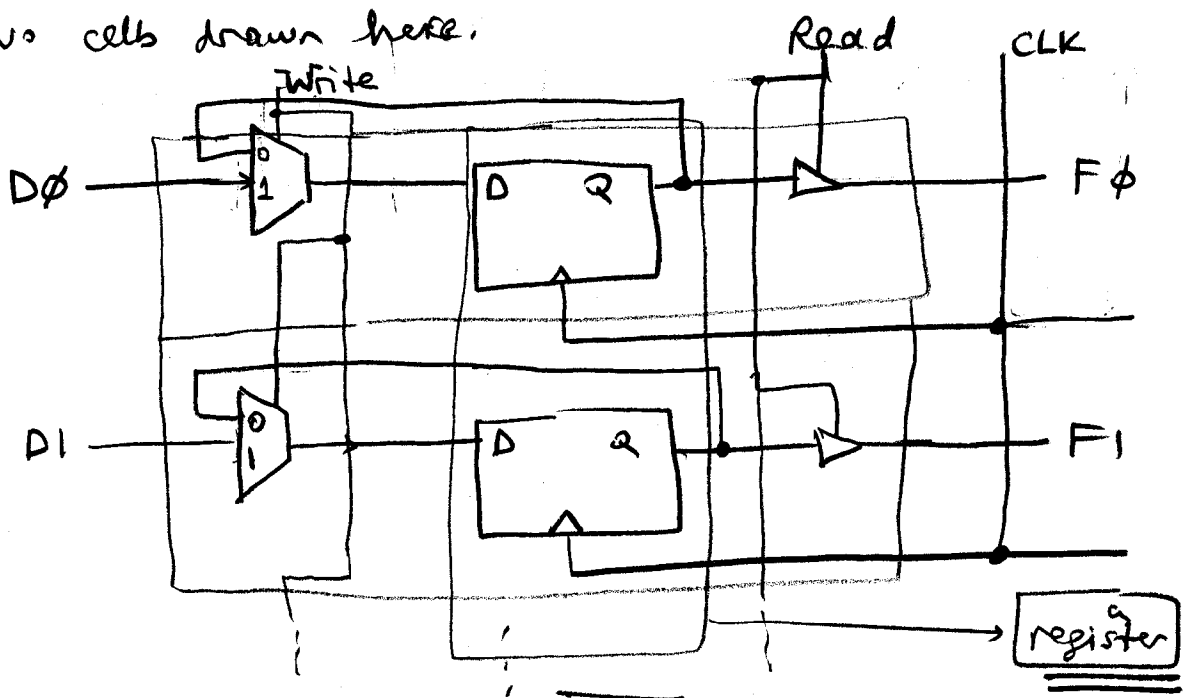


The control lines Read, $\overline{\text{Read}}$ run vertically.

The data lines run horizontally.

Note how the control signals need to be distributed to the cells.

 Now, in computer architecture, we also want structures that can achieve the following:




called a "serial input"

This is called a shift-register.

[Example usage: Design a "divide by 2" circuit, - divide by 2 mean, you need to shift the contents to the right by 1. (we will talk more about arithmetic circuits later.)


Interface: (Schematic): (4-bit s.r.)

 

Q: How do we implement a "shift register" using ffls?

[Ask class]

EX: 4-bit shift register

 



At each positive edge, contents will shift to the right by 1 (and Q0 will get overwritten)

Now, what if we wanted:

* Input: Load := 1: Load 4 bits - into the shift register


• Load := 0: shift using a serial input
(called a Parallel-Access Shift Register)
- and we want Interface Schematics

- How can we implement this?

  

make sure to take the outputs from the output of the ffs - that way they will be Synchronous. Do not put them after mux!

Note the structure:

 

- Very often, we need counters in digital circuits.

Example: Count the number of cars on street.

If #cars ≥ 1000 , raise a flag.



- Counters can be implemented using flip flops

Example: Design a circuit that counts the number of clock pulses (┌: rising clock edges); from 0, 1, 2, ..., 7 and then wraps back to 0, ..., 7 and again.

and Resets to 0 when Rst is asserted

→ synchronous

  Answer: First, find a representation; need 3 bits



Then, let's display the operation. *with use a ff for each.*

clock cycle	Q ₂	Q ₁	Q ₀
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

Key question is, how can we decide what the next state of each flip flop will be?


- We need to write each next state in terms of the previous states, such that it will apply to every transition.

[~~Ans~~ - counter design using more formal/general methods:
- illustrate how to implement load, enable, clear, reset,
for counters.]


Let us return to our examples

- Counting sequence: 0, 1, 2, 3, 4, 5, 6, 7, 0, 1, ...
(Counts the # of active clock edges)
- Each count represents a "state".
- When counter is reset, it should go to 0, in a synchronous fashion.
- See next page for the state diagram.

- Interface schematic:

 

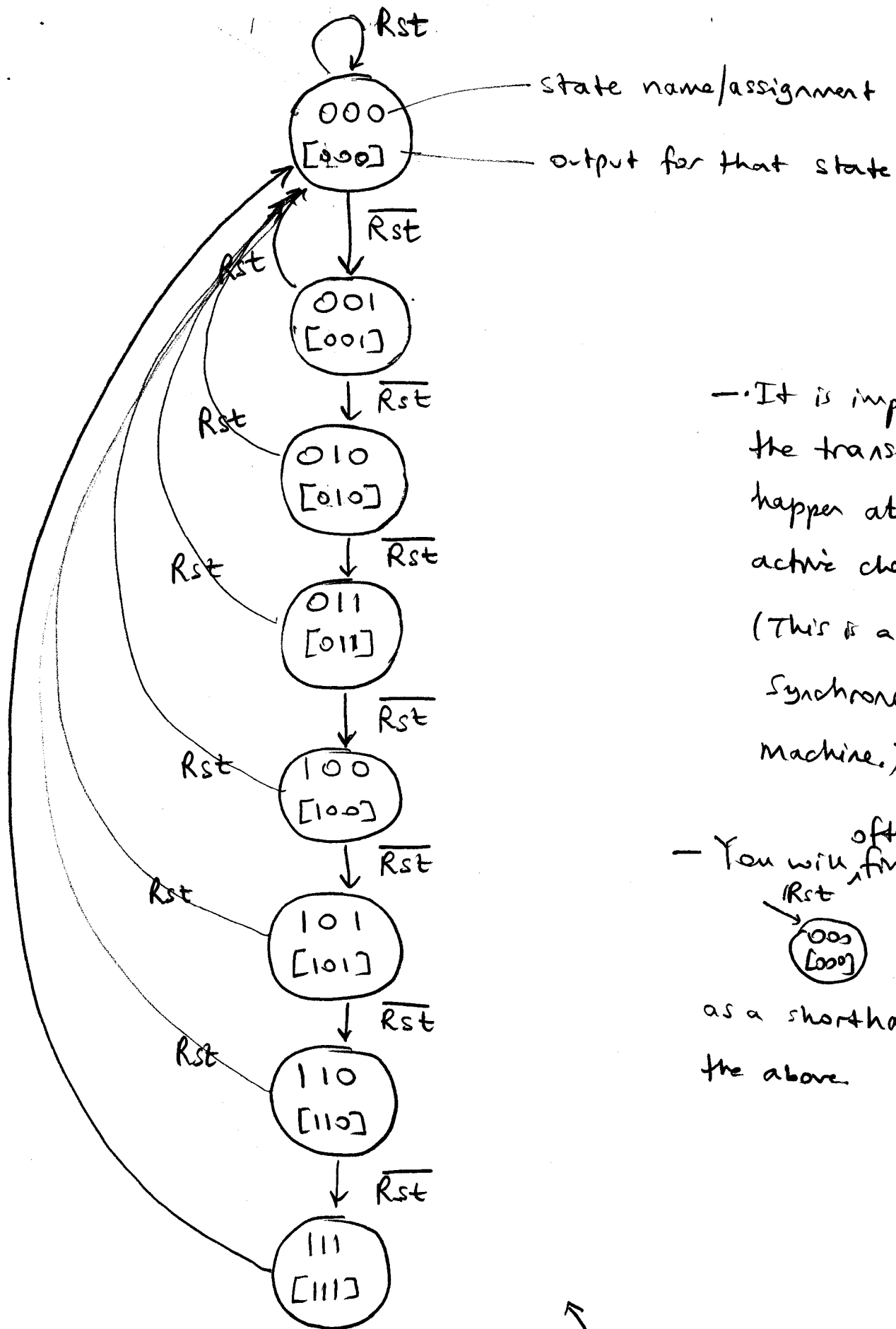- Rst is the only input here besides the clock.



- It is implied that the transitions happen at the active clock edge. (This is a Synchronous machine.)

- You will ^{often} find that $\overset{Rst}{\rightarrow}$ $\begin{matrix} 000 \\ [000] \end{matrix}$ as a shorthand for the above.

↑ called a state diagram.

State table :

Input		current state			next state			output		
		Q_2	Q_1	Q_0	Q_2^+	Q_1^+	Q_0^+	Z_2	Z_1	Z_0
placeholder)	1	Q_2	Q_1	Q_0	0	0	0	z_2	z_1	z_0
	0	0	0	0	0	0	1	0	0	0
		0	0	1	0	1	0	0	0	1
		0	1	0	0	1	1	0	1	0
		0	1	1	1	0	0	0	1	1
		1	0	0	1	0	1	1	0	0
		1	0	1	1	1	0	1	0	1
		1	1	0	1	1	1	1	1	0
		1	1	1	0	0	0	1	1	1

[A finite state machine in which the output is a function of only the current state (and not of the current input) is called a Moore machine.]
(later..)

Mapping the state table to a D flip-flop implementation
(by hand):

- Do a K-map for each next-state variable and each output variable. Then, minimize logic.

- In this example:

$$\begin{aligned} Z_2 &= Q_2 \\ Z_1 &= Q_1 \\ Z_0 &= Q_0 \end{aligned}$$

}

already in minimum form

- Examine next-state variables:

$Q_0^+ = (Rst)'. (Q_0')$

read directly from state table.

(for Rst=0)

Q_0^+	Q_2, Q_1	Q_1			
	Q_0	00	01	11	10
0	0	0	1	1	0
1	1	1	0	0	1

$$Q_1^+ \Big|_{Rst=0} = \overline{Q_1} \cdot Q_0 + Q_1 \cdot \overline{Q_0} (= Q_1 \oplus Q_0)$$

$Q_1^+ = (Rst)'. [Q_1 \oplus Q_0]$