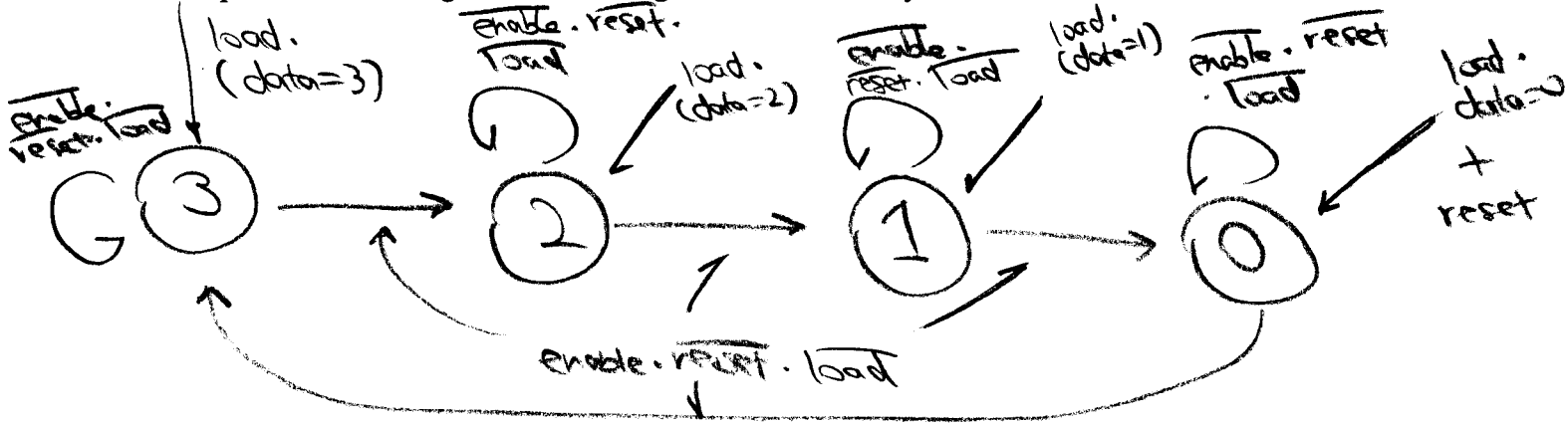


Synchronous Down Counter

Make a synchronous down counter that counts down from 3 to 0 and takes in synchronous reset, enable, load, and data. Reset takes precedence over all other inputs, and upon reset the counter should go to 0. Upon load, the FSM goes to whatever state is on the input data. If neither load or reset is high, the FSM goes to the next state on positive clock edge if enable is high. Otherwise it stays in its current state.



```
module DownCounter(Reset, Load, Enable, Data, Count, clk);
```

```
input Reset, Load, Enable, clk;
input [1:0]Data;
output [1:0]Count;
reg [1:0]Count;
```

```
always @(posedge clk)
begin
```

```
    if(Reset)
    Count <= 0;
```

```
    else if(Load)
    Count <= Data;
```

```
    else if(Enable && Count==0 )
    Count <= 3;
```

```
    else if(Enable)
    Count <= Count - 1;
```


```
end
```

```
endmodule
```

Adder Mealy FSM

Implement the adder from lab 5 in mealy form. Inputs are 2 bits, A and B. The outputs should be the sum and carry bits.

01/10
10/10
11/11

 

Input:				Output:			
A	B	Sum	Carry	A	B	Sum	Carry
0	0	x	0	x	x	0	0
0	0	x	1	x	x	1	0
0	1	x	0	0	0	1	0
0	1	x	1	0	0	0	1
1	0	x	0	x	x	1	0
1	0	x	1	x	x	0	1
1	1	x	0	x	x	0	1
1	1	x	1	x	x	1	1

```
module DownCounter(A, B, Sum, Cout, clk);
```

```
input A, B, clk;
```

```
output Sum;
```

```
output Cout;
```

```
reg Cout;
```

```
wire Sum;
```

```
assign Sum = (A ^ B) ^ Cout;
```

```
wire CoutNext;
```

```
assign CoutNext = (Cout && (A || B)) && (~Cout && A && B);
```

```
always @ (posedge clk)
```

```
    Cout <= CoutNext;
```

```
endmodule
```

Synchronous and Asynchronous Flip Flops

Implement 2 D Flip Flops, one synchronous and the other asynchronous

Asynchronous:

```
module DFF(D, clk, R, Q);
```

```
input D, clk, R;
```

```
output Q;
```

```
reg Q;
```

```
always@(posedge clk or posedge R)
```

```
begin
```

```
    if(R)
```

```
        Q<=0;
```

```
    else
```

```
        Q<=D;
```

```
end
```

```
endmodule
```

Synchronous:

```
module DFF(D, clk, R, Q);
```

```
input D, clk, R;
```

```
output Q;
```

```
reg Q;
```

```
always@(posedge clk)
```

```
begin
```

```
    if(R)
```

```
        Q<=0;
```

```
    else
```

```
        Q<=D;
```

```
end
```

```
endmodule
```