

## COURSE READER PROBLEMS

32) Implement the following Boolean functions in CMOS. Report the total number of transistors used in each. [use the minimum number possible.]


(a)  $F_1 = (A \cdot B)'$  (NAND)

(b)  $F_2 = A \cdot B$  (AND)

(c)  $F_3 = A \cdot B + C$

(d)  $F_4 = (A' + B) \cdot (C + D)$ .

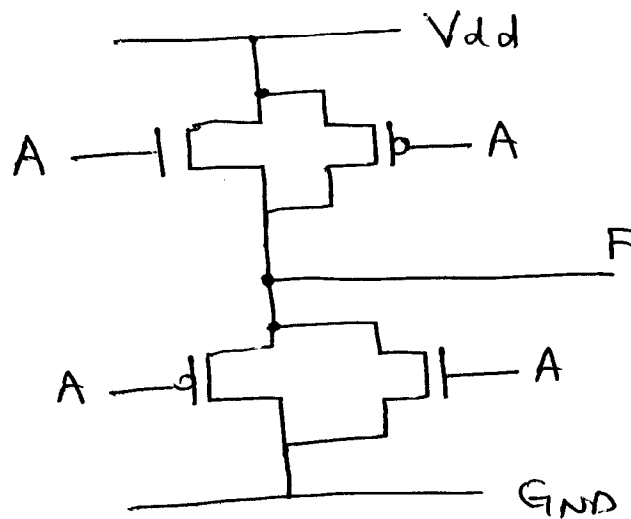33) Your friend suggests the following structure for a NOT gate: (to implement  $F = A'$ ),



(a) Will this work correctly?

(b) Point out any problems you see with this.