

# Combinational Logic Building Blocks and Bus Structure

ECE 152A – Fall 2006

## Reading Assignment

- Brown and Vranesic
  - 3 Implementation Technology
    - 3.8 Practical Aspects
      - 3.8.7 Passing 1s and 0s Through Transistor Switches
      - 3.8.8 Fan-In and Fan-Out in Logic Gates
        - Tri-State Buffers (only this section of 3.8.8)
    - 3.9 Transmission Gates
      - 3.9.2 Multiplexer Circuit

## Reading Assignment

- Brown and Vranesic (cont)
  - 6 Combinational-Circuit Building Blocks
    - 6.1 Multiplexers
      - 6.1.1 Synthesis of Logic Functions Using Multiplexers
      - 6.1.2 Multiplexer Synthesis Using Shannon's Expansion
    - 6.2 Decoders
      - 6.2.1 Demultiplexers
    - 6.3 Encoders
      - 6.3.1 Binary Encoders
      - 6.3.2 Priority Encoders
    - 6.4 Code Converters

## Reading Assignment

- Roth
  - 9 Multiplexers, Decoders and Programmable Logic
    - 9.1 Introduction
    - 9.2 Multiplexers
    - 9.3 Three State Buffers
    - 9.4 Decoders and Encoders

## Multiplexer


- Passes one of several data inputs to output
  - Generally  $2^n$  data inputs and always a single data output
  - $n$  control lines determine which input is “steered” to the output
- Allows logical (not “tri-state” or electrical) implementation of buses
  - Buses and register transfer operations fundamental to digital system design

## Multiplexer

- Also possible to implement arbitrary combinational logic with multiplexers
  - Universal, combinational logic element
- Also known as “Data Selector” and “Mux”
- In sequential operation, provides parallel to serial conversion
 
# Two-to-One Multiplexer

■  $F = \text{Select}' \cdot x_0 + \text{Select} \cdot x_1$



December 5, 2006

ECE 152A - Digital Design Principles


7

# Four-to-One Multiplexer

- *i*<sup>th</sup> data input ANDed with minterm *m<sub>i</sub>*
  - Embedded circuit generating minterms will become known as a decoder

$$f = \bar{s}_1\bar{s}_0w_0 + \bar{s}_1s_0w_1 + s_1\bar{s}_0w_2 + s_1s_0w_3$$

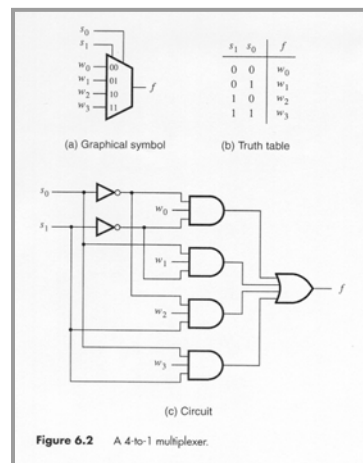$m_0w_0$      $m_1w_1$      $m_2w_2$      $m_3w_3$




December 5, 2006

ECE 152A - Digital Design Principles

8
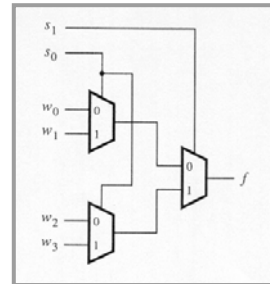
## Building Larger Multiplexers

- 4-to-1 (4:1) Mux using 2-to-1 (2:1) Muxes
  - Simple and modular
  - Adds 2 levels of gate (propagation) delay




December 5, 2006

ECE 152A - Digital Design Principles

9

## Building Larger Multiplexers

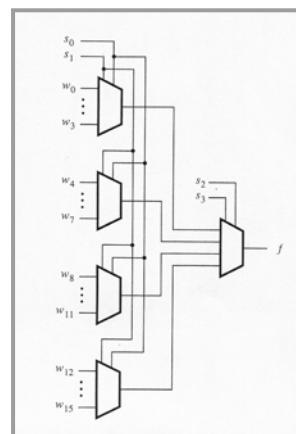- 16:1 Mux constructed from 4:1 Muxes
  - Expandable to 32:1 and 64:1 with additional 2:1 and/or 4:1 Muxes
    - With additional levels of propagation delay




December 5, 2006

ECE 152A - Digital Design Principles

10
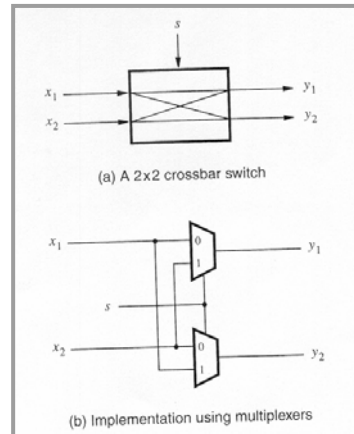
## Multiplexer Application

- Crossbar Switch
  - In general, n-inputs by n-outputs
    - Connectivity is any input to any output
  - Important component of networking hardware
    - The bigger, the faster, the better...



December 5, 2006

ECE 152A - Digital Design Principles

11

## Combinational Design Using Multiplexers

- Input variables applied to Mux select lines
  - “Steer” (constant) value of function to output
    - Allows implementation of n-variable function with  $2^n$ -to-1 multiplexer
  - “Steer” derived function (a variable, its complement, the constant 1 or the constant 0) to the output
    - Allows implementation of n-variable function with  $2^{n-1}$ -to-1 multiplexer




December 5, 2006

ECE 152A - Digital Design Principles

12


# Combinational Design Using Multiplexers

   - Example 1: XOR Function
  - Using a 4:1 Mux
  - The modified Truth Table
    - Possibilities are  $x, x', 0, 1$
  - The 2-input XOR using a 2:1 Mux



# Combinational Design Using Multiplexers

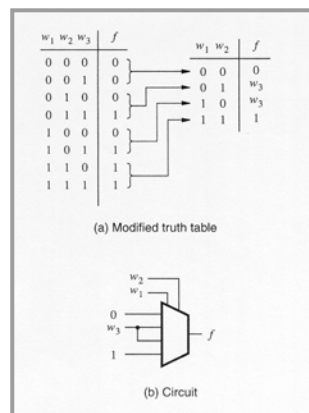- Example 2 : Three input majority function
  - Three input function with  $(2^{n-1}-to-1)$  4:1 Mux



## Combinational Design Using Multiplexers

- Multiplexer Synthesis Using Shannon's Expansion
  - By adding gate level circuitry to Mux inputs, an arbitrary combinational function can be realized with a 2-to-1 Mux
    - Externally generating a function of one of the variables

*Shannon's Expansion Theorem* Any Boolean function  $f(w_1, \dots, w_n)$  can be written in the form

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

## Combinational Design Using Multiplexers

- Example 3 : Three input majority function with 2:1 Mux
  - Algebraic expansion

$$f(w_1, w_2, w_3) = (w_1 w_2 + w_1 w_3 + w_2 w_3)$$


$$f = w_1'(0w_2 + 0w_3 + w_2 w_3) + w_1(1w_2 + 1w_3 + w_2 w_3)$$

$$f = w_1'(w_2 w_3) + w_1(w_2 + w_3)$$



## Combinational Design Using Multiplexers

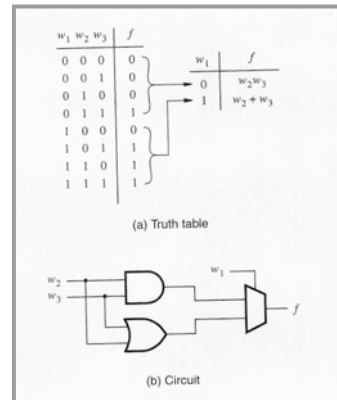- Example 3: Three input majority function with 2:1 Mux
  - Truth Table and circuit implementation



December 5, 2006

ECE 152A - Digital Design Principles

17

## Combinational Design Using Multiplexers

- Shannon's Expansion with 4:1 Mux
  - Three input majority function
    - Expansion in terms of  $w_1$  and  $w_2$ 
      - Verifies earlier (heuristic) solution

$$\begin{aligned}
 f(w_1, w_2, w_3) &= (w_1w_2 + w_1w_3 + w_2w_3) \\
 f &= w_1'w_2'(00 + 0w_3 + 0w_3) + w_1'w_2(01 + 0w_3 + 1w_3) \\
 &\quad + w_1w_2'(10 + 1w_3 + 0w_3) + w_1w_2(11 + 1w_3 + 1w_3) \\
 f &= w_1'w_2'(0) + w_1'w_2(w_3) + w_1w_2'(w_3) + w_1w_2(1)
 \end{aligned}$$

December 5, 2006

ECE 152A - Digital Design Principles

18

## Multiplexers and Buses

- Bus allows data transfers between multiple sources and single or multiple destinations over a shared path (wires)
  - Bus includes multiple bits
    - Parallel data bus
  - Only one source on the bus at any time
    - Bus contention


December 5, 2006

ECE 152A - Digital Design Principles

19

## Multiplexers and Buses

 - Example below illustrates two, four-bit words (X and Y) multiplexed onto the Z bus
  - Register transfer operations
    - $A' : Z \leftarrow X$ ,  $A : Z \leftarrow Y$




December 5, 2006

ECE 152A - Digital Design Principles

20
 
# Tri-State Outputs

- Utilizes third, high impedance output state
  - In Hi-Z state, output appears as an open circuit to bus connection
  - Mux disconnects from bus logically, tri-state output device disconnects electrically



# Tri-State Outputs (cont)


- Flavors of tri-state outputs and control
- Bus implementation

| B | A | C |
|---|---|---|
| 0 | 0 | Z |
| 0 | 1 | Z |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

| B | A | C |
|---|---|---|
| 0 | 0 | Z |
| 0 | 1 | Z |
| 1 | 0 | 1 |
| 1 | 1 | 1 |


| B | A | C |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | Z |
| 1 | 1 | Z |

| B | A | C |
|---|---|---|
| 0 | 0 | Z |
| 0 | 1 | Z |
| 1 | 0 | Z |
| 1 | 1 | Z |

 
 
## NMOS and PMOS Transistors

- Recall static CMOS circuits
  - Logic high output passed to output through PMOS transistor(s)
    - PMOS transistor passes “good” 1 and “bad” 0
  - Logic low output passed to output through NMOS transistor(s)
    - NMOS transistor passes “good” 0 and “bad” 1
  - “Good” 0s and 1s are GND and  $V_{DD}$
  - “Bad” 0s and 1s have degraded DC voltage (logic) levels



December 5, 2006

ECE 152A - Digital Design Principles

23

## NMOS and PMOS Transistors

- Degradation of DC signal levels is a result of the “threshold voltage” ( $V_T$ ) of transistor and the “body effect”
  - To “turn on” the transistor, the gate to source voltage ( $V_{GS}$ ) must exceed the transistor’s threshold voltage ( $V_T$ )
    - An NMOS transistor has a positive  $V_T$
    - A PMOS transistor has a negative  $V_T$
  - The threshold voltage itself is increased by the body effect by a factor of  $\sim 1.5$


December 5, 2006

ECE 152A - Digital Design Principles

24
 
## NMOS and PMOS Transistors

- For the inverter below, assume the NMOS device has a  $V_T$  of 1V ( $V_{GS} > 1V$ ) and the PMOS device has a  $V_T$  of -1V ( $V_{GS} < -1V$ ) and  $V_{DD} = 5V$




Input = 5V,  $V_{GS}(T1) = 5V$  (off),  $V_{GS}(T2) = 5V$  (on)  
Output = 0V (GND)

Input = 0V,  $V_{GS}(T1) = -5V$  (on),  $V_{GS}(T2) = 0V$  (off),  
Output = 5V ( $V_{DD}$ )

 
## NMOS and PMOS Transistors

- Bad 1s (NMOS) and Bad 0s (PMOS)
  - $V_A = V_{DD} - V_T$  (NMOS)
    - Input going high; turns off at  $V_{GS} = V_T$
  - $V_B = -V_T$  (PMOS)
    - Input going low; turns off at  $V_{GS} = V_T$



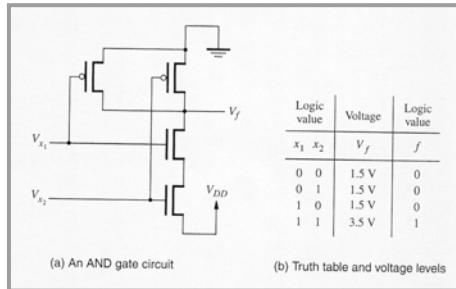
# CMOS AND Gate

- Note degradation in DC signal (logic) levels
  - AND Gates are never built this way in CMOS



 
# The CMOS Transmission Gate

- When enabled, the CMOS Transmission Gate:
  - Passes “good” 1s (through the PMOS transistor)
  - Passes “good” 0s (through the NMOS transistors)
- When disabled, the CMOS Transmission gate acts like a Tri-State Buffer



# CMOS Transmission Gate MUX

 - 2:1 Multiplexer implementation with transmission gates




December 5, 2006

ECE 152A - Digital Design Principles

29
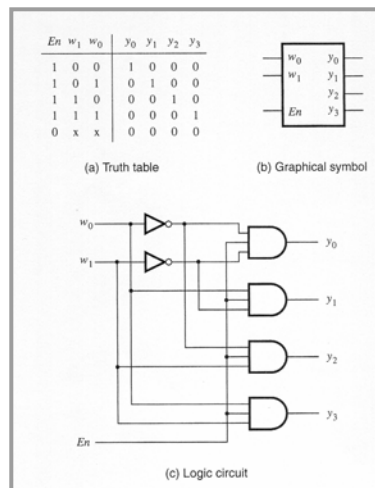
# Decoders

- 2-to-4 Decoder shown
  - 2-to- $2^n$  in general
  - Enable input allows construction of decoder tree and demultiplexer
  - Generates all minterms when enabled
    - Multiple output circuits
  - One hot decoding




December 5, 2006

ECE 152A - Digital Design Principles

30
 
## Decoder Tree

- One-bit expansion (3-to-8) by adding external decoding circuitry




December 5, 2006

ECE 152A - Digital Design Principles

31
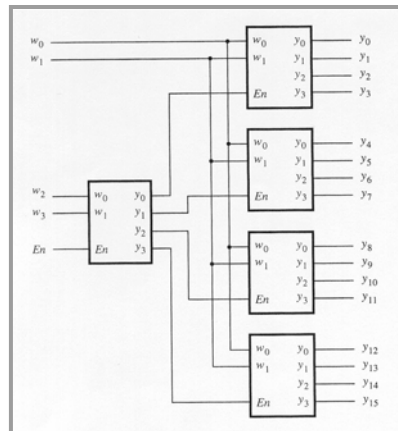
## Decoder Tree

- Two-bit expansion (4-to-16) by adding another 2-to-4 decoder



December 5, 2006


ECE 152A - Digital Design Principles

32


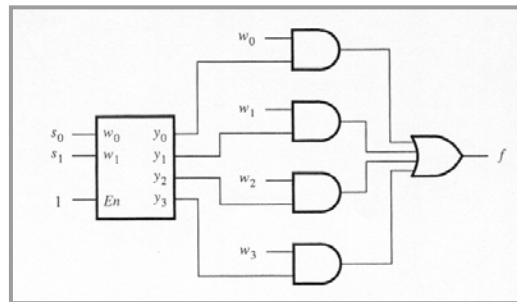
## Decoder Applications

- Multiplexer from decoder
  - Recall “embedded decoder”




December 5, 2006

ECE 152A - Digital Design Principles

33
 
## Decoder Applications

- Multiple Output Circuits
  - Full Adder using 3 X 8 Decoder



$$\begin{aligned} \text{Sum} &= m1 + m2 + m4 + m7 \\ &= x'y'z + x'yz' + xy'z' + xyz \end{aligned}$$

$$\begin{aligned} \text{Carry} &= m3 + m5 + m6 + m7 \\ &= x'yz + xy'z + xyz' + xyz \end{aligned}$$


December 5, 2006

ECE 152A - Digital Design Principles

34

## Decoder Applications

### ■ Decoder Bus Control/Multiplexer

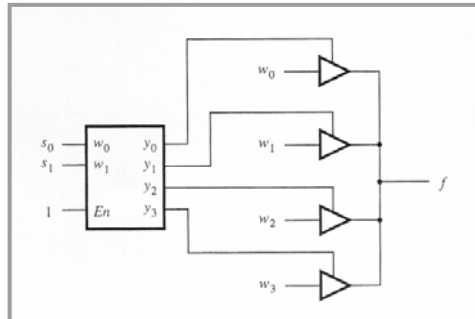

December 5, 2006

ECE 152A - Digital Design Principles

35

## Demultiplexers

- Serial to parallel conversion
  - Send a single data bit to a specific address
- A 1-to- $2^n$  demultiplexer is implemented using an  $n$ -to- $2^n$  decoder
  - The (value of) the data is applied via the enable input
- Valuable circuit in sequential circuits
  - Not so much in combinational circuits
- Also referred to as Dmux's

December 5, 2006



ECE 152A - Digital Design Principles

36

# Encoders
  
## Binary Encoders


- “One hot” input, binary (or other code) representation output
  - Reverse of decoder



# Encoders

 
## Priority Encoders

- Used in prioritizing interrupts (or other events)



# Code Converters
 
## ■ BCD to 7-Segment Display Code Converter



| $w_3$ | $w_2$ | $w_1$ | $w_0$ | $a$ | $b$ | $c$ | $d$ | $e$ | $f$ | $g$ |
|-------|-------|-------|-------|-----|-----|-----|-----|-----|-----|-----|
| 0     | 0     | 0     | 0     | 1   | 1   | 1   | 1   | 1   | 1   | 0   |
| 0     | 0     | 0     | 1     | 0   | 1   | 1   | 0   | 0   | 0   | 0   |
| 0     | 0     | 1     | 0     | 1   | 1   | 0   | 1   | 1   | 0   | 1   |
| 0     | 0     | 1     | 1     | 1   | 1   | 1   | 1   | 0   | 0   | 1   |
| 0     | 1     | 0     | 0     | 0   | 1   | 1   | 0   | 0   | 1   | 1   |
| 0     | 1     | 0     | 1     | 1   | 0   | 1   | 1   | 0   | 1   | 1   |
| 0     | 1     | 1     | 0     | 1   | 0   | 1   | 1   | 1   | 1   | 1   |
| 0     | 1     | 1     | 1     | 1   | 1   | 1   | 0   | 0   | 0   | 0   |
| 1     | 0     | 0     | 0     | 1   | 1   | 1   | 1   | 1   | 1   | 1   |
| 1     | 0     | 0     | 1     | 1   | 1   | 1   | 1   | 0   | 1   | 1   |

(c) Truth table