

```

//Top module for lab4
module State_Machine (tail_lights,clock,left,right,brake,hazards,reset);
//Input Ports
input  clock,left,right,brake,hazards,reset;
//Output Ports
//output rc,rb,ra,la,lb,lc;
output [5:0] tail_lights;
//Input Ports data type
wire  clock,left,right,brake,hazards,reset;
//Output Ports
//reg   rc,rb,ra,la,lb,lc;
reg [5:0] tail_lights;
//Internal Constants
//Declare all the possible states
parameter OFF = 6'b000000;
parameter ON = 6'b111111;
parameter LAR0 = 6'b001000;
parameter LBR0 = 6'b011000;
parameter L1R0 = 6'b111000;
parameter L1RA = 6'b111100;
parameter L1RB = 6'b111110;
parameter L0RA = 6'b000100;
parameter L0RB = 6'b000110;
parameter L0R1 = 6'b000111;
parameter LAR1 = 6'b001111;
parameter LBR1 = 6'b011111;

reg [5:0] current_state;
reg [5:0] next_state;

//Here, we start by the having all leds OFF
initial begin
    current_state = OFF;
end

//We are assigning neg clok edge for state changes
//Similiar to : we are using neg clock edge for writing
//and pos edge for reading or checking states
always @(negedge clock)
begin: FSM_SEQ
    current_state = next_state;
    tail_lights = next_state;
end

//Pos edge clock for checking states
always @(posedge clock) begin

    // we start first by checking the reset
    if (reset == 1)
        next_state <= OFF; // if reset enabled then all leds are off

    //Check for hazard-like request
    else if ((right == 1 && left == 1) || hazards == 1)begin
        if (brake == 1 || current_state == OFF)
            next_state = ON; //Brakes given priority over hazards
        else

```

```
        next_state = OFF;
    end

    //Handle brake requests not involving turn signals or hazards
    else if (right == 0 && left == 0)begin
        if (brake == 0)
            next_state = OFF;
        else
            next_state = ON;
    end

    //Handle turn-signal requests
    //Write your own version of code for handling the turn signals

end

endmodule
```