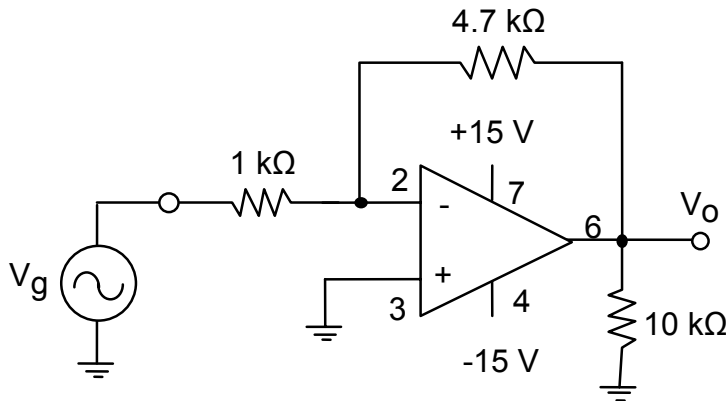



ECE 2A Lab 4 Pre Lab Questions

1. What is the gain of the following circuit?



2. Does the 10KΩ resistor at the output have any affect on the gain, assuming an ideal op amp?

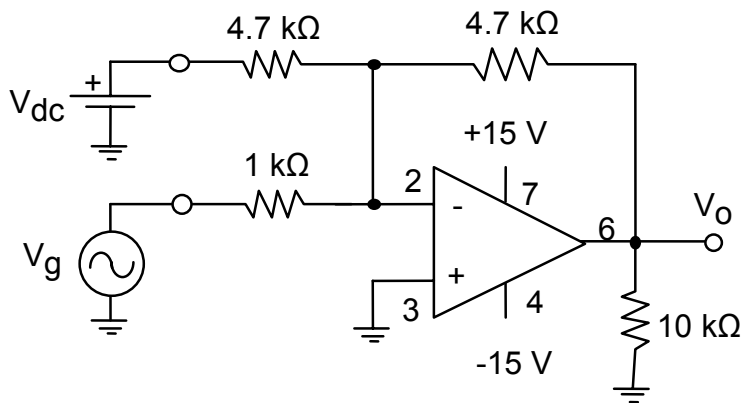3. What is the relationship between the output voltage and the inputs V_g and V_{dc} in the following circuit?



4. What is the gain of the following circuit?

