

Name: Solutions

ECE 2A–Spring 2008

Perm No. _____

Prof. K. Banerjee

UNIVERSITY OF CALIFORNIA, SANTA BARBARA
Department of Electrical and Computer Engineering

MIDTERM EXAMINATION-ECE124A

Room: NH 1111, May 12, 3:30-4:45 PM

READ CAREFULLY:


- **This is an OPEN BOOK/NOTES Exam. However, only the course Text Book + notes + homeworks are allowed. Any other material is not allowed. Calculators OK.**
- **READ the questions carefully before answering. Include all your answers in locations specified on these pages. Show ALL WORKING used to arrive at answers. Use space provided for all working. Use the back sides if necessary. There are 9 pages including the cover page. Be sure to write Your NAME/Perm No. on EVERY PAGE.**

Question	Scores
#1	/ 30
#2	/ 25
#3	/ 20
#4	/ 25
TOTAL	/ 100

Good Luck!

1. (30 pts): (suggested time: 25 minutes)

Find the current flowing through the resistance R_1 of the circuit shown below if the resistances are equal to $R_1 = 10 \, \Omega$, $R_2 = 20 \, \Omega$, and $R_3 = 30 \, \Omega$, and the potentials of points 1, 2, and 3 are equal to $V_1 = 10 \, \text{V}$, $V_2 = 6 \, \text{V}$, and $V_3 = 5 \, \text{V}$. Which resistor dissipates the maximum power?

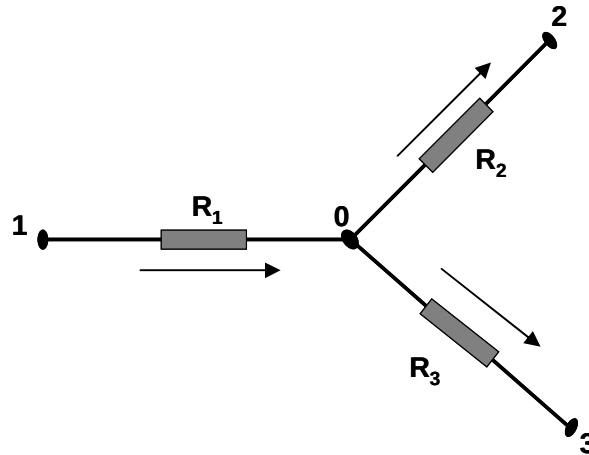**Solution:**

Assume voltage at node 0 = V_x

Assuming current is entering from a and leaving to 2 and 3 (which is intuitive as node 1 is at highest potential).

The KCL at node 0 becomes :

$$\frac{-(10 - V_x)}{10} + \frac{(V_x - 6)}{20} + \frac{(V_x - 5)}{30} = 0;$$

(convention used is entering current = -ve and leaving as ve)

Solving, we get $V_x = 8 \, \text{V}$.

$$\text{Current flowing through } R_1 = \frac{10 - 8}{10} = 0.2 \, \text{A}$$

$$\text{Current flowing through } R_2 = \frac{8 - 6}{20} = 0.1 \, \text{A}$$

$$\text{Current flowing through } R_3 = \frac{8 - 5}{30} = 0.1 \, \text{A}$$

Power dissipated by $R_1 = 0.4 \, \text{W}$

Power dissipated by $R_2 = 0.2 \, \text{W}$

Name: Solutions

ECE 2A–Spring 2008

Perm No. _____


Prof. K. Banerjee

Power dissipated by $R_3 = 0.3 \text{ W}$


R_1 dissipates max. Power.

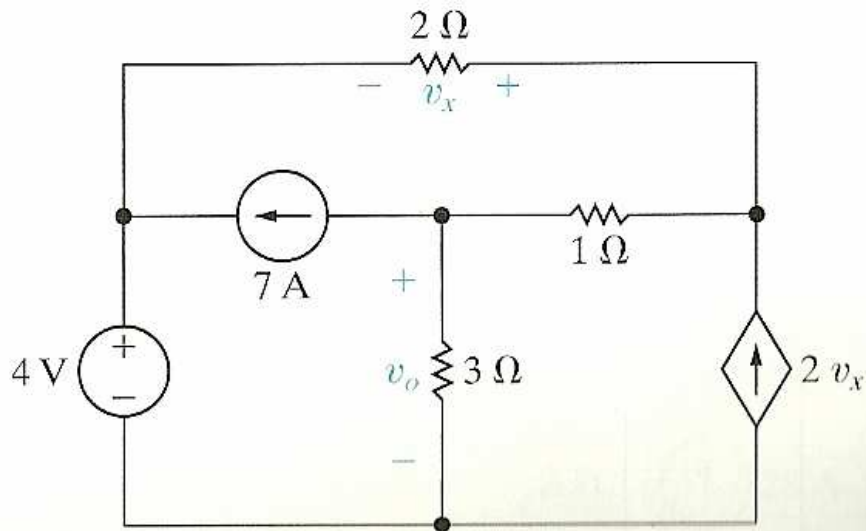2. (25 pts): (suggested time: 20 minutes)

Use the node-voltage method to find the value of v_o in the circuit below:



Solution :

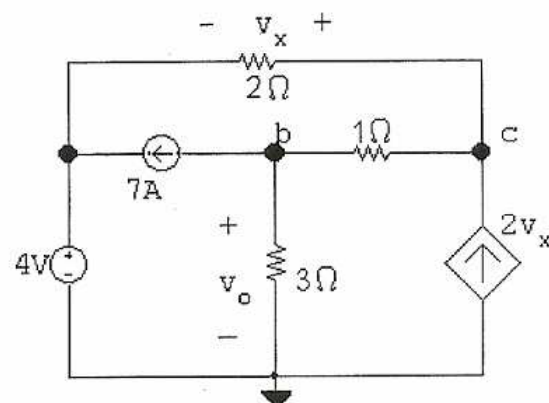

The two node voltage equations are:

$$7 + \frac{v_b}{3} + \frac{v_b - v_c}{1} = 0$$

$$-2v_x + \frac{v_c - v_b}{1} + \frac{v_c - 4}{2} = 0$$

The constraint equation for the dependent source is:

$$v_x = v_c - 4$$

Place these equations in standard form:

$$v_b \left(\frac{1}{3} + 1 \right) + v_c(-1) + v_x(0) = -7$$


$$v_b(-1) + v_c \left(1 + \frac{1}{2} \right) + v_x(-2) = \frac{4}{2}$$

$$v_b(0) + v_c(1) + v_x(-1) = 4$$


Solving, $v_o = v_b = 1.5 \text{ V}$ Also, $v_c = 9 \text{ V}$ and $v_x = 5 \text{ V}$.

3. (20 pts): (suggested time: 15 minutes)

Find the Thevenin equivalent with respect to the terminals a,b for the circuit shown below. :

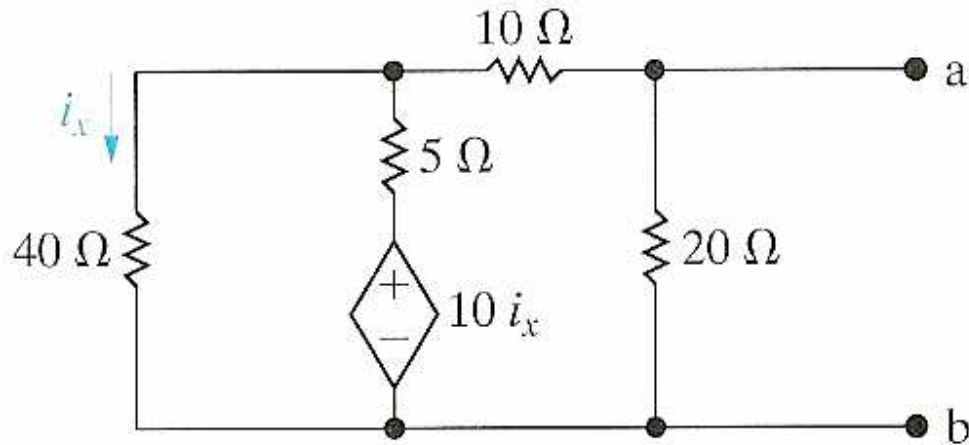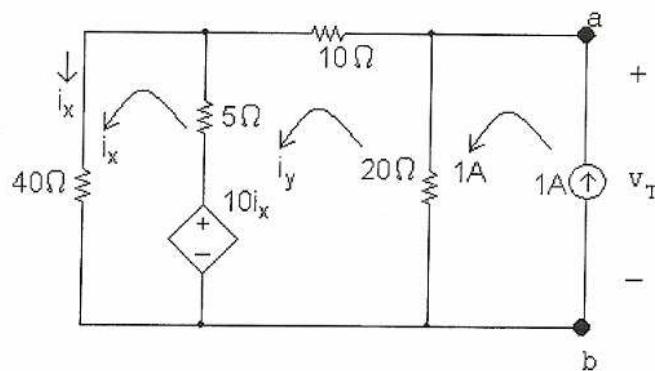**Solution :**

$V_{Th} = 0$ since there are no independent sources in the circuit. To find R_{Th} , apply a 1 A test source and calculate the voltage drop across the test source. Use the mesh current method.



The mesh current equations for the two meshes on the left:

$$-10i_x + 5(i_x - i_y) + 40i_x = 0$$

$$10i_x + 20(i_y - 1) + 10i_y + 5(i_y - i_x) = 0$$

Place these equations in standard form:

$$i_x(-10 + 5 + 40) + i_y(-5) = 0$$


$$i_x(10 - 5) + i_y(20 + 10 + 5) = 20$$

Solving, $i_x = 80 \text{ mA}$; $i_y = 560 \text{ mA}$

Find the voltage drop across the 1 A source:

$$v_T = 20(1 - 0.56) = 8.8 \text{ V}$$
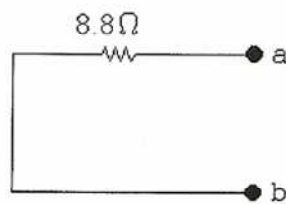
$$\therefore R_{Th} = v_T / 1 \text{ A} = 8.8 / 1 = 8.8 \Omega$$




4. (25 pts): (suggested time: 20 minutes)

The signal voltage v_g in the circuit shown in figure below is described by the following equations:

$$v_g = 0 \quad t \leq 0,$$

$$v_g = 10\sin(\pi/3)t \text{ V}, \quad 0 \leq t \leq \infty$$

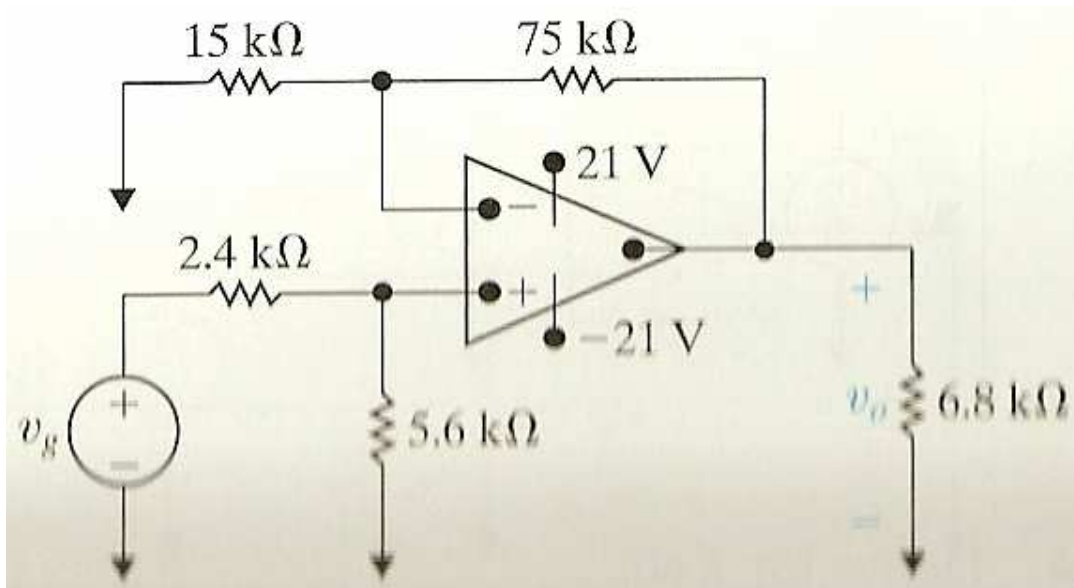Sketch v_o versus t , assuming the op-amp is ideal.



Solution :

$$v_p = \frac{5.6}{8.0} v_g = 0.7 v_g = 7 \sin(\pi/3)t \text{ V}$$

$$\frac{v_n}{15,000} + \frac{v_n - v_o}{75,000} = 0$$

$$6v_n = v_o; \quad v_n = v_p$$

$$\therefore v_o = 42 \sin(\pi/3)t \text{ V} \quad 0 \leq t \leq \infty$$

$$v_o = 0 \quad t \leq 0$$

At saturation

$$42 \sin\left(\frac{\pi}{3}\right)t = \pm 21; \quad \sin \frac{\pi}{3}t = \pm 0.5$$

$$\therefore \frac{\pi}{3}t = \frac{\pi}{6}, \quad \frac{5\pi}{6}, \quad \frac{7\pi}{6}, \quad \frac{11\pi}{6}, \quad \text{etc.}$$

$$t = 0.50 \text{ s}, \quad 2.50 \text{ s}, \quad 3.50 \text{ s}, \quad 5.50 \text{ s}, \quad \text{etc.}$$

