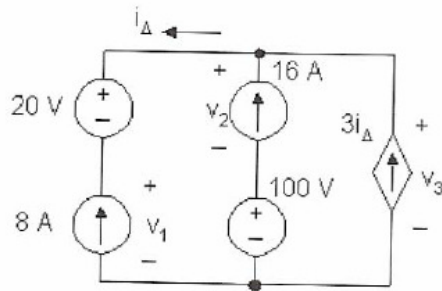


ECE2A SPRING-2008
Homework#2 Solutions

1.)

- [a] Yes, Kirchhoff's laws are not violated. (Note that $i_{\Delta} = -8$ A.)
- [b] No, because the voltages across the independent and dependent current sources are indeterminate. For example, define v_1 , v_2 , and v_3 as shown:



Kirchhoff's voltage law requires

$$v_1 + 20 = v_3$$

$$v_2 + 100 = v_3$$

Conservation of energy requires

$$-8(20) - 8v_1 - 16v_2 - 16(100) + 24v_3 = 0$$

or

$$v_1 + 2v_2 - 3v_3 = -220$$

Now arbitrarily select a value of v_3 and show the conservation of energy will be satisfied. Examples:


If $v_3 = 200$ V then $v_1 = 180$ V and $v_2 = 100$ V. Then

$$180 + 200 - 600 = -220 \text{ (CHECKS)}$$

If $v_3 = -100$ V, then $v_1 = -120$ V and $v_2 = -200$ V. Then

$$-120 - 400 + 300 = -220 \text{ (CHECKS)}$$

2.)

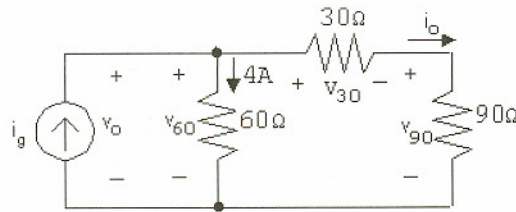

[a] Write a KVL equation clockwise around the right loop:

$$-v_{60} + v_{30} + v_{90} = 0$$

From Ohm's law,

$$v_{60} = (60 \Omega)(4 \text{ A}) = 240 \text{ V}, \quad v_{30} = 30i_o, \quad v_{90} = 90i_o$$

Substituting,

$$-240 \text{ V} + 30i_o + 90i_o = 0 \quad \text{so} \quad 120i_o = 240 \text{ V}$$

$$\text{Thus} \quad i_o = \frac{240 \text{ V}}{120} = 2 \text{ A}$$

Now write a KCL equation at the top middle node, summing the currents leaving:

$$-i_g + 4 \text{ A} + i_o = 0 \quad \text{so} \quad i_g = 4 \text{ A} + 2 \text{ A} = 6 \text{ A}$$

[b] Write a KVL equation clockwise around the left loop:

$$-v_o + v_{60} = 0 \quad \text{so} \quad v_o = v_{60} = 240 \text{ V}$$

[c] Calculate power using $p = vi$ for the source and $p = Ri^2$ for the resistors:

$$p_{\text{source}} = -v_o i_g = -(240 \text{ V})(6 \text{ A}) = -1440 \text{ W}$$

$$p_{60\Omega} = 4^2(60) = 960 \text{ W}$$


$$p_{30\Omega} = 30i_o^2 = (30)2^2 = 120 \text{ W}$$

$$p_{90\Omega} = 90i_o^2 = (90)2^2 = 360 \text{ W}$$

$$\sum P_{\text{dev}} = 1440 \text{ W} \quad \sum P_{\text{abs}} = 960 + 120 + 360 = 1440 \text{ W}$$

3.)


[a] Plot v_t

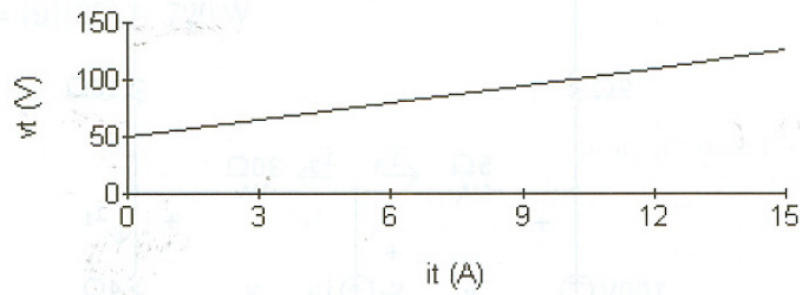


From the plot:

$$R = \frac{\Delta v}{\Delta i} = \frac{(125 - 50)}{(15 - 0)} = 5 \Omega$$

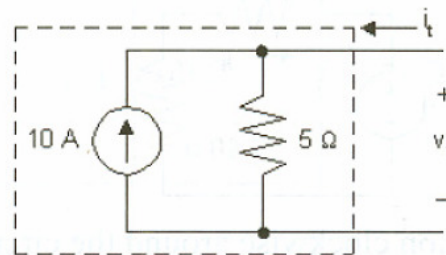When $i_t = 0$, $v_t = 50$ V; therefore the ideal current source has a current of 10 A



[b]

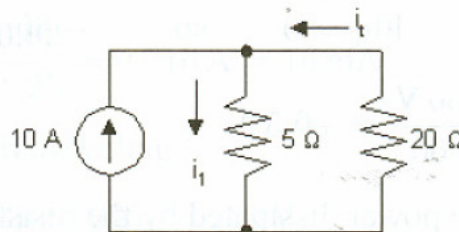

$$10 + i_t = i_1 \quad \text{and} \quad 5i_1 = -20i_t$$

Therefore, $10 + i_t = -4i_t$ so $i_t = -2$ A

4.)

[a] Start with the $22.5\ \Omega$ resistor. Since the voltage drop across this resistor is 90 V , we can use Ohm's law to calculate the current:

$$i_{22.5\ \Omega} = \frac{90\text{ V}}{22.5\ \Omega} = 4\text{ A}$$

Next we can calculate the voltage drop across the $15\ \Omega$ resistor by writing a KVL equation around the outer loop of the circuit:

$$-240\text{ V} + 90\text{ V} + v_{15\ \Omega} = 0 \quad \text{so} \quad v_{15\ \Omega} = 240 - 90 = 150\text{ V}$$

Now that we know the voltage drop across the $15\ \Omega$ resistor, we can use Ohm's law to find the current in this resistor:

$$i_{15\ \Omega} = \frac{150\text{ V}}{15\ \Omega} = 10\text{ A}$$

Write a KCL equation at the middle right node to find the current through the $5\ \Omega$ resistor. Sum the currents entering:

$$4\text{ A} - 10\text{ A} + i_{5\ \Omega} = 0 \quad \text{so} \quad i_{5\ \Omega} = 10\text{ A} - 4\text{ A} = 6\text{ A}$$

Write a KVL equation clockwise around the upper right loop, starting below the $4\ \Omega$ resistor. Use Ohm's law to express the voltage drop across the resistors in terms of the current through the resistors:

$$-v_{4\ \Omega} + 90\text{ V} + (5\ \Omega)(-6\text{ A}) = 0 \quad \text{so} \quad v_{4\ \Omega} = 90\text{ V} - 30\text{ V} = 60\text{ V}$$

Using Ohm's law we can find the current through the $4\ \Omega$ resistor:

$$i_{4\ \Omega} = \frac{60\text{ V}}{4\ \Omega} = 15\text{ A}$$

Write a KCL equation at the middle node. Sum the currents entering:


$$15\text{ A} - 6\text{ A} - i_{20\ \Omega} = 0 \quad \text{so} \quad i_{20\ \Omega} = 15\text{ A} - 6\text{ A} = 9\text{ A}$$

Use Ohm's law to calculate the voltage drop across the $20\ \Omega$ resistor:

$$v_{20\ \Omega} = (20\ \Omega)(9\text{ A}) = 180\text{ V}$$

All of the volta

in the figure below:

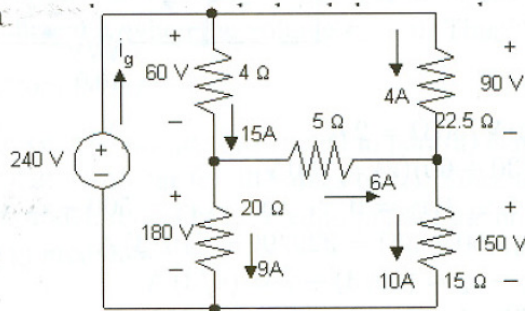

Calculate the power dissipated by the resistors using the equation $p_R = Ri_R^2$:

$$p_{4\ \Omega} = (4)(15)^2 = 900\text{ W} \quad p_{20\ \Omega} = (20)(9)^2 = 1620\text{ W}$$

$$p_{5\ \Omega} = (5)(6)^2 = 180\text{ W} \quad p_{22.5\ \Omega} = (22.5)(4)^2 = 360\text{ W}$$

$$p_{15\ \Omega} = (15)(10)^2 = 1500\text{ W}$$

[b] We can calculate the current in the voltage source, i_g by writing a KCL equation at the top middle node:

$$i_g = 15 \text{ A} + 4 \text{ A} = 19 \text{ A}$$

Now that we have both the voltage and the current for the source, we can calculate the power supplied by the source:

$$p_g = -240(19) = -4560 \text{ W} \quad \text{thus} \quad p_g \text{ (supplied)} = 4560 \text{ W}$$

[c] $\sum P_{\text{dis}} = 900 + 1620 + 180 + 360 + 1500 = 4560 \text{ W}$


Therefore,

$$\sum P_{\text{supp}} = \sum P_{\text{dis}}$$

5.)

[a] $i_o = 0$ because no current can exist in a single conductor connecting two parts of a circuit.

[b]

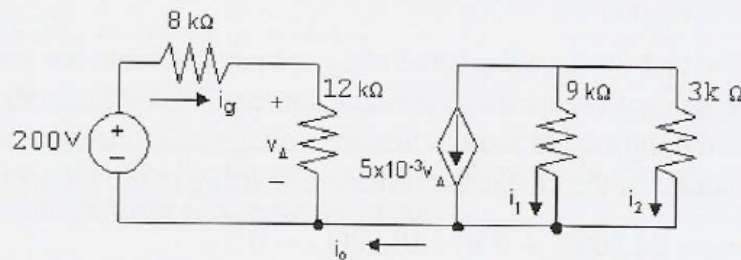

$$-200 + 8000i_g + 12,000i_g = 0 \quad \text{so} \quad i_g = 200/20,000 = 10 \text{ mA}$$

$$v_{\Delta} = (12 \times 10^3)(10 \times 10^{-3}) = 120 \text{ V}$$

$$5 \times 10^{-3}v_{\Delta} = 0.6 \text{ A}$$

$$9000i_1 = 3000i_2 \quad \text{so} \quad i_2 = 3i_1$$

$$0.6 + i_1 + i_2 = 0 \quad \text{so} \quad 0.6 + i_1 + 3i_1 = 0 \quad \text{thus} \quad i_1 = -0.15 \text{ A}$$

[c] $i_2 = 3i_1 = -0.45 \text{ A}$

6.)

[a] $5 \parallel 20 = 100/25 = 4 \Omega$ $5 \parallel 20 + 9 \parallel 18 + 10 = 20 \Omega$
 $9 \parallel 18 = 162/27 = 6 \Omega$ $20 \parallel 30 = 600/50 = 12 \Omega$
 $R_{ab} = 5 + 12 + 3 = 20 \Omega$

[b] $5 + 15 = 20 \Omega$ $30 \parallel 20 = 600/50 = 12 \Omega$
 $20 \parallel 60 = 1200/80 = 15 \Omega$ $3 \parallel 6 = 18/9 = 2 \Omega$
 $15 + 10 = 25 \Omega$ $3 \parallel 6 + 30 \parallel 20 = 2 + 12 = 14 \Omega$
 $25 \parallel 75 = 1875/100 = 18.75 \Omega$ $26 \parallel 14 = 364/40 = 9.1 \Omega$
 $18.75 + 11.25 = 30 \Omega$ $R_{ab} = 2.5 + 9.1 + 3.4 = 15 \Omega$

[c] $3 + 5 = 8 \Omega$ $60 \parallel 40 = 2400/100 = 24 \Omega$
 $8 \parallel 12 = 96/20 = 4.8 \Omega$ $24 + 6 = 30 \Omega$
 $4.8 + 5.2 = 10 \Omega$ $30 \parallel 10 = 300/40 = 7.5 \Omega$
 $45 + 15 = 60 \Omega$ $R_{ab} = 1.5 + 7.5 + 1.0 = 10 \Omega$

7.)

[a] $v_{9\Omega} = (1)(9) = 9 \text{ V}$

$$i_{2\Omega} = 9/(2 + 1) = 3 \text{ A}$$

$$i_{4\Omega} = 1 + 3 = 4 \text{ A};$$

$$v_{25\Omega} = (4)(4) + 9 = 25 \text{ V}$$

$$i_{25\Omega} = 25/25 = 1 \text{ A};$$

$$i_{3\Omega} = i_{25\Omega} + i_{9\Omega} + i_{2\Omega} = 1 + 1 + 3 = 5 \text{ A};$$

$$v_{40\Omega} = v_{25\Omega} + v_{3\Omega} = 25 + (5)(3) = 40 \text{ V}$$

$$i_{40\Omega} = 40/40 = 1 \text{ A}$$

$$i_{5\parallel 20\Omega} = i_{40\Omega} + i_{25\Omega} + i_{4\Omega} = 1 + 1 + 4 = 6 \text{ A}$$

$$v_{5\parallel 20\Omega} = (4)(6) = 24 \text{ V}$$

$$v_{32\Omega} = v_{40\Omega} + v_{5\parallel 20\Omega} = 40 + 24 = 64 \text{ V}$$

$$i_{32\Omega} = 64/32 = 2 \text{ A};$$


$$i_{10\Omega} = i_{32\Omega} + i_{5\parallel 20\Omega} = 2 + 6 = 8 \text{ A}$$

$$v_g = 10(8) + v_{32\Omega} = 80 + 64 = 144 \text{ V}.$$

[b] $P_{20\Omega} = \frac{(v_{5\parallel 20\Omega})^2}{20} = \frac{24^2}{20} = 28.8 \text{ W}$

8.)

[a]

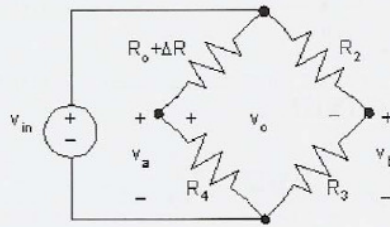

$$v_a = \frac{v_{in} R_4}{R_o + R_4 + \Delta R}$$

$$v_b = \frac{R_3}{R_2 + R_3} v_{in}$$

$$v_o = v_a - v_b = \frac{R_4 v_{in}}{R_o + R_4 + \Delta R} - \frac{R_3}{R_2 + R_3} v_{in}$$

When the bridge is balanced,

$$\frac{R_4}{R_o + R_4} v_{in} = \frac{R_3}{R_2 + R_3} v_{in}$$

$$\therefore \frac{R_4}{R_o + R_4} = \frac{R_3}{R_2 + R_3}$$

$$\begin{aligned} \text{Thus, } v_o &= \frac{R_4 v_{in}}{R_o + R_4 + \Delta R} - \frac{R_4 v_{in}}{R_o + R_4} \\ &= R_4 v_{in} \left[\frac{1}{R_o + R_4 + \Delta R} - \frac{1}{R_o + R_4} \right] \\ &= \frac{R_4 v_{in} (-\Delta R)}{(R_o + R_4 + \Delta R)(R_o + R_4)} \\ &\approx \frac{-(\Delta R) R_4 v_{in}}{(R_o + R_4)^2} \end{aligned}$$

[b] $\Delta R = 0.03 R_o$

$$R_o = \frac{R_2 R_4}{R_3} = \frac{(1000)(5000)}{500} = 10,000 \Omega$$


$$\Delta R = (0.03)(10^4) = 300 \Omega$$

$$\therefore v_o \approx \frac{-300(5000)(6)}{(15,000)^2} = -40 \text{ mV}$$


$$\begin{aligned} \text{[c] } v_o &= \frac{-(\Delta R) R_4 v_{in}}{(R_o + R_4 + \Delta R)(R_o + R_4)} \\ &= \frac{-300(5000)(6)}{(15,300)(15,000)} \\ &= -39.2157 \text{ mV} \end{aligned}$$

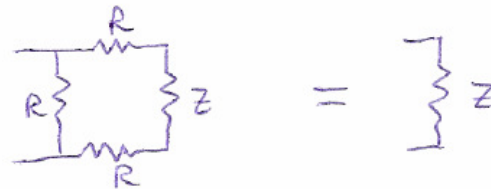9.)

IF ADDING A STEP TO THE LADDER DOES NOT CHANGE THE EFFECTIVE RESISTANCE, THEN ~~THE~~ ^{THE} EQUIVALENT RESISTANCE OF AN ADDED STEP, INCLUDING THE TERMINATION, Z , MUST BE THE SAME AS Z ITSELF:



↓

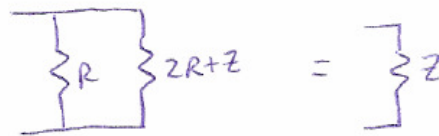

$$\frac{R(2R+Z)}{R+2R+Z} = Z \Rightarrow Z^2 + 2RZ - 2R^2 = 0$$

$$Z = \frac{-2R \pm \sqrt{4R^2 + 8R^2}}{2}$$


SINCE Z MUST BE POSITIVE,

$$\underline{Z = -R + \sqrt{3}R = (\sqrt{3} - 1)R}$$



10.)

FROM SYMMETRY NODES 4+5 MUST BE AT THE SAME POTENTIAL;
 LIKEWISE NODES 3+6 MUST BE AT THE SAME POTENTIAL. SINCE NO CURRENT
 WILL FLOW IN A WIRE CONNECTED BETWEEN NODES AT EQUAL POTENTIAL,
 WE CAN ADD A WIRE BETWEEN NODES 4+5 WITHOUT CHANGING
 THE CIRCUIT, AND LIKEWISE BETWEEN 3+6,

SO THE CIRCUIT BECOMES

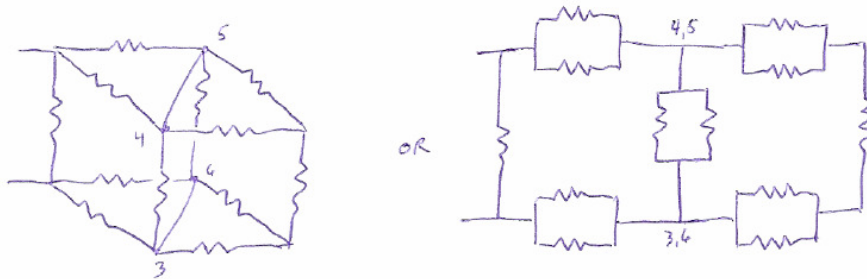

WITH ALL RESISTORS $= R$ THIS REDUCES TO

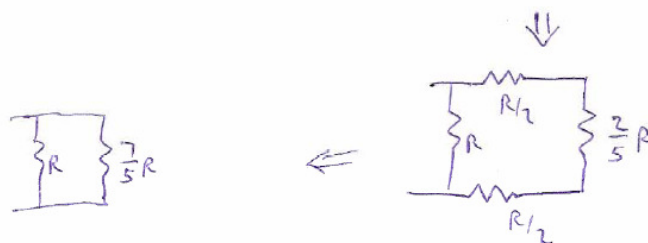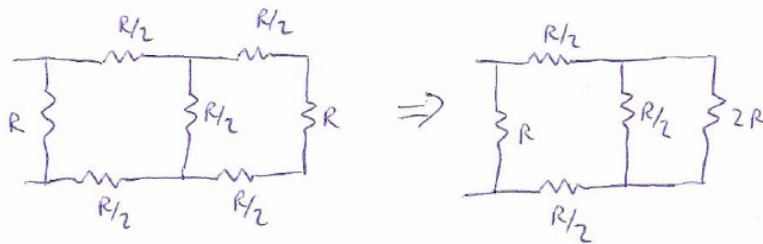

//

$$\underline{\underline{\frac{7}{12} R}}$$