

Problem 1:

[a] $v = L \frac{di}{dt}$

$$\frac{di}{dt} = 18[t(-10e^{-10t}) + e^{-10t}] = 18e^{-10t}(1 - 10t)$$

$$v = (50 \times 10^{-6})(18)e^{-10t}(1 - 10t) \\ = 0.9e^{-10t}(1 - 10t) \text{ mV}, \quad t > 0$$

[b] $p = vi$

$$v(200 \text{ ms}) = 0.9e^{-2}(1 - 2) = -121.8 \mu\text{V}$$

$$i(200 \text{ ms}) = 18(0.2)e^{-2} = 487.2 \text{ mA}$$

$$p(200 \text{ ms}) = (-121.8 \times 10^{-6})(487.2 \times 10^{-3}) = -59.34 \mu\text{W}$$

[c] delivering

[d] $w = \frac{1}{2}Li^2 = \frac{1}{2}(50 \times 10^{-6})(487.2 \times 10^{-3})^2 = 5.93 \mu\text{J}$

[e] The energy is a maximum where the current is a maximum:

$$\frac{di_L}{dt} = 18[t(-10)e^{-10t} + e^{-10t}] = 18e^{-10t}(1 - 10t)$$

$$\frac{di_L}{dt} = 0 \quad \text{when} \quad t = 0.1 \text{ s}$$

$$i_{\max} = 18(0.1)e^{-1} = 662.2 \text{ mA}$$

$$w_{\max} = \frac{1}{2}(50 \times 10^{-6})(662.2 \times 10^{-3})^2 = 10.96 \mu\text{J}$$

Problem 2 :

$$[a] \quad v = \frac{1}{0.5 \times 10^{-6}} \int_0^{500 \times 10^{-6}} 50 \times 10^{-3} e^{-2000t} dt - 20$$

$$= 100 \times 10^3 \frac{e^{-2000t}}{-2000} \Big|_0^{500 \times 10^{-6}} - 20$$

$$= 50(1 - e^{-1}) - 20 = 11.61 \text{ V}$$

$$w = \frac{1}{2} C v^2 = \frac{1}{2} (0.5)(10^{-6})(11.61)^2 = 33.7 \mu\text{J}$$

$$[b] \quad v(\infty) = 50 - 20 = 30 \text{ V}$$

$$w(\infty) = \frac{1}{2} (0.5 \times 10^{-6})(30)^2 = 225 \mu\text{J}$$

Problem 3:

$$5 \parallel (12 + 8) = 4 \text{ H}$$

$$4 \parallel 4 = 2 \text{ H}$$

$$15 \parallel (8 + 2) = 6 \text{ H}$$

$$3 \parallel 6 = 2 \text{ H}$$

$$6 + 2 = 8 \text{ H}$$

Problem 4:

$$\left(\frac{1}{C + C_{eq}} + \frac{1}{C} \right)^{-1} = C_{eq}$$

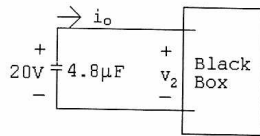
Solving this gives the answer

Problem 5:

$$C_1 = 10 + 2 = 12 \mu\text{F}$$

$$\frac{1}{C_2} = \frac{1}{12 \mu} + \frac{1}{8 \mu} \quad \therefore \quad C_2 = 4.8 \mu\text{F}$$

$$v_o(0) + v_1(0) = -5 + 25 = 20 \text{ V}$$

[a]

$$\begin{aligned} v_2 &= -\frac{1}{4.8 \times 10^{-6}} \int_0^t 1.92 \times 10^{-3} e^{-20x} dx + 20 \\ &= -400 \frac{e^{-20x}}{-20} \bigg|_0^t + 20 \\ &= 20(e^{-20t} - 1) + 20 \\ &= 20e^{-20t} \text{ V}, \quad t \geq 0 \end{aligned}$$

$$\begin{aligned} \text{[b]} \quad v_o &= -\frac{1}{8 \times 10^{-6}} \int_0^t 1.92 \times 10^{-3} e^{-20x} dx - 5 \\ &= -240 \frac{e^{-20x}}{-20} \bigg|_0^t - 5 \\ &= 12(e^{-20t} - 1) - 5 \\ &= 12e^{-20t} - 17 \text{ V}, \quad t \geq 0 \end{aligned}$$

$$\begin{aligned} \text{[c]} \quad v_1 &= -\frac{1}{12 \times 10^{-6}} \int_0^t 1.92 \times 10^{-3} e^{-20x} dx + 25 \\ &= -160 \frac{e^{-20x}}{-20} \bigg|_0^t + 25 \\ &= 8(e^{-20t} - 1) + 25 \\ &= 8e^{-20t} + 17 \text{ V}, \quad t \geq 0 \end{aligned}$$

$$\begin{aligned} \text{[d]} \quad i_1 &= -10 \times 10^{-6} \frac{d}{dt} [8e^{-20t} + 17] \\ &= -10 \times 10^{-6} (-20) 8e^{-20t} \\ &= 1.6e^{-20t} \text{ mA}, \quad t > 0 \end{aligned}$$

$$\begin{aligned} \text{[e]} \quad i_2 &= -2 \times 10^{-6} \frac{d}{dt} [8e^{-20t} + 17] \\ &= -2 \times 10^{-6} (-20) 8e^{-20t} \\ &= 0.32e^{-20t} \text{ mA}, \quad t > 0 \end{aligned}$$

CHECK: $i_1 + i_2 = 1.92e^{-20t} \text{ mA} = i_o$

Problem 6:

$$\text{[a]} \quad v_{ab} = L_1 \frac{d(i_1 - i_2)}{dt} + M \frac{di_2}{dt}$$

$$0 = L_1 \frac{d(i_2 - i_1)}{dt} - M \frac{di_2}{dt} + M \frac{d(i_1 - i_2)}{dt} + L_2 \frac{di_2}{dt}$$

Collecting coefficients of $[di_1/dt]$ and $[di_2/dt]$, the two mesh-current equations become

$$v_{ab} = L_1 \frac{di_1}{dt} + (M - L_1) \frac{di_2}{dt}$$

and

$$0 = (M - L_1) \frac{di_1}{dt} + (L_1 + L_2 - 2M) \frac{di_2}{dt}$$

Solving for $[di_1/dt]$ gives

$$\frac{di_1}{dt} = \frac{L_1 + L_2 - 2M}{L_1 L_2 - M^2} v_{ab}$$

from which we have

$$v_{ab} = \left(\frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} \right) \left(\frac{di_1}{dt} \right)$$

$$L_{ab} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

b] If the magnetic polarity of coil 2 is reversed, the sign of M reverses, therefore

$$L_{ab} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$

Problem 7:

Cap of 2 & 3 mf are in series, so their $C_{eq} = 1.2$ mf.

$Q = CV$, so $Q = 110 \times 1 \times 10^{-3} = 0.11$ C

Since 1 mf & 1.2 mf are in parallel,

0.11 C = 2.2×10^{-3} V

$V = 50$ V

$Q_1 = 50 \times 10^{-3} = 0.05$ C

$Q_{conn} = 0.11 - 0.05 = 0.06$ C.

Problem 8:

With no finger touching and equal 10 pF capacitors

$$v(t) = \frac{10}{20}(v_s(t)) + 0 = 0.5v_s(t)$$

With a finger touching

Let C_e = equivalent capacitance of person touching lamp

$$C_e = \frac{(10)(100)}{110} = 9.091 \text{ pF}$$

Then $C + C_e = 10 + 9.091 = 19.091 \text{ pF}$

$$\therefore v(t) = \frac{10}{29.091}v_s = 0.344v_s$$

$$\therefore \Delta v(t) = (0.5 - 0.344)v_s = 0.156v_s$$