

ECE 2C Mid-Term Exam B Solutions

May 8, 2012

Do not open exam until instructed to.

Closed book: Crib sheet and 1 page personal notes permitted

There are 2 problems on this exam, and you have 75 minutes.

Use any and all reasonable approximations (5% accuracy is fine.), **AFTER STATING and approximately Justifying them.**


Name: _____

Problem	Points Received	Points Possible
1a		10
1b		4
1c		10
1d		15
1e		5
1f		10
1g		10
2a		15
2b		15
2c		5
total		100

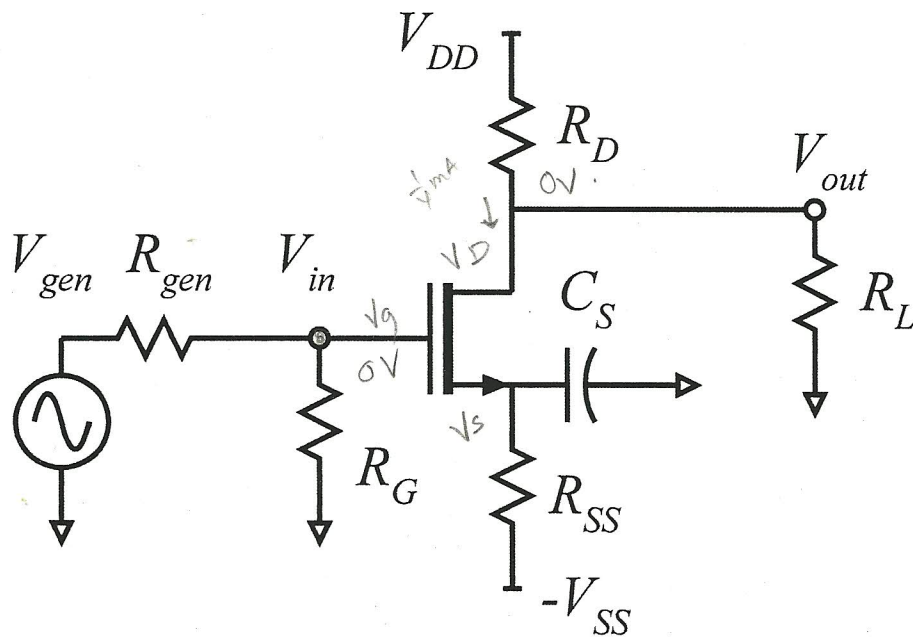Problem 1, 65 points

Transistor circuit analysis

You will be working on the circuit below:



Q1 is a mobility-limited FET, ie. $I_d = (\mu C_{ox} W_g / 2L_g)(V_{gs} - V_{th})^2(1 + \lambda V_{ds})$ where $(\mu C_{ox} W_g / 2L_g) = 4 \text{ mA/V}^2$, $\lambda = 0.1 \text{ V}^{-1}$, and $V_{th} = 0.5 \text{ V}$.

$V_{DD} = +4.0 \text{ Volts}$, $-V_{SS} = -4 \text{ Volts}$

C_S is very big and has negligible AC impedance.

$R_L = 10 \text{ kOhm}$, $R_{gen} = 100 \text{ kOhm}$, $R_G = 900 \text{ kOhm}$

Part a, 10 points

DC bias.

Q1 is to be biased with $1/4$ mA drain current.

The drain of Q1 is to be biased at 0.0 Volts

Ignore λ while solving this part

Find: $R_{SS} = \underline{13 \text{ k}\Omega}$ $R_D = \underline{16 \text{ k}\Omega}$

$$I_d = \frac{\mu C_{ox} W}{2L} (V_{gs} - V_{th})^2 (1 + \lambda V_{ds}) = \frac{1}{4} \text{ mA}$$


4 mA/V^2

$$\frac{1}{4} \text{ mA} = \frac{4 \text{ mA}}{\text{V}^2} (V_{gs} - 0.5)^2$$

$$V_{gs} = 0.75 \text{ V}$$

$$R_{SS} \left(\frac{1}{4} \text{ mA} \right) = 3.25 \text{ V}$$
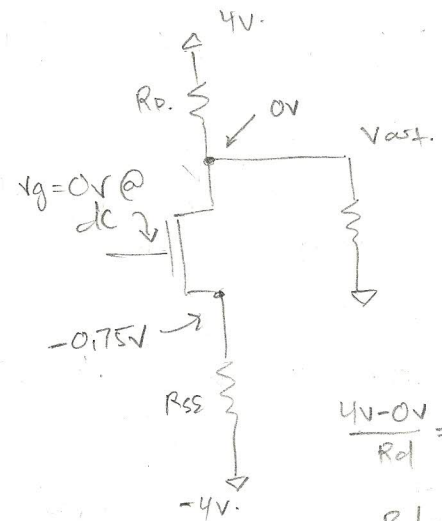
$$\underline{R_{SS} = 13 \text{ k}\Omega}$$




$$\frac{4\text{V} - 0\text{V}}{R_D} = \frac{1}{4} \text{ mA}$$

$$\underline{R_D = 16 \text{ k}\Omega}$$

Part b, 5 points

DC bias

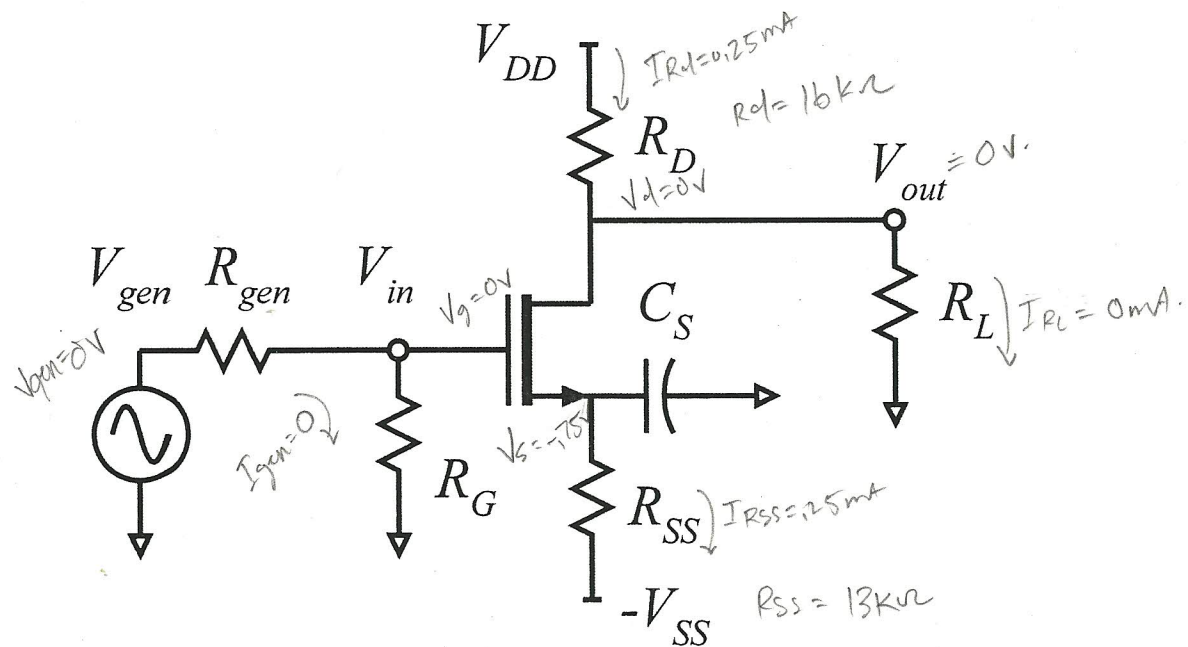

On the circuit diagram above, label the DC voltages at **ALL** nodes and the DC currents through **ALL** resistors

Part c, 10 points

Find the small signal parameters of Q1. Use the mobility-limited model.

$$g_m = 2.15 \text{ mS}$$

$$R_{DS} = 43 \text{ k}\Omega$$


$$I_d = \left(\frac{\mu \cdot C_{ox} \cdot W_g}{2 L_g} \right) (V_{gs} - V_{th})^2 (1 + \lambda V_{ds})$$

$$g_m = \frac{\partial I_d}{\partial V_{gs}} = 2 \left(\frac{\mu C_{ox} W_g}{2 L_g} \right) (V_{gs} - V_{th}) (1 + \lambda V_{ds})$$
$$= 2 (4 \text{ mA/V}^2) (0.75 \text{ V}) (1 + (0.1 \text{ V}^{-1}) (0.75 \text{ V})) = 2.15 \text{ mS}$$

$$R_{ds} = \frac{\partial V_{ds}}{\partial I_d} = \frac{V_{ds} + \frac{1}{\lambda}}{I_d} = \frac{0.75 \text{ V} + \frac{1}{0.1 \text{ V}^{-1}}}{0.0025 \text{ A}} = 43 \text{ k}\Omega$$

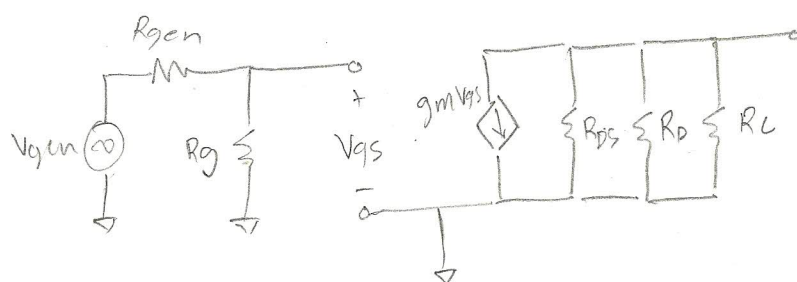Part d, 15 points

Replacing the transistor with its small-signal model, draw a small-signal equivalent circuit diagram for the amplifier. Give values for all elements on the diagram.



$$R_{gen} = 100 \text{ k}\Omega$$

$$R_g = 900 \text{ k}\Omega$$

$$R_L = 10 \text{ k}\Omega$$

$$g_m = 0.00215 \text{ S}$$


$$R_{ds} = 43 \text{ k}\Omega$$

$$R_d = 16 \text{ k}\Omega$$

B-EXAM


problem 1

e. From the small signal model we have:

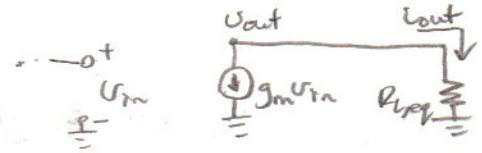

$$\begin{aligned} v_{out} &= -i_{out} R_{L,eq} = -g_m v_{in} (R_D \parallel R_L \parallel R_{os}) \\ &= (-2.105 \text{ mA/V}) (43 \text{ k}\Omega \parallel 16 \text{ k}\Omega \parallel 10 \text{ k}\Omega) v_{in} \\ &= -11.33 v_{in} \Rightarrow \boxed{\frac{v_{out}}{v_{in}} = -11.33 \text{ V/V}} \end{aligned}$$

f.

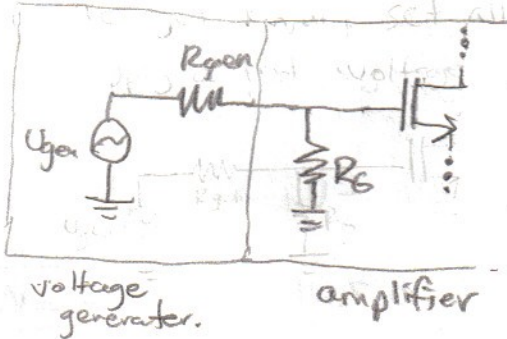

To get R_{in} , pretend the input of the "amplifier" is disconnected from the "voltage generator" circuit, and calculate the resistance seen by the gate.

$$R_{in} = R_G \parallel R_{gate} \quad \text{for MOSFETs } R_{gate} = \infty$$

$$R_{in} = R_G$$

$$\therefore \boxed{R_{in,amp} = 900 \text{ k}\Omega}$$

To find $\frac{v_{in}}{v_{gen}}$ note that R_{gen}, R_G form a voltage divider:

$$\Rightarrow v_{in} = \frac{R_G}{R_G + R_{gen}} v_{gen} \Rightarrow \boxed{\frac{v_{in}}{v_{gen}} = \frac{900 \text{ k}\Omega}{1 \text{ M}\Omega} = 0.9 \text{ V/V}}$$

And finally

$$\frac{v_{out}}{v_{gen}} = \frac{v_{out}}{v_{in}} \cdot \frac{v_{in}}{v_{gen}} = (-11.33)(0.9) = \boxed{-10.2 \text{ V/V} = \frac{v_{out}}{v_{gen}}}$$

B-EXAM

problem 1

9- cutoff $\Rightarrow V_{gs} - V_{th} = 0 \Rightarrow I_d = 0$

As per the lecture notes (BJT common emitter / MOSFET common source);

$$\begin{aligned}\Delta V_{out} &= -R_{Leq} \Delta I_d = -R_{Leq} (0 - I_d) \\ &= (R_L \parallel R_D \parallel R_{os}) I_D = (0.25 \text{ mA})(5.383 \text{ k}\Omega)\end{aligned}$$

$$\boxed{\Delta V_{out} \uparrow = 1.346 \text{ V}}$$

knee voltage $\Rightarrow V_{ds} = V_{gs} - V_{th}$

As per the same lecture notes:

$$\Delta V_{out} = V_d = V_{ds} - V_s = V_{gs} - V_{th} - V_s$$

$$= 0.75 \text{ V} - 0.5 \text{ V} - 0.75 \text{ V} = \boxed{-0.5 \text{ V} = \Delta V_{out}}$$

$$\boxed{\Delta V_{out} \downarrow = 0.5 \text{ V}}$$

Problem 2, 35 points

Small signal analysis, Nodal analysis

Part a, 15 points

In the circuit at right, the transistors both have

$$g_{m1} = g_{m2} = g_m \text{ and}$$



$$R_{CE1} = R_{CE2} = \infty. \text{ Further, } \beta = \infty,$$

so

$$R_{BE1} = R_{BE2} = \infty$$

V_{CC} and $-V_{EE}$ are DC bias voltages, while I_0 is a DC bias current source.

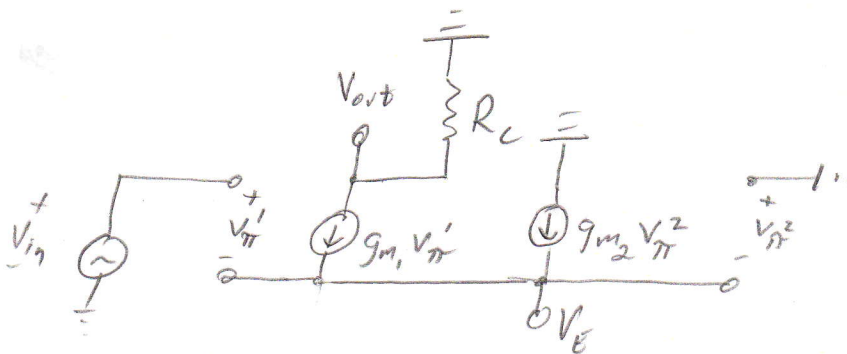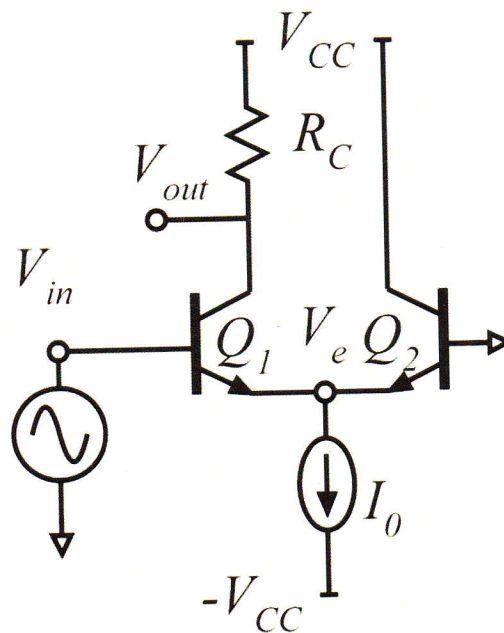Replacing the two transistors with their small-signal models, draw below a small-signal diagram of the circuit. Be sure to label the nodes V_{in} , V_{out} , and V_e in the diagram.



Part b, 15 points

Using nodal analysis, determine an algebraic expression for V_{out}/V_{in}

Nodal equation at V_E : $V_E = g_{m1} V_{in} / (g_{m1} + g_{m2})$

Nodal equation at V_{out} : $V_{out}/R_c + g_{m1} (V_{in} - V_E) = 0$

$V_{out}/V_{in} = -R_c \left(\frac{g_{m1} g_{m2}}{g_{m1} + g_{m2}} \right) = -R_c \left(\frac{g_{m1}^2}{2g_{m1}} \right) = -\frac{R_c g_{m1}}{2}$

$-g_{m2} V_{\pi 2} - g_{m1} V_{\pi 1} = 0$; $V_{\pi 2} = -V_E$; $V_{\pi 1} = V_{in} - V_E$
 $+g_{m2} V_E + g_{m1} (V_E - V_{in}) = 0$

$V_E (g_{m1} + g_{m2}) = g_{m1} V_{in}$ (5 pts)

$V_{out}/R_c + g_{m1} V_{\pi 1} = 0$

$V_{out}/R_c + g_{m1} (V_{in} - V_E) = 0$ (5 pts)

$V_{out}/R_c + g_{m1} V_{in} - g_{m1} \left[\frac{g_{m1} V_{in}}{g_{m1} + g_{m2}} \right] = 0$

$V_{out}/V_{in} = R_c \left[\frac{g_{m1}^2}{g_{m1} + g_{m2}} - g_{m1} \right] = -R_c \left(\frac{g_{m1} g_{m2}}{g_{m1} + g_{m2}} \right)$ (5 pts)

Part C, 5 points

$$R_C = 1 \text{ k}\Omega, g_m = 100 \text{ mS}.$$

Find the numerical value of V_{out}/V_{in} :

$$V_{out}/V_{in} = -50$$