

ECE PS 1 SOLUTIONS

(a) Given:

$$V_T = 0.25 \text{ V}$$

$$\mu_{\text{sat}} \text{ Cox } W_g = 1.0 \text{ mA/V}$$


$$\lambda = 0 \text{ V}^{-1}$$

$$R_{g1} = 1 \text{ M}\Omega$$

$$V_{dd} = 1.0 \text{ V}$$

$$I_d = 0.1 \text{ mA}$$

$$V_{ds} = 0.6 \text{ V}$$

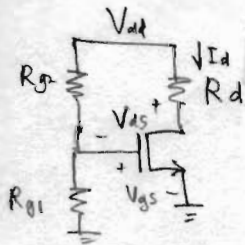

$$I_d = \mu_{\text{sat}} \text{ Cox } W_g (V_{gs} - V_T) (1 + \lambda V_{ds})$$

$$\Rightarrow V_{gs} = V_T + \frac{I_d}{\mu_{\text{sat}} \text{ Cox } W_g (1 + \lambda V_{ds})}$$

$$= 0.25 \text{ V} + \frac{10^{-4} \text{ A}}{(10^{-3} \text{ A/V})(1)}$$

$$= 0.35 \text{ V}$$

$$V_s = 0 \text{ V} \Rightarrow V_g = V_{gs} = 0.35 \text{ V}$$

$$I_{Rg1} = \frac{V_g}{R_{g1}} = \frac{0.35 \text{ V}}{1 \text{ M}\Omega} = 0.35 \mu\text{A}$$

$$I_{Rg2} = \frac{V_{dd} - V_g}{R_{g2}} = I_{Rg1}$$

$$\Rightarrow R_{g2} = \frac{V_{dd} - V_g}{I_{Rg1}} = \frac{1.0 - 0.35}{0.35 \times 10^{-6}} = \boxed{1.86 \text{ M}\Omega = R_{g2}}$$

$$R_d = \frac{V_{dd} - V_d}{I_d} = \frac{1 - 0.6}{1 \text{ mA}} = \boxed{4 \text{ k}\Omega = R_d}$$

(b) $\mu_{\text{sat}} \text{ Cox } W_g$ increased by 10%:

$$\mu_{\text{sat}} \text{ Cox } W_g = 1.1 \text{ mA/V}$$

 V_{gs} remains unchanged

$$I_d = \mu_{\text{sat}} \text{ Cox } W_g (V_{gs} - V_T) (1 + \lambda V_{ds})$$

$$= (0.0011 \text{ A/V})(0.35 \text{ V} - 0.25 \text{ V})(1)$$

$$\boxed{I_d = 0.11 \text{ mA}}$$

$$V_{dd} - V_d = I_d R_d = (0.00011 \text{ A})(4000 \Omega) = \boxed{0.56 \text{ V} = V_{ds}}$$

power supply increased by 10%:

$$V_{dd} = 1.1 \text{ V}$$

$$V_{gs} = \frac{R_{g1}}{R_{g1} + R_{g2}} V_{dd} = \frac{1 \text{ M}\Omega}{1 \text{ M}\Omega + 1.86 \text{ M}\Omega} \times 1.1 \text{ V} = 0.385 \text{ V}$$

$$I_d = \mu_{\text{sat}} \text{ Cox } W_g (V_{gs} - V_T) (1 + \lambda V_{ds})$$

$$= (10^{-3} \text{ A/V})(0.385 - 0.25)(1) = \boxed{0.135 \text{ mA} = I_d}$$

$$V_{dd} - V_d = I_d R_d = (0.135)(4) = \boxed{0.56 \text{ V} = V_{ds}}$$

1c) Given:

$$V_{dd} = 2V$$

$$V_T = 0.25V$$

$$\mu C_{ox} W_g / 2L_g = 1 \text{ mA/V}^2$$

$$\lambda = 0 \text{ V}^{-1}$$

$$I_{Rg1} = I_{Rg2} = 10 \mu A$$

$$I_d = 1 \text{ mA}$$

$$V_{ds} = 0.7V$$

$$I_d = (\mu C_{ox} W_g / 2L_g) (V_{gs} - V_T)^2 (1 + \lambda V_{ds})$$

$$\Rightarrow V_{gs} = V_T + \left(\frac{I_d}{(\mu C_{ox} W_g / 2L_g) (1 + \lambda V_{ds})} \right)^{1/2}$$

$$= 0.25 + \left(\frac{10^{-3}}{(10^{-3}) (1)} \right)^{1/2} = 1.25V \Rightarrow V_{gs} - V_T > V_{ds} \Rightarrow \text{linear mode.}$$

use following eqn. to solve for V_{gs} :

$$I_d = \left(\frac{\mu C_{ox} W_g}{L_g} \right) \left[(V_{gs} - V_T) V_{ds} - \frac{V_{ds}^2}{2} \right]$$

$$1 \text{ mA} = 2(1 \text{ mA/V}^2) \left[(V_{gs} - 0.25) 0.7 - 0.7^2/2 \right] \Rightarrow V_{gs} = 1.31V$$

$$R_{g1} = \frac{V_{gs}}{I_{Rg1}} = \frac{1.31V}{10 \mu A} = 130k\Omega = R_{g1} \quad R_d = \frac{V_{dd} - V_{ds}}{I_d} = \frac{2 - 0.7}{1 \text{ mA}} = 1.3k\Omega = R_d$$

$$R_{g2} = \frac{V_{dd} - V_{gs}}{I_{Rg2}} = \frac{2 - 1.31V}{10 \mu A} = 70k\Omega = R_{g2}$$

1d) Given:

$$V_T = -0.25V$$

$$\mu_{sat} C_{ox} W_g = 0.3 \text{ mA/V}$$

$$V_{ss} = 1V$$

$$I_{Rg1} = I_{Rg2} = 2 \mu A$$

$$I_d = 100 \mu A$$

$$V_s = 0.9V$$

$$V_d = 0.1V$$

$$I_d = \mu_{sat} C_{ox} W_g (-V_{gs} + V_T) (1 + \lambda V_{ds})$$

$$\Rightarrow V_{gs} = V_T - \frac{I_d}{(\mu_{sat} C_{ox} W_g) (1 + \lambda V_{ds})}$$

$$= -0.25 - \frac{100 \times 10^{-6}}{3 \times 10^{-4}} = -0.58V$$

$$V_g = V_{gs} + V_s = -0.58 + 0.9 = 0.32V$$

$$R_{g1} = \frac{V_g}{I_{Rg1}} = \frac{0.32}{2 \times 10^{-6}} = 160k\Omega = R_{g1}$$

$$R_{g2} = \frac{V_{ss} - V_g}{I_{Rg2}} = \frac{1 - 0.32}{2 \times 10^{-6}} = 340k\Omega = R_{g2}$$

$$R_s = \frac{V_{ss} - V_s}{I_d} = \frac{1 - 0.9}{10^{-4}} = 1k\Omega = R_s$$

$$R_d = \frac{V_d}{I_d} = \frac{0.1}{10^{-4}} = 1k\Omega = R_d$$

2a) Given:

$$\beta = 100$$

$$V_{CC} = 3.3V$$

$$V_C = 2.5V$$

$$V_E = 1V$$

$$I_{R_{b2}} = 100\mu A$$

$$I_C = 1mA$$

$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{3.3 - 2.5}{10^{-3}} = \boxed{800\Omega = R_C}$$

$$I_B = \frac{I_C}{\beta} = \frac{10^{-3}A}{100} = 0.01mA$$

$$I_E = (\beta + 1) I_B = 1.01mA$$

$$R_{EE} = \frac{V_E}{I_E} = \frac{1}{1.01 \times 10^{-3}} = \boxed{990\Omega = R_{EE}}$$


$$V_B = V_{BE} + V_E = 0.7 + 1 = 1.7V$$

$$R_{b2} = \frac{V_B}{I_{R_{b2}}} = \frac{1.7}{10^{-4}} = \boxed{17k\Omega = R_{b2}}$$

$$I_{R_{b1}} = I_B + I_{R_{b2}} = 100\mu A + 0.01mA = 110\mu A$$

$$R_{b1} = \frac{V_{CC} - V_B}{I_{R_{b1}}} = \frac{3.3 - 1.7}{110 \times 10^{-6}} = \boxed{14.5k\Omega = R_{b1}}$$

2b) $\beta = 200$:

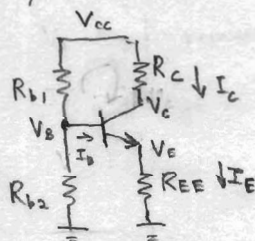

Nodal analysis at V_B :

$$\frac{V_B - V_{CC}}{R_{b1}} + I_B + \frac{V_B}{R_{b2}} = 0 \quad \text{--- (1)}$$

Assuming $V_{BE(on)} = 0.7V$

$$V_B = V_{BE} + V_E = V_{BE(on)} + (\beta + 1) I_B R_{EE} \quad \text{--- (2)}$$

Plugging (2) into (1) gives:

$$\left[V_{BE(on)} + (\beta + 1) I_B R_{EE} \right] \left(\frac{1}{R_{b1}} + \frac{1}{R_{b2}} \right) + I_B - \frac{V_{CC}}{R_{b1}} = 0$$

Solving for I_B gives $I_B = 5.23\mu A$

$$V_C = V_{CC} - \beta I_B R_C = 3.3 - (200)(5.23 \times 10^{-6})(800) = \boxed{2.46V = V_C}$$

$$V_E = (\beta + 1) I_B R_{EE} = (201)(5.23 \times 10^{-6})(990) = 1.04V$$

$$V_B = V_{BE(on)} + (\beta + 1) I_B R_{EE} = 0.7 + (201)(5.23 \times 10^{-6})(990) = 1.74V$$

$$V_{BE} > 0$$

$\Rightarrow$ forward active mode

$$V_{BC} < 0$$

$$I_C = \beta I_B = (200)(5.23 \times 10^{-6}) = \boxed{1.046mA = I_C}$$

2b) V_{CC} increased by 10%:

$$V_{CC} = 3.63 \text{ V.}$$

Using similar analysis as in previous part, we get

$$\left[V_{BE(on)} + (\beta + 1) I_B R_{EE} \right] \left(\frac{1}{R_{b1}} + \frac{1}{R_{b2}} \right) + I_B - \frac{V_{CC}}{R_{b2}} = 0$$

$$\Rightarrow I_B = 11.68 \mu\text{A}$$

$$V_C = V_{CC} - \beta I_B R_C = 3.63 - (100)(11.68 \times 10^{-6})(800) = \boxed{2.42 \text{ V} = V_C}$$

$$V_E = (\beta + 1) I_B R_{EE} = (101)(11.68 \times 10^{-6})(990) = 1.17 \text{ V}$$

$$V_B = V_{BE(on)} + (\beta + 1) I_B R_{EE} = 0.7 + (101)(11.68 \times 10^{-6})(990) = 1.89 \text{ V}$$

$$V_{BE} > 0$$

$$V_{BC} < 0 \Rightarrow \text{fwd active mode}$$

$$I_C = \beta I_B = \boxed{1.168 \text{ mA} = I_C}$$

2c) Given:

$$\beta = 300$$

$$V_{EE} = 5 \text{ V}$$

$$V_C = 2 \text{ V}$$

$$V_E = 3 \text{ V}$$

$$I_C = 0.1 \text{ mA}$$

$$I_{R_{b2}} = 10 \mu\text{A}$$

$$I_B = \frac{I_C}{\beta} = \frac{10^{-4} \text{ A}}{300} = 0.33 \mu\text{A}$$

$$R_{EE} = \frac{V_{EE} - V_E}{(\beta + 1) I_B} = \frac{5 - 3}{(301)(0.33 \times 10^{-6})} = \boxed{20 \text{ k}\Omega = R_{EE}}$$

$$R_C = \frac{V_C}{I_C} = \frac{2}{10^{-4}} = \boxed{20 \text{ k}\Omega = R_C}$$

$$V_B = V_E - V_{EB} = 3 - 0.7 = 2.3 \text{ V}$$

$$R_{b2} = \frac{V_{EE} - V_B}{I_{R_{b2}}} = \frac{5 - 2.3}{10^{-5}} = \boxed{270 \text{ k}\Omega = R_{b2}}$$

$$I_{R_{b1}} = I_{R_{b2}} - I_B = 10 \mu\text{A} - 0.33 \mu\text{A} = 9.67 \mu\text{A}$$

$$R_{b1} = \frac{V_B}{I_{R_{b1}}} = \frac{2.3}{9.67 \times 10^{-6}} = \boxed{240 \text{ k}\Omega = R_{b1}}$$