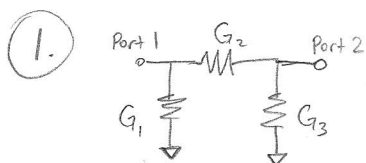


ECE 2C HW #3 Solutions Spring 2012



- a) Compute the 2-port Y parameters
b) Compute the 2-port Z parameters


$$\begin{aligned} G_1 &= 1 \text{ nS} \\ G_2 &= 4 \text{ mS} \\ G_3 &= 3 \text{ mS} \end{aligned}$$



$$R_1 = \frac{1}{G_1} = 1 \times 10^9 \Omega$$

$$R_2 = \frac{1}{G_2} = 250 \Omega$$


$$R_3 = \frac{1}{G_3} = 333 \Omega$$

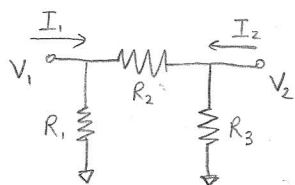

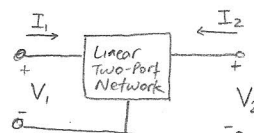- a) G is the electrical conductance of a circuit element.

For resistors, like in this problem, $G = \frac{1}{R} = \frac{I}{V}$.

For a linear 2-port network, we want to relate V_1, I_1, V_2 , and I_2 .



$$\begin{cases} I_1 = Y_{11}V_1 + Y_{12}V_2 \\ I_2 = Y_{21}V_1 + Y_{22}V_2 \end{cases} \quad \text{or, in matrix form, } \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Now we want to find the Y parameters.

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{\frac{V_1}{R_1 \parallel R_2}}{V_1} = \frac{1}{R_1 \parallel R_2} = G_1 + G_2 \approx \underline{4 \text{ mS}}$$

$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = \frac{-\frac{V_2}{R_2}}{V_2} = -\frac{1}{R_2} = -G_2 = \underline{-4 \text{ mS}}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \frac{-\frac{V_1}{R_2}}{V_1} = -\frac{1}{R_2} = -G_2 = \underline{-4 \text{ mS}}$$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{\frac{V_2}{R_2 \parallel R_3}}{V_2} = \frac{1}{R_2 \parallel R_3} = G_2 + G_3 = \underline{7 \text{ mS}}$$

$$\Rightarrow Y = \begin{bmatrix} 4 & -4 \\ -4 & 7 \end{bmatrix} \text{ mS}$$


- b) To find the Z parameters, we could repeat the process in part (a) using

$$\begin{cases} V_1 = Z_{11}I_1 + Z_{12}I_2 \\ V_2 = Z_{21}I_1 + Z_{22}I_2 \end{cases} \Leftrightarrow \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

or, we could note that $\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}^{-1}$.

$$\Rightarrow Z = \begin{bmatrix} \frac{1}{3} & \frac{1}{3} \\ \frac{1}{3} & \frac{1}{3} \end{bmatrix} \text{ k}\Omega$$

2.

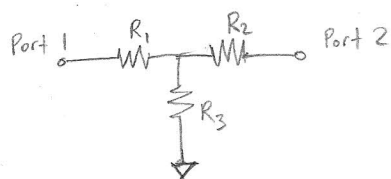

- a) Compute the 2-port Y parameters.
b) Compute the 2-port Z parameters.

$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 2 \text{ k}\Omega$$

$$R_3 = 6 \text{ k}\Omega$$

a) Same approach as problem 1.

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{1}{R_1 + (R_2 \parallel R_3)} = \frac{1}{2.5 \text{ k}\Omega} = 0.4 \text{ mS}$$

$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = \left. \frac{-V_A}{R_1} \right|_{V_1=0} = -\frac{1}{R_1} \left(\frac{R_1 \parallel R_3}{R_2 + (R_1 \parallel R_3)} \right) = -0.3 \text{ mS}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \left. \frac{-V_A}{R_2} \right|_{V_1=0} = -\frac{1}{R_2} \left(\frac{R_2 \parallel R_3}{R_1 + (R_2 \parallel R_3)} \right) = -0.3 \text{ mS}$$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{1}{R_2 + (R_1 \parallel R_3)} = \frac{1}{2.86 \text{ k}\Omega} = 0.35 \text{ mS}$$

$$Y = \begin{bmatrix} 0.4 & -0.3 \\ -0.3 & 0.35 \end{bmatrix} \text{ mS}$$

b) Same approach as problem 1.

$$Z = Y^{-1} = \begin{bmatrix} 0.4 & -0.3 \\ -0.3 & 0.35 \end{bmatrix}^{-1}$$

$$Z = \begin{bmatrix} 7 & 6 \\ 6 & 8 \end{bmatrix} \text{ k}\Omega$$

③. At a signal frequency of 1 GHz, find the Y parameters.

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


Note that this circuit is identical to the one in problem 1, except with capacitors and inductor instead of resistors. So, we can use the same equations, just replacing G (conductance) with Y (admittance).

$$\begin{aligned} Y_{11} &= Y_1 + Y_2 = Y_{C_1} + Y_L \\ &= j2\pi \text{ mS} + \frac{1}{j2\pi} \text{ S} \\ &\approx j(6.28) - j(159.16) \text{ mS} \approx \underline{-j152.9 \text{ mS}} \end{aligned}$$

$$\begin{aligned} Y_{12} &= Y_{21} = -Y_2 = -Y_L \\ &= -\frac{1000}{j2\pi} \text{ mS} \approx \underline{-j159.16 \text{ mS}} \end{aligned}$$

$$\begin{aligned} Y_{22} &= Y_2 + Y_3 = Y_L + Y_{C_2} \\ &= \frac{1000}{j2\pi} \text{ mS} + j4\pi \text{ mS} \\ &\approx \underline{-j146.6 \text{ mS}} \end{aligned}$$
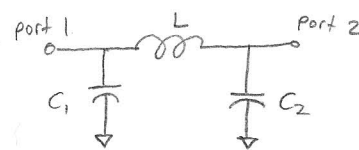
$$Y \approx \begin{bmatrix} -j(153) & -j(159) \\ -j(159) & -j(147) \end{bmatrix} \text{ mS}$$



$$\begin{aligned} C_1 &= 1 \text{ pF} \\ C_2 &= 2 \text{ pF} \\ L &= 1 \text{ nH} \end{aligned}$$

$$\begin{aligned} Z_{C_1} &= \frac{1}{j\omega C_1} = \frac{1}{j2\pi(1\text{GHz})(1\text{pF})} \\ &= \frac{1}{j2\pi} \text{ k}\Omega \end{aligned}$$


$$\begin{aligned} Z_{C_2} &= \frac{1}{j\omega C_2} = \frac{1}{j2\pi(1\text{GHz})(2\text{pF})} \\ &= \frac{1}{j4\pi} \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} Z_L &= j\omega L = j2\pi(1\text{GHz})(1\text{nH}) \\ &= j2\pi \Omega \end{aligned}$$

$$Y_1 = Y_{C_1} = \frac{1}{Z_{C_1}} = j2\pi \text{ mS}$$


$$Y_3 = Y_{C_2} = \frac{1}{Z_{C_2}} = j4\pi \text{ mS}$$
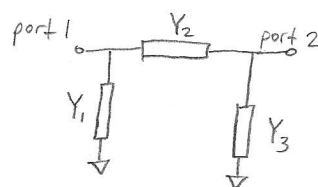
$$Y_2 = Y_L = \frac{1}{Z_L} = \frac{1}{j2\pi} \text{ S} = \frac{1000}{j2\pi} \text{ mS}$$



same as problem 1!

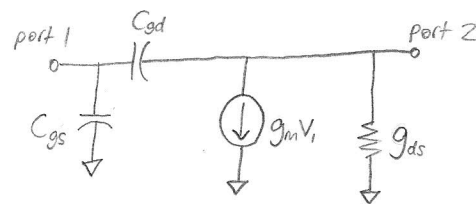4. Simple FET model. (a) As a function of frequency, find algebraic expressions for the Y parameters. If $C_{gs} = 1 \text{ pF}$, $C_{gd} = 0.1 \text{ pF}$, $g_m = 100 \text{ mS}$, $g_{ds} = 1 \text{ mS}$, make plots of the real and imaginary parts as a function of frequency. (b) Now setting $C_{gd} = 0 \text{ fF}$, compute an algebraic expression of H_{21} as a function of frequency.



$$a) \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad \text{Ground port 2} \Rightarrow \begin{array}{c} I_1 \rightarrow \\ V_1 \text{ --- } C_{gs} \text{ --- } \downarrow \\ \quad \quad \quad \downarrow C_{gd} \end{array} \quad C_{gs} + C_{gd} \text{ in parallel.} \Rightarrow Z_{eq} = \frac{1}{j\omega(C_{gs} + C_{gd})}$$

$$= \frac{I_1}{V_1} \left(\frac{V_1}{Z_{Cgs \parallel Cgd}} \right) = \frac{1}{Z_{Cgs \parallel Cgd}} = Y_{Cgs \parallel Cgd}$$

$$= \underline{j\omega(C_{gs} + C_{gd})}$$

$$Y_{eq} = j\omega(C_{gs} + C_{gd})$$

$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad \text{Ground port 1} \Rightarrow \begin{array}{c} I_1 \rightarrow \\ \downarrow C_{gd} \text{ --- } V_2 \\ \quad \quad \downarrow \end{array} \Rightarrow \begin{array}{c} I_1 \rightarrow \\ \downarrow C_{gd} \text{ --- } V_2 \end{array}$$

$$= \frac{1}{V_2} \left(\frac{-V_2}{Z_{Cgd}} \right) = -Y_{Cgd}$$

$$= \underline{-j\omega C_{gd}} \quad Y_{Cgd} = j\omega C_{gd}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} \quad \text{Ground port 2} \Rightarrow \begin{array}{c} V_1 \text{ --- } C_{gd} \text{ --- } \downarrow I_2 \\ \quad \quad \downarrow C_{gs} \end{array} \Rightarrow \begin{array}{c} V_1 \text{ --- } C_{gd} \text{ --- } \text{Node A} \\ \quad \quad \downarrow g_m V_1 \end{array}$$


$$= \underline{g_m - j\omega C_{gd}} \quad \text{b/c KCL at Node A:}$$

$$I_2 + \frac{V_1 - 0}{Z_{Cgd}} - g_m V_1 = 0$$

$$I_2 = g_m V_1 - V_1 Y_{Cgd} = (g_m - j\omega C_{gd}) V_1$$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} \quad \text{Ground port 1} \Rightarrow \begin{array}{c} \downarrow C_{gd} \text{ --- } V_2 \\ \quad \quad \downarrow g_m V_1 \\ \quad \quad \downarrow g_{ds} \end{array}$$
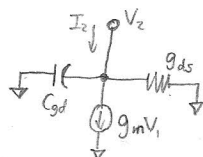
$$= \underline{g_{ds} + j\omega C_{gd}}$$



$$\text{KCL: } I_2 + \frac{0 - V_2}{Z_{Cgd}} + \frac{0 - V_2}{R_{ds}} - g_m V_1 = 0$$

$$I_2 = Y_{Cgd} V_2 + g_{ds} V_2$$

$$= (g_{ds} + j\omega C_{gd}) V_2$$

$$Y = \begin{bmatrix} j\omega(C_{gs} + C_{gd}) & -j\omega C_{gd} \\ g_m - j\omega C_{gd} & g_{ds} + j\omega C_{gd} \end{bmatrix} S$$

$$\text{where } \omega = 2\pi f$$

$$\text{real}(Y_{11}) = 0 \quad \text{imag}(Y_{11}) = \omega(C_{gs} + C_{gd})$$

$$\text{real}(Y_{12}) = 0 \quad \text{imag}(Y_{12}) = -\omega C_{gd}$$

$$\text{real}(Y_{21}) = 0 \quad \text{imag}(Y_{21}) = -\omega C_{gd}$$



$$\text{real}(Y_{22}) = 0 \quad \text{imag}(Y_{22}) = \omega C_{gd}$$

$$C_{gs} = 1 \times 10^{-12} \text{ F}$$


$$C_{gd} = 0.1 \times 10^{-12} \text{ F}$$

$$G_m = 0.1 \text{ S}$$

$$G_{ds} = 0.001 \text{ S}$$

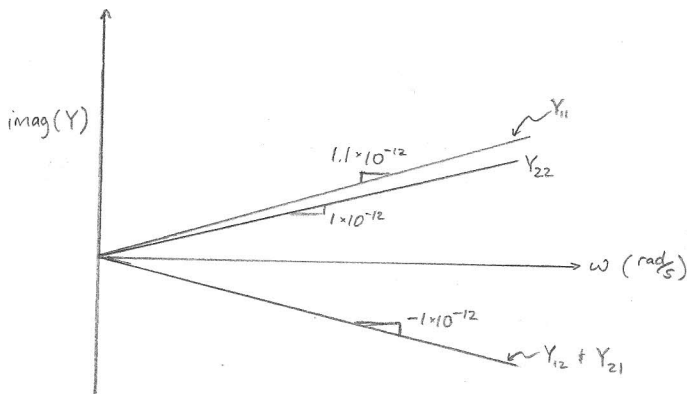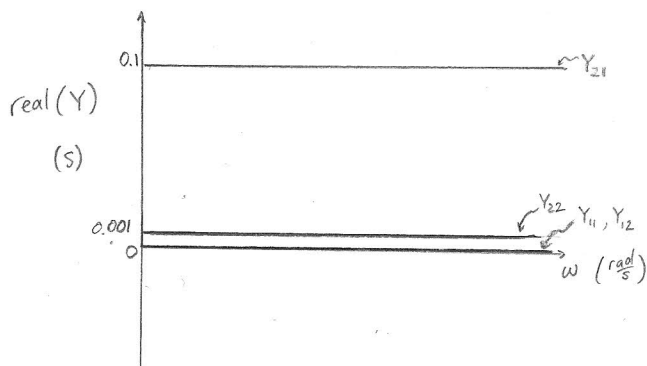

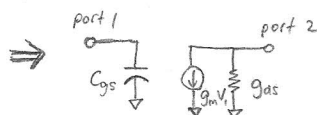b) If $C_{gd} = 0$, $Z_{Cgd} = \frac{1}{j\omega C_{gd}} \rightarrow \infty$,
 C_{gd} acts as open circuit.



Hybrid Parameters: $\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} H_{11} & H_{12} \\ H_{21} & H_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$

$$H_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = Z_{Cgs} = \frac{1}{j\omega C_{gs}}$$

$$H_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = 0 \quad \text{since } I_1=0 \Rightarrow V_1=0$$

$$H_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = \frac{g_m V_1}{V_1 Y_{Cgs}} = \frac{g_m}{j\omega C_{gs}} \Rightarrow \boxed{H_{21} = \frac{g_m}{j\omega C_{gs}}}$$

$$H_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{V_2 g_{ds}}{V_2} = g_{ds} \quad \text{since } I_1=0 \Rightarrow V_1=0 \Rightarrow V_1=0$$

$$H = \begin{bmatrix} \frac{1}{j\omega C_{gs}} & 0 \\ \frac{g_m}{j\omega C_{gs}} & g_{ds} \end{bmatrix}$$

5) $I_a = k_p \left(V_g + \frac{V_a}{\mu} \right)^{3/2}$

a) $g_{out} \triangleq \frac{\partial I_a}{\partial V_a} = \frac{\partial}{\partial V_a} \left[k_p \left(V_g + \frac{V_a}{\mu} \right)^{3/2} \right]$
 $= \frac{3}{2} \left[k_p \left(V_g + \frac{V_a}{\mu} \right)^{1/2} \right] \frac{1}{\mu}$ by chain rule.

$$g_{out} = \boxed{\frac{3k_p}{2\mu} \left(V_g + \frac{V_a}{\mu} \right)^{1/2}}$$

$g_m \triangleq \frac{\partial I_a}{\partial V_g} = \frac{\partial}{\partial V_g} \left[k_p \left(V_g + \frac{V_a}{\mu} \right)^{3/2} \right]$
 $= \frac{3}{2} k_p \left(V_g + \frac{V_a}{\mu} \right)^{1/2} (1)$ by chain rule.

$$g_m = \boxed{\frac{3k_p}{2} \left(V_g + \frac{V_a}{\mu} \right)^{1/2}}$$

b) We don't know k_p and μ , so we must estimate g_{out} and g_m from the IV curves.
 At $V_a = 200 \text{ V}$ and $V_g = -0.5 \text{ V}$, $I_a \approx 3.3 \text{ mA}$.

$g_{out} = \frac{\partial I_a}{\partial V_a} \approx \frac{\Delta I_a}{\Delta V_a}$ is approximately the slope of the IV curve.

At $V_a = 200 \text{ V}$, $V_g = -0.5 \text{ V}$, $g_{out} \approx \frac{3.8 - 2.75 \text{ mA}}{225 - 175 \text{ V}} = 0.021 \text{ mS}$

$g_m = \frac{\partial I_a}{\partial V_g} \approx \frac{\Delta I_a}{\Delta V_g}$

At $V_a = 200 \text{ V}$, $g_m \approx \frac{4.5 - 2.25 \text{ mA}}{0 - (-1) \text{ V}} = 2.25 \text{ mS}$

$$\boxed{\begin{array}{l} g_{out} \approx 0.021 \text{ mS} \\ g_m \approx 2.3 \text{ mS} \end{array}}$$