

problem 1

given: $\mu_{\text{sat}} C_{\text{ox}} W_g = 1.0 \text{ mA/V}$

$$V_{\text{th}} = 0.25 \text{ V}$$


$$\lambda = 0.25 \text{ V}^{-1}$$

$$V_{\text{ds}} = 1 \text{ V}$$

$$V_{\text{gs}} = 0.5 \text{ V}$$

$$I_{\text{d}} = \mu_{\text{sat}} C_{\text{ox}} W_g (V_{\text{gs}} - V_{\text{th}}) (1 + \lambda V_{\text{ds}})$$

small signal model:

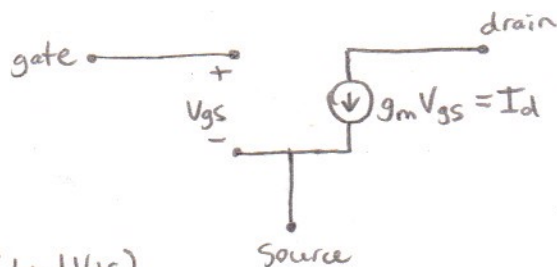

- calculate transconductance:

$$g_m \triangleq \frac{\partial I_{\text{d}}}{\partial V_{\text{gs}}} = \mu_{\text{sat}} C_{\text{ox}} W_g (1 + \lambda V_{\text{ds}}) = (1.0 \text{ mA/V}) (1.25 \text{ V/V}) = \boxed{1.25 \text{ mA/V}}$$

- calculate output conductance:

$$G_{\text{ds}} \triangleq \frac{\partial I_{\text{d}}}{\partial V_{\text{ds}}} = \mu_{\text{sat}} C_{\text{ox}} W_g (V_{\text{gs}} - V_{\text{th}}) \lambda = (1.0 \text{ mA/V}) (0.25 \text{ V}) (0.25 \text{ V}^{-1}) = \boxed{62.5 \mu\text{A/V}}$$

problem 2

given: $\mu C_{\text{ox}} W_g / 2L_g = 0.8 \text{ mA/V}^2$

$$\lambda = 0.25 \text{ V}^{-1}$$

$$V_{\text{ds}} = 1.5 \text{ V}$$

$$I_{\text{d}} = 0.25 \text{ mA}$$

$$I_{\text{d}} = (\mu C_{\text{ox}} W_g / 2L_g) (V_{\text{gs}} - V_{\text{th}})^2 (1 + \lambda V_{\text{ds}})$$

small signal model:

(same as Problem 1)

- calculate gate overdrive:

$$V_{\text{gs}} - V_{\text{th}} = \sqrt{\frac{I_{\text{d}}}{(\mu C_{\text{ox}} W_g / 2L_g) (1 + \lambda V_{\text{ds}})}} = \sqrt{\frac{0.25 \text{ mA}}{(0.8 \text{ mA/V}^2) (1.375 \text{ V/V})}} = 0.4767 \text{ V}$$

- calculate transconductance and output conductance:

$$g_m \triangleq \frac{\partial I_{\text{d}}}{\partial V_{\text{gs}}} = 2(\mu C_{\text{ox}} W_g / 2L_g) (V_{\text{gs}} - V_{\text{th}}) (1 + \lambda V_{\text{ds}}) = 2(0.8 \text{ mA/V}^2) (0.4767 \text{ V}) (1.375 \text{ V/V}) \approx \boxed{1.05 \text{ mA/V}}$$

$$G_{\text{ds}} \triangleq \frac{\partial I_{\text{d}}}{\partial V_{\text{ds}}} = \frac{\lambda I_{\text{d}}}{1 + \lambda V_{\text{ds}}} = \frac{(0.25 \text{ V}^{-1}) (0.25 \text{ mA})}{1.375 \text{ V/V}} = \boxed{45.4 \mu\text{A/V}}$$

problem 3

given: same as problem 2, except $V_{ds} = 1V$

- gate overdrive:

$$V_{gs} - V_{th} = \sqrt{\frac{I_d}{(\mu C_{ox} W_g / 2 L_g)(1 + \lambda V_{ds})}} = \sqrt{\frac{0.25 \text{ mA}}{(0.8 \text{ mA/V}^2)(1.25 \text{ V/V})}} = 0.5 \text{ V}$$

- calculate transconductance & output conductance:

$$g_m \triangleq \frac{\partial I_d}{\partial V_{gs}} = 2(\mu C_{ox} W_g / 2 L_g)(V_{gs} - V_{th})(1 + \lambda V_{ds})$$
$$= 2(0.8 \text{ mA/V})(0.5 \text{ V})(1.25 \text{ V/V}) = \boxed{1 \text{ mA/V}}$$

$$G_{ds} \triangleq \frac{\partial I_d}{\partial V_{ds}} = \lambda(\mu C_{ox} W_g / 2 L_g)(V_{gs} - V_{th})^2$$
$$= (0.25 \text{ V}^{-1})(0.8 \text{ mA/V})(0.25 \text{ V}^2) = \boxed{50 \mu\text{A/V}}$$


problem 4

given: $\beta = 100$ we have small signal model:

$$V_A = 50V$$

$$V_{CE} = 1.5V$$

$$I_C = 0.2 \text{ mA}$$

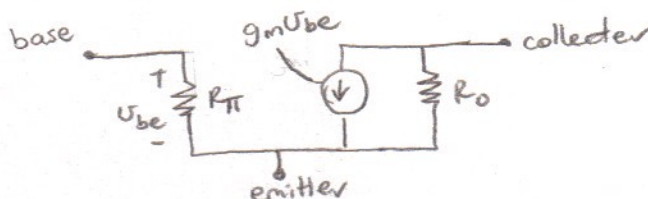

Assuming room temperature operation, $V_T = \frac{kT}{q} = 25.8 \text{ mV}$.

$$g_m = \left. \frac{\partial I_C}{\partial V_{be}} \right|_{V_{ce} \text{ constant}} = \frac{I_C}{V_T} = \frac{0.2 \text{ mA}}{25.8 \text{ mV}} = \boxed{7.75 \text{ mA/V} = g_m}$$

$$G_{ce} = \left. \frac{\partial I_C}{\partial V_{ce}} \right|_{V_{be} \text{ const}} = \frac{I_C}{V_{CE} + V_A} = \frac{0.2 \text{ mA}}{51.5 \text{ V}} = \boxed{3.88 \mu\text{A/V} = G_{ce}}$$

To compute the input impedance we start with

$$g_m = \frac{\alpha}{r_e} = \frac{\beta}{(\beta+1)r_e} = \frac{\beta}{R_{\pi}} \Rightarrow R_{\pi} = \frac{\beta}{g_m} = \boxed{12.9 \text{ k}\Omega = R_{\pi}}$$

problem 5

a. given: $V_t = 0.25V$ need: $I_d = 0.5mA$
 $\lambda = 0.1V^{-1}$ $V_{gs} = 0.4mA$
 $L_g = 130nm$ $W_g = ?$
 $\mu = 300 cm^2/Vs$
 $T_{ox} = 1.2nm$

Assuming SiO_2 we have $\epsilon_r = 3.8$. So,

$$C_{ox} = \frac{\epsilon_r \epsilon_0}{T_{ox}} = \frac{3.8 (8.854 \times 10^{-12} F \cdot m^{-1})}{1.2 \times 10^{-9} m} \approx 28 mF/m^2$$

For mobility limited case we need $V_{ds} > V_{knee} = V_{gs} - V_{th}$. Therefore,

$$I_d = (\mu C_{ox} W_g / 2L_g) (V_{gs} - V_t)^2 (1 + \lambda V_{ds})$$
$$> (\mu C_{ox} / 2L_g) (V_{gs} - V_t)^2 (1 + \lambda V_{gs} - \lambda V_t) W_g$$

Or, under the approximation (see lecture notes) that $1 + \lambda V_{ds} \approx 1$,

$$W_g = \frac{2(0.5mA)(130 \times 10^{-9}m)}{(300 cm^2/Vs) \left(\frac{1m}{100cm}\right)^2 (28mF/m^2) (0.15V)^2} = \boxed{6.88 \mu m}$$

b. Here, $V_d = V_{dd} - I_d R_d = 2V - (0.5mA) R_d = 1V$

$$\Rightarrow R_d = \frac{1V}{0.5mA} = \boxed{2k\Omega}$$

Now we determine R_{g1} and R_{g2} so that constraints are met:

$$\bullet V_{gs} = 0.4V, V_{DD} = 2V \Rightarrow \frac{R_{g2}}{R_{g1} + R_{g2}} = \frac{0.4}{2} = \frac{1}{5} \Rightarrow R_{g1} = 4R_{g2}$$

$$\bullet R_{in}^* = R_{g1} \parallel R_{g2} = 1M\Omega$$

* Note:

R_{in} does not include

R_{gen} , is just impedance

seen by gate of

NMOS.

$$\Rightarrow \frac{1}{R_{g1}} + \frac{4}{R_{g1}} = \frac{5}{R_{g1}} = \frac{1}{1M\Omega}$$

$$\Rightarrow R_{g1} = 5(1M\Omega) = \boxed{5.0 M\Omega = R_{g1}}$$

$$R_{g2} = \frac{1}{4} R_{g1} = \boxed{1.25 M\Omega = R_{g2}}$$

thanks
Justin
Liang!

c.

$$g_m \triangleq \frac{\partial I_D}{\partial V_{GS}} = (\mu C_{ox} W_g / L_g) (V_{GS} - V_{th}) (1 + \lambda V_{DS})$$

here, all the quantities are as before except:

$$W_g = 6.77 \mu m \quad \text{and} \quad V_{DS} = V_d = 1V$$


$$\Rightarrow g_m = (0.03 \text{ m}^2/\text{V}) (28 \text{ mF/m}^2) (6.77 \mu m) (0.15 \text{ V}) (1.1 \text{ V/V}) / 130 \times 10^{-9} \text{ m}$$

$$= \boxed{7.22 \text{ mA/V}}$$

And,

$$G_{OS} \triangleq \frac{\partial I_D}{\partial V_{OS}} = \frac{\lambda I_D}{1 + \lambda V_{DS}} = \frac{(0.1 \text{ V}^{-1}) (0.5 \text{ mA})}{1.1 \text{ V/V}} = \boxed{45.5 \mu\text{A/V}}$$

d.

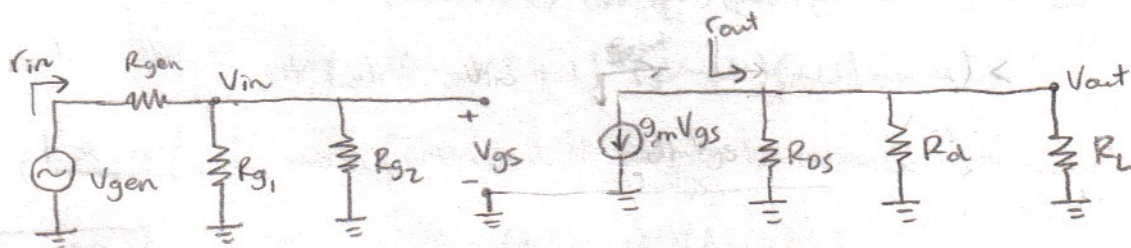

e.

Summary of resistor values:

$$R_{gen} = 50 \text{ k}\Omega$$

$$R_{OS} = \frac{1}{G_{OS}} = 22 \text{ k}\Omega$$

$$R_{G1} = 1.667 \text{ M}\Omega$$

$$R_D = 2 \text{ k}\Omega$$

$$R_{G2} = 1.111 \text{ M}\Omega$$

$$R_L = 100 \text{ k}\Omega$$

$$R_{G1} \parallel R_{G2} = 1 \text{ M}\Omega$$

Therefore, with r_{in} and r_{out} as defined in diagram,

$$r_{in} = R_{gen} + R_{G1} \parallel R_{G2} = \boxed{1.05 \text{ M}\Omega = r_{in}}$$

$$r_{out} = R_{OS} \parallel R_D \parallel R_L = \boxed{1.8 \text{ k}\Omega = r_{out}}$$

$$\Rightarrow \frac{V_{in}}{V_{GS}} = \frac{R_{G1} \parallel R_{G2}}{R_{gen} + R_{G1} \parallel R_{G2}} \quad V_{GS} = \frac{20}{21} V_{gen} \Rightarrow \boxed{\frac{V_{in}}{V_{gen}} = 0.952}$$

So,

$$\frac{V_{out}}{V_{in}} = \frac{-g_m V_{GS} r_{out}}{V_{GS}} = \boxed{-13 \text{ V/V} = \frac{V_{out}}{V_{in}}}$$

$$\frac{V_{out}}{V_{gen}} = \frac{V_{out}}{V_{in}} \cdot \frac{V_{in}}{V_{gen}} = \boxed{-12.4 \text{ V/V} = \frac{V_{out}}{V_{gen}}}$$

problem 6

a. given:

$$V_T = \pm 0.25V$$

$$\lambda = 0.1V^{-1}$$

$$L_g = 0.45\mu m$$

$$T_{ox} = 0.8nm$$

$$\mu_{sat,N} = 10^7 cm/s$$

$$\mu_{sat,P} = 5 \times 10^6 cm/s$$

$$W_{g,N} = 5\mu m$$

$$W_{g,P} = 10\mu m$$

$$V_{dd} = 1V$$

$$V_{in} = 0.5$$

• Determine C_{ox} , assuming $SiO_2 \rightarrow \epsilon_r = 3.8$

$$C_{ox} = \frac{\epsilon_r \epsilon_0}{T_{ox}} = \frac{(3.8)(8.854 \times 10^{-12} F \cdot m^{-1})}{0.8 \times 10^{-9} m} = 42.1 mF/m^2$$

Now, compare drain currents for NMOS/PMOS

$$I_{D,N} = I_{D,P} \iff C_{ox} W_{g,N} \mu_{sat,N} (1 + \lambda V_{out})(V_{in} - V_{th,N})$$

$$= C_{ox} W_{g,P} \mu_{sat,P} (1 + \lambda (V_{dd} - V_{out}))(V_{dd} - V_{in} + V_{th,P})$$

But in this case (plug in values to verify)

$$W_{g,N} \mu_{sat,N} = W_{g,P} \mu_{sat,P} \quad \text{and} \quad V_{in} - V_{th,N} = V_{dd} - V_{in} + V_{th,P}$$

$$\Rightarrow 1 + \lambda (V_{dd} - V_{out}) = 1 + \lambda V_{out} \Rightarrow \boxed{V_{out} = \frac{V_{dd}}{2} = 0.5V}$$

And so,

$$I_{D,P} = I_{D,N} = C_{ox} W_{g,N} \mu_{sat,N} (1 + \lambda V_{out})(V_{in} - V_{th,N})$$

$$= (42.1 mF/m^2)(10^7 cm/s)(5\mu m)(1.05)(0.25V) = \boxed{5.53 mA = I_D}$$


$$b. \quad g_{m,N} = \frac{\partial I_{D,N}}{\partial V_{gs}} = C_{ox} W_{g,N} \mu_{sat,N} (1 + \lambda V_{out}) = \boxed{22.1 mA/V = g_{m,N}}$$

$$g_{m,P} = C_{ox} W_{g,P} \mu_{sat,P} (1 + \lambda V_{out}) = \boxed{22.1 mA/V = g_{m,P}}$$


$$G_{ds,N} = \frac{\partial I_{D,N}}{\partial V_{ds}} = \frac{\lambda I_{D,N}}{1 + \lambda V_{out}} = \boxed{0.527 mA/V = G_{ds,N}}$$

$$G_{ds,P} = \frac{\lambda I_{D,P}}{1 + \lambda (V_{dd} - V_{out})} = \boxed{0.527 mA/V = G_{ds,P}}$$

c.

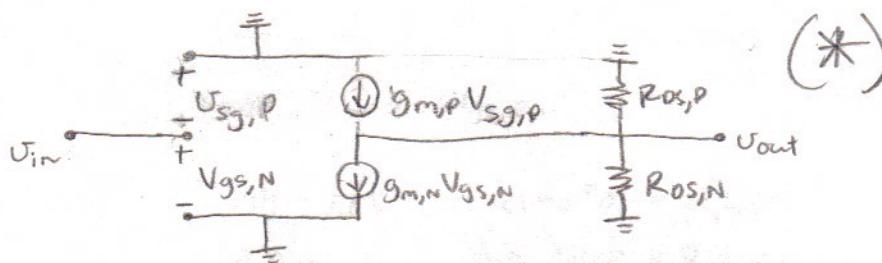

||

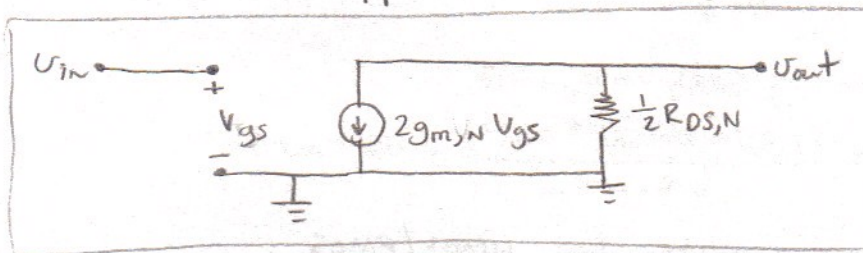


d.

using the diagram above,

$$\frac{V_{out}}{V_{in}} = - \frac{2g_{m,n} V_{gs} \cdot \frac{1}{2} R_{DS,N}}{V_{gs}} = - \frac{g_{m,n}}{G_{DS,N}} \approx \boxed{-42 \text{ V/V}}$$

(*) Note that this is identical to:

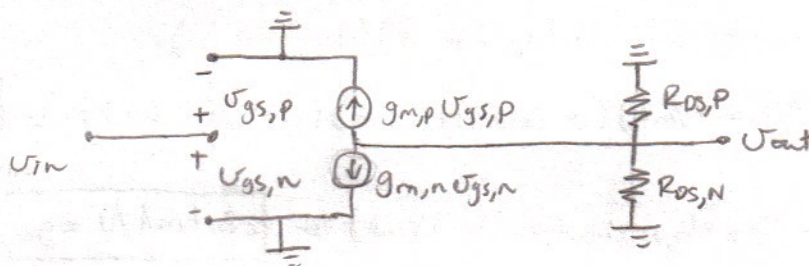

From which we obtain the simplified diagram since

- $V_{gs,p} = V_{gs,n} = V_{in}$
- $g_{m,p} = g_{m,n}$
- $R_{DS,p} = R_{DS,n}$