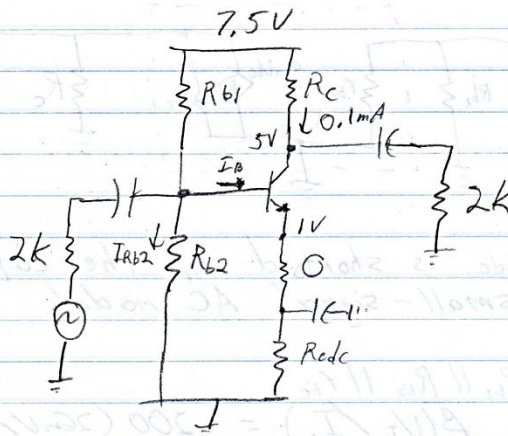


Homework

#5

Problem 1



$$\beta = 200$$

$$V_{cc} = 100V$$

$$I_{Rb2} = 20 \cdot I_B = I_C = 0.1mA$$

$$V_E = 1V \quad V_B \approx 1.7V \quad V_{CB} > 0 \Rightarrow \text{linear active}$$

$$\beta I_B = I_C$$

$$200 I_B = 0.1mA$$

$$I_B = 0.5 \mu A$$

$$I_{Rb2} = 20 \cdot 0.5 \mu A = 10 \mu A$$


$$I_{Rb1} = 10.5 \mu A$$

$$a.) \quad R_{b2} = \frac{1.7V}{10 \mu A} = 170 k\Omega$$

$$R_{b1} = \frac{7.5V - 1.7V}{10.5 \mu A} = 552 k\Omega$$

$$R_C = \frac{7.5V - 5V}{0.1mA} = 25 k\Omega$$
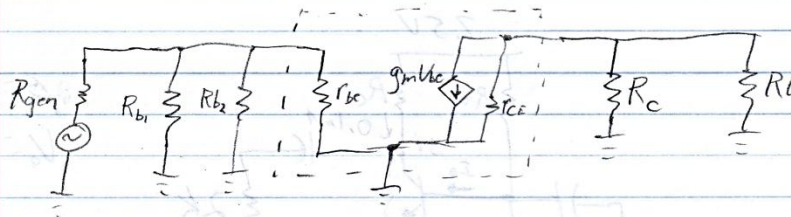
$$R_{edc} = \frac{1V}{0.1mA + 0.5 \mu A} = 9.95 k\Omega$$



Note: r_{ce} is shorted by the capacitor in the small-signal AC model.

$$R_{in} = R_{b1} \parallel R_{b2} \parallel r_{bc}$$


$$r_{bc} = r_{be} = \beta(V_T / I_C) = 200(26\text{mV} / 0.1\text{mA}) = 52\text{k}\Omega$$

$$R_{in} = 552\text{k} \parallel 170\text{k} \parallel 52\text{k} = 37.1\text{k}\Omega$$

$$R_{out} = r_{ce} \parallel R_c$$

$$r_{ce} = r_o = |V_A| / I_C = 100\text{V} / 0.1\text{mA} = 1\text{M}\Omega$$
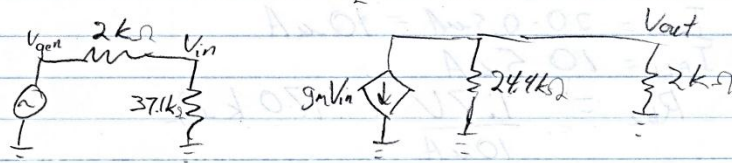
$$R_{out} = 1\text{M}\Omega \parallel 25\text{k}\Omega = 24.4\text{k}\Omega$$



$$g_m = I_C / V_T = 0.1\text{mA} / 26\text{mV} = 3.8\text{mS}$$

$$b) \frac{V_{out}}{V_{in}} = -g_m \frac{V_{in}}{V_{in}} \cdot R_{out} \parallel R_L = -3.8\text{mS} \cdot 24.4\text{k} \parallel 2\text{k} = -7.0$$

$$\frac{V_{in}}{V_{gen}} = \frac{R_{in}}{R_{in} + R_{gen}} = \frac{37.1\text{k}}{37.1\text{k} + 2\text{k}} = 0.949$$

$$\frac{V_{out}}{V_{gen}} = \frac{V_{out}}{V_{in}} \cdot \frac{V_{in}}{V_{gen}} = -7.0 \cdot 0.949 = -6.7$$

c) As found above

$$R_{in} = 37.1\text{k}\Omega \quad R_{out} = 24.4\text{k}\Omega$$

$$d.) R_{eq} = 25k \parallel 2k = 1.85k\Omega$$


$$\Delta V_{out} \uparrow_{max} = I_{cq} \cdot R_{eq} = 0.1mA \cdot 1.85k\Omega = 0.185V$$

$$V_{ceQ} = 5V - 1V = 4V$$

$$V_{cemin} = V_{ce sat} \approx 0.5V$$

$$\Delta V_{ce} \downarrow_{max} = 4V - 0.5V = 3.5V$$

Problem # 2

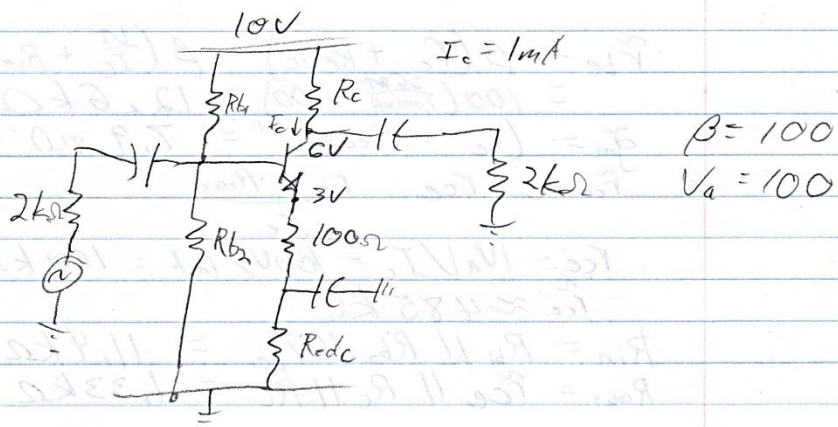

$$I_{Rb2} = 20 I_B \quad I_c = 1mA$$

$$V_c = 3V \quad V_b \approx 3.7V \quad V_{cb} > 0 \rightarrow \text{linear active}$$

$$\beta I_B = I_c$$

$$100 I_B = 1mA$$

$$I_B = 10\mu A$$



$$I_{Rb2} = 20\mu A \quad I_{Rb1} = 21\mu A$$

$$a.) R_{b2} = 3.7V / 20\mu A = 185k\Omega$$

$$R_{b1} = (10V - 3.7V) / 21\mu A = 300k\Omega$$

$$R_c = (10V - 6V) / 1mA = 4k\Omega$$
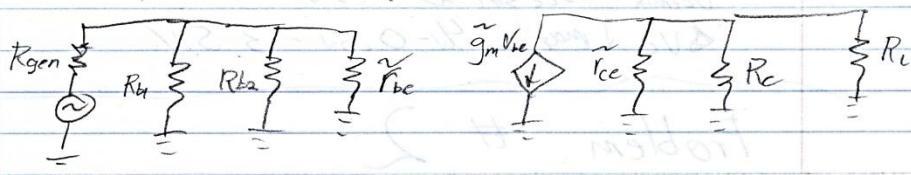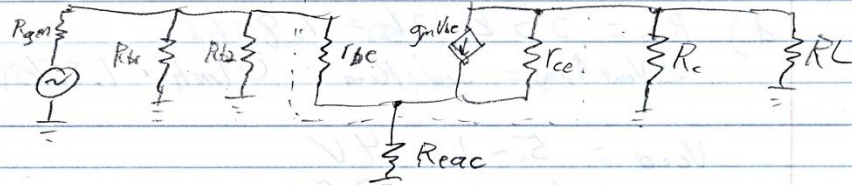
$$R_{ec} = \frac{3 - (1mA + 10\mu A) \cdot 100\Omega}{1mA + 10\mu A} = 2.9k\Omega$$



$$\tilde{r}_{be} = \beta (r_e + R_{eac}) = \beta \left(\frac{V_T}{I_E} + R_{eac} \right)$$

$$= 100 \left(\frac{26 \text{ mV}}{1.001 \text{ mA}} + 100 \right) = 12.6 \text{ k}\Omega$$

$$\tilde{g}_m = (r_e + R_{eac})^{-1} = 7.9 \text{ m}\Omega^{-1}$$


$$\tilde{r}_{ce} \approx r_{ce} \parallel \frac{r_e + R_{eac}}{r_e}$$

$$r_{ce} = |V_A| / I_c = 100 \text{ V} / 1 \text{ mA} = 100 \text{ k}\Omega$$

$$\tilde{r}_{ce} \approx 485 \text{ k}\Omega$$

$$R_{in} = R_{b1} \parallel R_{b2} \parallel \tilde{r}_{be} = 11.4 \text{ k}\Omega$$
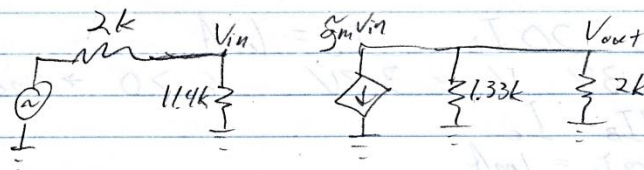
$$R_{out} = \tilde{r}_{ce} \parallel R_c \parallel R_L = 1.33 \text{ k}\Omega$$



$$b.) \frac{V_{out}}{V_{in}} = -g_m V_{in} R_{out} \parallel R_L \cdot \frac{V_{in}}{V_{in}} = -7.9 \text{ m}\Omega^{-1} \cdot 1.33 \text{ k}\Omega / 2 \text{ k}\Omega$$

$$V_{out} / V_{in} = -6.3$$

$$\frac{V_{in}}{V_{gen}} = \frac{R_{in}}{R_{in} + R_{gen}} = \frac{11.4 \text{ k}\Omega}{11.4 \text{ k}\Omega + 12.73 \text{ k}\Omega} = 0.896$$

$$\frac{V_{out}}{V_{gen}} = \frac{V_{out}}{V_{in}} \cdot \frac{V_{in}}{V_{gen}} = -6.3 \cdot 0.896 = -5.64$$

c.) As found above

$$R_{in} = 11.4 k\Omega \quad R_{out} = 1.33 k\Omega$$

d.) $R_{eq} = R_L || R_c = 4k || 2k = 1.33 k\Omega$


$$\Delta V_{out} \uparrow_{max} = I_{cc} R_{eq} = 1mA \cdot 1.33k = 1.33V$$

$$V_{ceq} = 6V - 3V = 3V$$

$$V_{ce min} = V_{ce sat} \approx 0.5V$$

$$\Delta V_{ce} \downarrow_{max} = 3 - 0.5V = 2.5V$$

Problem 3

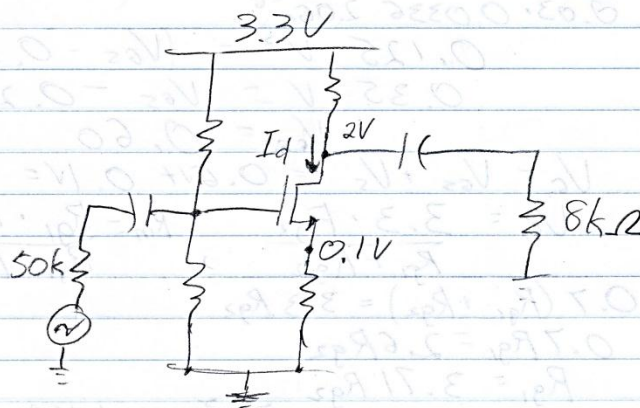

$$T_{ox} = 1nm, \quad L_g = 130nm, \quad V_t = 0.25V$$

$$\mu = 300 cm^2/(Vs), \quad \lambda = 0$$

a.) $I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L_g} (V_{gs} - V_t)^2 (1 + \lambda V_{ds})$

For $I_D = 0.5mA$, $V_{gs} = 0.5V$

$$C_{ox} = \frac{\epsilon_r \epsilon_0}{T_{ox}} = \frac{3.8 \epsilon_0}{1nm} = 0.0336 F/m^2$$

(Assuming SiO_2)

$$0.5mA = \frac{1}{2} \frac{300 cm^2}{Vs} \cdot 0.0336 \frac{F}{m^2} \cdot \frac{W}{130nm} \cdot (0.5 - 0.25)^2 V$$

$$0.5 \text{ e}^{-3} \text{ A} = \frac{1 \text{ V}^2 \cdot 0.03 \text{ m}^2}{32 \text{ V} \cdot \text{s}} \cdot \frac{0.0336 \text{ A} \cdot \text{s}}{\text{V} \cdot \text{m}^2} \cdot \frac{\text{V}_g}{130 \text{ e}^{-9} \text{ m}}$$

$$0.5 \text{ e}^{-3} \text{ A} = \frac{\text{V}_g \cdot 0.03 \cdot 0.0336 \text{ A}}{32 \cdot 130 \text{ e}^{-9} \text{ m}}$$

$$\text{V}_g = \frac{0.5 \text{ e}^{-3} \cdot 32 \cdot 130 \text{ e}^{-9} \text{ A} \cdot \text{m}}{0.03 \cdot 0.0336 \text{ A}} = 2.06 \times 10^{-6} \text{ m}$$

$$\text{V}_g = 2.06 \text{ } \mu\text{m}$$

$$\text{b.) } 1 \text{ mA} = \frac{1}{2} \cdot \frac{0.03 \text{ m}^2}{\text{V} \cdot \text{s}} \cdot \frac{0.0336 \text{ A} \cdot \text{s}}{\text{V} \cdot \text{m}^2} \cdot \frac{2.06 \text{ e}^{-6}}{130 \text{ e}^{-9}} (\text{V}_{\text{GS}} - 0.25)^2$$

$$\frac{2 \text{ e}^{-2} \cdot 130 \text{ e}^{-9} \text{ V}^2}{0.03 \cdot 0.0336 \cdot 2.06 \text{ e}^{-6}} = (\text{V}_{\text{GS}} - 0.25)^2$$

$$0.125 \text{ V}^2 = (\text{V}_{\text{GS}} - 0.25)^2$$

$$0.35 \text{ V} = \text{V}_{\text{GS}} - 0.25$$

$$\text{V}_{\text{GS}} = 0.60$$

$$\text{V}_G = \text{V}_{\text{GS}} + \text{V}_S = 0.6 \text{ V} + 0.1 \text{ V} = 0.7 \text{ V}$$

$$\text{V}_G = \frac{3.3 \cdot R_{g2}}{R_{g1} + R_{g2}}, \quad R_{\text{in}} = \frac{R_{g1} \cdot R_{g2}}{R_{g1} + R_{g2}} = 1 \text{ M}\Omega$$

$$0.7 (R_{g1} + R_{g2}) = 3.3 R_{g2}$$


$$0.7 R_{g1} = 2.6 R_{g2}$$

$$R_{g1} = 3.71 R_{g2}$$

$$1 \text{ M}\Omega = \frac{3.71 R_{g2}^2}{4.71 R_{g2}}, \quad 1 \text{ M}\Omega = 0.788 R_{g2}$$


$$R_{g2} = 1.27 \text{ M}\Omega$$
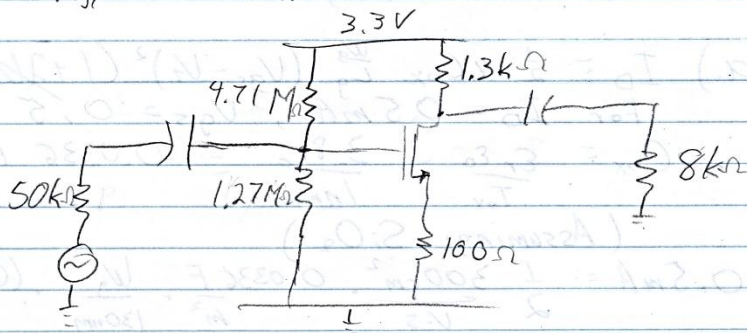
$$R_{g1} = 3.71 \cdot 1.27 \text{ M}\Omega = 4.71 \text{ M}\Omega$$



$$R_d = \frac{3.3 - 2V}{1mA} = 1.3k\Omega$$

$$R_s = \frac{0.1V}{1mA} = 100\Omega$$

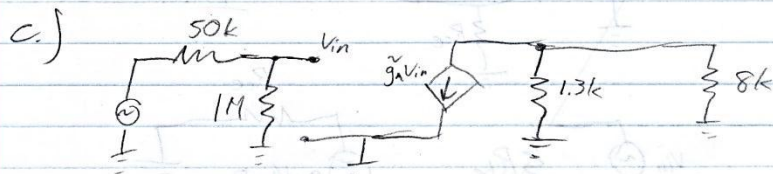

$$\lambda = 0 \rightarrow V_{ce} = \infty \Rightarrow \tilde{r}_{ce}$$

$$R_{out} = R_c$$

$$R_{in} = 1M\Omega$$

$$R_{out} = 1.3k\Omega$$

$$\tilde{g}_m = \frac{g_m}{1 + g_m R_s}$$

$$g_m = \mu C_{ox} (W_g/L_g) \cdot (V_{GS} - V_{th})$$

$$g_m = \frac{0.03 \text{ m}^2}{V \cdot s} \cdot \frac{0.0336 \text{ A} \cdot s}{V \cdot \text{m}^2} \cdot \frac{2.06 \cdot 10^{-6}}{130 \cdot 10^{-9}} \cdot (0.6 - 0.25) V$$

$$g_m = 5.6 \text{ m}\Omega^{-1}$$

$$\tilde{g}_m = \frac{5.6 \text{ m}\Omega^{-1}}{1 + 5.6 \text{ m}\Omega^{-1} \cdot 100\Omega} = 3.6 \text{ m}\Omega^{-1}$$



$$R_{eq} = R_{out} \parallel R_c = 1.3k \parallel 8k = 1.12k\Omega$$

$$\frac{V_{out}}{V_{in}} = \frac{-\tilde{g}_m V_{in} R_{eq}}{V_{in}} = -3.6 \text{ m}\Omega^{-1} \cdot 1.12k = -4.0$$

$$V_{in} = \frac{R_{in}}{R_{in} + R_s} V_{gen} = \frac{1M}{1M + 50k} V_{gen} = 0.952$$

$$V_{out} = \frac{V_{out}}{V_{in}} \cdot \frac{V_{in}}{V_{gen}} = 0.952 \cdot -4.0 = -3.84$$

Problem 4

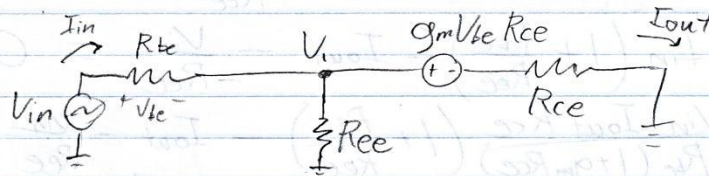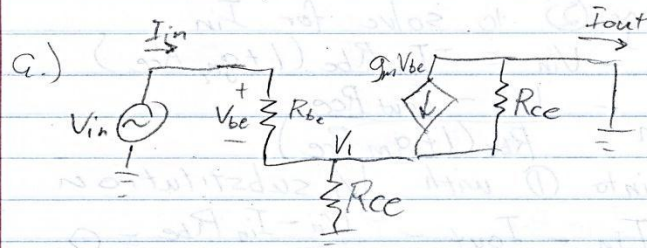

Using KCL at the central node

$$① \quad I_{in} - I_{out} - V_i / R_{ce} = 0$$

$$I_{out} = \frac{V_i - g_m V_{be} R_{ce}}{R_{ce}}$$

$$V_{be} = I_{in} R_{be}$$

$$I_{out} = \frac{V_i - g_m I_{in} R_{be} R_{ce}}{R_{ce}}$$

$$V_i = V_{in} - I_{in} R_{be}$$

$$② \quad I_{out} = \frac{V_{in} - I_{in} R_{be} (1 + g_m R_{ce})}{R_{ce}}$$

Plug this and the V_i substitution back into 1

$$I_{in} - \frac{V_{in} - I_{in} R_{be} (1 + g_m R_{ce})}{R_{ce}} - \frac{V_{in} - I_{in} R_{be}}{R_{ce}} = 0$$

$$V_{in} \left(\frac{1}{R_{ce}} + \frac{1}{R_{ce}} \right) = I_{in} \left(1 + \frac{R_{be} (1 + g_m R_{ce})}{R_{ce}} + \frac{R_{be}}{R_{ce}} \right)$$

$$\frac{V_{in}}{I_{in}} = \left[1 + \frac{R_{be} (1 + g_m R_{ce})}{R_{ce}} + \frac{R_{be}}{R_{ce}} \right] \cdot (R_{ce} \parallel R_{ce})$$

For extrinsic transconductance

Rearrange ② to solve for I_{in}

$$I_{out} R_{ce} - V_{in} = -I_{in} R_{be} (1 + g_m R_{ce})$$

$$I_{in} = \frac{V_{in} - I_{out} R_{ce}}{R_{be} (1 + g_m R_{ce})}$$

Plug into ① with V_i substitution

$$I_{in} - I_{out} - \frac{V_{in} - I_{in} R_{be}}{R_{ce}} = 0$$

$$I_{in} \left(1 + \frac{R_{be}}{R_{ce}}\right) - I_{out} - \frac{V_{in}}{R_{ce}} = 0$$

$$\frac{V_{in} - I_{out} R_{ce}}{R_{be} (1 + g_m R_{ce})} \left(1 + \frac{R_{be}}{R_{ce}}\right) - I_{out} - \frac{V_{in}}{R_{ce}} = 0$$

$$I_{out} \left[1 + \frac{R_{ce}}{R_{be} (1 + g_m R_{ce})} \left(1 + \frac{R_{be}}{R_{ce}}\right)\right]$$

Rearranging / simplifying

$$I_{out} \left[1 + \frac{R_{be} + R_{ce}}{R_{be} (1 + g_m R_{ce})}\right] = \frac{V_{in} \left[\left(1 + \frac{R_{be}}{R_{ce}}\right) - \frac{1}{R_{ce}}\right]}{R_{be} (1 + g_m R_{ce})}$$


$$\frac{I_{out}}{V_{in}} = \frac{\left[\left(1 + \frac{R_{be} + R_{ce}}{R_{be} (1 + g_m R_{ce})}\right) - \frac{1}{R_{ce}}\right]}{R_{be} (1 + g_m R_{ce})}$$

$$\frac{I_{out}}{V_{in}} = \frac{\left[1 + \frac{R_{be} + R_{ce}}{R_{be} (1 + g_m R_{ce})}\right]}{R_{be} (1 + g_m R_{ce})}$$

With a bit of work this reduces to

$$\frac{I_{out}}{V_{in}} = \frac{R_{ce} - g_m R_{be} R_{ce}}{R_{ce} (2R_{be} + R_{ce} + g_m R_{be} R_{ce})}$$

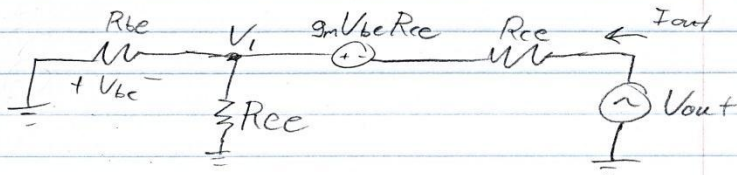b.) The circuit is the same as (a) but with the source on the other side



By KCL

$$\textcircled{1} \quad -\frac{V_1}{R_{be}} - \frac{V_1}{R_{ce}} + I_{out} = 0$$

Note the redefined direction of I_{out}

$$V_{be} = -V_1$$

$$V_1 = V_{out} - g_m V_1 R_{ce} - I_{out} R_{ce}$$

$$V_1 (1 + g_m R_{ce}) = V_{out} - I_{out} R_{ce}$$

$$V_1 = \frac{V_{out} - I_{out} R_{ce}}{1 + g_m R_{ce}}$$

Plug this into $\textcircled{1}$

$$-\frac{V_1}{R_{be}} - \frac{V_1}{R_{ce}} + I_{out} = 0$$

$$-\left(\frac{V_{out} - I_{out} R_{ce}}{1 + g_m R_{ce}} \right) \left(\frac{1}{R_{be}} + \frac{1}{R_{ce}} \right) + I_{out} = 0$$

$$\frac{V_{out}}{1 + g_m R_{ce}} \left(\frac{1}{R_{be}} + \frac{1}{R_{ce}} \right) = I_{out} \left[1 + \frac{R_{ce}}{(1 + g_m R_{ce})} \left(\frac{1}{R_{be}} + \frac{1}{R_{ce}} \right) \right]$$

$$\frac{V_{out}}{I_{out}} = \frac{1 + \frac{R_{ce}}{1 + g_m R_{ce}} \left(\frac{1}{R_{be}} + \frac{1}{R_{ce}} \right)}{\frac{1}{1 + g_m R_{ce}} \left(\frac{1}{R_{be}} + \frac{1}{R_{ce}} \right)}$$

With a little work this reduces to

$$\frac{V_{out}}{I_{out}} = R_{ce} + (1 + g_m R_{ce}) \cdot (R_{be} \parallel R_{ce})$$