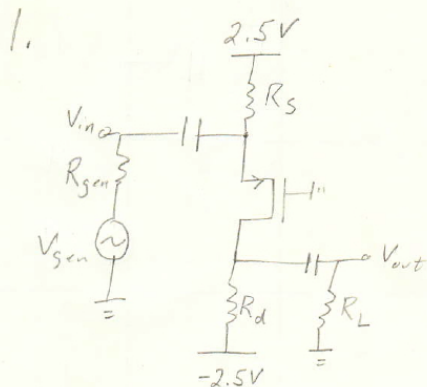




$$K_P = \frac{1}{2} \mu_P C_{ox} \frac{W}{L} = 0.345 \text{ (W/L) mA/V}^2$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.9 \epsilon_0}{t_{ox}} = 3.45 \cdot 10^{-6} \text{ F/cm}^2$$

$$\lambda = 0.05 \text{ V}^{-1}; L = 130 \text{ nm}$$

$$R_L = 10 \text{ k}\Omega; R_{gen} = 200 \Omega$$

a) DC Bias

$$i_D = 1 \text{ mA}; V_{GS} = -0.7 \text{ V}; V_{DS} = -1.7 \text{ V}$$

$$i_D = K_P (|V_{GS}| - V_{th})^2 (1 + \lambda |V_{DS}|)$$


$$\Rightarrow K_P = \frac{i_D}{(|V_{GS}| - V_{th})^2 (1 + \lambda |V_{DS}|)} = 10.24 \text{ mA/V}^2 = (0.345) \text{ (W/L) mA/V}^2$$

$$\Rightarrow W = 3.86 \mu\text{m}$$

$$V_S = 2.5 \text{ V} - i_D R_S = 0.7 \text{ V} \Rightarrow R_S = 1.8 \text{ k}\Omega$$


$$V_D = -2.5 \text{ V} + i_D R_D = -1.0 \text{ V} \Rightarrow R_D = 1.5 \text{ k}\Omega$$

b) Small Signal Model

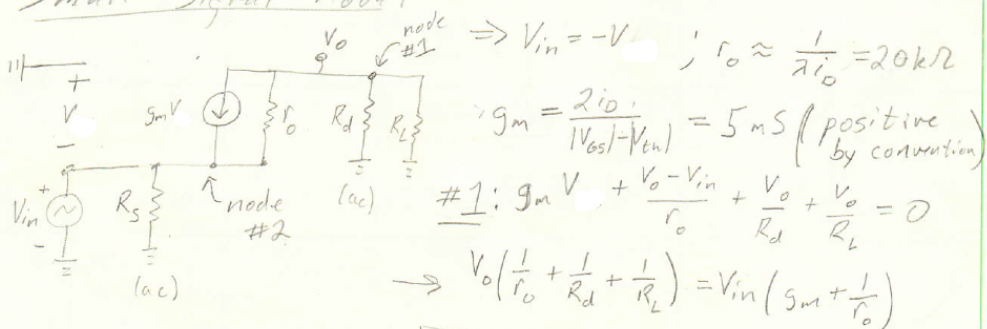


$$\Rightarrow V_o/V_{in} = \frac{R_d R_L (g_m r_o + 1)}{R_d R_L + R_L r_o + R_d r_o} = 6.18 = V_o/V_{in}$$

1. b) (cont.)

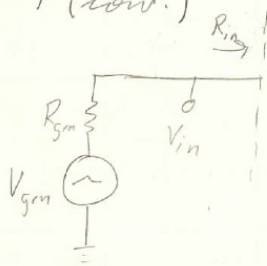

$$\Rightarrow \left[\frac{V_{in}}{V_{gen}} = \left(\frac{R_{in}}{R_{gm} + R_{in}} \right) = 0.486 \right]$$
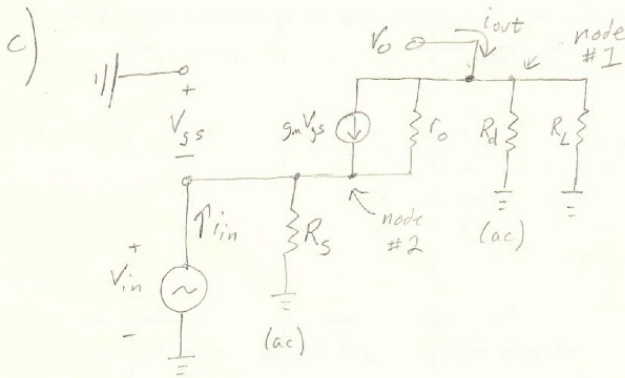
$$\left[\frac{V_{out}}{V_{gen}} = \left(\frac{V_{out}}{V_{in}} \right) \left(\frac{V_{in}}{V_{gen}} \right) = 3.00 \right]$$



Node #2: $i_{in} = V_{in}/R_S - g_m V_{GS} + \frac{V_{in} - V_o}{r_o} = V_{in} \left(\frac{1}{R_S} + g_m + \frac{1}{r_o} \right) - \frac{V_o}{r_o}$

$$i_{in} = V_{in} \left[\frac{1}{R_S} + g_m + \frac{1}{r_o} - \left(\frac{V_{out}}{V_{in}} \right) \frac{1}{r_o} \right] \Rightarrow \left[R_{in} = V_{in}/i_{in} = 189 \, \Omega \right]$$

Node #1

$$i_{out} = \frac{V_o}{R_D} + \frac{V_o - V_{in}}{r_o} + g_m V_{GS}$$

$$i_{out} \approx V_o \left(\frac{1}{R_D} + \frac{1}{r_o} \right) \Rightarrow \left[R_{out} = V_{out}/i_{out} = 1.4 \, k\Omega \right]$$


Alternatively $R_{out} \approx R_D \parallel r_{ds}(1 + g_m R_S) = 1.5 \, k\Omega$

1. (cont.)

d) Seek: Maximum positive- and negative-going outputs.

- Here we continue to assume high frequency so that we can replace βh with ∞ .

The amplifier becomes;

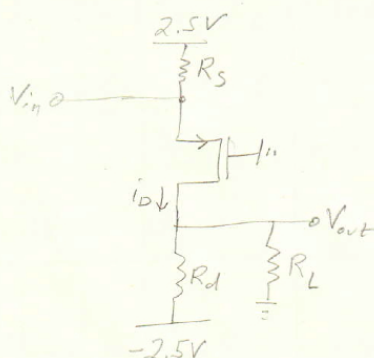

- Clearly the amplifier will no longer work when the transistor is off. Evidently this occurs when $V_{in} = 0.3V = |V_{th}|$.

What is V_{out} at this point?

$$\text{Clearly } i_D \rightarrow 0 \Rightarrow V_{out} \rightarrow (-2.5V) \left(\frac{R_L}{R_D + R_L} \right) = -2.17 \text{ V}$$

Since $V_{out} = V_{DS}$ even when $V_{in} \rightarrow 0$, obviously the transistor is in saturation at this point. This implies that for $V_{in} > 0.3V$, the amplifier is working in the proper regime.

$$\text{thus, } V_{outmin} = -2.17 \text{ V}$$

$\Rightarrow$ the max negative voltage swing is:

$$V_{out\downarrow} = |V_{out(at\text{ bias})} - V_{outmin}|$$

Note that for AC analysis, $V_{out(at\text{ bias})}$ is no longer 1V!

$$\text{Instead, } V_{out} \approx \left(\frac{R_D R_L}{R_D + R_L} \right) \left(-\frac{2.5V}{R_D} + 1mA \right) = -0.87 \text{ V (neglecting } r_o)$$

1. d) (cont.)

$$\text{thus, } V_{out} \downarrow = \left[-2.17 V + 0.87 V \right] = 1.3 V$$

This simple analysis proves the well-known

$$\text{formula } V_{out} \downarrow = \omega_{id} (R_d \parallel R_L) = 1.3 V$$

To find the maximum output voltage, we set V_{in} and V_{out} to satisfy the saturation

$$\text{condition: i.e. } |V_{DS}| = |V_{GS}| - |V_{th}|$$


$$|V_{DS}| = |V_{out} - V_{in}| = V_{in} - V_{out} \quad \text{since } V_{in} > V_{out}$$

$$|V_{GS}| = |V_{in}| = V_{in} \quad ; \quad |V_{th}| = 0.3$$

$$\Rightarrow V_{in} - V_{out} = V_{in} - 0.3 \Rightarrow V_{out} = 0.3 \quad (V_{out} \text{ maximum})$$

$$\text{thus, } V_{gs} := |V_{out}(\text{at bias}) - V_{out}(\text{max})|$$
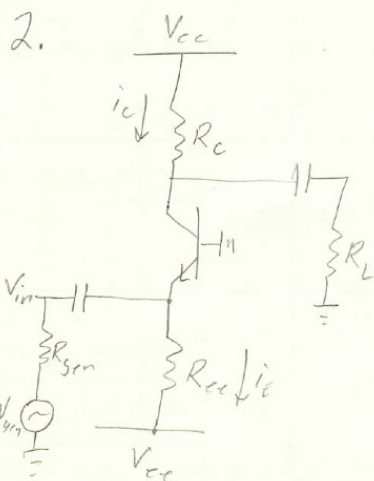
$$V_{gs} = \left[-0.87 V - 0.3 V \right] = 1.17 V$$



a) DC Bias

$$0V - V_{BE} - I_E R_{EE} = V_{CC}$$

$$R_{EE} = \frac{-V_{CC} - V_{BE}}{I_E} = \frac{+3.3V - 0.7V}{0.5mA}$$


$$\Rightarrow R_{EE} = 5.2 \text{ k}\Omega$$

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$R_C = \frac{V_{CC} - V_{CE}}{I_C} = \frac{3.3V - 1.0V}{(1 + \frac{1}{\beta}) I_E}$$

$$\Rightarrow R_C = 4.65 \text{ k}\Omega$$

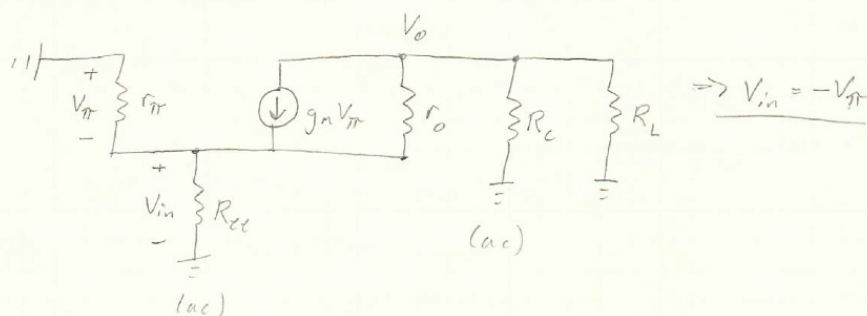b) The small signal model not neglecting the Early effect is:



$$\Rightarrow V_o / r_o - g_m V_{in} + V_o / R_C + V_o / R_L = 0$$

$$V_o \left(\frac{1}{r_o} + \frac{1}{R_C} + \frac{1}{R_L} \right) = g_m V_{in} \Rightarrow V_o / V_{in} = \frac{g_m r_o R_C R_L}{R_C R_L + r_o (R_C + R_L)}$$

$$g_m \approx \frac{I_C}{V_T} = 19.3 \text{ mS}; r_o \approx \frac{V_A}{I_C} = 200 \text{ k}\Omega \Rightarrow V_o / V_{in} = 26.80$$

2. b) (-cont.) - Using nodal analysis and the S.S. model:

$$i_{in} = -V_{in}/r_{\pi} + g_m V_{in} + V_{in}/r_o \quad \left(\begin{array}{l} \text{evaluate for } V_{out} \rightarrow \frac{1}{s} + 0 \\ \text{find input impedance} \end{array} \right)$$

$$\Rightarrow V_{in}/i_{in} = \left(-\frac{1}{r_{\pi}} + g_m + \frac{1}{r_o} \right)^{-1}$$

$$\Rightarrow R_{in} \approx 52.3 \, \Omega$$

→



$$\Rightarrow V_{in}/V_{gm} = 0.343 \quad \Rightarrow V_{out}/V_{gm} = 9.20$$

c) From (b), $R_{in} = 52.3 \, \Omega$

From the small signal model, it is clear that

$$R_{out} = R_L \parallel R_C \parallel r_o = \left(\frac{1}{R_C} + \frac{1}{r_o} \right)^{-1} = 4.5 \, k\Omega = R_{out}$$

d) At bias current using the small-signal approximation ($V_{out} \rightarrow \infty$),

We have $V_{out}(\text{at bias})$ • $(V_{o-3.3})/R_c + V_o/R_L = 0.5 \text{mA} \rightarrow V_o = 1.7 \text{V}$

$V_{out}(\text{max})$ occurs when $i_c = i_E = 0$

$$\Rightarrow V_{out}(\text{max}) = V_{cc} \left(\frac{R_L}{R_c + R_L} \right) = 1.0 \, \text{V}$$

$$\Rightarrow V_{out} \uparrow = 1.7 \, \text{V} - 1.0 \, \text{V} = 0.7 \, \text{V}$$

2. d) (cont.)

$V_{out(min)}$ occurs when the BJT is pushed into saturation. $\Rightarrow V_{ce} = 0.5V$


$$V_{ce} = V_o - V_{in} = 0.5V$$

$$1 - V_{in}/V_o = 0.5/V_o$$

$$V_o = 0.5 / (1 - 1/A_v) = 0.52V$$

$$V_{o_downswing} = 1.7V - 0.52V = 1.18V$$

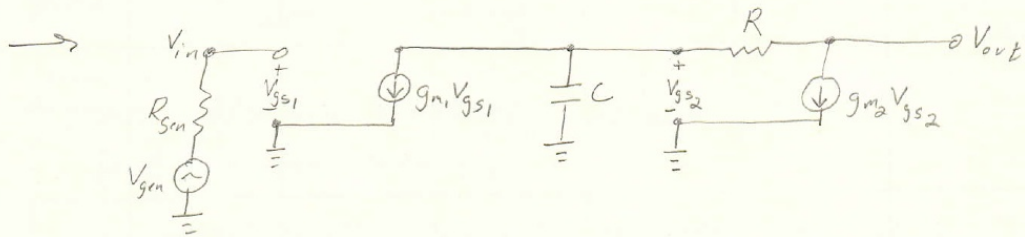3. Because $C_{gs} = C_{gd} = 0$, and $R_{ds} \rightarrow \infty$, we can use the
 a) most simple small signal model for the MOSFET's,
 however C is small and cannot be replaced with a short.



b) Clearly the infinite impedance going into the gate
 implies $V_{gs1} = V_{in}$. Obviously $V_{in} = V_{gs1}$.

Our 2 nodal equations are:

$$V_{gs2}(sC) + g_{m1}V_{gs1} + \frac{V_{gs2} - V_{out}}{R} = 0; \quad \frac{V_{gs2} - V_{out}}{R} = g_{m2}V_{gs2}$$

$$\rightarrow V_{gs2}\left(sC + \frac{1}{R}\right) + g_{m1}V_{in} - \frac{V_{out}}{R} = 0 \quad \left| \rightarrow V_{gs2} = V_{out}(1 - g_{m2}R)^{-1} \right.$$

$$V_{out}\left[\frac{(sC + \frac{1}{R})}{(1 - g_{m2}R)} - \frac{1}{R}\right] = -g_{m1}V_{in}$$

$$V_{out}\left[\frac{RCs + 1 - (1 - g_{m2}R)}{R(1 - g_{m2}R)}\right] = -g_{m1}V_{in}$$

$$V_{out}/V_{in} = -g_{m1}\left(\frac{1 - g_{m2}R}{Cs + g_{m2}}\right) = \frac{g_{m1}(g_{m2}R - 1)}{g_{m2}}\left(\frac{1}{1 + \frac{Cs}{g_{m2}}}\right)$$

Using the values given, $V_{out}/V_{in} = 58 \left(\frac{1}{1 + 10^{-10}s}\right)$

3. (cont.) c) Intuitively some may expect that this circuit would have low-pass behavior. This is reflected in the TF and there is a zero as $s \rightarrow \infty$. Pole at $\omega = 10^6 \rightarrow (f_{c1} = 1.6 \text{ GHz})$

d) See attached plot

e) Let's redo the problem and solve the ODE rather than just using the TF directly.

$$V_{gs2} = V_{out} (1 - g_{m2} R)^{-1}$$

and:

$$C \frac{dV_{gs2}}{dt} + V_{gs2}/R + g_{m1} V_{in} - V_{out}/R = 0$$

$$\frac{C}{(1 - g_{m2} R)} \frac{dV_{out}}{dt} + \frac{V_{out}}{R(1 - g_{m2} R)} - V_{out}/R = -g_{m1} V_{in}$$

$$\frac{dV_{out}}{dt} + V_{out} \left(\frac{1}{RC} - \frac{(1 - g_{m2} R)}{RC} \right) = \frac{-g_{m1} (1 - g_{m2} R)}{C} V_{in}$$

$$\frac{dV_{out}}{dt} + V_{out} \left(\frac{g_{m2}}{C} \right) = \frac{g_{m1} (g_{m2} R - 1)}{C} V_{in}$$

define $C/g_{m2} = \tau$; $\frac{g_{m1} (g_{m2} R - 1)}{C} V_{in} = K$ for $t \geq 0$

$$V_{out} = x$$

$$\Rightarrow \frac{dx}{dt} + \frac{x}{\tau} = K; \text{ this common differential equation is simple to solve.}$$

3. e) (cont.) $\frac{dx}{dt} + \frac{x}{\tau} = K$

For steady state $\frac{dx}{dt} \rightarrow 0$.

define $x_f = K\tau$ (final value of x)

$$\Rightarrow \frac{dx}{dt} = -\frac{(x - K\tau)}{\tau} = -\frac{(x - x_f)}{\tau}$$

$$\frac{dx}{x - x_f} = -\frac{1}{\tau} dt$$

$$\Rightarrow \int_{x(0)}^{x(t)} \frac{dx}{x - x_f} = \int_0^t -\frac{dt}{\tau}$$

$$\ln(x(t) - x_f) - \ln(x(0) - x_f) = -\frac{t}{\tau}$$

$$\Rightarrow \frac{x(t) - x_f}{x(0) - x_f} = e^{-t/\tau}$$

$$\rightarrow x(t) = (x(0) - x_f)e^{-t/\tau} + x_f$$

Because voltage cannot instantaneously change across a capacitor, $x(0) = 0$



$$\Rightarrow x(t) = x_f (1 - e^{-t/\tau})$$

$$\Rightarrow V_{out}(t) = \left(\frac{g_{m1}(g_{m2}R - 1)}{C} \right) \left(\frac{C}{g_{m2}} \right) V_{in}/_{t \geq 0} (1 - e^{-g_{m2}t/C})$$

$$\boxed{V_{out}(t) = (5.8 \text{ V})(1 - e^{-t/10^{-10} \text{ sec}}) \quad t \geq 0}$$

See attached plot.

4.

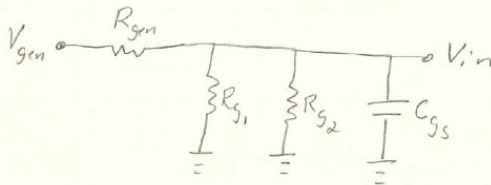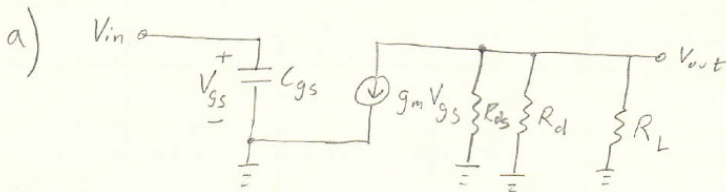

Note that R_{ds} is given to be 100Ω .

This is quite low!

$R_{ds} \approx \frac{1}{\lambda I_D} \Rightarrow \text{large } I_D \text{ or large } \lambda!!$

b) Nodal Equations: $-g_m V_{gs} = V_{out}/R_d + V_{out}/R_L + V_{out}/R_{ds}$

Clearly $V_{in} = V_{gs}$

$$\frac{V_{in} - V_{gen}}{R_{gen}} + \frac{V_{in}}{R_{g1}} + \frac{V_{in}}{R_{g2}} + V_{in} s C_{gs} = 0$$

$$\Rightarrow V_{in} \left(\frac{1}{R_{gen}} + \frac{1}{R_{g1}} + \frac{1}{R_{g2}} + s C_{gs} \right) = \frac{V_{gen}}{R_{gen}}$$

$$\Rightarrow V_{in}/V_{gen} = \frac{R_{g1} R_{g2}}{R_{g1} R_{g2} + R_{gen} R_{g2} + R_{gen} R_{g1} + s C_{gs} R_{gen} R_{g1} R_{g2}}$$

Using the values given; $V_{in}/V_{gen} = \frac{0.714}{1 + s/7 \cdot 10^7}$

And $V_{out} \left(\frac{1}{R_d} + \frac{1}{R_L} + \frac{1}{R_{ds}} \right) = -g_m V_{in} \Rightarrow V_{out}/V_{in} = \frac{-g_m}{\left(\frac{1}{R_d} + \frac{1}{R_L} + \frac{1}{R_{ds}} \right)} = -1.98$

$$\Rightarrow V_{out}/V_{gen} = \frac{-1.41}{1 + s/7 \cdot 10^7}$$

4. (cont.) c) Clearly there is a zero as $s \rightarrow \infty$ (and)

d) See attached plot Pole at $s = 7 \cdot 10^7$

e) Resolving, (not required) $\Rightarrow f_c = 11.1 \text{ MHz}$

$$V_{out}/V_{in} = -1.98 \left(\frac{1}{R_{gen}} + \frac{1}{R_{S1}} + \frac{1}{R_{S2}} \right)$$

$$V_{in} (7 \cdot 10^{-6} \Omega^{-1}) + C_{gs} dV_{in}/dt = \frac{V_{gen}}{200 \text{ k}\Omega} \quad (\text{nodal analysis})$$


$$dV_{in}/dt + \left(\frac{V_{in}}{7 \cdot 10^{-7} \text{ sec}} \right) = 5 \cdot 10^7 V_{gen}$$

$$\Rightarrow V_{in}(t) = 7.14 \text{ mV} (1 - e^{-t/1.42 \cdot 10^{-8}}) \quad (\text{see prob. 3 for justification})$$

$$V_{out} = (-14.1 \text{ mV V}) (1 - e^{-t/1.42 \cdot 10^{-8}})$$

for $V_{gen} = 10 \text{ mV}$ step at $t = 0$.

5.

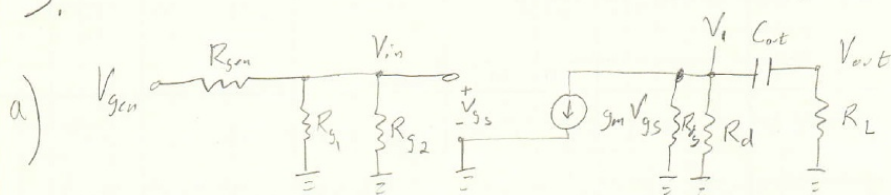

b) Clearly $V_{in} = V_{gs}$; Note: R_{ds} given to be very small!!

Nodal Eqn's: $\frac{V_{in} - V_{gen}}{R_{Sen}} + \frac{V_{in}}{R_{S1}} + \frac{V_{in}}{R_{S2}} = 0 \Rightarrow \frac{V_{in}}{V_{gen}} = \frac{R_{S1} R_{S2}}{R_{S1} R_{S2} + R_{Sen} (R_{S1} + R_{S2})}$

$$\frac{V_1}{R_{Ds}} + (V_1 - V_{out}) s C_{out} + V_1 / R_d + g_m V_{gs} = 0; (V_{out} - V_1) s C_{out} + V_{out} / R_L = 0$$

$$V_1 (s C_{out} + \frac{1}{R_d} + \frac{1}{R_{Ds}}) - s C_{out} V_{out} + g_m V_{in} = 0 \Rightarrow V_1 = V_{out} \left(\frac{1}{R_L s C_{out}} + 1 \right)$$

$$-g_m V_{in} = V_{out} \left[\left(s C_{out} + \frac{R_{Ds} + R_d}{R_d R_{Ds}} \right) \left(\frac{1}{R_L s C_{out}} + 1 \right) - s C_{out} \right] = V_{out} \left(\frac{1}{R_L} + s C_{out} + \frac{R_{Ds} + R_d}{R_d R_{Ds} s C_{out}} + \frac{R_{Ds} + R_d}{R_d R_{Ds}} - s C_{out} \right)$$

$$-g_m V_{in} = V_{out} \left(\frac{R_d R_{Ds} s C_{out} + R_{Ds} + R_d + (R_{Ds} + R_d) R_L s C_{out}}{R_{Ds} R_d R_L s C_{out}} \right)$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = - \frac{400}{202 s + 1005} = -1.98 \left(\frac{s}{1 + 0.2 s} \right)$$

Using the values given;

$$\frac{V_{in}}{V_{gen}} = 0.714$$

$$\Rightarrow \frac{V_{out}}{V_{gen}} = -1.41 s / (1 + 0.2 s)$$

5. c) One should predict a zero transfer function at

DC and this is indeed present in the TF.

There is no zero this time as $s \rightarrow \infty$, reflecting the fact that C_{gs} and C_{gd} cannot always be ignored.

$\Rightarrow$ 1 zero at $s=0$; pole at $s = 1/0.2$ ($\omega_{f_i} = 0.795 \text{ Hz}$)

d) See attached plot

e) For fun, let's solve this from the beginning.

$$\text{at } V_o: \frac{d}{dt}(V_{out} - V_i) C_{out} + V_{out}/R_L = 0 \Rightarrow \frac{d}{dt}(V_i - V_{out}) C_{out} = V_{out}/R_L$$

$$\frac{dV_i}{dt} = \frac{dV_{out}}{dt} + V_{out}/R_L C_{out} \Rightarrow V_i = V_{out} + \frac{1}{R_L C_{out}} \int_0^t V_{out} dt$$

$$\text{at } V_i: \frac{d}{dt}(V_i - V_{out}) C_{out} + g_m V_{in} + V_i/R_d + V_i/R_{ds} = 0$$

$$\Rightarrow V_{out}/R_L + g_m V_{in} + \frac{R_d + R_{ds}}{R_d R_{ds}} V_{out} + \frac{1}{R_L C_{out}} \int_0^t V_{out} dt = 0$$

This simple integral equation is easy to solve.
Let's use the Laplace transform!

$$\mathcal{L}\{V_{out}\} \left(\frac{1}{R_L} + \frac{R_d + R_{ds}}{R_d R_{ds}} \right) + \frac{R_d + R_{ds}}{R_L R_d C_{out} R_{ds}} \frac{\mathcal{L}\{V_{out}\}}{s} = -g_m \mathcal{L}\{V_{in}\}$$

$\rightarrow$

5.e) (cont.)


$$\rightarrow V_{out}(t) = -14.1 \text{ mV} e^{-0.2t} \quad ; t > 0$$

Email Questions/comments to:

anthony.mcfadden@umail.usb.edu