
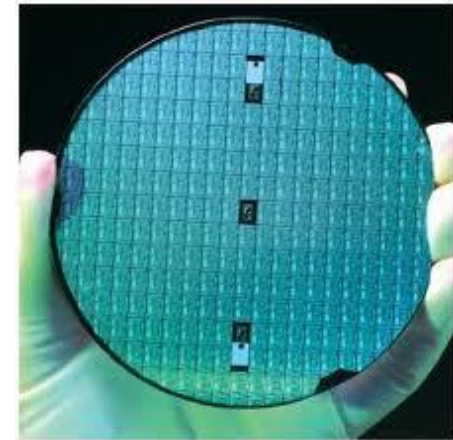
 


Structure of silicon crystal

 


ECE 122A

VLSI Principles

Lectures 16/17

Prof. Kaustav Banerjee
Electrical and Computer Engineering
University of California, Santa Barbara
E-mail: kaustav@ece.ucsb.edu

Semiconductor Memories....

 

Memory Design...

- ❑ Increasing number of transistors in uprocessors are devoted to **cache memories**....more than 60%, see ITRS for more details.....
- ❑ At the **system level**: high-performance workstations and desktops have **several Gbytes** of memory
- ❑ **Audio** (MP3), **Video players** (MPEG4) and **GPUs** require large amount of memory
- ❑ Can we store Memory using **registers**?yes but the **area** required will be excessive (need > 10 transistors/bit)
- ❑ Memory cells are therefore combined into **large arrays**, which minimizes the overhead caused by the peripheral circuits and increases **storage density**
- ❑ Memory design can be classified as **high-performance, high density, low-power circuit design**

Memory Classification

- ❑ Size
- ❑ Timing Parameters
- ❑ Function
- ❑ Access Pattern


Memory Size

- Depends on the **level of abstraction**
- **Bits**: (used by circuit designers) are equivalent to the number of individual cells (FFs or Registers) to store data
- **Bytes**: (used by chip designers) are groups of 8 or 9 bits or their multiples: Kbyte, Mbyte, Gbyte, Tbyte
- **Words**: (used by system designers) represent a basic computational entity. For example, a group of **32 bits represent a word** in a computer that operates on 32 bit data

Timing Parameters

- ❑ **READ-Access Time:** time it takes to retrieve (read) from the memory. This is equal to the delay between the read request and the moment the data becomes available at the O/P.
- ❑ **WRITE-Access Time:** time elapsed between a write request and the final writing of the input data into the memory
- ❑ **CYCLE Time:** minimum time required between successive reads or writes

Memory Timing: Definitions

 

Note: Read and Write cycles do not necessarily have the same length but are considered to be equal for simplicity of system design.

Function

❑ Read-Only Memory (ROM):

- encode the information into the circuit topology-by removing or adding transistors. The topology is hard wired and the **data cannot be modified....can only be read**.
- They belong to the class of **Non-volatile** memories. Disconnection of the supply voltage does not result in a loss of the stored data.

❑ Read-Write Memories (RWM): called as **RAM** (Random-Access Memories).

- **Static** (retains data if V_{dd} is retained): example SRAM
- **Dynamic** (needs periodic refreshing): example DRAM
- They use active circuitry to store information and belong to the class of **Volatile** memories.

Function....cont'd

❑ **Non-Volatile Read-Write (NVRWM):**

- Recent Non-Volatile Memories can read and write---although write function is substantially slower
- Novel, cheap and dense: Fastest growing among semiconductor memories

❑ **Examples:**

- EPROM: Electrically Programmable ROM
- E²PROM: Electrically Erasable and Programmable ROM
- Flash memory

Access Pattern

❑ Random-Access (RAM):

- memory locations can be read or written in a random manner
- Most ROMs and NVRWMs allow random access....but “RAM” is used for the RWMs only

❑ Serial Access:

- Restricts the order of access. Results in faster access times, smaller area, or allows special functionality
- Examples: (Video Memories)
 - FIFO (first-in first-out)
 - LIFO (last-in first-out)
 - Shift Register

❑ Content-Addressable Memory (CAM): (non-random access)

- Also known as associative memory
- Doesn't use an address to locate the data.....rather **uses a word of data itself as input**... when input data matches a data word stored in memory array, a MATCH flag is raised
- Important component of the cache architecture of most microprocessors

Semiconductor Memory Classification

Read-Write Memory		Non-Volatile Read-Write Memory	Read-Only Memory
Random Access	Non-Random Access	EPROM E ² PROM FLASH	Mask-Programmed Programmable (PROM)
SRAM DRAM	FIFO LIFO Shift Register CAM		

Where does your brain's memory fit into these classification schemes?

More Classification


❑ I/O Architecture:

- Based on the number of data input and output ports
- Most memories use a single I/O port
- **Multiport memories** offer higher bandwidth
 - Example: register files used in RISC processors
 - Adds more complexity to the design

❑ Application:


- Embedded Memories in SoCs
- For massive storage (multiples of Tbytes and beyond), more cost effective solutions are to use **magnetic tapes** and **optical disks**---they however, tend to be slower and provide limited access pattern

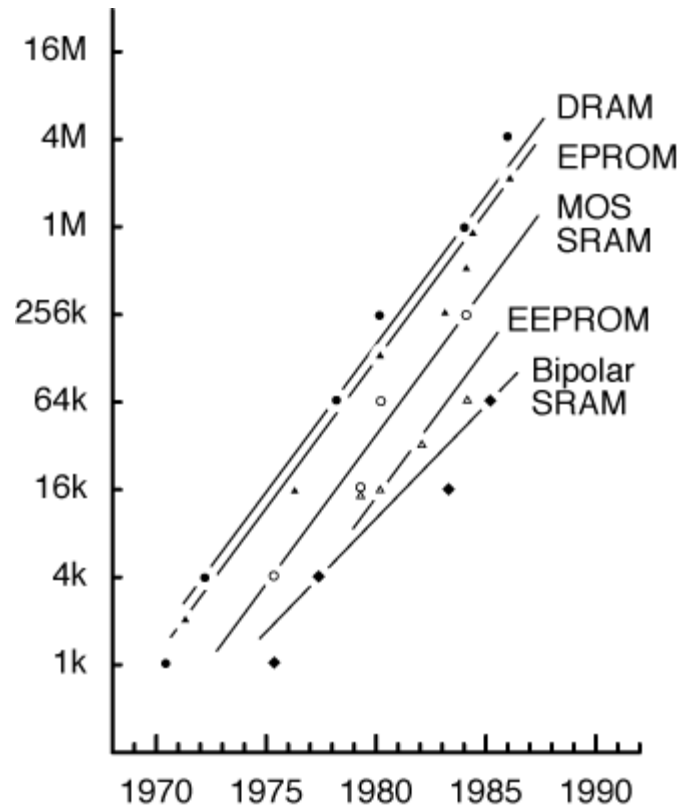Semiconductor Memory Trends (up to the 90's)




Memory Size as a function of time: $\times 4$ every three years

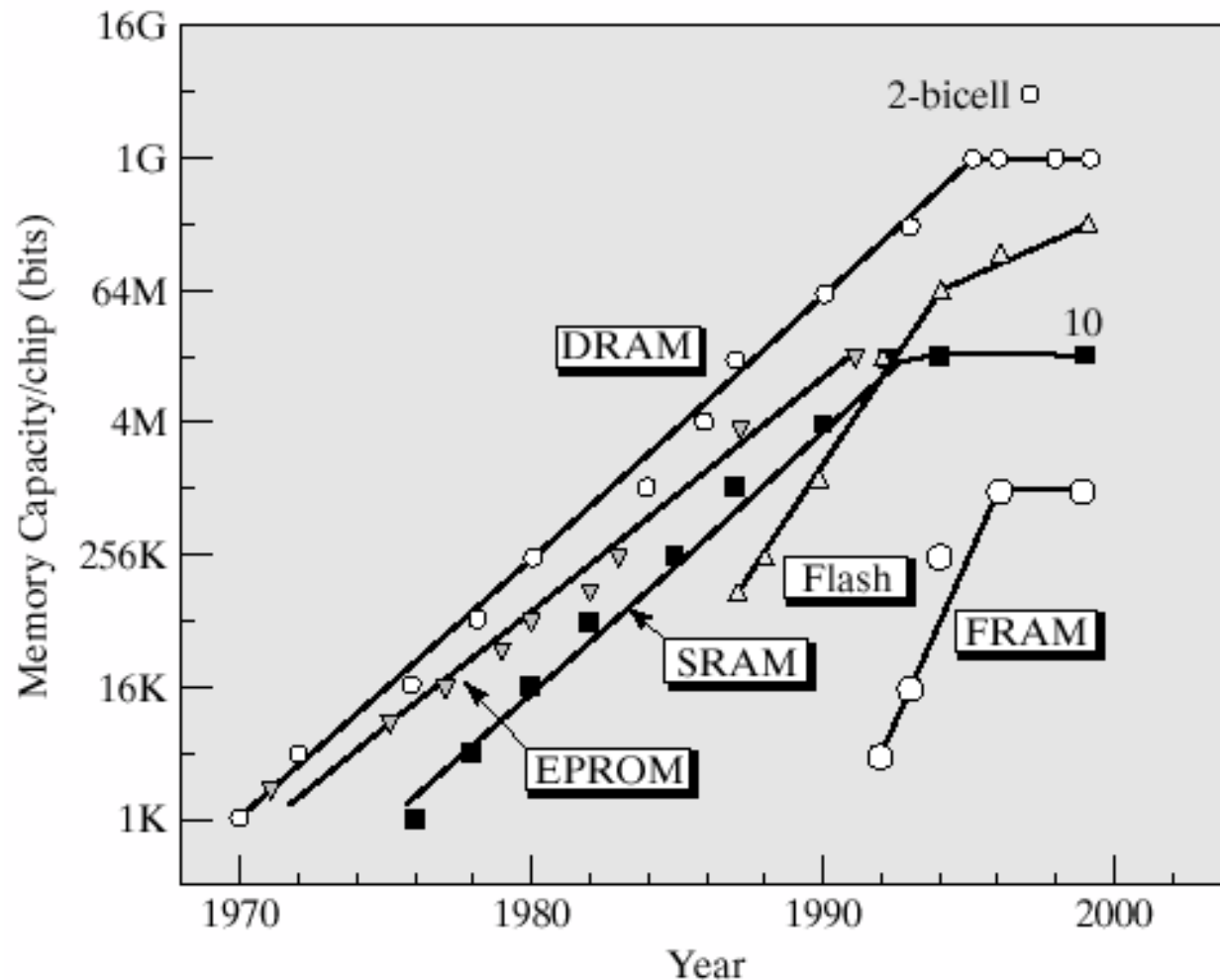Semiconductor Memory Trends (more recent...)




From [Itoh01]

Trends in Memory Cell Area

 


From [Itoh01]

Semiconductor Memory Trends

 


Technology feature size for different SRAM generations

Memory Architecture: Decoders

 

 
Intuitive architecture for $N \times M$ memory
Too many select signals:
 N words == N select signals



Decoder reduces the number of select signals
 $K = \log_2 N$

Decoder Basic

 
- ❑ Recall that a decoder is a combinational circuit with **k inputs** and at most **2^k outputs**.
- ❑ Its characteristics property is that for every combination of input values only **ONE** output =1 at the same time.
- ❑ Used to route input data to specific output line.



For example: for $a=b=c=0$, only $S0 = 1$

Array-Structured Memory Architecture

 Problem: consider ~1 million ($N=2^{20}$) 8-bit ($M=2^3$) words, ASPECT RATIO is very large!!! or HEIGHT $\gg$ WIDTH, cannot be implemented and will result in very slow design.....



Solution: Make vertical and horizontal dimensions of the same order of magnitude

Store multiple words in one row

Use a column decoder to select the correct word

← **Amplify swing to rail-to-rail amplitude**
For interfacing to the external world


← **Selects appropriate word**

OK for 64 Kbits to 256 Kbits beyond which speed degrades as length, C, and R of word/bit lines increase excessively

Peripheral circuitry is needed to recover the desired digital signal properties

Hierarchical Memory Architecture


For Larger Memories....

 

Advantages:

1. Shorter wires within blocks: faster access times
2. Block address activates only 1 block => power savings

Block Diagram of 4 Mbit SRAM

 

**32 blocks, each
containing 128 Kbits**

**Each block is
structured as an
array of 1024 rows
and 128 columns**

[Hirose90]

Read-Write Memories (RAM)

❑ **STATIC (SRAM)**

Data stored as long as supply is applied

Large (6 transistors/cell)

Fast

Differential

❑ **DYNAMIC (DRAM)**

Periodic refresh required

Small (1-3 transistors/cell)

Slower

Single Ended

6-transistor CMOS SRAM Cell

Should be minimum sized to achieve high memory density.....

READ Operation:

Assume 1 is stored at Q


Assume both BLs are held high before the read.

Read cycle started by asserting the WL, enables PTs M5 and M6

During a correct read operation values stored in Q and $\bar{Q}$ are transferred to the bit lines leaving BL at its precharge value and by discharging BL through M1-M5

A "0" can be read in a similar manner (now BL gets discharged through M6 and M3)

 Major advantage of dual BL: Q is clamped to V_{DD} by BL and prevents any inadvertent toggling of the INV pair




SRAM cell should be as small as possible.....but reliable operation requires careful sizing...

CMOS SRAM Analysis (Read “1” operation)

Transistor sizing is needed to avoid writing 1 accidentally, i.e., voltage at $\bar{Q}$ becomes $> V_M$ of Inv M3-M4

M1 must be stronger than M5

 $\overline{Q}$ must stay low enough so that there is no substantial current through M3-M4 INV



As difference between BL and BLB builds up, the sense amp. is activated to accelerate the reading process

$$k_{n,M5} \left((V_{DD} - \Delta V - V_{Tn}) V_{DSATn} - \frac{V_{DSATn}^2}{2} \right) = k_{n,M1} \left((V_{DD} - V_{Tn}) \Delta V - \frac{\Delta V^2}{2} \right)$$


(M5 in saturation) (M1 in linear)

$$\Delta V = \frac{V_{DSATn} + CR(V_{DD} - V_{Tn}) - \sqrt{V_{DSATn}^2(1 + CR) + CR^2(V_{DD} - V_{Tn})^2}}{CR}$$

Value of the ripple voltage

CR = cell ratio = M1/M5

CMOS SRAM Analysis (Read)

 

$$CR = \frac{W_1/L_1}{W_5/L_5}$$

**Choose
M5 to be
minimum
size and
M1 > M5**

Node voltage must stay below the V_{th} of M3: CR must be >1.2

CMOS SRAM Analysis (Write)



Assume that $Q=1$

To write a 0 in the cell: set $\overline{BL}=1$ and $BL=0$

Similar to applying a reset pulse to an SR latch. FF will change state if sized properly

$\overline{Q}$ cannot be pulled high due to the sizing of M5 and M1 already done for reading

New value must be written through M6

  

Reliable writing of the cell is ensured if we can pull node Q low enough—below the V_{th} of M1

$$k_{n, M6} \left((V_{DD} - V_{Tn}) V_Q - \frac{V_Q^2}{2} \right) = k_{p, M4} \left((V_{DD} - |V_{Tp}|) V_{DSATp} - \frac{V_{DSATp}^2}{2} \right)$$


(M6 in linear) (M4 in saturation)

$$V_Q = V_{DD} - V_{Tn} - \sqrt{(V_{DD} - V_{Tn})^2 - 2 \frac{\mu_p}{\mu_n} PR \left((V_{DD} - |V_{Tp}|) V_{DSATp} - \frac{V_{DSATp}^2}{2} \right)},$$

PR = pull-up ratio of cell = M4/M6

CMOS SRAM Analysis (Write)

 Dependence of V_Q on Pull-up Ratio.....lower PR gives lower V_Q



$$PR = \frac{W_4 / L_4}{W_6 / L_6}$$


Should be low to keep V_Q low

PR between the PMOS (M4) pull-up and the NMOS (M6) Pass Transistor must be < 1.8 to keep $V_{tn} < 0.4$ V


Performance of SRAM

- ❑ Read operation is more critical. It requires discharging of the large bit line capacitance through the stack of 2 transistors (M1-M5)
- ❑ Write time is dominated by the propagation delay of the cross-coupled inverter pair, since the drivers that set BL and $\overline{BL}$ can be large
- ❑ Sense amplifiers used to accelerate Read time....as the difference between BL and $\overline{BL}$ builds up, sense amplifier is activated, and it discharges one of the bit lines

Sense Amp Operation

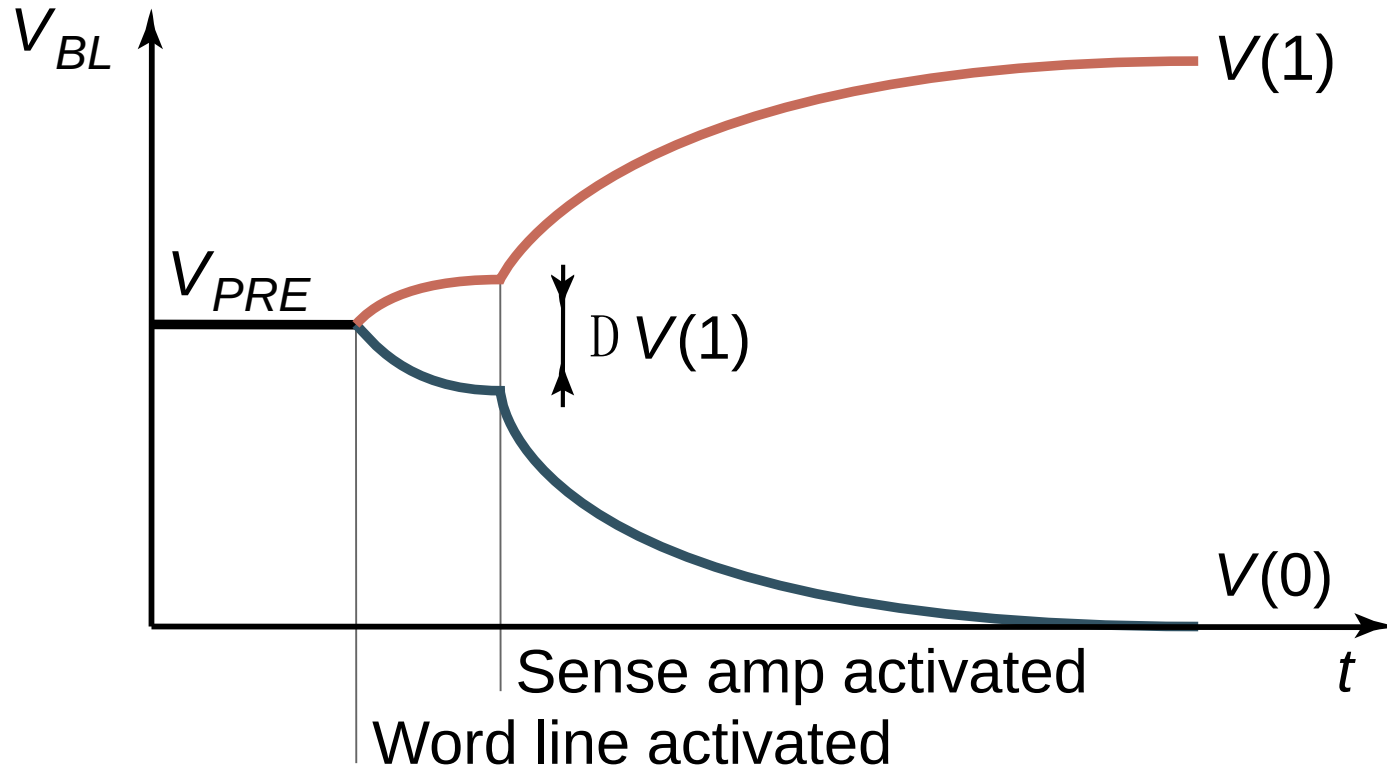


6T-SRAM — Layout

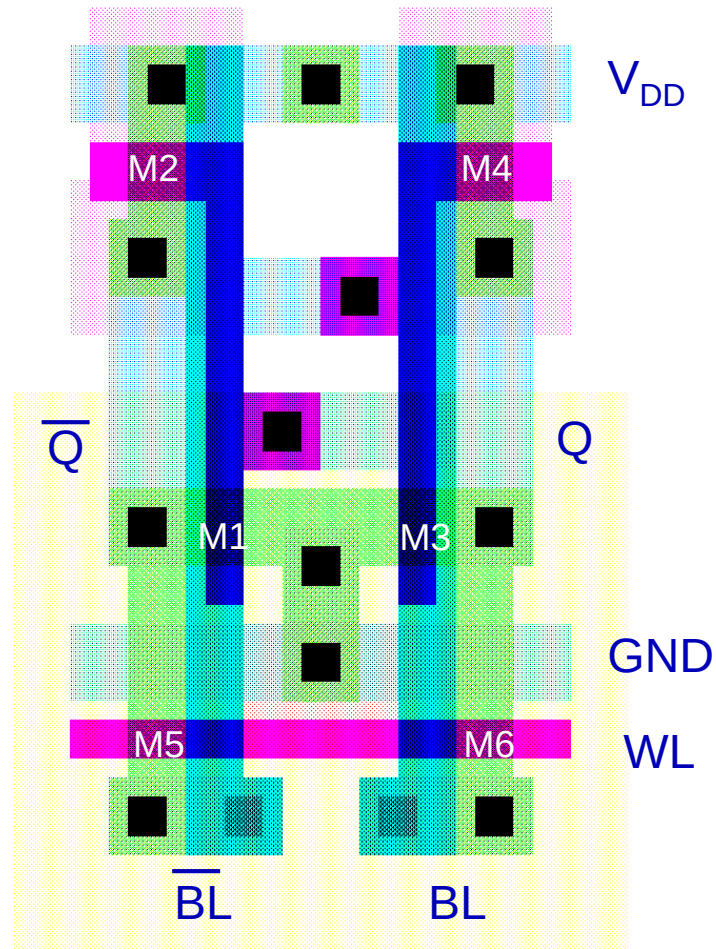

6T SRAM
Takes
significant
area...the two
PMOS need
n-wells

Resistive-load (4T) SRAM Cell

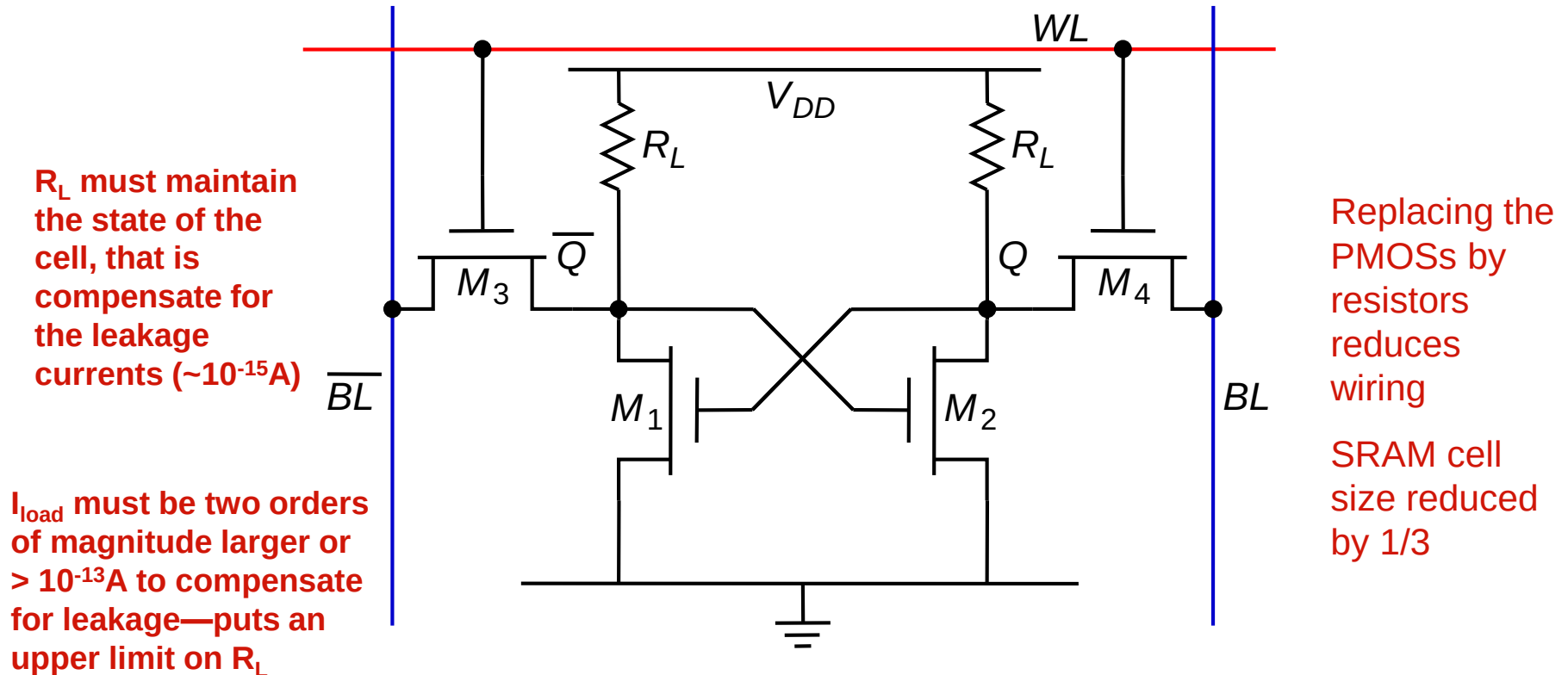Reduce area using resistive load inverters...simplifies writing



Static power dissipation -- Want R_L large (use undoped poly)
Bit lines precharged to V_{DD} to address t_p problem

SRAM Characteristics

Table 12-2 Comparison of CMOS SRAM cells used in 1-Mbit memory (from [Takada91])



	Complementary CMOS	Resistive Load	TFT Cell
Number of transistors	6	4	4 (+2 TFT)
Cell size	58.2 μm^2 (0.7- μm rule)	40.8 μm^2 (0.7- μm rule)	41.1 μm^2 (0.8- μm rule)
Standby current (per cell)	10^{-15} A	10^{-12} A	10^{-13} A

Instead of PMOS devices, use parasitic devices on top of cell structure using thin-film transistors (TFTs)


Use high V_t

However, embedded SRAM cells---used in microprocessor caches, employ 6T cells.

6-T CMOS SRAM Cell: Static Noise Margin

  

Butterfly Curve

 



The SNM (hold margin) can be estimated graphically by the **length of the side of the square** fitted between the VTCs and having the longest diagonal.

As noise increases at the two nodes above, the reverse VTC for INV1 moves upward, while the VTC for INV2 moves to the left (**worst case**)

Once they both move by the SNM value, the curves meet at only two points.....at A' and B'..... and any further noise flips the data.

Static Noise Margin (SNM)

 
 
- ❑ **Hold Margin:** How strongly the node storing '1' and the node storing '0' are coupled to V_{DD} and V_{SS} respectively.
- ❑ **Read Margin:** The difference between V_{TRIP} and V_{READ} (max. voltage at Q)
- ❑ **Write Margin:** The maximum voltage on a bit-line that allows writing to the cell, while the other bit-line is at V_{DD} . (not determined by the butterfly curve)



SNM Dependencies

- Dependence on V_{DD} : SNM for a bitcell with ideal VTCs is still limited to $V_{DD}/2$
- Dependence on sizing

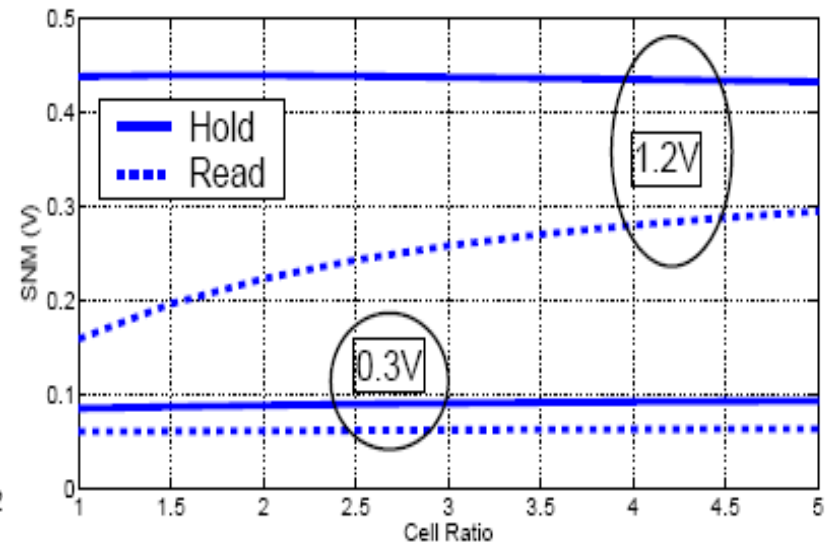 Here, Cell ratio = size of PD device over size of access device





3-Transistor DRAM Cell (Early Days)

1 Kbit memory: Intel

Still used in some ASICs

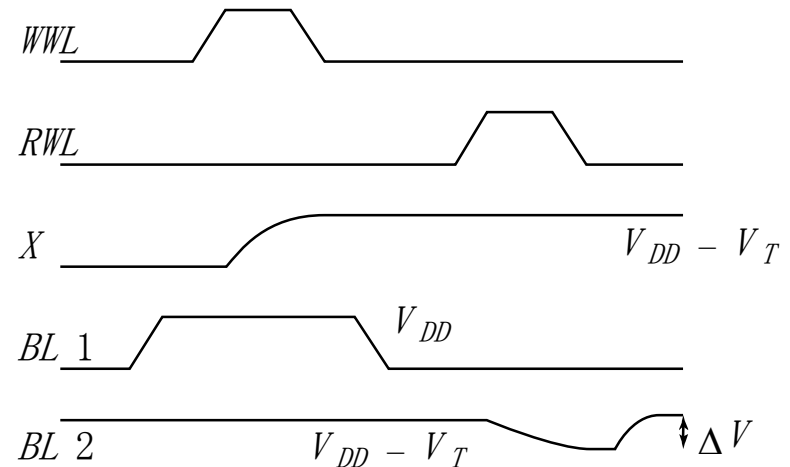 Dynamic: since it involves charge storage on a capacitor



Cell is **written** by placing value on BL1 and asserting Write Word Line (WWL=1)

Data retained as charge stored on Cs once WWL=0



For reading the cell, $RWL=1$

M2 can be on or off depending on stored value

BL2 is either clamped to Vdd or is precharged to either Vdd or Vdd-Vt

M2-M3 pulls BL2 low when X=1, otherwise BL2 remains high (cell is inverting: senses the inverse value of the stored signal)

3T-DRAM — Layout

 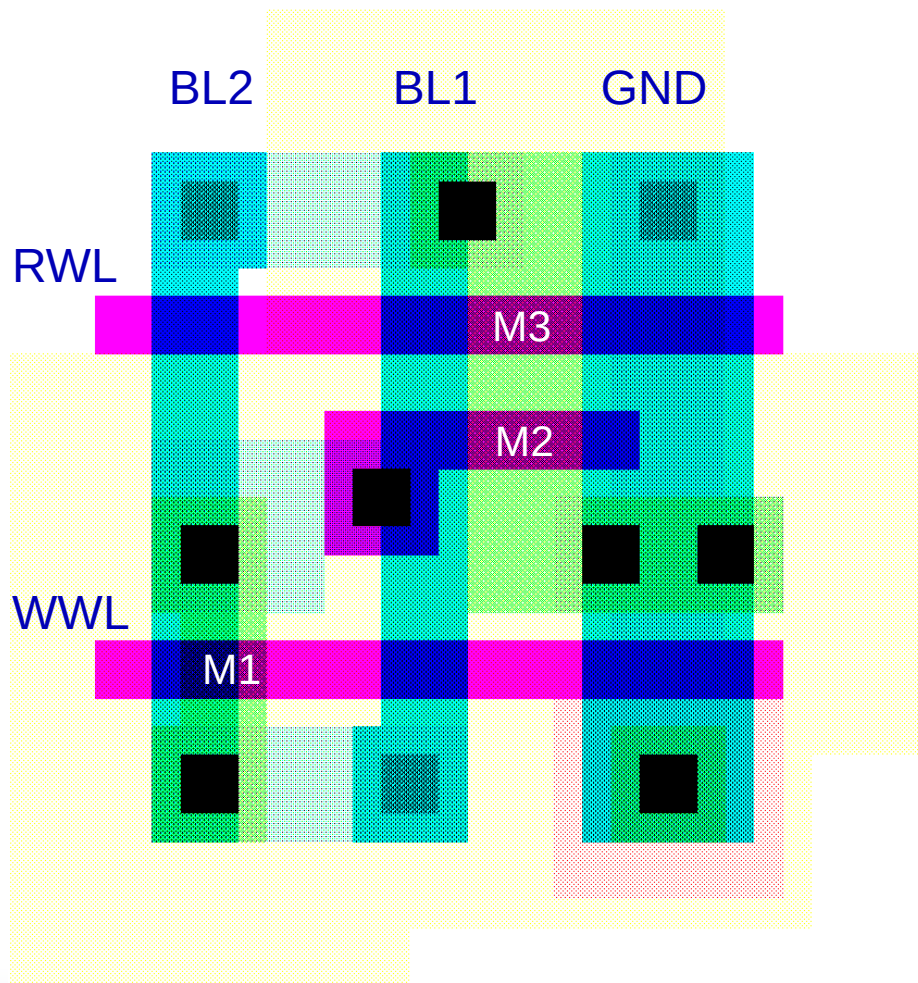

Unlike SRAM, no constraint on device sizes

Read operation is non-destructive


No special process steps needed

Value at node X = $V_{WWL} - V_{tn}$

This reduces the current through M₂ during read operation and increases read access time: can use a higher value of V_{WWL} to avoid this

1-Transistor DRAM Cell

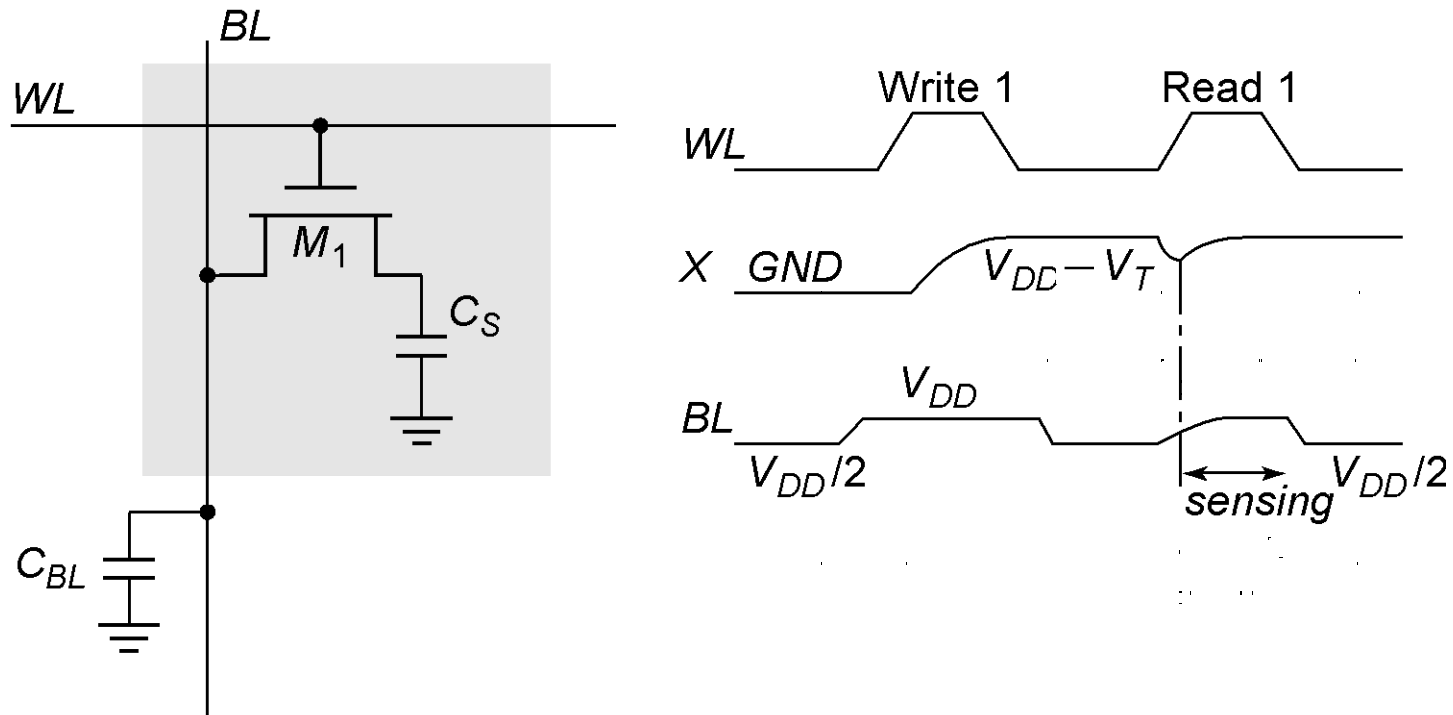Most pervasive in commercial memory design



Write: Place data on BL and assert WL, depending on data value, C_S is 1 or 0

Read: before read, precharge BL to V_{PRE}

After $WL=1$, charge redistribution takes place between bit line and storage capacitance resulting in a voltage change on BL

$$\Delta V = V_{BL} - V_{PRE} = V_{BIT} - V_{PRE} \frac{C_S}{C_S + C_{BL}}$$


Charge transfer ratio (1-10%)

V_{BIT} is initial voltage on C_S . V_{BL} is final voltage on BL after charge redistribution. Voltage swing is small since $C_S \ll C_{BL}$; typically around 250 mV.


DRAM Cell Observations

- ❑ 1T DRAM requires a sense amplifier for each bit line, due to charge redistribution read-out.
- ❑ DRAM memory cells are single ended in contrast to SRAM cells.
- ❑ The read-out of the 1T DRAM cell is destructive; read and refresh operations are necessary for correct operation.
- ❑ Unlike 3T cell, 1T cell requires presence of an extra capacitance that must be explicitly included in the design.
- ❑ When writing a “1” into a DRAM cell, a threshold voltage is lost. This charge loss can be circumvented by bootstrapping the word lines to a higher value than V_{DD}

1-T DRAM Cell

 

Cross-section

 


Layout

Uses Polysilicon-Diffusion Capacitance
Expensive in Area



SEM of poly-diffusion capacitor 1T-DRAM



Advanced 1T DRAM Cells

 


Trench Cell

  


Stacked-capacitor Cell

Non-Volatile Memory

 
Flash Memory (with Floating Gate (FG) Transistor)



 N-type device
CG: control gate
COX: control oxide
FG: floating gate
TOX: tunnel oxide



NAND vs. NOR circuit

 

*Devices can be
Randomly accessed*

Both SG devices needed for read out

NAND vs. NOR

Merits of NAND

- ① High speed programming
- ② High speed erasing

Demerits of NAND

- ① Slow random access
- ② Byte programming can not be performed



- Applications -

- Suitable for Data memory
(Handy terminal, Voice recorder, DSC, Fax modem, etc)

Merits of NOR

- ① High speed random access
- ② Byte programming

Demerits of NOR


- ① Slow programming
- ② Slow speed erasing



- Applications -

- Suitable for replacement of EPROM
- Suitable for control memory
(BIOS, Cellular, HDD, etc)

Scaling issues

 

thin COX/TOX -> leakage current -> short retention time
small cell-to-cell distance -> V_{th} perturbation by adjacent cells

Promising solution: low dimensional materials

3-D ICs : Multiple Active Si Layers

K. Banerjee et al., Proceedings of the IEEE, 2001

- **Advantages**

- Reduce Interconnect Length by **Vertically Stacking** Multiple Si Layers
- Reduce **Chip Area**, power dissipation and improve Chip Performance
- **Heterogeneous integration** possible, e.g., memory, digital, analog, optical, etc. using different substrates (Si, III-V etc)

