
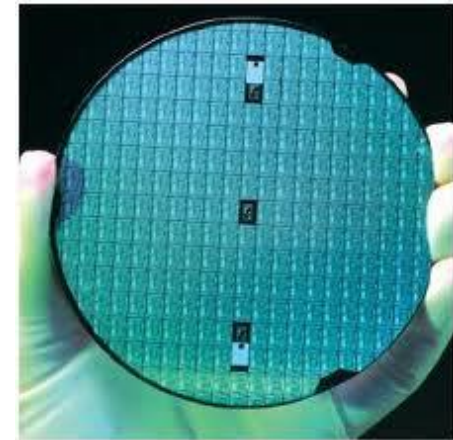
 


Structure of silicon crystal

 



ECE 122A

VLSI Principles

Lecture 9

Prof. Kaustav Banerjee
Electrical and Computer Engineering
University of California, Santa Barbara
E-mail: kaustav@ece.ucsb.edu



CMOS Inverter

  

Two Inverters


Share power and ground

Abut cells

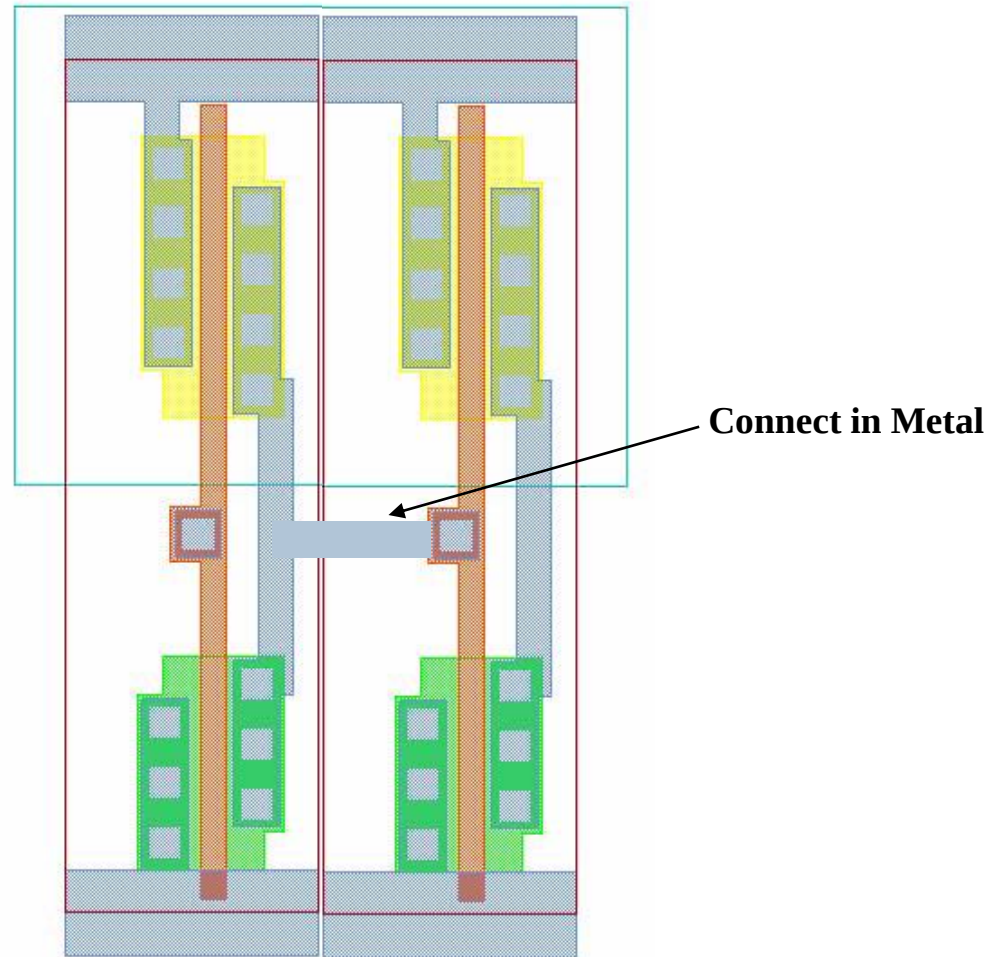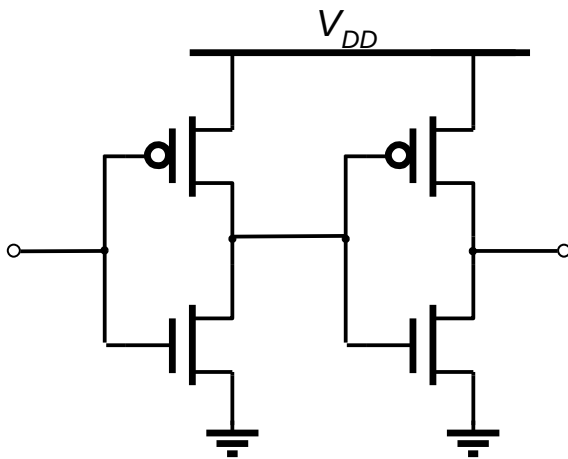


CMOS Inverter

First-Order DC Analysis

 


$$\begin{aligned} V_{OL} &= 0 \\ V_{OH} &= V_{DD} \\ V_M &= f(R_n, R_p) \end{aligned}$$

CMOS Inverter: Transient Response

 

$V_{out} =$ (a) Low-to-high

 


(b) High-to-low

$$t_{pHL} = f(R_{on} \cdot C_L) \\ = 0.69 R_{on} C_L$$


Note: C_L is composed of drain diffusion capacitances of NMOS/PMOS, wire caps (if any), and the input cap. of the fanout gates.....

The Transistor as a Switch

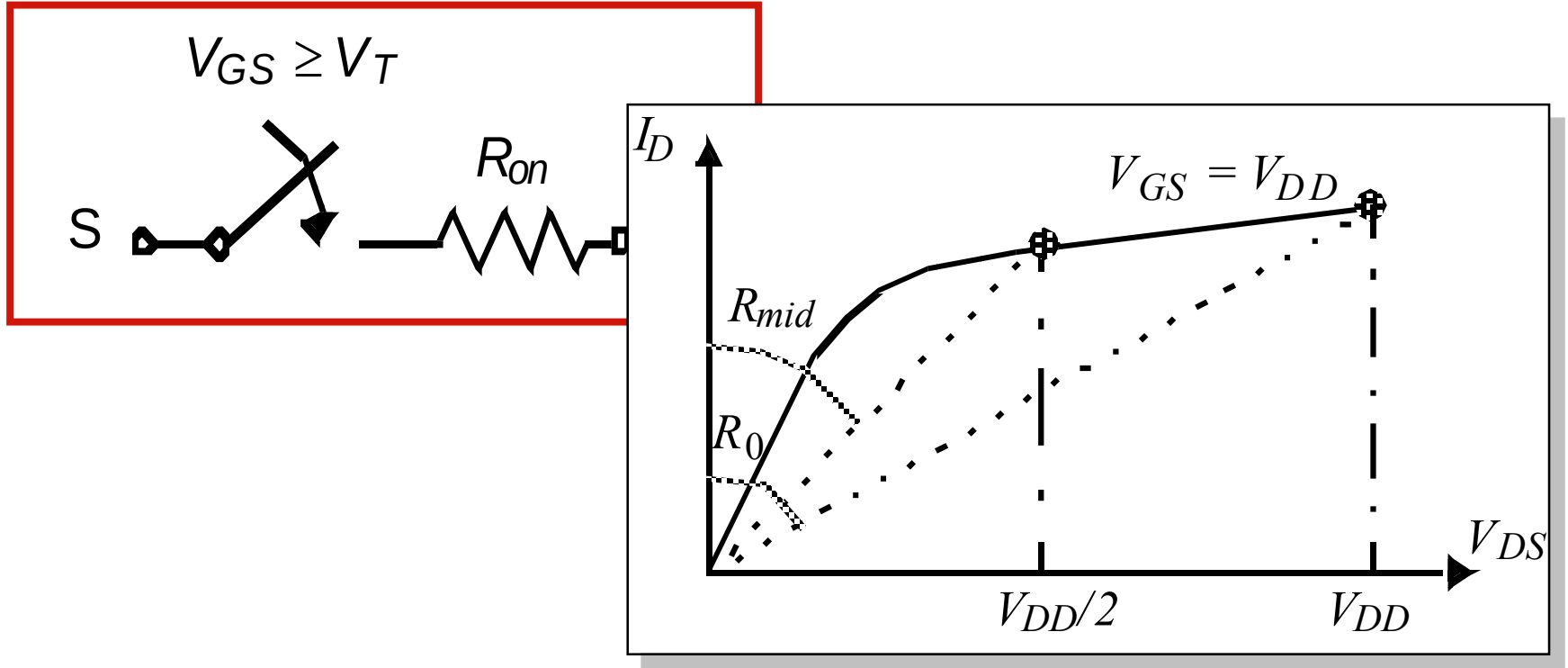

$$R_{eq} = \frac{1}{2} \left(\frac{V_{DD}}{I_{DSAT}(1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT}(1 + \lambda V_{DD}/2)} \right) \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{5}{6} \lambda V_{DD} \right)$$

The Transistor as a Switch

 

As V_{DD} increases, drain current increases....for both NMOS and PMOS

The Transistor as a Switch


Table 3.3 Equivalent resistance R_{eq} ($W/L = 1$) of NMOS and PMOS transistors in 0.25 μm CMOS process (with $L = L_{min}$). For larger devices, divide R_{eq} by W/L .

V_{DD} (V)	1	1.5	2	2.5
NMOS ($k\Omega$)	35	19	15	13
PMOS ($k\Omega$)	115	55	38	31


Resistive-load Inverter

- ❑ Requires only NMOS transistor and resistor
- ❑ When $V_{in} = 0$:
 - NMOS is OFF ($V_{GS} = 0$)
 - No current through NMOS or resistor
 - $V_{out} \approx V_{cc}$
- ❑ When $V_{in} = V_{cc}$:
 - NMOS is ON ($V_{GS} = V_{cc}$)
 - NMOS ON resistance $\ll R$
 - $V_{out} \approx 0$

 
Not suitable for VLSI: large area of R , DC power dissipation.



 
Remember: if body terminal not shown, it is connected to gnd for NMOS, V_{cc} for PMOS



Resistive-load Inverter

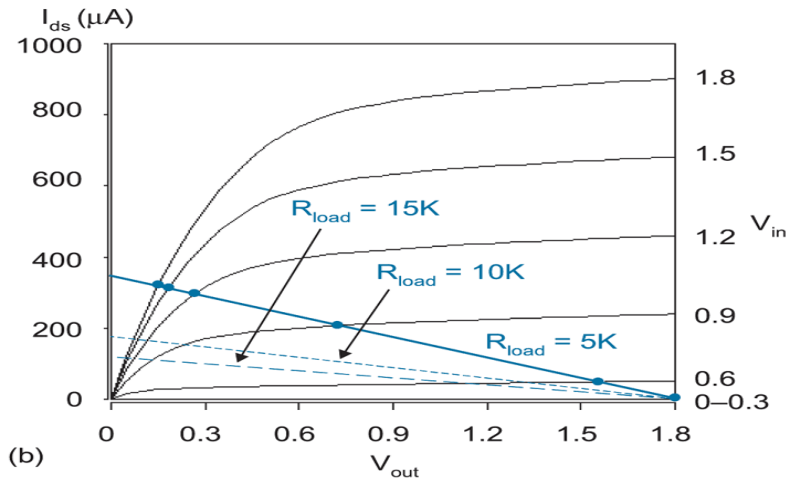

$$I_{ds} = V_{cc}/R_{load}$$

 


As R_{load} increases, V_{TC} becomes sharper!

Larger R_{load} = smaller PU transistor...LO skewed...

FIG 2.29 Generic nMOS inverters with resistive or constant current load


Pseudo-NMOS Inverter

- ❑ Replace resistor with “always-on” PMOS transistor
- ❑ Easier to implement in standard process than large resistance value
- ❑ PMOS load transistor:
 - ON when $V_{GS} < V_T \rightarrow V_{GS} = -V_{CC}$: transistor always on
 - Linear when $V_{DS} > V_{GS} - V_T \rightarrow V_{out} - V_{CC} > -V_{CC} - V_T \rightarrow V_{out} > -V_T$
 - Saturated when $V_{DS} < V_{GS} - V_T \rightarrow V_{out} - V_{CC} < -V_{CC} - V_T \rightarrow V_{out} < -V_T$

 


Remember:
 $V_T(\text{PMOS}) < 0$

Pseudo-NMOS Inverter

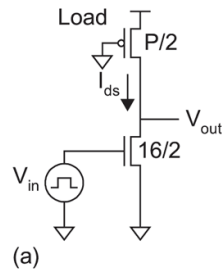

 **Compare with
resistive-load
inverter!**



**Note: Smaller
Width of PMOS
(P) means larger V_{out}
resistance**


 
 



FIG 2.30 Pseudo-nMOS inverter and DC transfer characteristics

Propagation Delay

Two CMOS Inverters...

 

CMOS inverter capacitances

 

Cap on Node f:

- **Junction cap:** $C_{db,p}$ and $C_{db,n}$
- **Gate (overlap) capacitance** $C_{gd,p}$ and $C_{gd,n}$ (beware of Miller effect)
- **Interconnect cap:** C_{int}
- **Receiver gate cap:** C_g

Assumption: V_{in} is driven by an ideal voltage source....with zero rise and fall times....hence the transistors are either in cut-off or saturation mode...hence, no channel capacitance

CMOS inverter capacitances

$$C_{load} = \underbrace{C_{db,n} + C_{db,p}} + \underbrace{C_{gd,n} + C_{gd,p}} + C_{int} + \underbrace{C_{gate}}$$

$$C_{db,n}, C_{db,p} = AK_{eq}C_{j0} + PK_{eqsw}C_{jsw}$$

$$C_{gd,n}, C_{gd,p} = 2WX_D C_{ox}$$


↑
Miller Effect

$$C_{gate} = WL_{drawn} C_{ox}$$

↑
For each gate

CMOS Inverter Propagation Delay


Approach 1

 


$$t_{pHL} = \frac{C_L V_{swing}/2}{I_{av}}$$

Note: $q = C V$

 CMOS Inverter Propagation Delay Approach 2



 
$$t_{pHL} = f(R_{on} \cdot C_L) \\ = 0.69 R_{on} C_L$$



Transient Response

 Due to C_{gd} of transistors: directly couples voltage at input to output before the transistors can even start to react to changes at the input---can affect gate performance



Symmetric inverter has $t_{pHL} = t_{pLH}$

$$t_p = 0.69 C_L (R_{eqn} + R_{eqp})/2$$


$$R_{eq} = \frac{1}{V_{DD}/2} \int_{V_{DD}/2}^{V_{DD}} \frac{V}{I_{DSAT}(1 + \lambda V)} dV \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{7}{9} \lambda V_{DD} \right)$$

with $I_{DSAT} = k' \frac{W}{L} \left((V_{DD} - V_T) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$


CMOS Inverter Delay as a function of V_{DD}

Same as the ON resistance of a transistor....

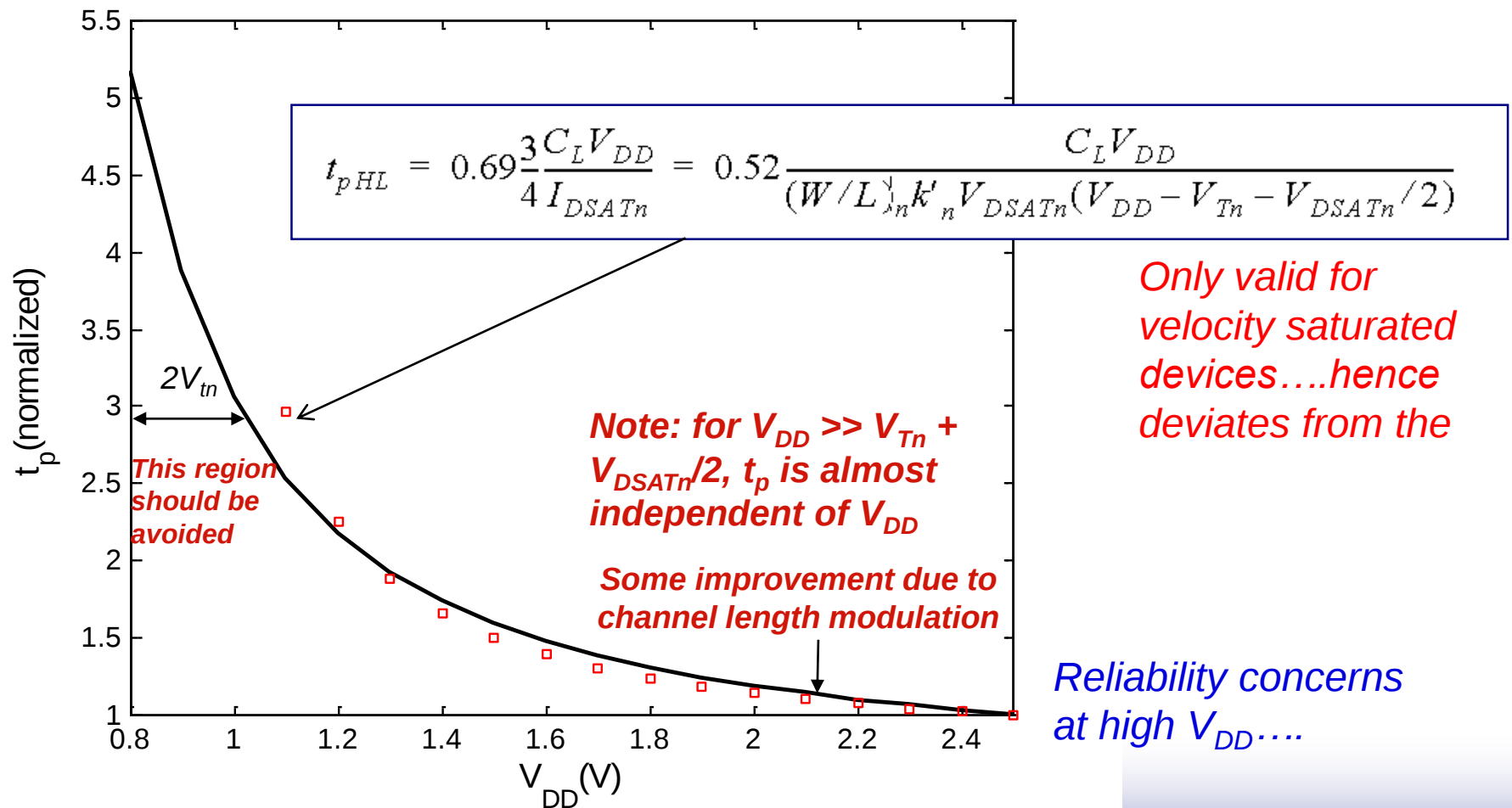
Trade off energy dissipation vs performance.....



Effect of Device Sizing

 


NMOS/PMOS ratio

 

If symmetry and noise margins are not of prime concern, inverter delay can be reduced by reducing the width of PMOS....

Impact of Rise Time on Delay

 

As the input signal changes gradually, both PMOS and NMOS conduct simultaneously....

$$t_{pHL} = \sqrt{t_{pHL(step)}^2 + (t_r/2)^2}$$

Design for Performance

- Keep load capacitances (C_L) small
 - Recall that three major components contribute to the load cap.
 - internal diffusion + overlap caps
 - interconnect cap.
 - fan-out (gate cap)
- Increase transistor sizes
 - watch out for self-loading!
- Increase V_{DD} (??)
 - watch out for reliability issues!

Power Dissipation

Where Does Power Go in CMOS?

- **Dynamic Power**

Due to charging/discharging of capacitors....

- **Leakage Power**

- *Subthreshold*


- *Gate*

- *Junction*

- **Short-Circuit Power**

When NMOS and PMOS are both turned ON....

Dynamic Power Dissipation

 

Note: Here C_L is an external capacitor....

$$\text{Energy/transition} = C_L * V_{dd}^2$$


$$\text{Power} = \text{Energy/transition} * f = C_L * V_{dd}^2 * f$$

- Energy/transition is not a function of transistor sizes!
- Need to reduce C_L , V_{dd} , and f to reduce power.

Energy taken from supply during transition:

$$E_{V_{DD}} = \int_0^{\infty} i_{V_{DD}}(t) V_{DD} dt = V_{DD} \int_0^{\infty} C_L \frac{dv_{out}}{dt} dt = C_L V_{DD} \int_0^{V_{DD}} dv_{out} = C_L V_{DD}^2$$

Dynamic Power Dissipation

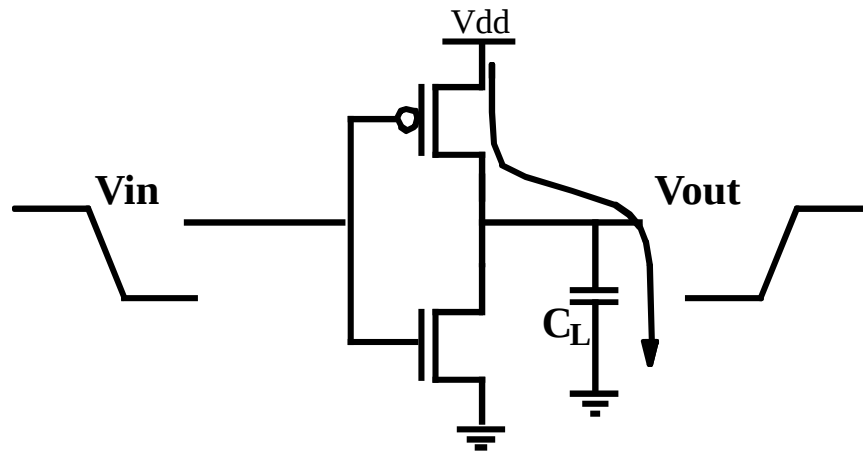

Note: during the discharge phase, charge is removed from C_L and its energy is dissipated in the NMOS

Energy taken from supply during transition:


$$E_{V_{DD}} = \int_0^{\infty} i_{V_{DD}}(t) V_{DD} dt = V_{DD} \int_0^{\infty} C_L \frac{dv_{out}}{dt} dt = C_L V_{DD} \int_0^{V_{DD}} dv_{out} = C_L V_{DD}^2$$

Energy stored in the capacitor:

$$E_C = \int_0^{\infty} i_{V_{DD}}(t) v_{out} dt = \int_0^{\infty} C_L \frac{dv_{out}}{dt} v_{out} dt = C_L \int_0^{V_{DD}} v_{out} dv_{out} = \frac{C_L V_{DD}^2}{2}$$

Where is the other half of the energy?Dissipated by the PMOS

 
Modification for Circuits with Reduced Swing



$$E_{0 \rightarrow 1} = C_L \cdot V_{dd} \cdot (V_{dd} - V_t)$$

- Can exploit reduced swing to lower power (e.g., reduced bit-line swing in memory)



Primary Leakage Mechanisms

 

Sub-threshold current one of most compelling issues in low-energy circuit design!


Subthreshold Leakage Component

  Subthreshold Slope = $S = 60 \text{ mV/decade}$ (for ideal transistor with $n=1$)



- Leakage control is critical for low-voltage operation


Reverse-Biased Diode Leakage

 


$$I_{DL} = J_S \times A$$

$J_S = 10\text{-}100 \text{ pA}/\mu\text{m}^2$ at 25 deg C for 0.25 μm CMOS
 J_S doubles for every 9 deg C!

Short Circuit Currents

 

(a)
CMOS
inverter.

 


(b) Voltage and current waveforms.

K. Banerjee and A. Mehrotra, IEEE Transactions on Electron Devices, Vol. 49, No. 11, 2002.

Fig. 5. Voltage and current waveforms of a CMOS inverter.

Static Power Consumption

 In the absence of switching....steady-state operation



Sources:

Due to all previously mentioned leakage currents.....

$$P_{stat} = P_{(In=1)} \cdot V_{dd} \cdot I_{stat}$$

Wasted energy ...

Should be avoided in almost all cases,
but could help reducing energy in others (e.g. sense amps)

Leakage

□ Effect of leakage current

- “Wasted” power: power consumed even when circuit is inactive
- Leakage power raises temperature of chip
- Can cause functionality problem in some circuits: memory, dynamic logic, etc.

□ Reducing transistor leakage

- Long-channel devices
- Small drain voltage
- Large threshold voltage V_T

Principles for Power Reduction

- ❑ Prime choice: Reduce voltage!
 - Recent years have seen an acceleration in supply voltage reduction
 - Design at very low voltages still open question (0.6 ... 0.9 V by 2010!)
- ❑ Reduce switching activity
- ❑ Reduce physical capacitance
 - Device Sizing

Leakage Power Reduction

□ Process scaling

- V_T reduces with each new process (historically)
- Leakage increases $\sim 10X$!

□ Leakage vs. performance tradeoff:

- For high-speed, need small V_T and L
- For low leakage, need high V_T and large L

□ One solution: dual- V_T process

- Low- V_T transistors: use in critical paths for high speed
- High- V_T transistors: use to reduce power

Scaling Theory:

Parameters		Constant Vdd scaling	Constant E scaling
Dimentions	Width = w	0.7	
	Length = L	0.7	
	Oxide thickness t_{ox}	0.7	
	Junction depth X_j	0.7	
Die Area		$(0.7)^2$	
Gate capacitance per unit area ($C_{gox} = \frac{\epsilon_{ox}}{t_{ox}}$)		$\frac{1}{0.7}$	
Gate capacitance ($C_g = wLC_{gox}$)		0.7	
Total Capacitance (C)		0.7	
Supply Voltage (V_{DD})		1	0.7
Current per device ($I_{DS} \propto \frac{w}{L} \frac{\epsilon_{ox}}{t_{ox}} (V_{gs} - V_{th}) V_{DD}$)		1	0.7
Intrinsic Gate Delay ($\tau = \frac{C_g \Delta V}{I_{AV}}$)		0.7	0.7
Frequency ($f \propto \frac{1}{\tau}$)		$\frac{1}{0.7}$	
Active Power Dissipation ($P_{active} = CV_{DD}^2 f$)		1	$(0.7)^2$
Energy-Delay Product ($CV_{DD}^2 \tau$)		$(0.7)^2 = 0.49$	$(0.7)^4 = 0.2401$
Power Dissipation density ($\frac{P_{active}}{Area}$)		$\frac{1}{(0.7)^2} \approx 2$	$\frac{(0.7)^2}{(0.7)^2} \approx 1$

