
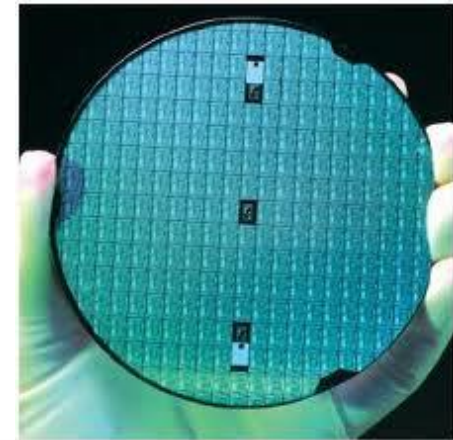
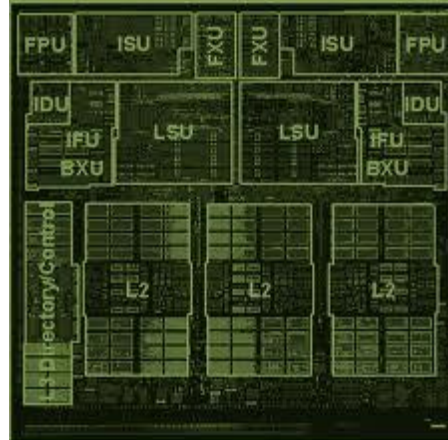


Structure of silicon crystal

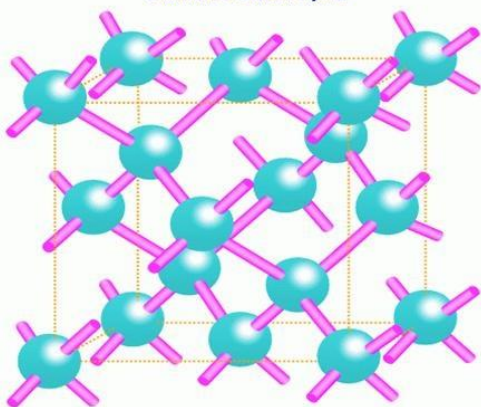


ECE 122A

VLSI Principles


Lecture 13

Prof. Kaustav Banerjee
Electrical and Computer Engineering
University of California, Santa Barbara
E-mail: kaustav@ece.ucsb.edu

The Wire

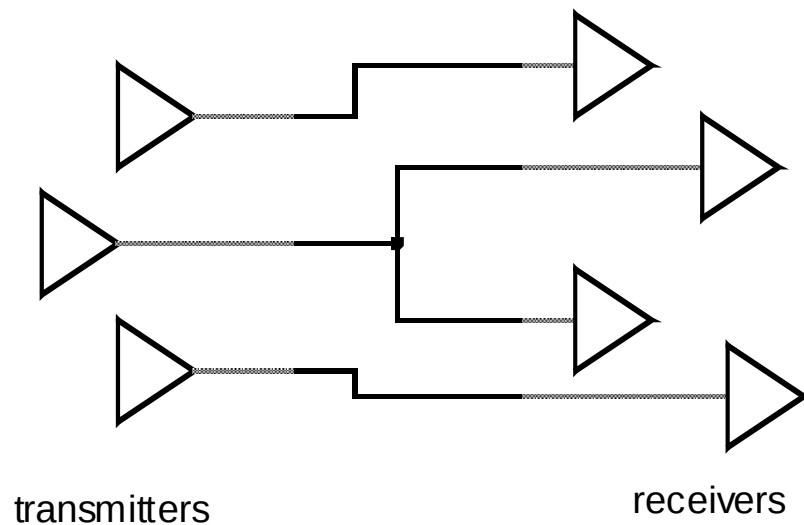


schematics

 

physical


Interconnect Impact on Chip

 

1. Process architecture challenge.

Interconnect delay has become the dominant factor determining chip performance.....

Wire Vs Gate Delay.....

 

Interconnect delay has become the dominant factor determining chip performance...


K. Banerjee et al., Proc. IEEE, May 2001.

Impact of Interconnect Parasitics

- ❑ Interconnect parasitics
 - affect performance and power consumption
 - affect reliability


- ❑ Classes of parasitics
 - Resistive
 - Capacitive
 - Inductive

Wire Resistance

 

$$R = \frac{\rho L}{HW}$$

 Sheet Resistance *Unit of*
 R_0 *" Ω/sq " or*
" $\Omega/\square$ "



Easier to compare wires with different (but uniform) thicknesses...

Interconnect Resistance

Material	ρ ($\Omega\text{-m}$)
Silver (Ag)	1.6×10^{-8}
Copper (Cu)	1.7×10^{-8}
Gold (Au)	2.2×10^{-8}
Aluminum (Al)	2.7×10^{-8}
Tungsten (W)	5.5×10^{-8}

Dealing with Resistance

- ❑ **Selective Technology Scaling**
- ❑ **Use Better Interconnect Materials**
 - reduce average wire-length
 - e.g. copper, silicides
- ❑ **More Interconnect Layers**
 - reduce average wire-length

Sheet Resistance

Material	Sheet Resistance ($\Omega/\square$)
n- or p-well diffusion	1000 – 1500
n^+ , p^+ diffusion	50 – 150
n^+ , p^+ diffusion with silicide	3 – 5
n^+ , p^+ polysilicon	150 – 200
n^+ , p^+ polysilicon with silicide	4 – 5
Aluminum	0.05 – 0.1

Example: Intel 0.25 micron Process


5 metal layers

Ti/Al - Cu/Ti/TiN

Polysilicon dielectric

LAYER	PITCH	THICK	A.R.
Isolation	0.67	0.40	-
Polysilicon	0.64	0.25	-
Metal 1	0.64	0.48	1.5
Metal 2	0.93	0.90	1.9
Metal 3	0.93	0.90	1.9
Metal 4	1.60	1.33	1.7
Metal 5	2.56	1.90	1.5
	μm	μm	

 Layer pitch, thickness and aspect ratio $=h/w$



Interconnect (RC) Delay

On-Chip VLSI interconnects can be modeled as RC elements

- *R is the wire resistance =*

ρ is the resistivity of the metal
$$\rho \frac{L}{A} = \rho \frac{L}{w \cdot h}$$

L is the wire length

A is the cross sectional area = wh (w is the width and h is the height of the wire)

- *C is the wire capacitance. For a parallel plate capacitor*

$$C = \epsilon_d \frac{A}{d}, \epsilon_d = k \epsilon_0$$

A is the area of the plate

d is the distance between the plates

k is the dielectric constant of the insulating material between the plates

ϵ_0 is the permittivity of free space

***If we can reduce both R and C ,
we can reduce wire delay.....***


Will better materials like copper and low-k dielectrics solve the interconnect problem?

Cu has lower resistivity than Al, and is more robust (reliable) than Al.....

Changing Interconnect Materials

- ❑ Replace Al wires by Cu wires
- ❑ Resistivity of Al = $2.65 \mu\Omega\text{-cm}$
@ Room Temp. (20-25 °C)
- ❑ Resistivity of Cu = $1.67 \mu\Omega\text{-cm}$
@ Room Temp. (20-25 °C)
- ❑ Reduction in R is not even a factor of 2.....

VLSI Interconnect Structure

 


Adjacent wires are orthogonal....why?

C_{intra} is the dominating capacitance.....why?

Capacitance: The Parallel Plate Model

1-dimensional model

Valid when, $W \gg t_{di}$

 


$$C_{int} = \frac{\epsilon_{di}}{t_{di}} WL$$

Permittivity

Material	ϵ_r
Free space	1
Aerogels	~ 1.5
Polyimides (organic)	3-4
Silicon dioxide	3.9
Glass-epoxy (PC board)	5
Silicon Nitride (Si_3N_4)	7.5
Alumina (package)	9.5
Silicon	11.7

Fringing Capacitance Model

 


Approximates the capacitance as the sum of two components:

$$C_{\text{wire}} = C_{\text{pp}} + C_{\text{fringe}} = \frac{W\epsilon_{\text{di}}}{t_{\text{di}}} + \frac{2\pi\epsilon_{\text{di}}}{\text{arccosh}\left(\frac{2t_{\text{di}}}{H} + 1\right)}$$

Orthogonal field between a wire of width $w = (W - H/2)$ and the ground plane

 Modeled by a cylindrical wire of diameter = H



Fringing Cap.

In parallel with..


Parallel plate Cap.

$$\text{arccosh}\left(\frac{2t_{\text{di}}}{H} + 1\right) \approx \ln\left(\frac{4t_{\text{di}}}{H} + 2\right)$$

as $t_{\text{di}} > 0.5H$

Fringing versus Parallel Plate

 
Saturates to
 $\sim 1\text{pF/cm}$ due to
fringing fields



Note: aspect ratio = H/W


(from [Bakoglu89])

Interconnect

 

- Usually interconnect layers alternate wire direction

Impact of Interwire Capacitance

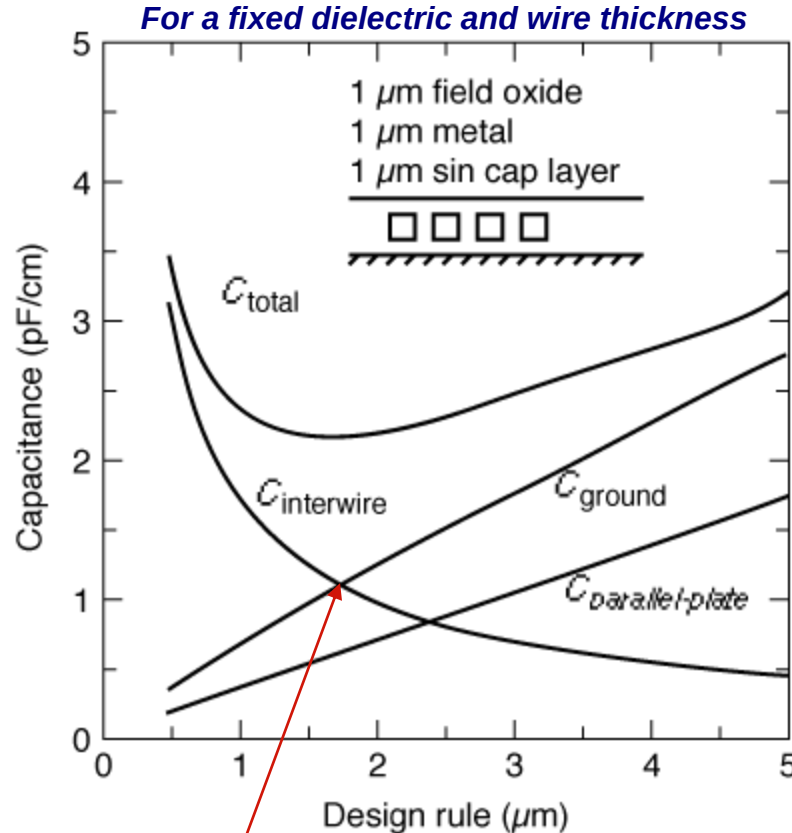

$H/W = 1.75$

- Reduce wire width, w
- Reduce spacing ($=w$)
- $C_{total} = C_{ground} + C_{interwire}$
- $C_{ground} = C_{p-p} + C_{fringing}$


Interwire capacitance (crosstalk), becomes important in a multi-level structure

More important for higher level wires that are far away from substrates

(from [Bakoglu89])


Interconnect Modeling

Capacitances of Driver-Wire-Load

 


Fanout


Simplified
Model

 

Wire Models

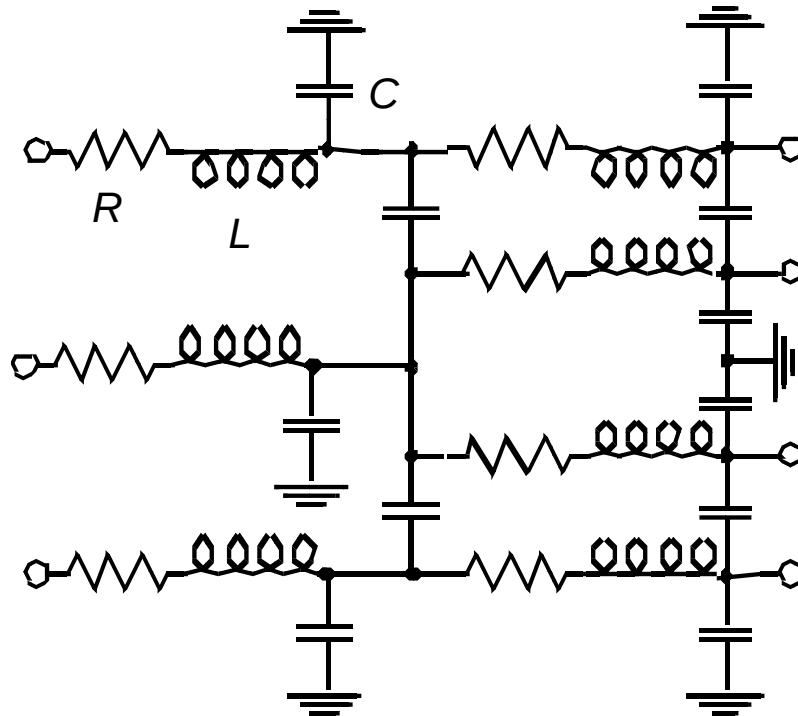



All-inclusive model

 


Capacitance-only

The Lumped Capacitor Model

  *Assuming no voltage drops along the wire....
i.e., wire is equipotential*



 If r is small and switching frequencies are not too high...



Advantage: Operation can be described by ordinary differential equation

The Lumped Capacitor Model

Operation of a simple RC circuit :

$$C_{lumped} \frac{dV_{out}}{dt} + \frac{V_{out} - V_{in}}{R_{driver}} = 0$$

If a step input is applied from 0 to V :

$$V_{out}(t) = \left(1 - e^{-t/\tau}\right)V$$

where $\tau = R_{driver} C_{lumped}$: time-constant of network


The time to reach 50% point can be calculated as :

$$t = \ln(2)\tau = 0.69\tau$$

If $R_{driver} = 10\text{K}\Omega$ and $C_{lumped} = 11\text{pF}$:

$t = 76\text{ns}$ (a very large number for high-performance digital circuits)

 Driver modeled as a voltage source and a source resistance (R_{driver}), $C_{lumped} = L \times c_{wire}$



Only impact on performance is due to the loading effect of the capacitor on the driving gate

The Lumped RC-Model


- On-chip metal wires at the semi-global and global tiers can be several millimeters long and can have significant resistance
- The equipotential assumption is no longer valid
- Need an RC model.....
- **A simple approach:** lump wire resistance of each segment into a single R and the global capacitance into a single C
 - This is called a lumped RC model....**pessimistic and inaccurate for long wires**
 - Should use a **distributed RC** model for such long wires

Then what is the use of the lumped RC model?

Lumped RC-Networks.....

- The **distributed RC model is complex**: involves partial differential equations, closed form solution does not exist
- However, the behavior of a distributed RC line can be **adequately modeled** by a simple RC network
- It is **more convenient** to reduce any driver-wire-load networks to an equivalent RC network and predict its first order response
- ***However, unlike the single R-C network analyzed earlier that had a single time constant (network pole), deriving the correct waveforms for a complex network becomes intractable***
 - Need to **solve a set of ordinary differential equations** with many time constants (poles and zeroes)....
 - Or, run time-consuming **SPICE simulations** for the entire network....

Elmore Delay Comes to the Rescue.....

 

RC Tree: unique resistive paths between s and any node i

Total resistance along this path is called the **path resistance** R_{ii}

e.g., path resistance between s and node 4:

$$R_{44} = R_1 + R_3 + R_4$$

Shared path resistance: resistance shared among the paths from root node s to nodes k and i


$$R_{ik} = \sum R_j \Rightarrow (R_j \in [path(s \rightarrow i) \cap path(s \rightarrow k)])$$

$$\text{Example: } R_{i4} = R_1 + R_3$$

$$R_{i2} = R_1$$

Elmore Delay-RC Chain (Branched)

 W. C. Elmore, "The transient response of damped linear networks," J. Appl. Phys., vol. 19, pp. 55–63, Jan. 1948.




If a step input V_{in} is applied at $t=0$

Elmore Delay at node i : $\tau_{Di} = \sum_{k=1}^N C_k R_{ik}$ **$N = \#$ of capacitances in the network**

(First-order time constant of the network)

Hence, $\tau_{D1} = C_1 \cdot R_{11} + C_2 \cdot R_{12} + \dots + C_n \cdot R_{1n} = C_1 \cdot R_1 + C_2 \cdot R_1 + \dots + C_n \cdot R_1$

Wire Model

 

For a chain, number of capacitances = number of nodes, hence,

For a non-branched RC chain: $\tau_{DN} = \sum_{i=1}^N C_i R_{ii}$ $t_{Di} = C_1 R_1 + C_2 (R_1 + R_2) + \dots + C_i (R_1 + R_2 + \dots + R_i)$

If wire modeled by N equal-length segments ($R_{seg} = rL/N$, $C_{seg} = cL/N$)

$$\tau_{DN} = \left(\frac{L}{N}\right)^2 (rc + 2rc + \dots + Nrc) = (rcL^2) \frac{N(N+1)}{2N^2} = RC \frac{N+1}{2N}$$




r and c represent the resistance and capacitance per unit length of the wire, respectively...

For large values of N:

$$\tau_{DN} = \frac{RC}{2} = \frac{rcL^2}{2}$$

The Distributed RC-line

  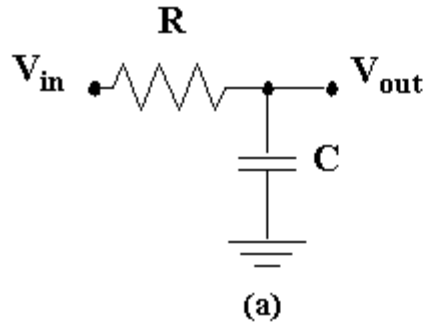(can be approximated by the lumped RC network model)




The diffusion equation

$$rc \frac{\partial V}{\partial t} = \frac{\partial^2 V}{\partial x^2}$$

$$\tau(V_{out}) = \frac{rc L^2}{2}$$

 Step-response of RC wire as a function of time and space




RC-Models

Voltage Range	Lumped RC-network	Distributed RC-network
0→50% (t_p)	0.69 RC	0.38 RC
0→63% (τ)	RC	0.5 RC
10%→90% (t_r)	2.2 RC	0.9 RC

Step Response of Lumped and Distributed RC Networks:
Points of Interest.

SPICE Wire (RC) Models:

 *accuracy of the model
determined by number of
stages*



RC Delay: Design Rules of Thumb


- rc delays should only be considered when $t_{pRC} \gg t_{pgate}$ of the driving gate or $0.38(rL).(cL) \gg t_{pgate}$
$$L_{crit} \gg \sqrt{t_{pgate}/0.38rc}$$

- rc delays should only be considered when the rise (fall) time at the line input is smaller than RC, the rise (fall) time of the line

$$t_{rise} < RC$$

- when not met, the change in the signal is slower than the propagation delay of the wire

Illustration of Rule: Driving an RC-line

 

$$R_w = r_w L$$

$$C_w = c_w L$$

Total Propagation Delay: $\tau_D = R_s C_w + \frac{R_w C_w}{2} = R_s C_w + 0.5 r_w c_w L^2$

Delay due to wire resistance becomes important when

$(R_w C_w / 2) \geq R_s C_w$ or when $L \geq 2R_s / r_w$

0 to 50% Response Delay: $t_p = 0.69 R_s C_w + 0.38 R_w C_w$