 


ECE 225
High Speed Integrated Circuit Design
Lecture 14

Prof. Kaustav Banerjee
Electrical and Computer Engineering
E-mail: kaustav@ece.ucsb.edu


Timing Issues

Flip-Flop – Based Timing




*Representation after
M. Horowitz, VLSI Circuits 1996.*

Flip-Flops and Dynamic Logic

 

Flip-flops are used only with static logic

Latch timing

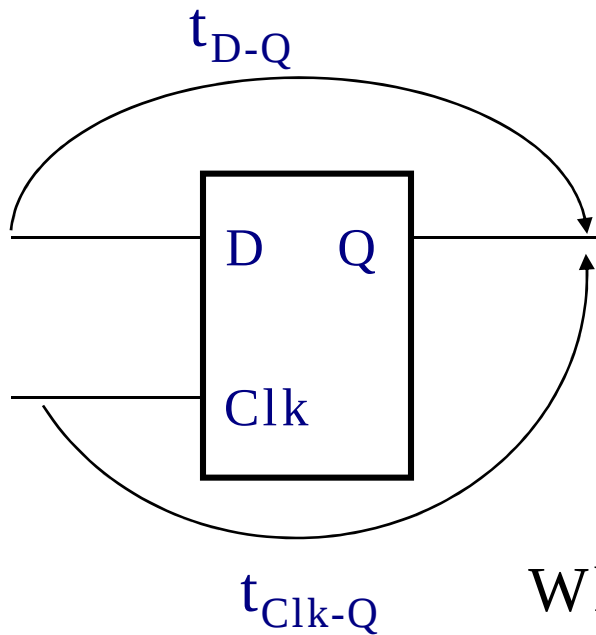



When data arrives
to transparent latch

Latch is a 'soft' barrier

When data arrives
to closed latch

Data has to be 're-launched'


Single-Phase Clock with Latches

  

Latch-Based Design


L1 latch is
transparent
when $\phi = 0$

L2 latch is transparent
when $\phi = 1$

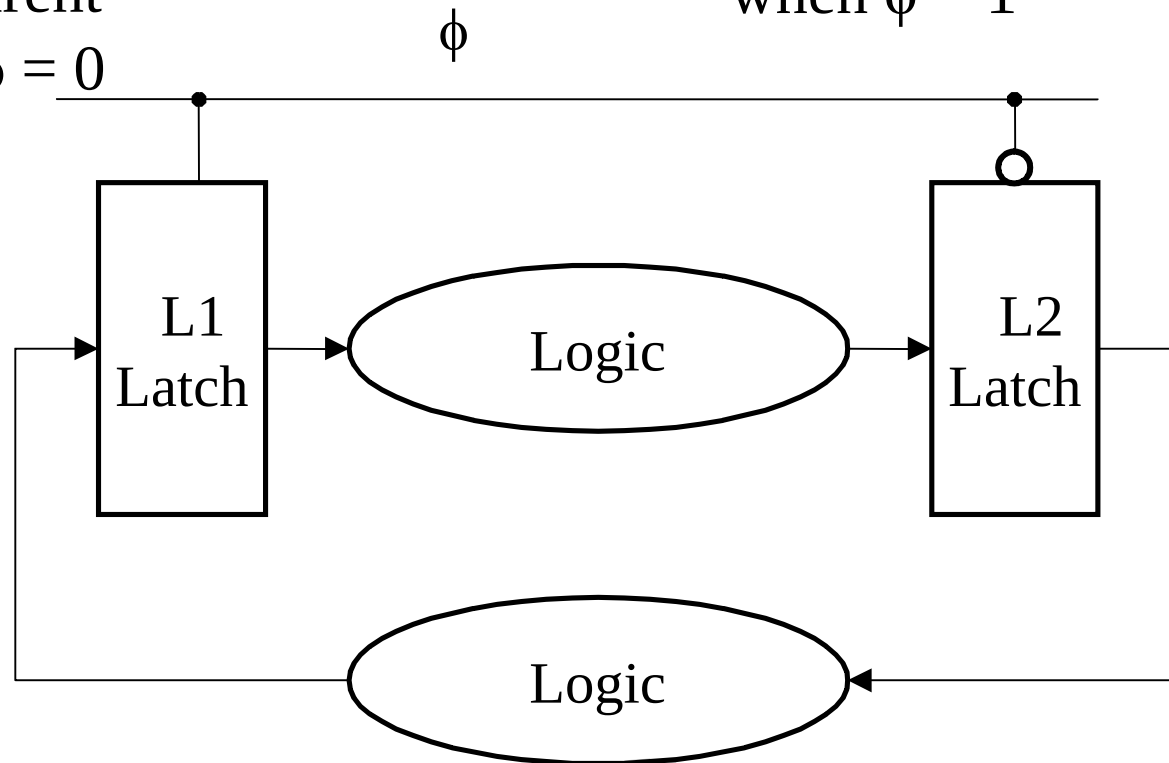


Slack-borrowing

 Slack-passing results from level sensitivity of latches and takes place if: $T_{CLK} < t_{pd,A} + t_{pd,B}$ and the logic functions correctly.




“a” valid well before edge 2, since previous block did not use its entire time allotment, producing slack time denoted by the shaded area. Now CLB_B starts computing using the slack provided by CLB_A, and completes before its allocated time (edge 4) and passes a small slack to the next cycle.

Latch-Based Timing

 

Can tolerate skew!

Self-timed and Asynchronous Design

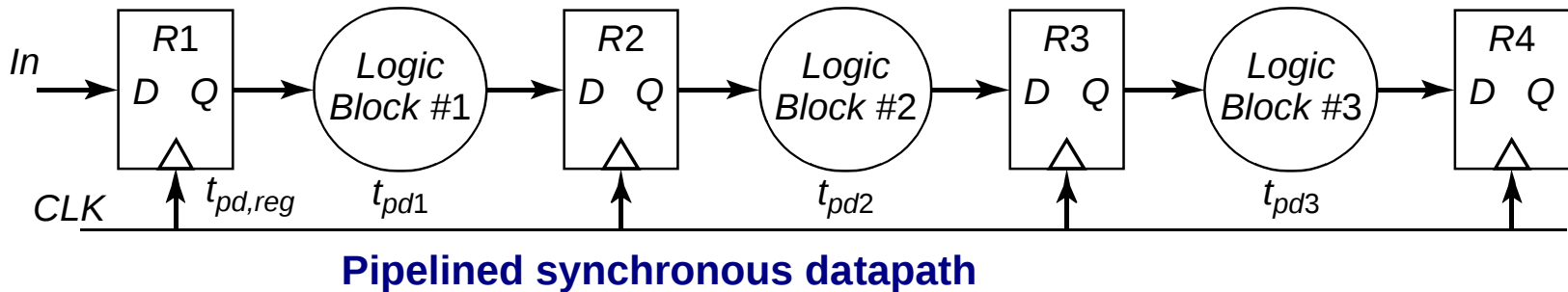

Functions of clock in synchronous design

- 1) Acts as completion signal: ensures that physical timing constraints are met
- 2) Ensures the correct ordering of events

Problems: skew, jitter, noise, system performance determined by slowest segment in pipeline

Alternatives to Synchronous Design


Truly asynchronous design

- 1) Completion is ensured by careful timing analysis**
- 2) Ordering of events is implicit in logic**

Self-timed design

- 1) Completion ensured by completion signal**
- 2) Ordering imposed by handshaking protocol**

Self-Timed Pipelined Datapath

 

The Handshaking protocol is used to communicate between adjacent combinational function that a particular computation has been completed

Self-Timed Designs

Features:

- ❑ Separates the physical and logical ordering functions implied in circuit timing
- ❑ The completion signal *Done* ensures that physical timing constraints are met
- ❑ Logical ordering of the operation is ensured by the *ack-req* scheme or the *HS* protocol
- ❑ Choice of protocol significantly impacts performance and robustness

Advantages:

- ❑ Timing signals generated locally—avoids overheads associated with distributing high-speed clocks
- ❑ Separating physical and logical ordering mechanisms results in potential increase in performance. In syn. systems the T_{CLK} must be large enough to account for the worst case delay
- ❑ Robust against temperature variations

Cons:

- ❑ Substantial circuit-level overhead

Completion Signal Generation: Dual Rail Coding

Requires introduction of redundancy in the data representation in order to signal that a particular bit is in either a transition or a steady-state mode

Power
dissipation can
be a problem!


B	B0	B1
in transition (or reset)	0	0
0	0	1
1	1	0
illegal	1	1

Two bits B0 and B1
are used to
represent a single
data bit B



Using Redundant Signal Encoding

Key idea in all redundant signal representations is to capture the transition state to indicate that the circuit is in evaluation mode and the output data are not valid


Dual Rail Coding Using Dynamic DCVSL

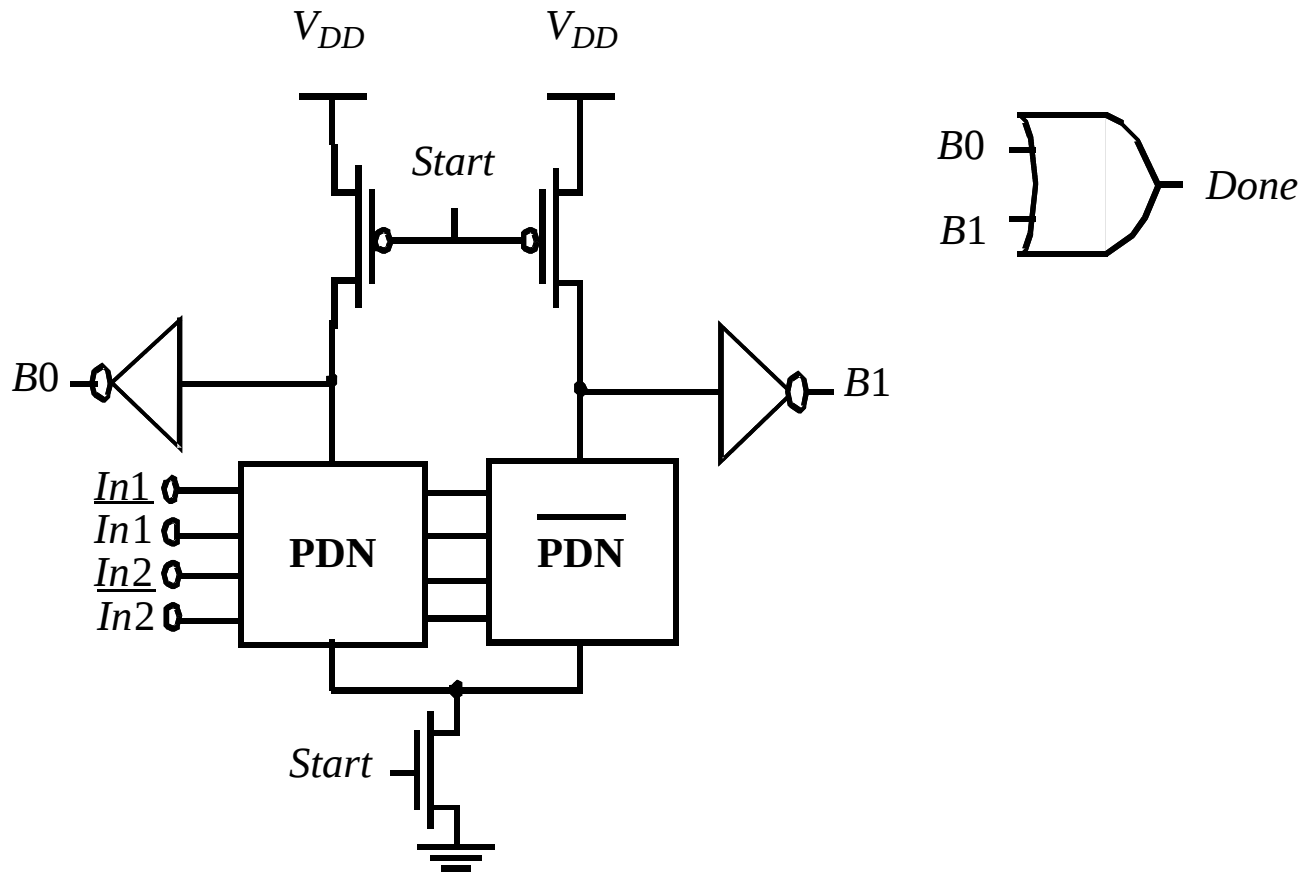

Example: A Self-Timed Adder

  


(a) Differential carry generation

 



(b) Completion signal

Completion Signal Generation

 


Widely used to generate the internal timing in memories


Completion Signal Using Current Sensing

 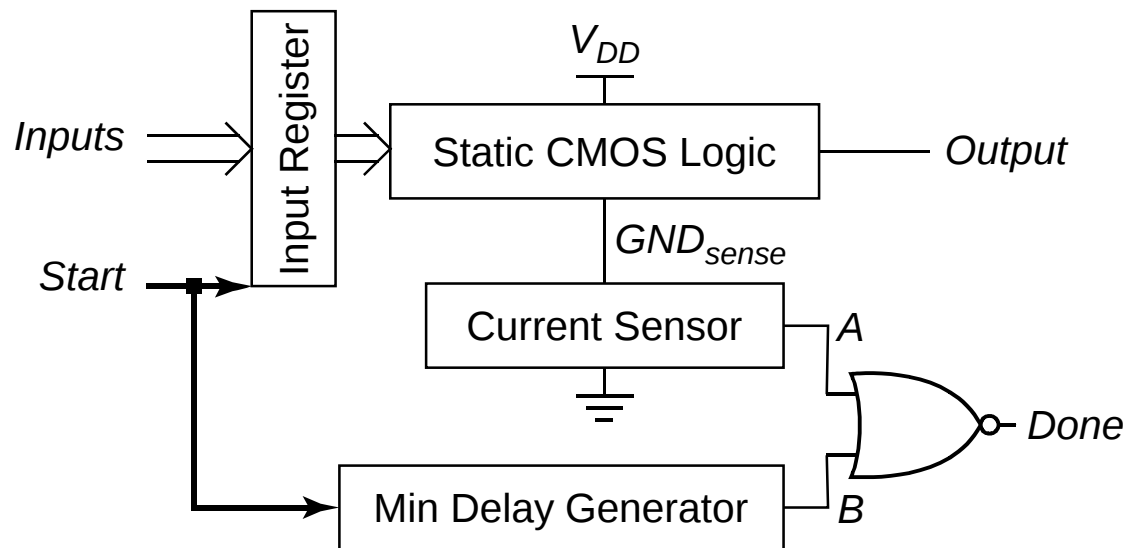

Hand-Shaking Protocol

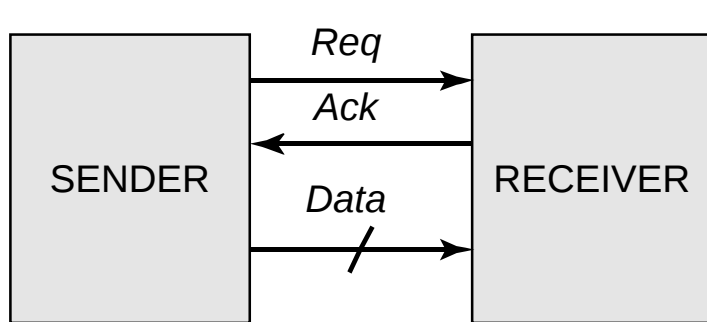


(a) Sender-receiver configuration

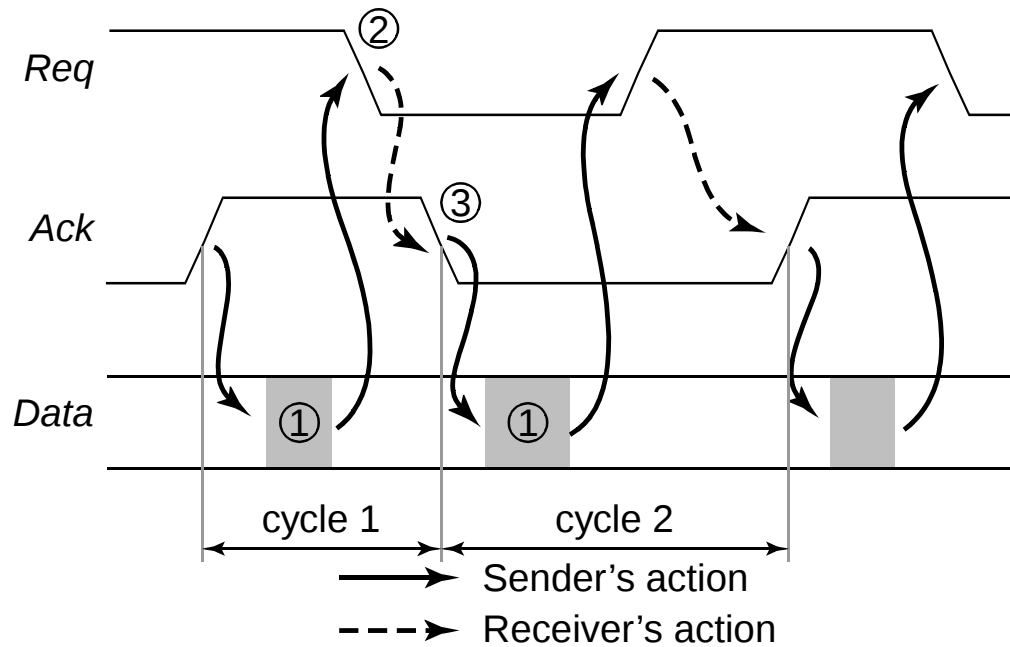

(b) Timing diagram

Two Phase Handshake


Event Logic – The Muller-C Element

 


(a) Schematic

A	B	F_{n+1}
0	0	0
0	1	F_n
1	0	F_n
1	1	1


(b) Truth table

 

(a) Logic

 


(b) Majority Function

 

(c) Dynamic


2-Phase Handshake Protocol

 

Advantage : FAST - minimal # of signaling events (important for global interconnect)

Disadvantage : edge - sensitive, has state


Example: Self-timed FIFO

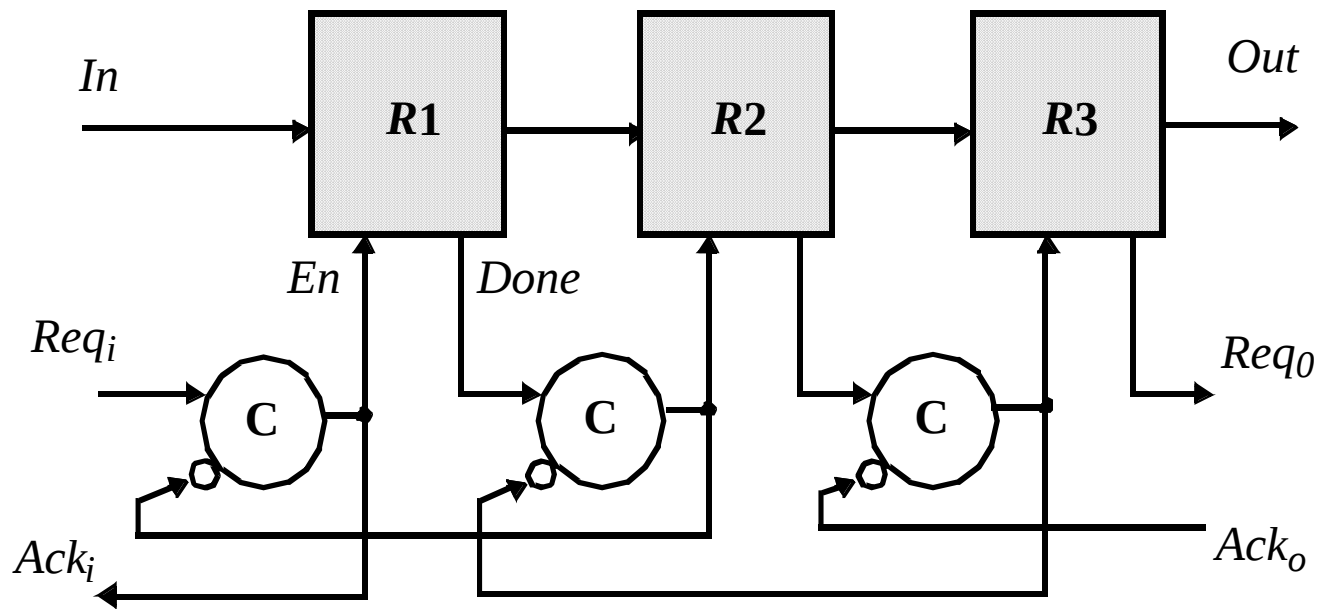


All 1s or 0s -> pipeline empty

Alternating 1s and 0s -> pipeline full

2-Phase Protocol

 


Example

 


From [Horowitz]


Example

 


Example

 

Example

 

4-Phase Handshake Protocol

 


Also known as RTZ



Slower, but unambiguous

4-Phase Handshake Protocol

Implementation using Muller-C elements

 


Self-Resetting Logic

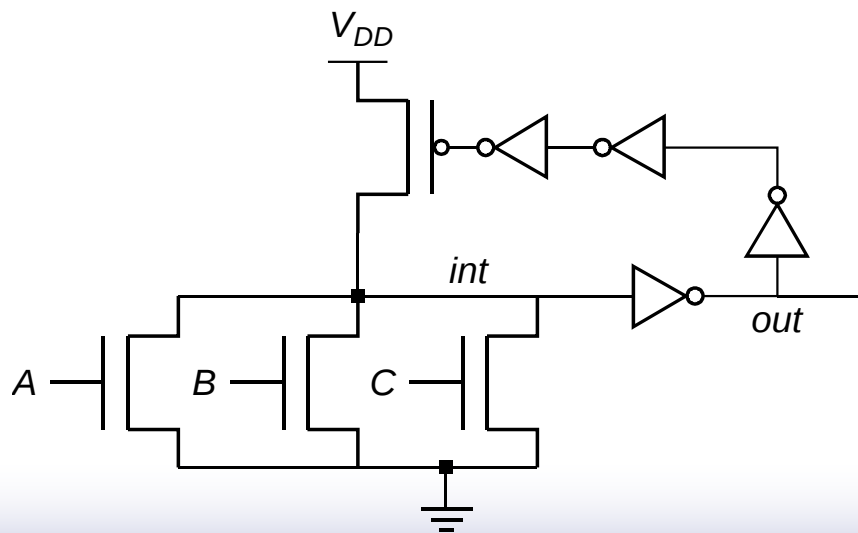 


*Post-charge
logic*

Clock-Delayed Domino

 


Asynchronous-Synchronous Interface

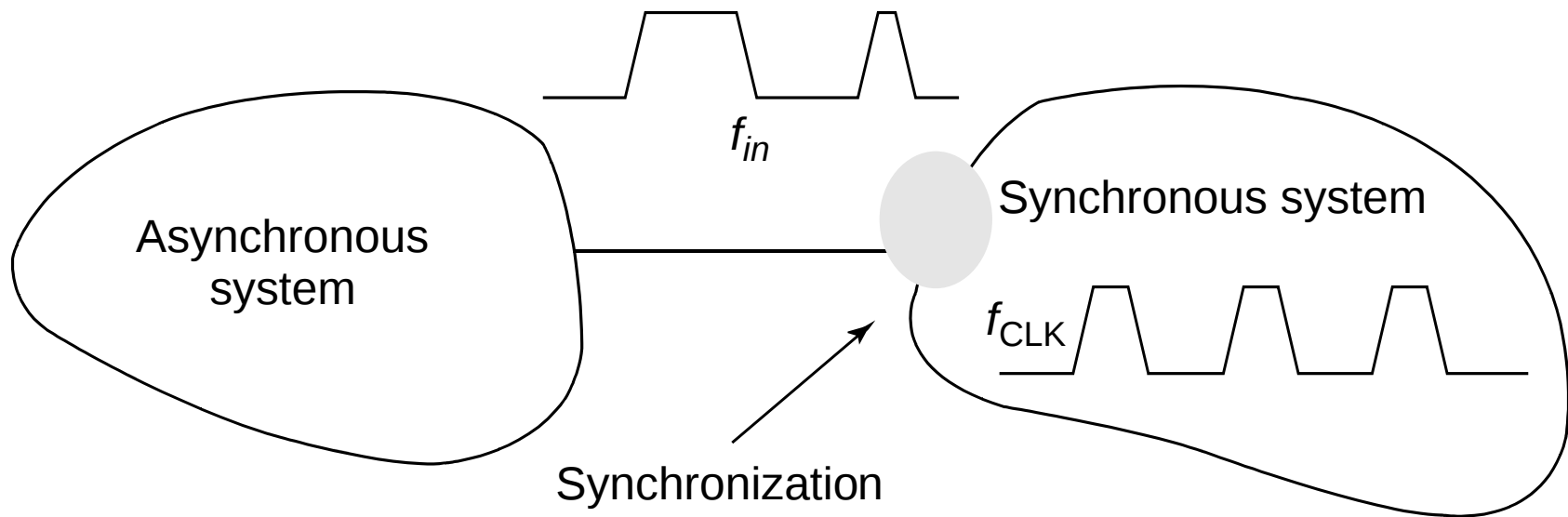

Synchronizers and Arbiters


- ❑ **Arbiter**: Circuit to decide which of 2 events occurred first
- ❑ **Synchronizer**: Arbiter with clock ϕ as one of the inputs
- ❑ **Problem**: Circuit HAS to make a decision in limited time - which decision is not important
- ❑ **Caveat**: It is impossible to ensure correct operation
- ❑ But, we can decrease the error probability at the expense of delay

A Simple Synchronizer

 

- Data sampled on rising edge of the clock
- Latch will eventually resolve the signal value, but ... this might take infinite time!


Synchronizer: Output Trajectories

 

Single-pole model for a flip-flop

$$v(t) = V_{MS} + (v(0) - V_{MS})e^{t/\tau}$$

Mean Time to Failure

 

$$N_{sync}(0) = \frac{P_{init}}{T_{\phi}} = \frac{\left(\frac{V_{IH} - V_{IL}}{V_{swing}} \right) t_r}{T_{signal}} \frac{1}{T_{\phi}}$$

$$N_{sync}(T) = \frac{P_{init} e^{-T/\tau}}{T_{\phi}} = \frac{(V_{IH} - V_{IL}) e^{-T/\tau}}{V_{swing}} \frac{t_r}{T_{signal} T_{\phi}}$$

Example

$$T_f = 10 \text{ nsec} = T$$

$$T_{\text{signal}} = 50 \text{ nsec}$$

$$t_r = 1 \text{ nsec}$$

$$t = 310 \text{ psec}$$


$$V_{IH} - V_{IL} = 1 \text{ V} (V_{DD} = 5 \text{ V})$$

$$N(T) = 3.9 \cdot 10^{-9} \text{ errors/sec}$$

$$\text{MTF}(T) = 2.6 \cdot 10^8 \text{ sec} = 8.3 \text{ years}$$

$$\text{MTF}(0) = 2.5 \mu\text{sec}$$


Influence of Noise

 


Low amplitude noise does not influence synchronization behavior

Typical Synchronizers


2 phase clocking circuit

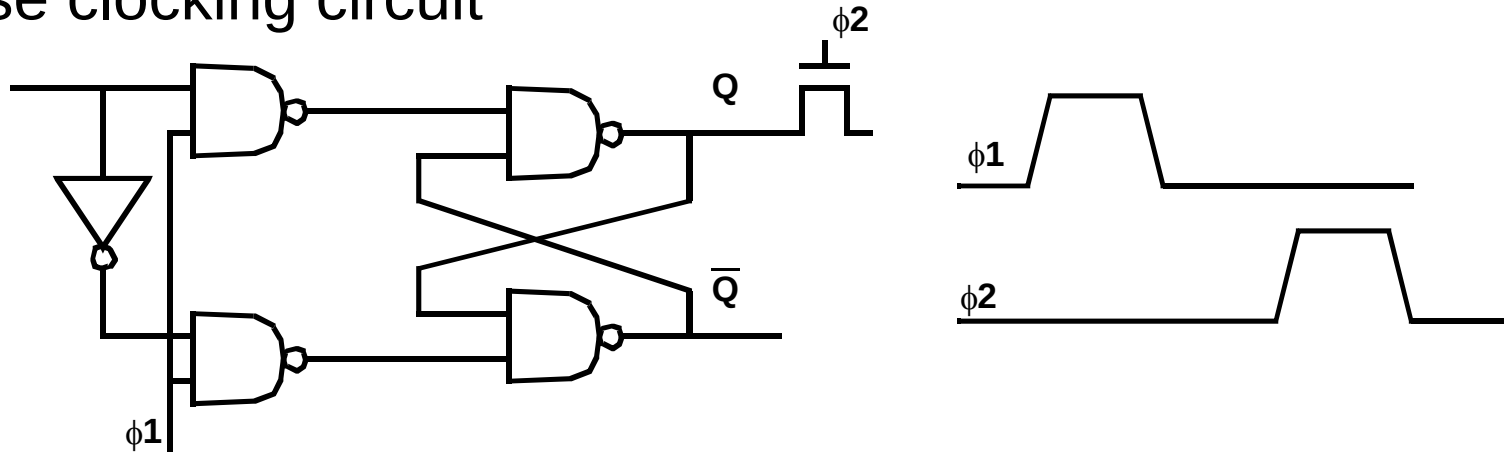


Using delay line

 


Cascaded Synchronizers Reduce MTF

 


Arbiters

 

(a) Schematic symbol

 


(b) Implementation

 


(c) Timing diagram


PLL-Based Synchronization

 

PLL Block Diagram

 


Phase Detector

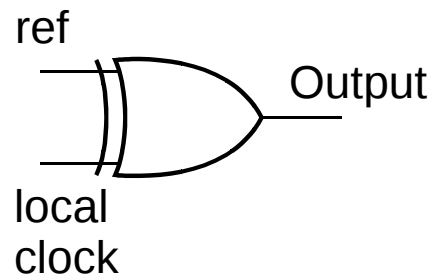


(a)

Output before filtering

 


(b)

 


(c)

*Transfer
characteristic*


Phase-Frequency Detector

 

(a) schematic

 


(b) state transition diagram

 


(c) Timing waveforms


PFD Response to Frequency

 


PFD Phase Transfer Characteristic

 

Charge Pump

 


PLL Simulation

 


Clock Generation using DLLs


Delay-Locked Loop (Delay Line Based)

 


Phase-Locked Loop (VCO-Based)

 


Delay Locked Loop

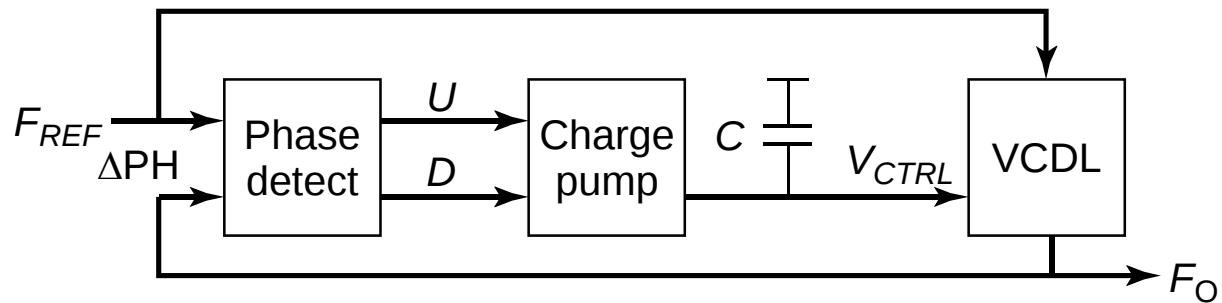

(a)

 

(b)

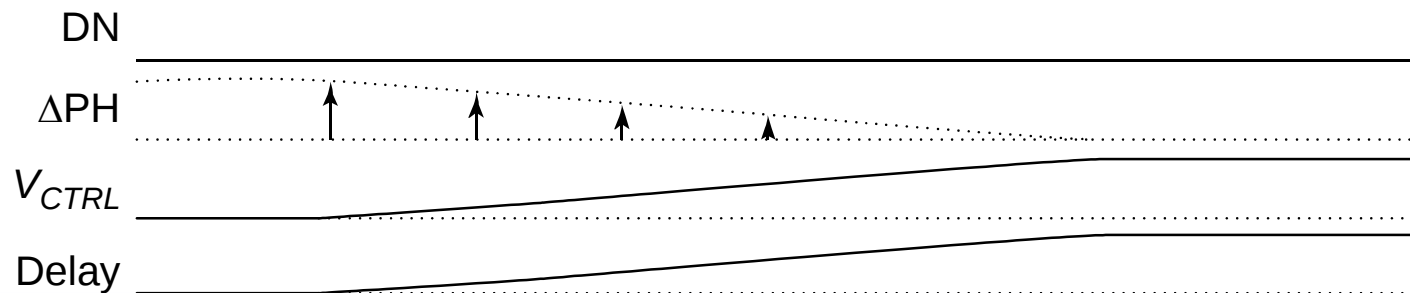

(c)

DLL-Based Clock Distribution

