

ECE 225

High-Speed Digital IC Design

Lecture 3

Review of Basic Circuit Styles

Prof. Kaustav Banerjee
Electrical and Computer Engineering
E-mail: kaustav@ece.ucsb.edu

Static and Dynamic CMOS

- ❑ In **static** circuits at every point in time (except when switching) the output is connected to either GND or V_{DD} via a low resistance path.
 - fan-in of n requires $2n$ (n N-type + n P-type) devices
- ❑ **Dynamic** circuits rely on the temporary storage of signal values on the capacitance of high impedance nodes.
 - requires only $n + 2$ ($n+1$ N-type and 1 P-type) transistors

Static and Dynamic CMOS Circuit Families

□ Static:

- **Complementary CMOS**
 - (robustness, low power, large fan-in expensive in terms of area and performance)
- **Ratioed Logic (pseudo-NMOS, DCVSL)**
 - (simple and fast at the expense of reduced NM and static power)
- **Pass-Transistor Logic (Transmission Gate)**
- -attractive for specific circuits: MUX, XOR-dominated logic such as Adders)

□ Dynamic:

- good for fast and complex gates, design process is harder due to parasitic effects, leakage puts an upper limit on the operating frequency of the circuit
 - **Domino Logic**
 - **np-CMOS**


Which style is best?

.....depends on ease of design, performance, power, area and robustness.

Complementary CMOS Logic


- ❑ Full rail-to-rail swing; **high noise margins**
- ❑ Logic levels not dependent upon the relative device sizes; **ratioless**
- ❑ Always a path to Vdd or Gnd in steady state; **low output impedance**
- ❑ Extremely **high input resistance**; nearly zero steady-state input current
- ❑ No direct path steady state between power and ground; **no static power dissipation**
- ❑ Propagation delay function of load capacitance and resistance of transistors

Static Complementary CMOS

 

PUN and PDN are **dual** logic networks


Inverter Threshold

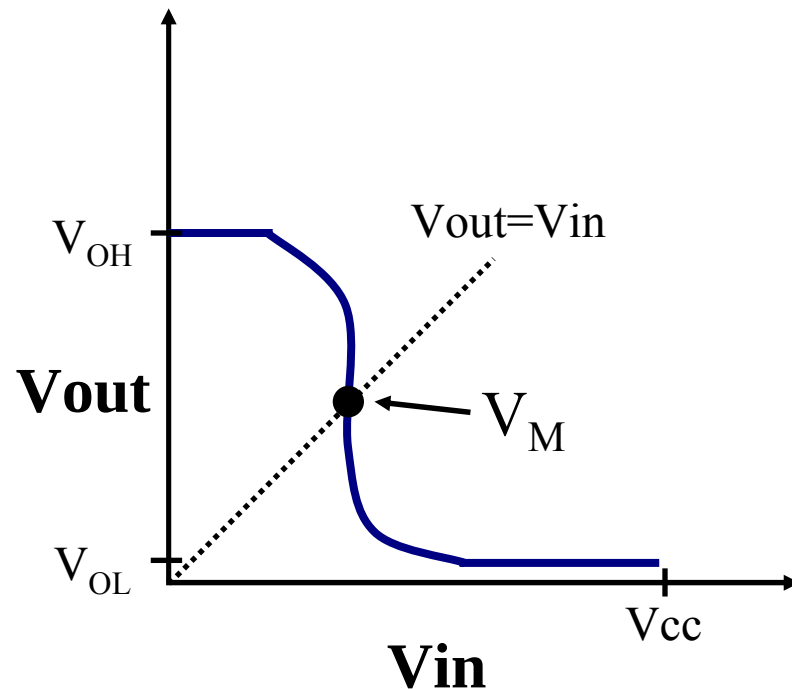

Inverter switching threshold:


- Point where voltage transfer curve intersects line $V_{out}=V_{in}$
- Represents the point at which the inverter switches state
- Normally, $V_M \approx V_{CC}/2$

Noise Margins

 

- V_{IL} and V_{IH} measure effect of input voltage on inverter output
- V_{IL} = largest input voltage recognized as logic '0'
- V_{IH} = smallest input voltage recognized as logic '1'
- Defined as point on VTC where slope = -1

Noise Margin (cont)

 

Ideally, noise margin should be as large as possible

- Noise margin is a measure of the *robustness* of an inverter
 - $N_{ML} = V_{IL} - V_{OL}$
 - $N_{MH} = V_{OH} - V_{IH}$
- Models a chain of inverters. Example:
 - First inverter output is V_{OH}
 - Second inverter recognizes input $> V_{IH}$ as logic '1'
 - Difference $V_{OH} - V_{IH}$ is "safety zone" for noise

Noise Margin (cont)

- Why are V_{IL} , V_{IH} defined as unity-gain point on VTC curve?
 - Assume there is noise on input voltage V_{in}

$$V_{out} = f(V_{in} + V_{noise})$$

- First-order approximation (Taylor Series):

$$V_{out} = f(V_{in}) + \frac{dV_{out}}{dV_{in}} V_{noise}$$


Note: $dV_{out}/dV_{in} = 0$ occurs only at the beginning and at the end of the VTC curve, elsewhere it is negative

- If gain (dV_{out}/dV_{in}) > 1 , noise will be amplified.
- If gain < 1 , noise is filtered. Therefore V_{IL} , V_{IH} ensure that gain < 1

CMOS Inverter Operation (summary)


Table 2.2 Relationships between voltages for the three regions of operation of a CMOS inverter			
	Cutoff	Linear	Saturated
nMOS	$V_{gsn} < V_{tn}$	$V_{gsn} > V_{tn}$	$V_{gsn} > V_{tn}$
	$V_{in} < V_{tn}$	$V_{in} > V_{tn}$	$V_{in} > V_{tn}$
		$V_{dsn} < V_{gsn} - V_{tn}$	$V_{dsn} > V_{gsn} - V_{tn}$
		$V_{out} < V_{in} - V_{tn}$	$V_{out} > V_{in} - V_{tn}$
pMOS	$V_{gsp} > V_{tp}$	$V_{gsp} < V_{tp}$	$V_{gsp} < V_{tp}$
	$V_{in} > V_{tp} + V_{DD}$	$V_{in} < V_{tp} + V_{DD}$	$V_{in} < V_{tp} + V_{DD}$
		$V_{dsp} > V_{gsp} - V_{tp}$	$V_{dsp} < V_{gsp} - V_{tp}$
		$V_{out} > V_{in} - V_{tp}$	$V_{out} < V_{in} - V_{tp}$

CMOS Inverter VTC

 


In which state do the transistors spend most of their time?

 Switching Threshold as a function of Transistor Ratio



Inverter Gain

0.25 μm CMOS, $V_{DD} = 2.5\text{V}$

 

Gain is mostly determined by technology parameters, especially channel length modulation, but also by V_{DD}

Note: approximately $V_M \propto V_{DD}$

Inverter Skew


 


FIG 2.26 Transfer characteristics of skewed inverters

Propagation Delay

CMOS inverter capacitances

 

Cap on Node f:


- Junction cap: $C_{db,p}$ and $C_{db,n}$
- Gate (overlap) capacitance $C_{gd,p}$ and $C_{gd,n}$ (beware of Miller effect)
- Interconnect cap: C_{int}
- Receiver gate cap: C_g

Transient Response

Due to C_{gd} of transistors: directly couples voltage at input to output before the transistors can even start to react to changes at the input---can affect gate performance

Symmetric inverter has

$$t_{pHL} = t_{pLH}$$

 

$$t_p = 0.69 C_L (R_{eqn} + R_{eqp})/2$$

$$R_{eq} = \frac{1}{V_{DD}/2} \int_{V_{DD}/2}^{V_{DD}} \frac{V}{I_{DSAT}(1 + \lambda V)} dV \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{7}{9} \lambda V_{DD} \right)$$

with $I_{DSAT} = k' \frac{W}{L} \left((V_{DD} - V_T) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$


Design for Performance

- ❑ Keep load capacitances (C_L) small
 - Recall that three major components contribute to the load cap.
 - internal diffusion + overlap caps
 - interconnect cap.
 - fan-out (gate cap)
- ❑ Increase transistor sizes
 - watch out for self-loading!
- ❑ Increase V_{DD} (??)
 - watch out for reliability issues!


Delay as a function of V_{DD}

Same as the ON resistance of a transistor....

 
Trade off energy dissipation vs performance.....



Device Sizing

 

NMOS/PMOS ratio

 


If symmetry and noise margins are not of prime concern, inverter delay can be reduced by reducing the width of PMOS....

Designing Combinational Logic Circuits

Analysis of CMOS gates

 □ Represent “on” transistors as resistors



- Transistors in series $\rightarrow$ resistances in series
 - Effective resistance = $2R$
 - Effective width = $\frac{1}{2} W$





Note: 1) As transistor width increases, its on resistance (R) decreases

2) If transistor channel length increases, R increases


Equivalent Inverter

- CMOS gates: many paths to V_{cc} and Gnd
 - Multiple values for V_M , V_{IL} , V_{OL} , etc
 - Different delays for each input combination
- Equivalent inverter
 - Represent each gate as an inverter with appropriate device width
 - Include only transistors which are on or switching
 - Calculate V_M , delays, etc using inverter equations

Switch Delay Model

    

Input Pattern Effects on Delay

 


2-input NAND

- Delay is dependent on the **pattern** of inputs
- Low to high transition
 - both inputs go low
 - delay is $0.69 R_p / 2 C_L$
 - one input goes low
 - delay is $0.69 R_p C_L$
- High to low transition
 - both inputs go high
 - delay is $0.69 2R_n C_L$

Delay Dependence on Input Patterns

 Simulated Low to High delay for a 2-input NAND




Input Data Pattern	Delay (psec)
A=B=0→1	69
A=1, B=0→1	62
A= 0→1, B=1	50
A=B=1→0	35
A=1, B=1→0	76
A= 1→0, B=1	57

Note: worst case L-H delay depends on which input (A or B) is driven low (due to internal node cap of PDN stack: source of M2)

NMOS = 0.5 μ m/0.25 μ m
PMOS = 0.75 μ m/0.25 μ m
 C_L = 100 fF

Delay Dependence on Input Patterns

 

2-input NAND

- ❑ **High to Low Delay** depends on the initial state of the internal nodes
- ❑ Example: when both inputs transition from 0 to 1, it is important to know the state of the internal node (between M1 and M2)
- ❑ **Worst case:** when internal node is initially charged up to $V_{DD} - V_{tn}$. This can be ensured by pulsing the A input from 1-0-1, while B only makes the 0-1 transition.

Bottom Line: Delay estimation can be a fairly complex affair and requires careful consideration of the internal node caps. and data patterns

Transistor Sizing

- ❑ Sizing for switching threshold
 - All inputs switch together
- ❑ Sizing for delay
 - Find **worst-case** input combination
- ❑ Find equivalent inverter, use inverter analysis to set device sizes

Transistor Sizing


What sizing will lead to a 2:1 equivalent inverter?

For effective $R_p = R_n$, we need $W_p = 2W_n$

Since two NMOS are in series, each should have $R_n/2$, hence each NMOS size, $W_n = 2$

Each PMOS should be such that $R_p = \text{effective } R_n$ (which corresponds to $W_n = 1$)

Hence, $W_p = 2$ (effective W_n) = 2

 


2-input NAND

For effective $R_p = R_n$, we need $W_p = 2W_n$

Also, since two PMOS are in series, each should have $R_p/2$

Hence, W_p of each should be $4W_n$

 


2-input NOR

Avoid stacking PMOS transistors in series....

Transistor Sizing a Complex CMOS Gate

 What sizing will lead to a 2:1 equivalent inverter?



Note: $A=3$ and $B=C=D=6$ will also give a 2:1 inverter but that will give higher output parasitic capacitance (due to larger D)

1. Start with a transistor in the PDN, that is (preferably) isolated (i.e., it can pull down the output node on its own)----D in this case
2. Assign a minimum size to this transistor ($W=1$ for D)
3. Now identify other paths in the PDN that can also discharge the output node: AB and AC in this case.
4. Size A, B, and C such that: each path will be electrically equivalent to the path through D (i.e., with same resistance), hence A, B and C should have $W=2$
5. Repeat the same for the PUN, keeping in mind that i) effective resistance of any path must equal the effective resistance of any path in the PDN, and ii) PMOS transistors will have to be sized (twice as large in this case) appropriately.


Note: here we ignored internal caps.

CMOS gate design: summary

- Designing a CMOS gate:
 - Find pulldown NMOS network from logic function or by inspection
 - Find pullup PMOS network
 - By inspection
 - Using logic function
 - Using dual network approach
 - Size transistors using equivalent inverter
 - Find worst-case pullup and pulldown paths
 - Size to meet rise/fall or threshold requirements

Inverter Chain Sizing

Load capacitance

 

$$C_L = C_{int} + C_{ext}$$

Internal Caps of Driver (C_{int}):

= Junction caps: $C_{db,12} +$

Gate caps: $C_{gd,12}$ (including Miller Caps.)

External Caps (C_{ext}):

= Interconnect cap: C_w

+ Receiver gate caps: $C_{g,43}$

Intrinsic delay of CMOS inverter

Let R_{eq} be the equivalent resistance of the gate (inverter), then delay (t_p) is defined as:

$$\begin{aligned} t_p &= 0.69 R_{eq} (C_{int} + C_{ext}) \\ &= 0.69 R_{eq} C_{int} \left(1 + \frac{C_{ext}}{C_{int}} \right) \\ &= t_{p0} \left(1 + \frac{C_{ext}}{C_{int}} \right) \end{aligned}$$

t_{p0} is the **intrinsic** delay

Impact of sizing on gate delay

Let S be the sizing factor

R_{ref} be the resistance of a reference gate (usually a minimum size gate)



C_{iref} be the internal capacitance of the reference gate

$$\begin{aligned}C_{int} &= S C_{iref}, \quad R_{eq} = \frac{R_{ref}}{S} \\t_p &= 0.69 \left(\frac{R_{ref}}{S} \right) (S C_{iref}) \left(1 + \frac{C_{ext}}{S C_{iref}} \right) \\&= 0.69 R_{ref} C_{iref} \left(1 + \frac{C_{ext}}{S C_{iref}} \right) \\&= t_{p0} \left(1 + \frac{C_{ext}}{S C_{iref}} \right)\end{aligned}$$

Hence:


1. Intrinsic delay is independent of gate sizing, and is determined only by technology and inverter layout
2. If S is made very large, gate delay approaches the intrinsic value but increases the area significantly

Inverter with Load

  

$$\text{Delay } (t_p) = kR_W(C_{int} + C_{ext}) = kR_W C_{int} + kR_W C_{ext} = \underbrace{kR_W C_{int}}_{t_{p0} \text{ (intrinsic delay)}} (1 + C_{ext}/C_{int})$$

Apply to Inverter Chain

 

$$t_p = t_{p1} + t_{p2} + \dots + t_{pN}$$

$$t_{p,j} = t_{p0} \left(1 + \frac{C_{gin,j+1}}{\gamma C_{gin,j}} \right)$$

$$t_p = \sum_{j=1}^N t_{p,j} = t_{p0} \sum_{i=1}^N \left(1 + \frac{C_{gin,j+1}}{\gamma C_{gin,j}} \right), \quad C_{gin,N+1} = C_L$$

Optimum Delay and Number of Stages

When each stage is sized by f and has same eff. fanout f :

$$\frac{C_L}{C_{g,N}} = \frac{C_{g,N}}{C_{g,N-1}} = \dots = \frac{C_{g,2}}{C_{g,1}} = f$$

$$\text{Hence, } f^N = C_L / C_{g,1} = F$$

F is the overall effective fanout of the circuit

Effective fanout of each stage: $f = \sqrt[N]{F}$

Minimum path delay:


$$t_p = N t_{p0} \left(1 + \sqrt[N]{F} / \gamma \right)$$

If N is too large, intrinsic delay of stages dominate, while if N is small, effective fanout of each stage (f) is large and the second term dominates

How to choose N?

Example

If N is given....

 

C_L/C_1 has to be evenly distributed across $N = 3$ stages:

$$f = \sqrt[3]{8} = 2$$

Optimum Number of Stages

For a given load, C_L and given input capacitance C_{in}
Find optimal sizing f

$$C_L = F \cdot C_{in} = f^N C_{in} \quad \text{with} \quad N = \frac{\ln F}{\ln f}$$

$$t_p = N t_{p0} \left(F^{1/N} / \gamma + 1 \right) = \frac{t_{p0} \ln F}{\gamma} \left(\frac{f}{\ln f} + \frac{\gamma}{\ln f} \right)$$

$$\frac{\partial t_p}{\partial f} = \frac{t_{p0} \ln F}{\gamma} \cdot \frac{\ln f - 1 - \gamma / f}{\ln^2 f} = 0$$

If self-loading is ignored....


For $\gamma = 0$, $f = e$, $N = \ln F$

$$f = \exp(1 + \gamma / f)$$

Optimum Effective Fanout f

Optimum f for given process defined by γ

$$f = \exp(1 + \gamma / f)$$


 


Optimum
tapering factor:

$$f_{opt} = 3.6$$

for $\gamma=1$

Fan-In Considerations

  


Distributed RC model
(Elmore delay)

Assuming all NMOS are equal size

$$t_{pHL} = 0.69 R_{eqn}(C_1 + 2C_2 + 3C_3 + 4C_L)$$


Propagation delay deteriorates rapidly as a function of fan-in – **quadratically** in the worst case.

t_p as a Function of Fan-In

 

Gates with a fan-in greater than 4 should be avoided.

t_p as a Function of Fan-Out

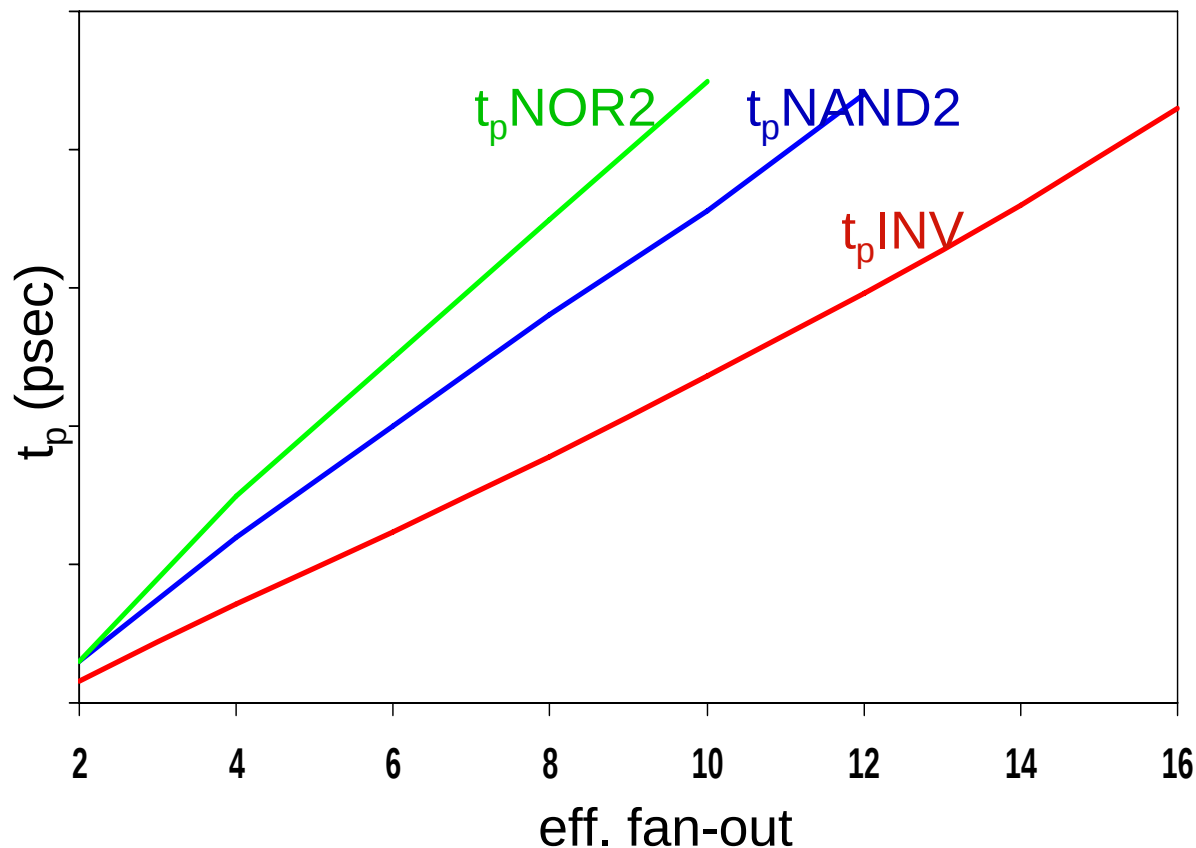

All gates have the same drive current.

Slope is a function of “driving strength”

Note: i) these lines are not going through the origin, ii) NAND and NOR have same intrinsic delay....


t_p as a Function of Fan-In and Fan-Out

- Fan-in: **quadratic** due to increasing resistance and capacitance
- Fan-out: each additional fan-out gate adds **two** gate capacitances to C_L

$$t_p = a_1 FI + a_2 FI^2 + a_3 FO$$

Fast Complex Gates: Design Technique 1

 - Transistor sizing
 - as long as fan-out capacitance dominates
- Progressive sizing (not so simple to layout!)



Distributed RC line

$$M1 > M2 > M3 > \dots > MN$$


(the transistor closest to the output is the smallest: has biggest R)

Can reduce delay by more than 20%; decreasing gains as technology shrinks


Fast Complex Gates: Design Technique 2

□ Transistor ordering

 Critical path is determined by the slowest arriving signal: In1



 delay determined by time to discharge C_L , C_1 and C_2




delay determined by time to discharge C_L



Fast Complex Gates: Design Technique 3

□ Alternative logic structures

$$F = ABCDEFGH$$

 


Using De Morgan's Law...

  

Fast Complex Gates: Design Technique 4

 - Isolating fan-in from fan-out using buffer insertion



Fast Complex Gates:

Design Technique 5

- Reducing the voltage swing

$$t_{pHL} = 0.69 (3/4 (C_L V_{DD}) / I_{DSATn})$$

$$= 0.69 (3/4 (C_L V_{swing}) / I_{DSATn})$$

- linear reduction in delay
 - also reduces power consumption
- But the following gate is much slower!
 - Or requires use of “sense amplifiers” on the receiving end to restore the signal level (memory design)

Sizing Logic Paths for Speed

- ❑ Frequently, input capacitance of a logic path is constrained
- ❑ Logic also has to drive some capacitance
- ❑ Example: ALU load in an Intel's microprocessor is 0.5pF
- ❑ How do we size the ALU datapath to achieve maximum speed?
- ❑ We have already solved this for the inverter chain – can we generalize it for any type of logic?

Minimizing Delay in Complex Logic Networks

$$\begin{aligned} \text{Delay} &= t_{p0} \left(1 + \frac{f}{\gamma} \right) (\text{inverter}) \\ &= t_{p0} \left(p + \frac{g \cdot f}{\gamma} \right) (\text{Complex gate}) \end{aligned}$$

Everything Normalized w.r.t an inverter:

$$g_{inv} = 1, p_{inv} = 1$$

f – effective fanout (*ratio of external load and input cap. of gate*)

p – ratio of intrinsic delays of complex gate and inverter
(value increases with complexity of gate)


g – logical effort: how much more input capacitance is presented by the complex gate to deliver the same output current as an inverter (depends only on circuit topology)

Logical Effort

- ❑ Inverter has the smallest logical effort and intrinsic delay of all static CMOS gates
- ❑ Logical effort of a gate is the ratio of its input capacitance to the inverter capacitance when sized to deliver the same current
- ❑ Logical effort increases with gate complexity


Logical Effort

 Logical effort is the ratio of input capacitance of a gate to the input capacitance of an inverter with the **same output current**



Inverter

$$g = 1$$

 


2-input NAND

$$g = 4/3$$

Since two NMOS are in series, each should have $R_n/2$, hence each NMOS size, $W_n = 2$

 Each PMOS should be such that $R_p = R_n$, or $W_p = W_n$



2-input NOR

$$g = 5/3$$

For $R_p = R_n$, we need $W_p = 2W_n$
Since two PMOS are in series, each should have $R_p/2$
or W_p of each should be $4W_n$

Delay in a Logic Gate

Gate delay:

$$d = h + p$$

effort delay intrinsic delay


Effort delay (or gate effort):

$$h = g f$$

logical effort effective fanout = C_{ext}/C_{in}

- **Logical effort** is a function of topology, independent of sizing
- Effective fanout (**electrical effort**) is a function of load/gate size


Logical Effort of Gates

 

Ratioed Logic


Ratioed Logic

 Need $N+1$ transistors vs $2N$ for complementary CMOS



Goal: to reduce the number of devices over complementary CMOS

Ratioed Logic: Resistive Load

 

- N transistors + Load

- $V_{OH} = V_{DD}$


- $V_{OL} = \frac{R_{PN}}{R_{PN} + R_L}$

*Ideally V_{OL} should be as small as possible.
Hence, R_L should be large...*




- Assymetrical response

- Static power consumption

- $t_{pL} = 0.69 R_L C_L$

 

Active Loads

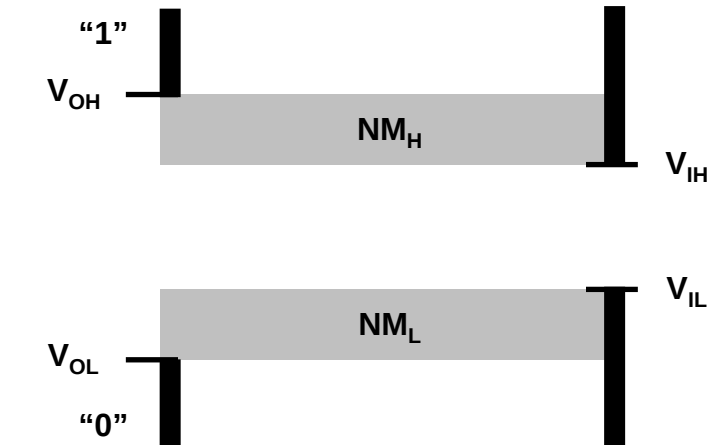  


$V_{OH} = V_{DD}$ (assuming $V_{OL} < V_{tn}$)

Ideally V_{OL} should be as small as possible. Hence, PMOS device should be minimum sized...

However, since V_{OL} is not 0 V, contention between PMOS and the PDN lowers the NM and results in static power dissipation.

Pseudo-NMOS

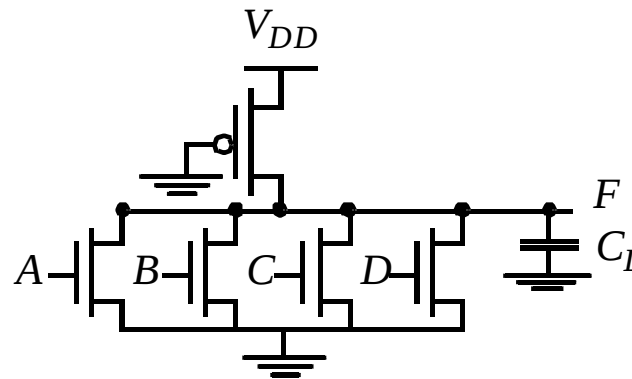

$$V_{OH} = V_{DD} \text{ (similar to complementary CMOS)}$$

To Find V_{OL} :

$$k_n \left((V_{DD} - V_{Tn}) V_{OL} - \frac{V_{OL}^2}{2} \right) + k_p ((-V_{DD} - V_{Tp}) V_{DSATp} - V_{DSATp}^2/2) = 0$$

Note: NMOS in linear mode, since ideally the output=0 V

Note: PMOS in saturation mode


$$V_{OL} = \mu_p/\mu_n W_p/W_n V_{DSATp}$$

Assuming V_{OL} is small relative to gate drive, $(V_{DD} - V_T)$, and $V_{Tp} = V_{Tn}$

SMALLER AREA & LOAD BUT STATIC POWER DISSIPATION!!!


Pseudo-NMOS VTC

 Sizing of the load device can be used to trade off parameters such as NM, delay, and power.....



A larger pull-up device improves performance but increases static power and degrades NM by increasing V_{OL}


Pass-Transistor Logic

 

- **N transistors**
- **No static consumption**

Allows primary inputs to drive gate terminals as well as source-drain terminals

Example: AND Gate

 

Ensures that gate is static: provides low impedance path when $B=0$

If $B=1$ then T1 is ON and T2 is OFF

Then $A=F$, i.e., if $A=1$, $F=1$ and if $A=0$, $F=0$

When $B=0$, T2 is ON and passes a Zero


Need fewer transistors: 4 to implement the AND: *lower cap.*

Need 6 to implement in static CMOS (4 for NAND and 2 for INV)

Note: F will charge only up to $V_{DD} - V_{tn}$


Also, V_{Tn} will be a function of V_F (increase due to RBB)

VTC of Pass-Transistor AND Gate

 

When $B = V_{DD}$, T1 is ON until the input reaches $V_{DD} - V_{Tn}$

 
When $A = V_{DD}$, and B makes a transition from 0 to 1, T2 is turned on until $V_{DD}/2$ and Output = 0. Once T2 is turned off, output follows the input B minus a threshold drop.




VTC of Pass Transistor Logic is data dependent

NMOS-Only Logic

Voltage Drop Issue:

 


$$V_x = V_{dd} - V_{Tn}(V_x)$$

 

Hence, pass transistor gates cannot be cascaded by connecting the output of a pass gate to the gate input of another pass transistor. They can only be cascaded in series....

NMOS-only Switch

 

*Difficult
to switch
off the
PMOS!*

V_B does not pull up to 2.5V, but $2.5V - V_{Tn}$


*Lower
switching
energy!*

Voltage loss causes static power consumption

NMOS has higher threshold than PMOS (body effect)

Solutions to the Voltage Drop Problem:

Solution 1: Level Restoring Transistor

 

Pass Transistor Logic
suffers from static power
dissipation and reduced
NMs

*At $B=V_{DD}$, if $A: 0$ to V_{DD}
 $V_x = V_{DD} - V_{Tn}$, $Out=0$,
 $M_r=ON$ and $V_x=V_{DD}$*


*Eliminates static power in
the Inverter*

*No static power between
 M_r and M_n*

- **Advantage: Full Swing**
- Restorer adds capacitance, takes away pull down current at X (for high to low transition at X, M_n must be stronger than M_r), can slow down gate
- Ratio problem

Restorer Sizing

 Need to size M_n and M_r to bring $V_x < V_M (=V_{DD}/2)$ (V_M is a function of $R1$ and $R2$) $R1$ and $R2$ are the equivalent on-resistances of $M1$ and $M2$




- **Upper limit on restorer size** when too large (R_r too small), V_x can't be brought below V_M
- Pass-transistor pull-down can have several transistors in stack

Transient Response: V_x vs. time

Solution 2: Single Transistor Pass Gate with $V_T=0$


 
Only Pass Transistor Devices have $V_T=0$



But even if $V_T=0$, there is still body effect...which prevents full swing!


WATCH OUT FOR LEAKAGE CURRENTS in the IDLE State!!!

Solution 3: Transmission Gate

 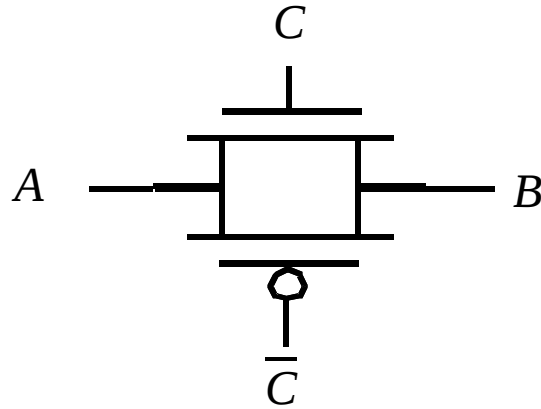

Acts like a
bidirectional switch
controlled by the
gate signal C

 When $C=1$, both
MOSFETS are ON
allowing the signal to
pass through the
gate ($A=B$, if $C=1$)




**Because of the
PMOS, C_L charges
to V_{dd}**

**Because of NMOS
 C_L discharges to 0**

Transmission Gate XOR

$B=1$: M1 and M2 act as an INV, Transmission gate is off and $F=\bar{A}B$

 $B=0$: M1 and M2 are off and Xgate is on, $F=AB$





Implementation requires only 6 transistors!

While a complementary CMOS implementation requires ??? transistors

Fast adder circuits and registers can also be implemented with Xgates

Resistance of Transmission Gate

  


$$R_n = (V_{DD} - V_{out}) / I_{dn}$$


$$R_p = (V_{out} - V_{DD}) / I_{dp}$$

Delay in Transmission Gate Networks

 
Delay of a chain of n Xgates (used in adders and deep MUXes) can be modeled using Elmore delay



(a) A chain of n Xgates

 

(b) Equivalent RC representation


 


(c) Buffer insertion in a chain of Xgates to lower delay

Dynamic CMOS

- ❑ In **static** circuits at every point in time (except when switching) the output is connected to either GND or V_{DD} via a low resistance path.
 - fan-in of n requires $2n$ (n N-type + n P-type) devices
- ❑ **Dynamic** circuits rely on the temporary storage of signal values on the capacitance of high impedance nodes.
 - requires only $n + 2$ ($n+1$ N-type and 1 P-type) transistors

Dynamic Gate

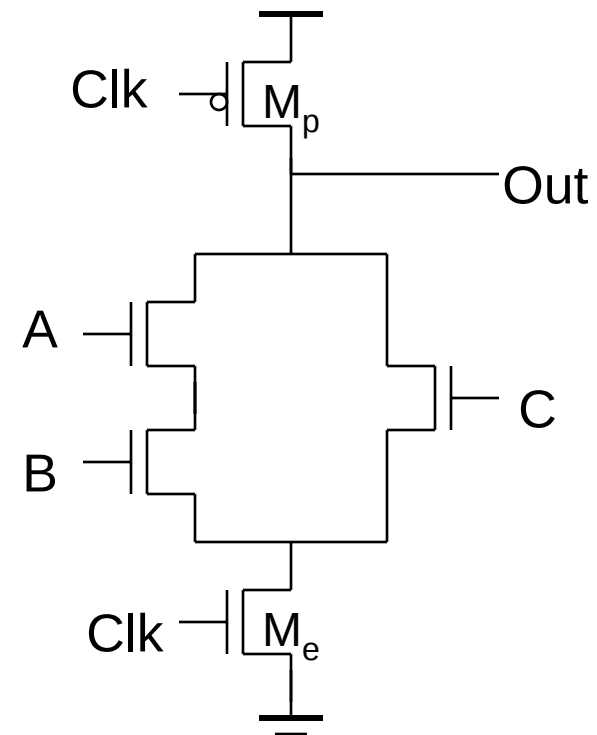 


Two phase operation

Precharge (CLK = 0)

Evaluate (CLK = 1)



Dynamic Gate

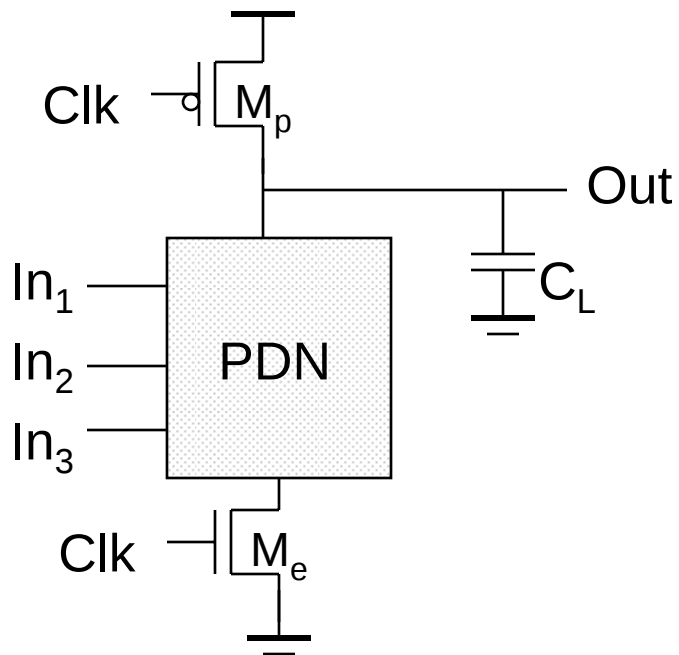

Two phase operation

Precharge (Clk = 0)

Evaluate (Clk = 1)

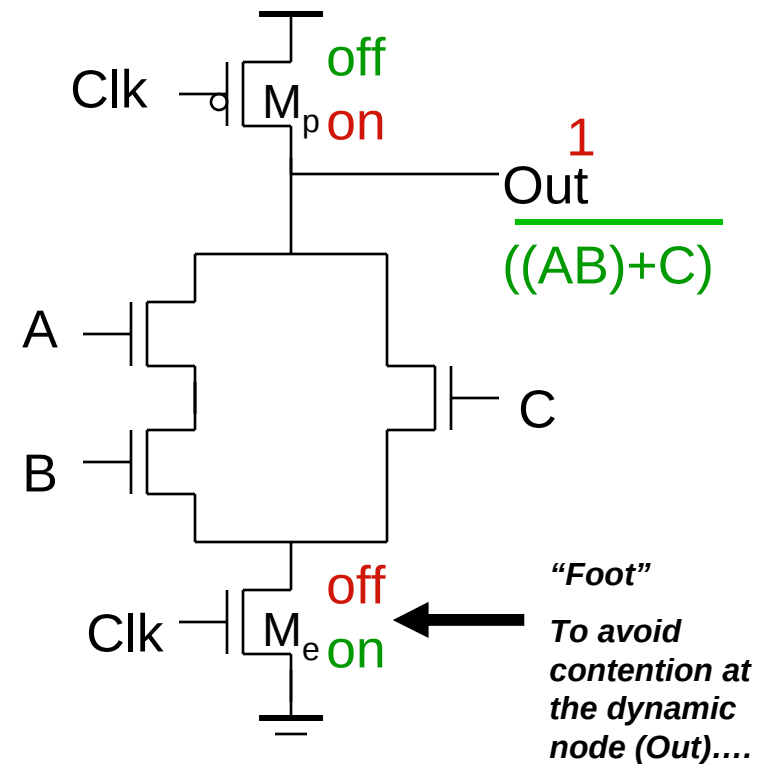 

$$\text{Out} = \overline{\text{CLK}} + \overline{(\text{AB}) + \text{C}} \cdot \text{CLK}$$

Conditions on Output

- During evaluation phase, the only possible path between output node and supply rail is to ground. Hence, once the output of a dynamic gate is discharged, it cannot be charged again until the next precharge operation.
- Inputs to the gate can make **at most** one transition during evaluation.
- Output can be in the **high-impedance state** during and after evaluation (if PDN is off), state is stored on C_L

Properties of Dynamic Gates

- ❑ Logic function is implemented by the PDN only
 - number of transistors is $N + 2$ (versus $2N$ for static complementary CMOS)
- ❑ Full swing outputs ($V_{OL} = \text{GND}$ and $V_{OH} = V_{DD}$)
- ❑ Non-ratioed - sizing of the devices does not affect the logic levels
- ❑ PDN starts to work as soon as the input signals exceed V_{Tn} , so V_M , V_{IH} and V_{IL} equal to V_{Tn}
- ❑ Low noise margin (NM_L)
- ❑ Needs a precharge/evaluate clock
- ❑ Faster switching speeds
 - reduced load capacitance due to **lower input** capacitance (C_{in}) due to lower number of transistors per gate and single transistor load per fan-in (reduced logical effort, $2/3$ for a 2-input dynamic NOR)
 - no I_{sc} , so all the current provided by PDN goes into discharging C_L

Properties of Dynamic Gates

□ Advantages:


- Lower physical capacitance: uses fewer transistors
- No glitching (dynamic gates can have at most one transition per CLK cycle)
- Only consumes dynamic power.....no static current path ever exists between V_{DD} and GND (including P_{sc})

□ In spite of the above.....overall power dissipation usually **higher** than static CMOS


- CLK power can be significant: extra load on Clk + transition every CLK cycle
- Number of transistors is more than the minimal set required for implementing logic
- Higher switching activity due to higher transition probabilities

Issues in Dynamic Design 1: Charge Leakage

A dynamic inverter

 

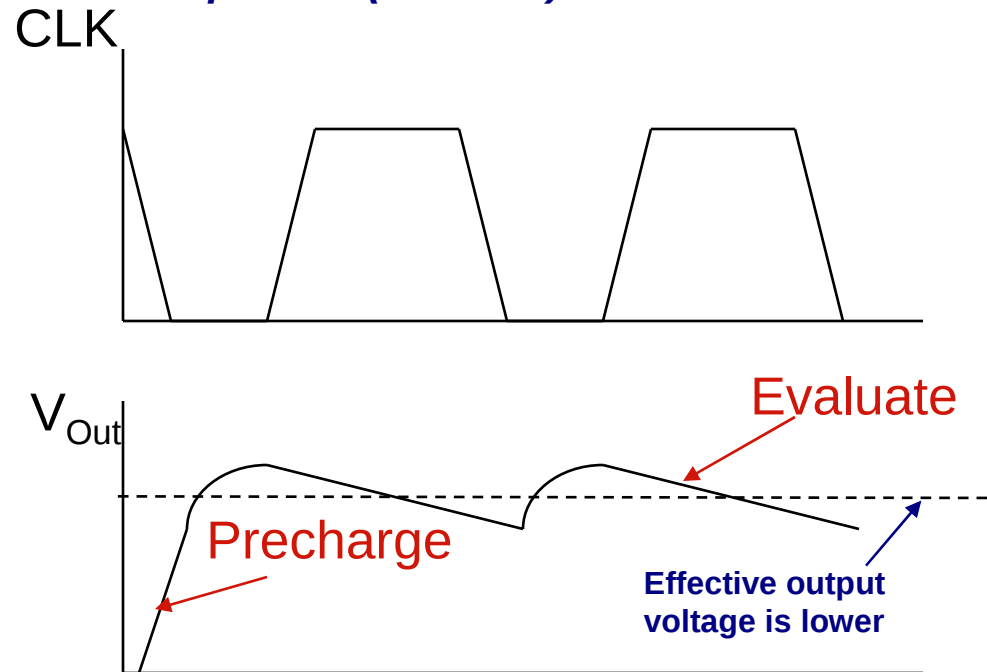Due to leakage, a minimal CLK rate required...(few KHz)




Leakage sources: reverse biased diode and subthreshold

Dominant component is subthreshold current

Note: leakage of precharge PMOS can partially compensate for the charge loss at the dynamic node


Solution to Charge Leakage

 Same approach as level restorer for pass-transistor logic



Contention between keeper and PDN---
strength of keeper must be less than that of the PDN to lower the out node well below the switching threshold of the next gate. Hence keeper size should be small.

 Issues in Dynamic Design 2: Charge Sharing



Charge stored originally on C_L is redistributed (shared) over C_L and C_A leading to reduced robustness


Output node voltage drops and cannot be recovered due to the dynamic nature of the circuit.

Charge Sharing

All inputs = 0 during pre-charge

Initial conditions: $V_{out}(t=0)=V_{DD}$ and $V_x(t=0)=0$

2 possible scenarios:

 

case 1) if $\Delta V_{out} < V_{Tn}$

$$C_L V_{DD} = C_L V_{out}(t) + C_a (V_{DD} - V_{Tn}(V_X))$$

or

$$\Delta V_{out} = V_{out}(t) - V_{DD} = -\frac{C_a}{C_L} (V_{DD} - V_{Tn}(V_X))$$

Final value of V_X


case 2) if $\Delta V_{out} > V_{Tn}$

V_{OUT} and V_X then reach the same value.....

$$\Delta V_{out} = -V_{DD} \left(\frac{C_a}{C_a + C_L} \right)$$

Which of these scenarios is valid?

Charge Sharing

 

Initial conditions: $V_{out}(t=0)=V_{DD}$ and $V_x(t=0)=0$

2 possible scenarios:

$\Delta V_{out} < V_{Tn}$ case I

$\Delta V_{out} > V_{Tn}$ case II

Which of these scenarios is valid?

First find the capacitance ratio: C_a/C_L

The boundary condition between the two cases can be determined by setting $\Delta V_{out} = V_{Tn}$.

Hence,

$$\frac{C_a}{C_L} = \frac{V_{Tn}}{V_{DD} - V_{Tn}}$$


Case I holds when the C_a/C_L ratio is smaller than the value defined above, otherwise **Case II** holds.

Overall, it is desirable to keep $\Delta V_{out} < |V_{Tp}|$ ---since the output of dynamic gate might be connected to a static inverter---low level of V_{out} will cause static power consumption. Also, V_{out} must not go below V_M of the inverter.

Charge Sharing Example


Dynamic 3-input EXOR gate

$$Out = A \oplus B \oplus C$$

 


Worst case change in Output is obtained by exposing the maximum number of internal capacitances to the output: this happens for $\overline{A}BC$ or $A\overline{B}\overline{C}$

Solution to Charge Redistribution

 


Precharge internal nodes (to V_{DD}) using a clock-driven transistor (at the cost of increased area and power)

 Issues in Dynamic Design 3: Backgate Coupling




Capacitive coupling between dynamic node Out1 and H-L transition at Out2 through the gate-drain and gate-source capacitance of M4

Backgate Coupling Effect

 

Coupling causes dynamic node Out1 to drop significantly, which further prevents Out2 from dropping all the way to zero---static power dissipation.

 Issues in Dynamic Design 4: Clock Feedthrough





Coupling between Out and Clk input of the precharge device due to **gate to drain capacitance** (includes both overlap and channel).

Hence, voltage of Out can rise above V_{DD} on the L-H Clk transition (assuming PDN is off). The fast rising (and falling edges) of the clock couple to Out.

Dynamic circuits need careful simulation!

Clk feedthrough can cause normally reverse biased junction diodes of the precharge transistor to become forward biased---causing electron injection into the substrate that can be collected by a nearby high-impedance node in the 1 state, eventually resulting in faulty operation.

Clock Feedthrough

  


Other Effects


- ❑ Capacitive coupling
- ❑ Substrate coupling
- ❑ Minority charge injection
- ❑ Supply noise (ground bounce)

Cascading Dynamic Gates

Simple cascoding doesn't work...

 

 As long as $Out1 > V_M$ ($\sim V_{Tn}$) of the second inverter, Out2 will decrease leading to reduced NMs




Solution: Set all inputs to 0 during precharge

For correct operation only 0 $\rightarrow$ 1 transitions should be allowed at inputs!

Domino Logic

 An n-type dynamic logic followed by a static inverter...




All inputs (are outputs of other Domino gates) are set to 0 at the end of precharge phase

Only 0 to 1 transition at the inputs during evaluation phase:
during evaluation, dynamic gate conditionally discharges and the output of the inverter makes a conditional transition from 0 to 1.

Domino Logic

 An n-type dynamic logic followed by a static inverter...




The static inverter **reduces the capacitance** of the dynamic output node by separating internal and load capacitances.....it also **increases the NM** (due to the low-impedance output)

The inverter can also be used to **drive a keeper** device to combat leakage and charge redistribution.

Why Domino?

A Domino chain

 


Precharge: all inputs=0

Evaluation: Output of domino1 either stays at 0 or makes a transition from 0 to 1, affecting the second gate. This effect might ripple through the whole chain...*like a line of falling dominos!*


Properties of Domino CMOS Logic

- ❑ Only non-inverting logic can be implemented (due to the static inverter)
 - Major limitation
 - Can be overcome using dual-rail domino (an expensive solution)
- ❑ Very high speed
 - Only rising edge delays, and $t_{pHL}=0$
 - static inverter can be skewed to match the fanout, which is already much smaller than in the complementary case, since only a single gate capacitance needs to be accounted for per fan-out gate.
 - Input capacitance reduced – smaller logical effort

Designing with Domino Logic

 

Footless Domino

 

If $ln_1=1$, $out_1=0$ and $ln_2=1$

On the falling edge of CLK, let $In_1 = 0$: but it takes two gate delays for In_2 to be 0, during which second gate cannot pre-charge its output (Out_2), since PDN is fighting the precharge-PMOS

Time taken to precharge equals the critical path delay!


Better to use the evaluation device....

Pre-charge is rippling – short-circuit current
A solution is to delay the clock for each stage

Differential (Dual Rail) Domino

Overcomes the non-inverting property of Domino Logic: used commercially in several microprocessors

Uses a pre-charged load....

 


Possible to implement any arbitrary function....but comes at the expense of increased power since a transition is guaranteed every CLK cycle irrespective of the input values....either $Out1$ or $Out2$ must make a 0 to 1 transition.

np-CMOS

Alternative to cascading dynamic gates....uses n-type and p-type dynamic logic

Exploits duality between n-tree and p-tree logic gates to eliminate cascading problem

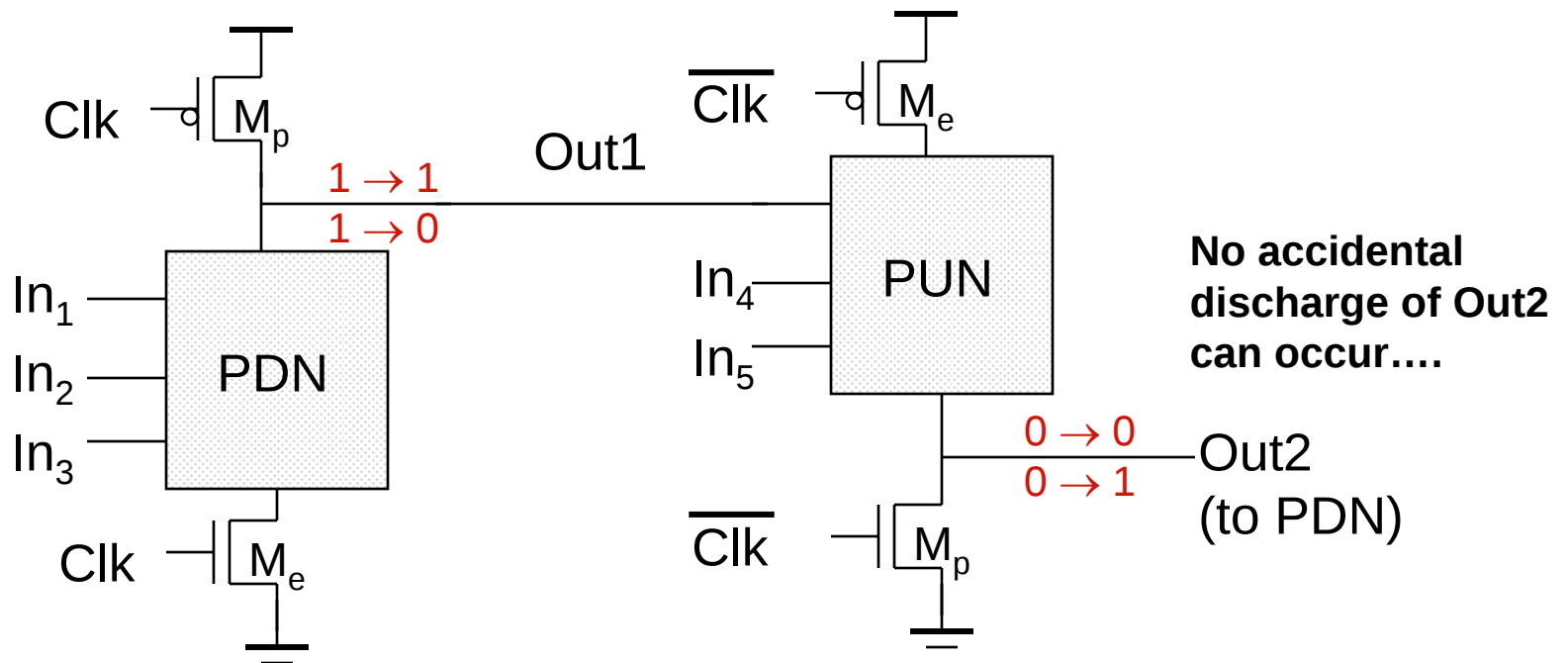No extra inverter at the outputs....unless output of n-tree (p-tree) needs to be connected to another n-tree (p-tree) gates



Only $0 \rightarrow 1$ transitions allowed at inputs of PDN

Only $1 \rightarrow 0$ transitions allowed at inputs of PUN

Drawback: p-tree gates are slower than the n-tree gates....needs proper skewing of PMOS....area penalty

No buffers---so dynamic nodes need to be routed between gates