
ECE 225

High Speed Digital IC Design

Lecture 4

Interconnect Technology and Scaling Issues-I

Prof. Kaustav Banerjee
Electrical and Computer Engineering
E-mail: kaustav@ece.ucsb.edu


Outline

❑ Interconnect and Technology Scaling


- ➔ ■ Interconnect technology: background and trends
- Interconnect parasitics: R-L-C
- Elmore delay formalism
- Interconnect scaling: implications for technology and design

Interconnect Technology: Past and Present

 A brief review of the past interconnect technologies.....(Al, AlCu, W-vias, Al-vias, silicides, doped poly etc)



Wire Vs Gate Delay.....

 

Interconnect delay has become the dominant factor determining chip performance...

K. Banerjee et al., Proc. IEEE, May 2001.

Interconnect Parasitics


❑ Interconnect parasitics

- affect performance and power consumption
- affect reliability

❑ Classes of parasitics


- Capacitive
- Resistive
- Inductive

Wire Resistance

 

$$R = \frac{\rho L}{HW}$$

Sheet Resistance
 R_0

 


By adjusting L/W ratios.....

Interconnect Material Resistivity

Material	ρ ($\Omega\text{-m}$) at room temp.
Silver (Ag)	1.6×10^{-8}
Copper (Cu)	1.7×10^{-8}
Gold (Au)	2.2×10^{-8}
Aluminum (Al)	2.7×10^{-8}
Tungsten (W)	5.5×10^{-8}

VLSI Interconnect Structure

 


- Adjacent wires are orthogonal...
- C_{intra} is the dominating capacitance...

Wire Capacitance: The Parallel Plate Model


1-dimensional model

Valid when, $W \gg t_{di}$

 

$$C_{int} = \frac{\epsilon_{di}}{t_{di}} WL$$

 Wire Capacitance: Fringing Vs Parallel Plate




*Saturates to
~1pF/cm due to
fringing fields*

Note: aspect ratio = H/W

(from [Bakoglu89])

Impact of Interwire Capacitance

 

$W/H = 1.75$

- Reduce wire width, w
- Reduce spacing ($=w$)
- $C_{total} = C_{ground} + C_{interwire}$
- $C_{ground} = C_{p-p} + C_{fringing}$

Interwire cap. (crosstalk) becomes important in a multi-level structure

More imp. For higher level wires that are far away from substrates

(from [Bakoglu89])

Accurate Interconnect Capacitance Extraction

- ❑ Requires full 3-D electromagnetic simulation
- ❑ FASTCAP (from MIT) is a widely used tool
 - See K. Nabors and J. White, “FastCap: a multipole accelerated 3-D capacitance extraction program,” IEEE Trans. Computer-Aided Des. Integr. Circuits Syst., vol. 10, no. 11, pp. 1447–1459, Nov. 1991.
- ❑ Can be time consuming for complex interconnect topologies

Permittivity of Materials

Material	ϵ_r
Free space	1
Aerogels	~ 1.5
Polyimides (organic)	3-4
Silicon dioxide	3.9
Glass-epoxy (PC board)	5
Silicon Nitride (Si_3N_4)	7.5
Alumina (package)	9.5
Silicon	11.7

RC Delay: Design Rules of Thumb

- ❑ RC delays should only be considered when $t_{pRC} \gg t_{pgate}$ of the driving gate

$$L_{crit} \gg \sqrt{t_{pgate}/0.38rc}$$


- ❑ RC delays should only be considered when the rise (fall) time at the line input is smaller than RC, the rise (fall) time of the line

$$t_{rise} < RC$$

- when not met, the change in the signal is slower than the propagation delay of the wire

Elmore Delay-RC Chain (Branched)

 W. C. Elmore, "The transient response of damped linear networks," *J. Appl. Phys.*, vol. 19, pp. 55–63, Jan. 1948.




If a step input V_{in} is applied at $t=0$

Elmore Delay at node i : $\tau_{Di} = \sum_{k=1}^N C_k R_{ik}$ (First-order time constant of the network)

$N = \#$ of capacitances in the network

Wire Model

 

For a non-branched RC chain:

$$\tau_{DN} = \sum_{i=1}^N C_i R_{ii} \quad t_{Di} = C_1 R_1 + C_2 (R_1 + R_2) + \dots + C_i (R_1 + R_2 + \dots + R_i)$$

If wire modeled by N equal-length segments ($R_{seg} = rL/N$, $C_{seg} = cL/N$)


$$\tau_{DN} = \left(\frac{L}{N}\right)^2 (rc + 2rc + \dots + Nrc) = (rcL^2) \frac{N(N+1)}{2N^2} = RC \frac{N+1}{2N}$$

For large values of N:

$$\tau_{DN} = \frac{RC}{2} = \frac{rcL^2}{2}$$

Definition of Inductance (L)

 $L_{ij} =$ geometrical constant of proportionality between the magnetic flux through victim loop j and the current running on aggressor loop i causing it



$$L_{ij} = \frac{\Psi_{i \rightarrow j}}{I_i} = \frac{1}{I_i} \int_{S_j} \mathbf{B}^{(i)} \cdot d\mathbf{S}_j \quad \Longrightarrow \quad L_{ij} = \frac{\mu_0}{4\pi} \oint_{C_j} \oint_{C_i} \frac{d\mathbf{l}_j \cdot d\mathbf{l}_i}{|\mathbf{r}_j - \mathbf{r}_i|}$$

See **A. E. Ruehli**, “Inductance calculations in a complex integrated circuit environment,” *IBM J. Res. Develop.*, pp. 470–481, Sept. 1972.

Accurate Interconnect Inductance Extraction

- ❑ Requires full 3-D electromagnetic simulation
- ❑ FASTHENRY (from MIT) is a widely used tool
 - See M. Kamon, M. J. Tsuk, and J. K. White, “FASTHENRY: A multipole-accelerated 3-D inductance extraction program,” IEEE Trans. Microwave Theory Techn., vol. 42, pp. 1750–1758, Sept. 1994.
 - Can be time consuming for complex interconnect topologies
 - Has limitations at very high frequencies....

On-Chip Inductance

- ❑ L starts to play a role at high GHz frequencies
- ❑ Effect increases for Cu: lower resistivity
- ❑ Can increase interconnect delay
- ❑ Can cause overshoot and undershoot effects
- ❑ Can cause switching noise: $L di/dt$ voltage drops

$$Z = R + j\omega L$$

inductance of a wire surrounded by a uniform dielectric:

$$c\ell = \epsilon\mu$$

c = cap. per unit length

l = inductance per unit length


From Maxwell's Laws:

$$v = \frac{1}{\sqrt{\ell c}} = \frac{1}{\sqrt{\epsilon \mu}} = \frac{c_0}{\sqrt{\epsilon_r \mu_r}}$$

v = propagation speed of EM wave

c₀ = speed of light in vacuum = 30 cm/ns

Wire Length Dependency of L Effects

 

$$l'_{min} = \frac{T_{rise} v}{2}$$

$$l'_{max} = \frac{2Z_0}{r}$$

R. Suaya et al., Advanced Metallization Conf. 2006

RLC Delay: Design Rules of Thumb

Wires in RLC domain:

$$t_{50\%} = \sqrt{LC} + \frac{\tau_{FO4}}{2} + 0.7Z_0C_{load} \quad \text{if}$$


$$\frac{rL}{Z_0} < 2\ln\left(\frac{4Z_0}{R_{driver} + Z_0}\right), \quad R_{driver} < 3Z_0$$

$$\text{where } Z_0 = \sqrt{l/c}$$

Also see: A. Deutsch, et al., “When are transmission-line effects important for on-chip interconnections?,” IEEE Trans. Microwave Theory Tech., vol. 45, pp. 1836–1846, Oct. 1997.

Repeater Insertion

 
- RC-Delay of wire increases quadratically with its length
- **Repeater** (inverter) or **buffer** insertion makes the delay increase proportional to its length
- Repeater size and inter-repeater separation can be optimized to give minimal delay



(from [Bakoglu89])

Driver-Interconnect-Load Equivalent Circuit

 - Interconnect segment of length l between two inverters



- V_{st} is the voltage at the input capacitance that controls the voltage source V_{tr}
- R_{tr} is the driver transistor resistance, C_p is output parasitic capacitance
- C_L is the load capacitance of next stage, r and c are interconnect resistance and capacitance per unit length respectively

Interconnect Scaling

Interconnect Scaling Scenarios

- Performance of a technology can be summarized by the time delay, t_d :

$$t_d = R_{tr} (C_P + C_L) + (R_{tr} c + r C_L) l + \frac{1}{2} r c l^2$$

intrinsic stage delay + load delay + interconnect delay

- If s is a scaling parameter: ratio of the feature size at a newer technology node to the feature size at an older node, then $s < 1$.
- Two simple scaling scenarios
 - scale metal pitch at constant thickness
 - scale metal pitch and the metal thickness

Interconnect Scaling

Implications of Technology Scaling on Technology Performance

- Scaling metal pitch at constant thickness.
 - load delay, line delay, and current density will scale as $1/s$, $1/s^2$, and $1/s$ respectively.
- Scaling metal pitch and the metal thickness.
 - load delay, line delay, and current density will scale as $1/s^2$, $1/s^2$, and $1/s^2$ respectively.
- Hence, interconnect delay begin to dominate technology performance and current density increases with scaling.

Interconnect Technology Scaling Trends

- Interconnect scaling requirements drive several technology enhancements:
 - use of low-dielectric constant (low-k) materials lowers the interconnect capacitance per unit length (c) and therefore reduces the delay time.
 - lower c helps in minimizing cross-talk noise.
 - lower c also helps to reduce the dynamic power dissipation during switching of gates.
 - lower interconnect resistance and higher current density requirements have driven the use of new metallization, such as Cu.