

ECE 225

High-Speed Digital IC Design

Lecture 3

Review of Basic Circuit Styles-1

Prof. Kaustav Banerjee
Electrical and Computer Engineering
E-mail: kaustav@ece.ucsb.edu

Static and Dynamic CMOS

- ❑ In **static** circuits at every point in time (except when switching) the output is connected to either GND or V_{DD} via a low resistance path.
 - fan-in of n requires $2n$ (n N-type + n P-type) devices
- ❑ **Dynamic** circuits rely on the temporary storage of signal values on the capacitance of high impedance nodes.
 - requires only $n + 2$ ($n+1$ N-type and 1 P-type) transistors

Static and Dynamic CMOS Circuit Families

□ Static:

- **Complementary CMOS**
 - (robustness, low power, large fan-in expensive in terms of area and performance)
- **Ratioed Logic (pseudo-NMOS, DCVSL)**
 - (simple and fast at the expense of reduced NM and static power)
- **Pass-Transistor Logic (Transmission Gate)**
- -attractive for specific circuits: MUX, XOR-dominated logic such as Adders)

□ Dynamic:

- good for fast and complex gates, design process is harder due to parasitic effects, leakage puts an upper limit on the operating frequency of the circuit
 - **Domino Logic**
 - **np-CMOS**


Which style is best?

.....depends on ease of design, performance, power, area and robustness.

Complementary CMOS Logic


- ❑ Full rail-to-rail swing; **high noise margins**
- ❑ Logic levels not dependent upon the relative device sizes; **ratioless**
- ❑ Always a path to Vdd or Gnd in steady state; **low output impedance**
- ❑ Extremely **high input resistance**; nearly zero steady-state input current
- ❑ No direct path steady state between power and ground; **no static power dissipation**
- ❑ Propagation delay function of load capacitance and resistance of transistors

Static Complementary CMOS

 

PUN and PDN are **dual** logic networks


Inverter Threshold

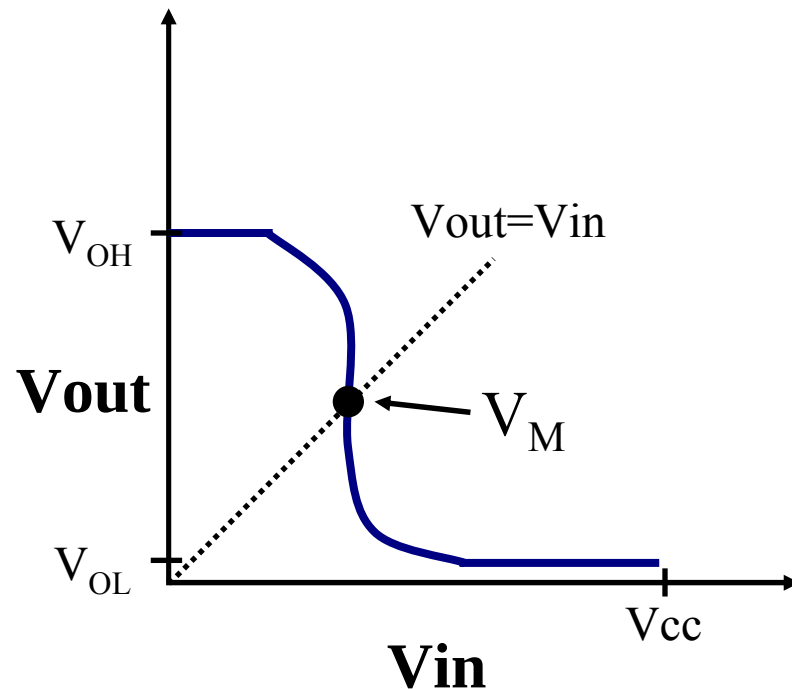

Inverter switching threshold:


- Point where voltage transfer curve intersects line $V_{out}=V_{in}$
- Represents the point at which the inverter switches state
- Normally, $V_M \approx V_{CC}/2$

Noise Margins

 

- V_{IL} and V_{IH} measure effect of input voltage on inverter output
- V_{IL} = largest input voltage recognized as logic '0'
- V_{IH} = smallest input voltage recognized as logic '1'
- Defined as point on VTC where slope = -1

Noise Margin (cont)

 

Ideally, noise margin should be as large as possible

- Noise margin is a measure of the *robustness* of an inverter
 - $N_{ML} = V_{IL} - V_{OL}$
 - $N_{MH} = V_{OH} - V_{IH}$
- Models a chain of inverters. Example:
 - First inverter output is V_{OH}
 - Second inverter recognizes input $> V_{IH}$ as logic '1'
 - Difference $V_{OH} - V_{IH}$ is "safety zone" for noise

Noise Margin (cont)

- Why are V_{IL} , V_{IH} defined as unity-gain point on VTC curve?
 - Assume there is noise on input voltage V_{in}

$$V_{out} = f(V_{in} + V_{noise})$$

- First-order approximation (Taylor Series):

$$V_{out} = f(V_{in}) + \frac{dV_{out}}{dV_{in}} V_{noise}$$


Note: $dV_{out}/dV_{in} = 0$ occurs only at the beginning and at the end of the VTC curve, elsewhere it is negative

- If gain (dV_{out}/dV_{in}) > 1 , noise will be amplified.
- If gain < 1 , noise is filtered. Therefore V_{IL} , V_{IH} ensure that gain < 1

CMOS Inverter Operation (summary)


Table 2.2 Relationships between voltages for the three regions of operation of a CMOS inverter			
	Cutoff	Linear	Saturated
nMOS	$V_{gsn} < V_{tn}$	$V_{gsn} > V_{tn}$	$V_{gsn} > V_{tn}$
	$V_{in} < V_{tn}$	$V_{in} > V_{tn}$	$V_{in} > V_{tn}$
		$V_{dsn} < V_{gsn} - V_{tn}$	$V_{dsn} > V_{gsn} - V_{tn}$
		$V_{out} < V_{in} - V_{tn}$	$V_{out} > V_{in} - V_{tn}$
pMOS	$V_{gsp} > V_{tp}$	$V_{gsp} < V_{tp}$	$V_{gsp} < V_{tp}$
	$V_{in} > V_{tp} + V_{DD}$	$V_{in} < V_{tp} + V_{DD}$	$V_{in} < V_{tp} + V_{DD}$
		$V_{dsp} > V_{gsp} - V_{tp}$	$V_{dsp} < V_{gsp} - V_{tp}$
		$V_{out} > V_{in} - V_{tp}$	$V_{out} < V_{in} - V_{tp}$

CMOS Inverter VTC

 


In which state do the transistors spend most of their time?

 Switching Threshold as a function of Transistor Ratio



Inverter Gain

0.25 μm CMOS, $V_{DD} = 2.5\text{V}$

 

Gain is mostly determined by technology parameters, especially channel length modulation, but also by V_{DD}

Note: approximately $V_M \propto V_{DD}$

Inverter Skew


 


FIG 2.26 Transfer characteristics of skewed inverters

Propagation Delay

CMOS inverter capacitances

 


Cap on Node f:

- Junction cap: $C_{db,p}$ and $C_{db,n}$
- Gate (overlap) capacitance $C_{gd,p}$ and $C_{gd,n}$ (beware of Miller effect)
- Interconnect cap: C_{int}
- Receiver gate cap: C_g

Transient Response

 Due to C_{gd} of transistors: directly couples voltage at input to output before the transistors can even start to react to changes at the input---can affect gate performance



Symmetric inverter has $t_{pHL} = t_{pLH}$

$$t_p = 0.69 C_L (R_{eqn} + R_{eqp})/2$$

$$R_{eq} = \frac{1}{V_{DD}/2} \int_{V_{DD}/2}^{V_{DD}} \frac{V}{I_{DSAT}(1 + \lambda V)} dV \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{7}{9} \lambda V_{DD}\right)$$

with $I_{DSAT} = k' \frac{W}{L} \left((V_{DD} - V_T) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$


Design for Performance

- ❑ Keep load capacitances (C_L) small
 - Recall that three major components contribute to the load cap.
 - internal diffusion + overlap caps
 - interconnect cap.
 - fan-out (gate cap)
- ❑ Increase transistor sizes
 - watch out for self-loading!
- ❑ Increase V_{DD} (??)
 - watch out for reliability issues!


Delay as a function of V_{DD}

Same as the ON resistance of a transistor....

 
Trade off energy dissipation vs performance.....



Device Sizing

 

NMOS/PMOS ratio

 


If symmetry and noise margins are not of prime concern, inverter delay can be reduced by reducing the width of PMOS....

Designing Combinational Logic Circuits

Analysis of CMOS gates

 □ Represent “on” transistors as resistors



- Transistors in series $\rightarrow$ resistances in series
 - Effective resistance = $2R$
 - Effective width = $\frac{1}{2} W$





Note: 1) As transistor width increases, its on resistance (R) decreases

2) If transistor channel length increases, R increases


Equivalent Inverter

- CMOS gates: many paths to V_{cc} and Gnd
 - Multiple values for V_M , V_{IL} , V_{OL} , etc
 - Different delays for each input combination
- Equivalent inverter
 - Represent each gate as an inverter with appropriate device width
 - Include only transistors which are on or switching
 - Calculate V_M , delays, etc using inverter equations

Switch Delay Model

    

Input Pattern Effects on Delay

 


2-input NAND

- Delay is dependent on the **pattern** of inputs
- Low to high transition
 - both inputs go low
 - delay is $0.69 R_p / 2 C_L$
 - one input goes low
 - delay is $0.69 R_p C_L$
- High to low transition
 - both inputs go high
 - delay is $0.69 2R_n C_L$

Delay Dependence on Input Patterns

 Simulated Low to High delay for a 2-input NAND




Input Data Pattern	Delay (psec)
A=B=0→1	69
A=1, B=0→1	62
A= 0→1, B=1	50
A=B=1→0	35
A=1, B=1→0	76
A= 1→0, B=1	57

Note: worst case L-H delay depends on which input (A or B) is driven low (due to internal node cap of PDN stack: source of M2)

NMOS = 0.5 μ m/0.25 μ m
PMOS = 0.75 μ m/0.25 μ m
 C_L = 100 fF

Delay Dependence on Input Patterns

 

2-input NAND

- ❑ **High to Low Delay** depends on the initial state of the internal nodes
- ❑ Example: when both inputs transition from 0 to 1, it is important to know the state of the internal node (between M1 and M2)
- ❑ **Worst case:** when internal node is initially charged up to $V_{DD} - V_{tn}$. This can be ensured by pulsing the A input from 1-0-1, while B only makes the 0-1 transition.

Bottom Line: Delay estimation can be a fairly complex affair and requires careful consideration of the internal node caps. and data patterns

Transistor Sizing

- ❑ Sizing for switching threshold
 - All inputs switch together
- ❑ Sizing for delay
 - Find **worst-case** input combination
- ❑ Find equivalent inverter, use inverter analysis to set device sizes

Transistor Sizing


What sizing will lead to a 2:1 equivalent inverter?

For effective $R_p = R_n$, we need $W_p = 2W_n$

Since two NMOS are in series, each should have $R_n/2$, hence each NMOS size, $W_n = 2$

Each PMOS should be such that $R_p = \text{effective } R_n$ (which corresponds to $W_n = 1$)

Hence, $W_p = 2$ (effective $W_n = 1$)

 


2-input NAND

For effective $R_p = R_n$, we need $W_p = 2W_n$

Also, since two PMOS are in series, each should have $R_p/2$

Hence, W_p of each should be $4W_n$

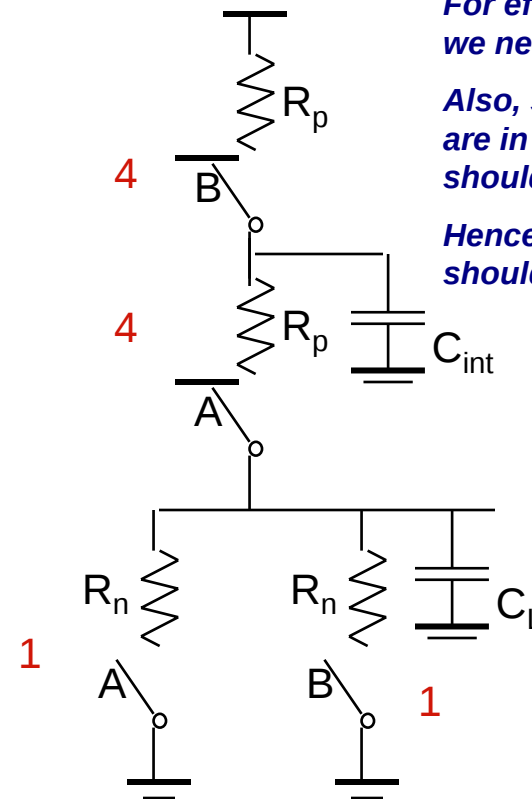
Avoid stacking PMOS transistors in series....



2-input NOR

Transistor Sizing a Complex CMOS Gate

 What sizing will lead to a 2:1 equivalent inverter?



Note: $A=3$ and $B=C=D=6$ will also give a 2:1 inverter but that will give higher output parasitic capacitance (due to larger D)

1. Start with a transistor in the PDN, that is (preferably) isolated (i.e., it can pull down the output node on its own)----D in this case
2. Assign a minimum size to this transistor ($W=1$ for D)
3. Now identify other paths in the PDN that can also discharge the output node: AB and AC in this case.
4. Size A, B, and C such that: each path will be electrically equivalent to the path through D (i.e., with same resistance), hence A, B and C should have $W=2$
5. Repeat the same for the PUN, keeping in mind that i) effective resistance of any path must equal the effective resistance of any path in the PDN, and ii) PMOS transistors will have to be sized (twice as large in this case) appropriately.

Note: here we ignored internal caps.

CMOS gate design: summary

- Designing a CMOS gate:
 - Find pulldown NMOS network from logic function or by inspection
 - Find pullup PMOS network
 - By inspection
 - Using logic function
 - Using dual network approach
 - Size transistors using equivalent inverter
 - Find worst-case pullup and pulldown paths
 - Size to meet rise/fall or threshold requirements