

ECE 225

High-Speed Digital IC Design


Lecture 4

Review of Basic Circuit Styles-2

Prof. Kaustav Banerjee
Electrical and Computer Engineering
E-mail: kaustav@ece.ucsb.edu

Inverter Chain Sizing

Load capacitance

 

$$C_L = C_{int} + C_{ext}$$

Internal Caps of Driver (C_{int}):

= Junction caps: $C_{db,12}$ +

Gate caps: $C_{gd,12}$ (including Miller Caps.)

External Caps (C_{ext}):

= Interconnect cap: C_w

+ Receiver gate caps: $C_{g,43}$

Intrinsic delay of CMOS inverter

Let R_{eq} be the equivalent resistance of the gate (inverter), then delay (t_p) is defined as:

$$\begin{aligned} t_p &= 0.69 R_{eq} (C_{int} + C_{ext}) \\ &= 0.69 R_{eq} C_{int} \left(1 + \frac{C_{ext}}{C_{int}} \right) \\ &= t_{p0} \left(1 + \frac{C_{ext}}{C_{int}} \right) \end{aligned}$$

t_{p0} is the **intrinsic** delay

Impact of sizing on gate delay

Let S be the sizing factor

R_{ref} be the resistance of a reference gate (usually a minimum size gate)



C_{iref} be the internal capacitance of the reference gate

$$\begin{aligned}C_{int} &= S C_{iref}, \quad R_{eq} = \frac{R_{ref}}{S} \\t_p &= 0.69 \left(\frac{R_{ref}}{S} \right) (S C_{iref}) \left(1 + \frac{C_{ext}}{S C_{iref}} \right) \\&= 0.69 R_{ref} C_{iref} \left(1 + \frac{C_{ext}}{S C_{iref}} \right) \\&= t_{p0} \left(1 + \frac{C_{ext}}{S C_{iref}} \right)\end{aligned}$$

Hence:


1. Intrinsic delay is independent of gate sizing, and is determined only by technology and inverter layout
2. If S is made very large, gate delay approaches the intrinsic value but increases the area significantly

Inverter with Load

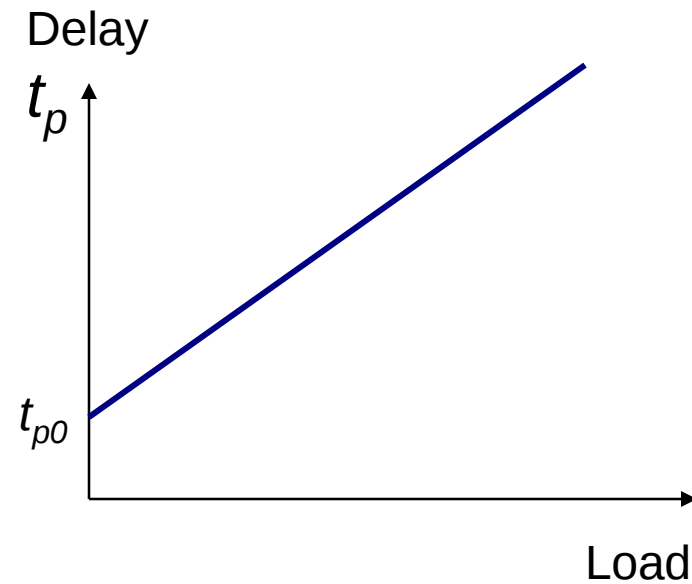 

$$\text{Delay } (t_p) = kR_W(C_{int} + C_{ext}) = kR_W C_{int} + kR_W C_{ext} = \underbrace{kR_W C_{int}}_{t_{p0} \text{ (intrinsic delay)}} (1 + C_{ext}/C_{int})$$

Apply to Inverter Chain

 

$$t_p = t_{p1} + t_{p2} + \dots + t_{pN}$$

$$t_{p,j} = t_{p0} \left(1 + \frac{C_{gin,j+1}}{\gamma C_{gin,j}} \right)$$

$$t_p = \sum_{j=1}^N t_{p,j} = t_{p0} \sum_{i=1}^N \left(1 + \frac{C_{gin,j+1}}{\gamma C_{gin,j}} \right), \quad C_{gin,N+1} = C_L$$

Optimum Delay and Number of Stages

When each stage is sized by f and has same eff. fanout f :

$$\frac{C_L}{C_{g,N}} = \frac{C_{g,N}}{C_{g,N-1}} = \dots = \frac{C_{g,2}}{C_{g,1}} = f$$

$$\text{Hence, } f^N = C_L / C_{g,1} = F$$

F is the overall effective fanout of the circuit

Effective fanout of each stage: $f = \sqrt[N]{F}$

Minimum path delay:


$$t_p = N t_{p0} \left(1 + \sqrt[N]{F} / \gamma \right)$$

If N is too large, intrinsic delay of stages dominate, while if N is small, effective fanout of each stage (f) is large and the second term dominates

How to choose N?

Example

If N is given....

 

C_L/C_1 has to be evenly distributed across $N = 3$ stages:

$$f = \sqrt[3]{8} = 2$$

Optimum Number of Stages

For a given load, C_L and given input capacitance C_{in}
Find optimal sizing f

$$C_L = F \cdot C_{in} = f^N C_{in} \quad \text{with} \quad N = \frac{\ln F}{\ln f}$$

$$t_p = N t_{p0} \left(F^{1/N} / \gamma + 1 \right) = \frac{t_{p0} \ln F}{\gamma} \left(\frac{f}{\ln f} + \frac{\gamma}{\ln f} \right)$$

$$\frac{\partial t_p}{\partial f} = \frac{t_{p0} \ln F}{\gamma} \cdot \frac{\ln f - 1 - \gamma / f}{\ln^2 f} = 0$$

If self-loading is ignored....


For $\gamma = 0$, $f = e$, $N = \ln F$

$$f = \exp(1 + \gamma / f)$$

Optimum Effective Fanout f

Optimum f for given process defined by γ

$$f = \exp(1 + \gamma / f)$$


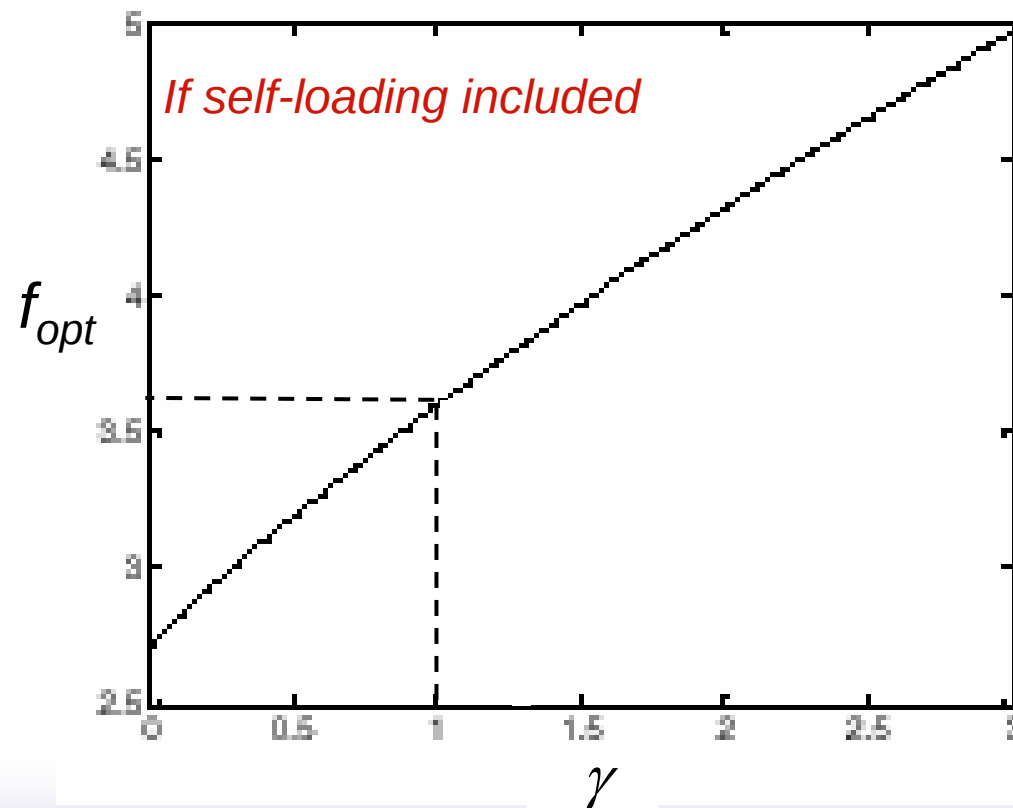


Optimum
tapering factor:

$$f_{opt} = 3.6$$

for $\gamma=1$

Fan-In Considerations

  


Distributed RC model
(Elmore delay)

Assuming all NMOS are equal size

$$t_{pHL} = 0.69 R_{eqn}(C_1 + 2C_2 + 3C_3 + 4C_L)$$


Propagation delay deteriorates rapidly as a function of fan-in – **quadratically** in the worst case.

t_p as a Function of Fan-In

 

Gates with a fan-in greater than 4 should be avoided.

t_p as a Function of Fan-Out

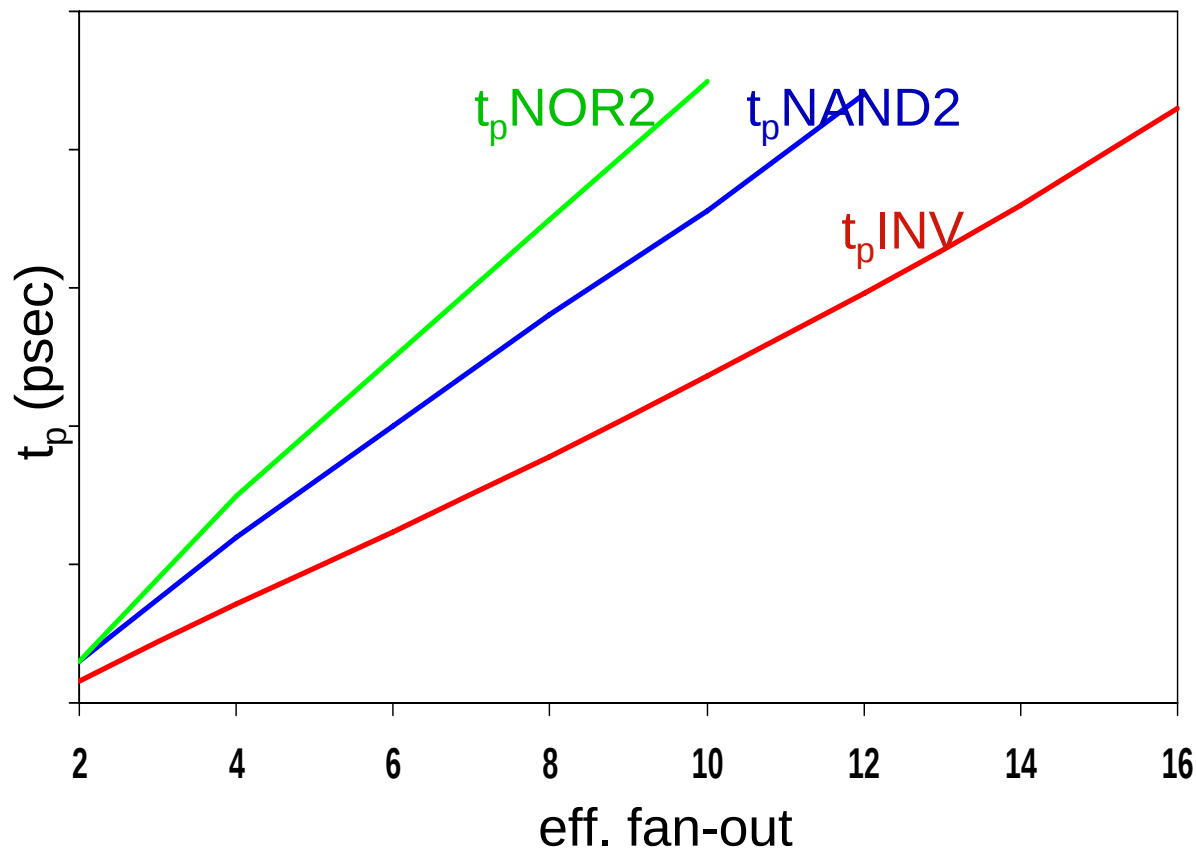

All gates have the same drive current.

Slope is a function of “driving strength”

Note: i) these lines are not going through the origin, ii) NAND and NOR have same intrinsic delay....


t_p as a Function of Fan-In and Fan-Out

- Fan-in: **quadratic** due to increasing resistance and capacitance
- Fan-out: each additional fan-out gate adds **two** gate capacitances to C_L

$$t_p = a_1 FI + a_2 FI^2 + a_3 FO$$

Fast Complex Gates: Design Technique 1

 - Transistor sizing
 - as long as fan-out capacitance dominates
- Progressive sizing (not so simple to layout!)



Distributed RC line

$$M1 > M2 > M3 > \dots > MN$$


(the transistor closest to the output is the smallest: has biggest R)

Can reduce delay by more than 20%; decreasing gains as technology shrinks


Fast Complex Gates: Design Technique 2

□ Transistor ordering

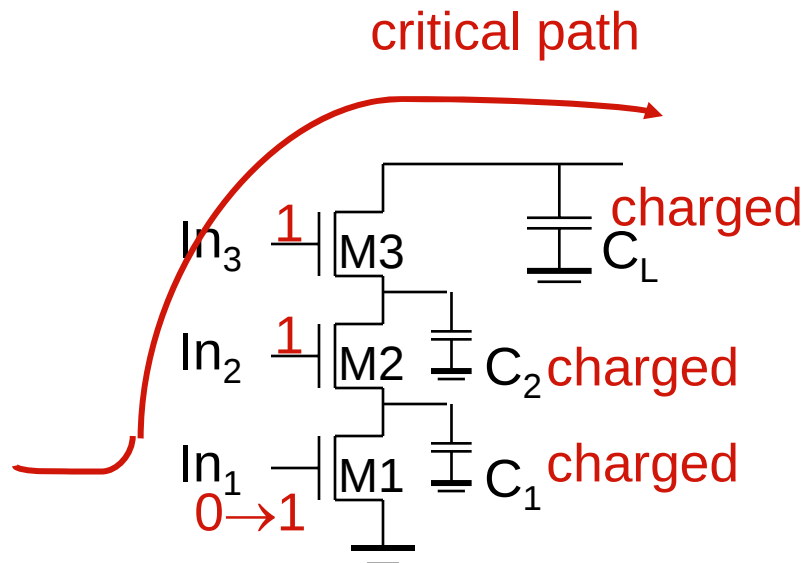Critical path is determined by the slowest arriving signal: In1



 delay determined by time to discharge C_L , C_1 and C_2




delay determined by time to discharge C_L



Fast Complex Gates: Design Technique 3

□ Alternative logic structures

$$F = ABCDEFGH$$

 


Using De Morgan's Law...

  

Fast Complex Gates: Design Technique 4

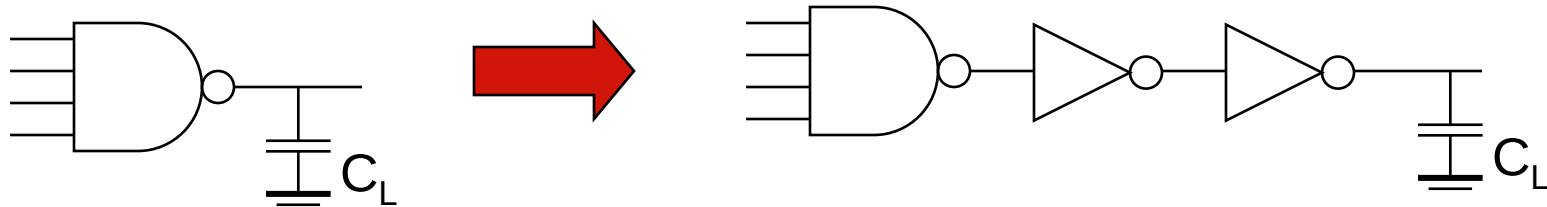- Isolating fan-in from fan-out using buffer insertion



Fast Complex Gates: Design Technique 5

- Reducing the voltage swing

$$t_{pHL} = 0.69 (3/4 (C_L V_{DD}) / I_{DSATn})$$

$$= 0.69 (3/4 (C_L V_{swing}) / I_{DSATn})$$

- linear reduction in delay
 - also reduces power consumption
- But the following gate is much slower!
 - Or requires use of “sense amplifiers” on the receiving end to restore the signal level (memory design)

Sizing Logic Paths for Speed

- ❑ Frequently, input capacitance of a logic path is constrained
- ❑ Logic also has to drive some capacitance
- ❑ Example: ALU load in an Intel's microprocessor is 0.5pF
- ❑ How do we size the ALU datapath to achieve maximum speed?
- ❑ We have already solved this for the inverter chain – can we generalize it for any type of logic?

Minimizing Delay in Complex Logic Networks

$$\begin{aligned} \text{Delay} &= t_{p0} \left(1 + \frac{f}{\gamma} \right) (\text{inverter}) \\ &= t_{p0} \left(p + \frac{g \cdot f}{\gamma} \right) (\text{Complex gate}) \end{aligned}$$

Everything Normalized w.r.t an inverter:

$$g_{inv} = 1, p_{inv} = 1$$

f – effective fanout (*ratio of external load and input cap. of gate*)

p – ratio of intrinsic delays of complex gate and inverter
(value increases with complexity of gate)


g – logical effort: how much more input capacitance is presented by the complex gate to deliver the same output current as an inverter (depends only on circuit topology)

Logical Effort

- ❑ Inverter has the smallest logical effort and intrinsic delay of all static CMOS gates
- ❑ Logical effort of a gate is the ratio of its input capacitance to the inverter capacitance when sized to deliver the same current
- ❑ Logical effort increases with gate complexity


Logical Effort

 Logical effort is the ratio of input capacitance of a gate to the input capacitance of an inverter with the **same output current**



Inverter


$$g = 1$$

 

2-input NAND

$$g = 4/3$$

 Since two NMOS are in series, each should have $R_n/2$, hence each NMOS size, $W_n = 2$
Each PMOS should be such that $R_p = R_n$, or $W_p = W_n$



2-input NOR

$$g = 5/3$$


For $R_p = R_n$, we need $W_p = 2W_n$
Since two PMOS are in series, each should have $R_p/2$
or W_p of each should be $4W_n$

Delay in a Logic Gate

Gate delay:

$$d = h + p$$


effort delay intrinsic delay

 

Effort delay (or gate effort):


$$h = g f$$

 logical effort effective fanout = C_{ext}/C_{in}



- **Logical effort** is a function of topology, independent of sizing
- Effective fanout (**electrical effort**) is a function of load/gate size


Logical Effort of Gates

 

Ratioed Logic


Ratioed Logic

 Need $N+1$ transistors vs $2N$ for complementary CMOS



Goal: to reduce the number of devices over complementary CMOS

Ratioed Logic: Resistive Load

 

- N transistors + Load

- $V_{OH} = V_{DD}$


- $V_{OL} = \frac{R_{PN}}{R_{PN} + R_L}$

*Ideally V_{OL} should be as small as possible.
Hence, R_L should be large...*





- Assymetrical response

- Static power consumption

- $t_{pL} = 0.69 R_L C_L$

 

Active Loads

 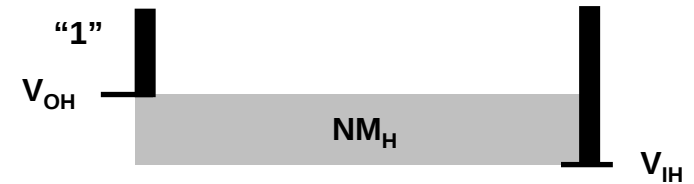  


$V_{OH} = V_{DD}$ (assuming $V_{OL} < V_{tn}$)

Ideally V_{OL} should be as small as possible. Hence, PMOS device should be minimum sized...

However, since V_{OL} is not 0 V, contention between PMOS and the PDN lowers the NM and results in static power dissipation.

Pseudo-NMOS

 

$$V_{OH} = V_{DD} \text{ (similar to complementary CMOS)}$$

To Find V_{OL} :

$$k_n \left((V_{DD} - V_{Tn}) V_{OL} - \frac{V_{OL}^2}{2} \right) + k_p ((-V_{DD} - V_{Tp}) V_{DSATp} - V_{DSATp}^2/2) = 0$$

Note: NMOS in linear mode, since ideally the output=0 V

Note: PMOS in saturation mode


$$V_{OL} = \mu_p/\mu_n W_p/W_n V_{DSATp}$$

Assuming V_{OL} is small relative to gate drive, $(V_{DD} - V_T)$, and $V_{Tp} = V_{Tn}$

SMALLER AREA & LOAD BUT STATIC POWER DISSIPATION!!!


Pseudo-NMOS VTC

 Sizing of the load device can be used to trade off parameters such as NM, delay, and power.....



A larger pull-up device improves performance but increases static power and degrades NM by increasing V_{OL}


Pass-Transistor Logic

 

- **N transistors**
- **No static consumption**

Allows primary inputs to drive gate terminals as well as source-drain terminals

Example: AND Gate

 

Ensures that gate is static: provides low impedance path when $B=0$

If $B=1$ then $T1$ is ON and $T2$ is OFF

Then $A=F$, i.e., if $A=1$, $F=1$ and if $A=0$, $F=0$

When $B=0$, $T2$ is ON and passes a Zero


Need fewer transistors: 4 to implement the AND: *lower cap.*

Need 6 to implement in static CMOS (4 for NAND and 2 for INV)

Note: F will charge only up to $V_{DD} - V_{tn}$


Also, V_{Tn} will be a function of V_F (increase due to RBB)

VTC of Pass-Transistor AND Gate

 

When $B = V_{DD}$, T1 is ON until the input reaches $V_{DD} - V_{Tn}$

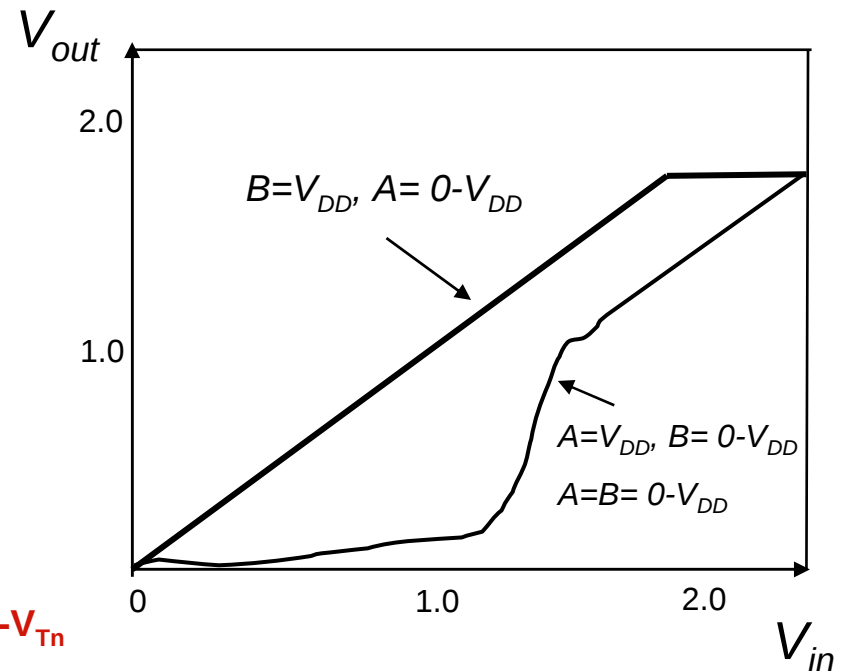
When $A = V_{DD}$, and B makes a transition from 0 to 1, T2 is turned on until $V_{DD}/2$ and Output = 0. Once T2 is turned off, output follows the input B minus a threshold drop.




VTC of Pass Transistor Logic is data dependent

NMOS-Only Logic

Voltage Drop Issue:

 


$$V_x = V_{dd} - V_{Tn}(V_x)$$

 

Hence, pass transistor gates cannot be cascaded by connecting the output of a pass gate to the gate input of another pass transistor. They can only be cascaded in series....

NMOS-only Switch

 

*Difficult
to switch
off the
PMOS!*

V_B does not pull up to 2.5V, but $2.5V - V_{Tn}$


*Lower
switching
energy!*

Voltage loss causes static power consumption

NMOS has higher threshold than PMOS (body effect)

Solutions to the Voltage Drop Problem:

Solution 1: Level Restoring Transistor

 

Pass Transistor Logic
suffers from static power
dissipation and reduced
NMs

*At $B=V_{DD}$, if $A: 0$ to V_{DD}
 $V_x = V_{DD} - V_{Tn}$, $Out=0$,
 $M_r=ON$ and $V_x=V_{DD}$*


*Eliminates static power in
the Inverter*

*No static power between
 M_r and M_n*

- **Advantage: Full Swing**
- Restorer adds capacitance, takes away pull down current at X (for high to low transition at X, M_n must be stronger than M_r), can slow down gate
- Ratio problem

Restorer Sizing

 Need to size M_n and M_r to bring $V_x < V_M (=V_{DD}/2)$ (V_M is a function of $R1$ and $R2$) $R1$ and $R2$ are the equivalent on-resistances of $M1$ and $M2$




- **Upper limit on restorer size** when too large (R_r too small), V_x can't be brought below V_M
- Pass-transistor pull-down can have several transistors in stack

Transient Response: V_x vs. time

Solution 2: Single Transistor Pass Gate with $V_T=0$


 
Only Pass Transistor Devices have $V_T=0$



But even if $V_T=0$, there is still body effect...which prevents full swing!


WATCH OUT FOR LEAKAGE CURRENTS in the IDLE State!!!

Solution 3: Transmission Gate

  

Acts like a
bidirectional switch
controlled by the
gate signal C

 When $C=1$, both
MOSFETS are ON
allowing the signal to
pass through the
gate ($A=B$, if $C=1$)




**Because of the
PMOS, C_L charges
to V_{dd}**

**Because of NMOS
 C_L discharges to 0**

Transmission Gate XOR

$B=1$: M1 and M2 act as an INV, Transmission gate is off and $F=\bar{A}B$

 $B=0$: M1 and M2 are off and Xgate is on, $F=AB$





Implementation requires only 6 transistors!

While a complementary CMOS implementation requires ??? transistors

Fast adder circuits and registers can also be implemented with Xgates

Resistance of Transmission Gate

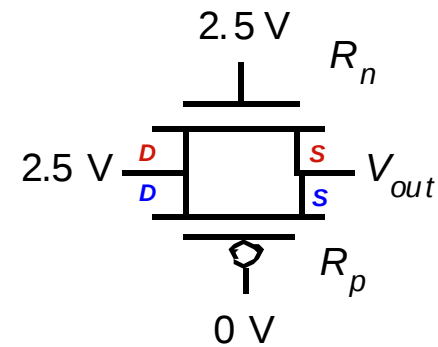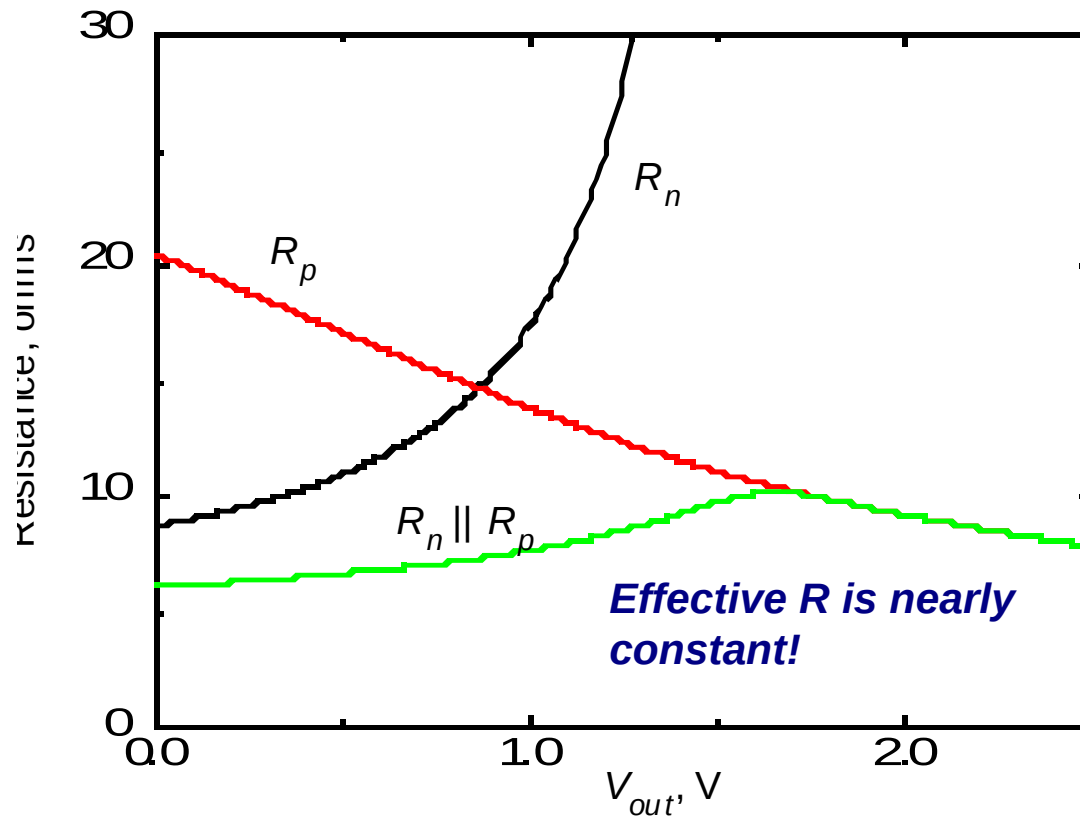


$$R_n = (V_{DD} - V_{out}) / I_{dn}$$


$$R_p = (V_{out} - V_{DD}) / I_{dp}$$

Delay in Transmission Gate Networks

 
Delay of a chain of n Xgates (used in adders and deep MUXes) can be modeled using Elmore delay



(a) A chain of n Xgates

 

(b) Equivalent RC representation

 

(c) Buffer insertion in a chain of Xgates to lower delay