

$$\beta = 100$$

$$V_{CC} = 3 \text{ Volts}$$

$$I_C = 1 \text{ mA}$$

$$V_C = 1.5 \text{ Volts}$$

$$\text{For } I_C = 1 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{1 \text{ mA}}{100}$$


$$\underline{I_B = 10 \mu\text{A} \text{ required}}$$

Now, on applying KVL to the output of the circuit we get

$$V_{CC} - I_C R_C - V_C = 0$$

$$\Rightarrow R_C = \frac{V_{CC} - V_C}{I_C} = \frac{(3 - 1.5) \text{ V}}{1 \text{ mA}}$$
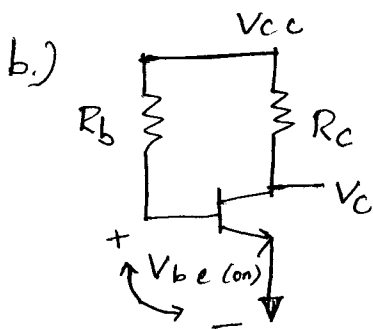
$$\Rightarrow \underline{R_C = 1.5 \text{ k}\Omega}$$



$$\beta = 100$$

$$V_{CC} = 3 \text{ Volts}$$

$$I_C = 200 \mu\text{A}$$

$$V_{CE} = 1.5 \text{ Volts}$$

$$V_{BE(\text{on})} = 0.7 \text{ Volts}$$

$$\text{For } I_C = 200 \mu\text{A}$$

$$I_B = \frac{I_C}{\beta} = \frac{200 \mu\text{A}}{100}$$

$$\underline{I_B = 2 \mu\text{A} \text{ required.}}$$


Now, applying KVL to the output of the circuit we get

$$V_{CC} - I_C R_C - V_C = 0 \Rightarrow R_C = \frac{V_{CC} - V_C}{I_C} = \frac{3 - 1.5 \text{ V}}{200 \mu\text{A}} = 7.5 \text{ k}\Omega$$

Applying KVL to the input of the circuit we get

$$V_{CC} - I_B R_B - V_{BE(\text{on})} = 0 \Rightarrow R_B = \frac{V_{CC} - V_{BE(\text{on})}}{I_B} = \frac{3 - 0.7}{2 \mu\text{A}} = 1.15 \text{ M}\Omega$$

c.) Bias stability of previous circuit:

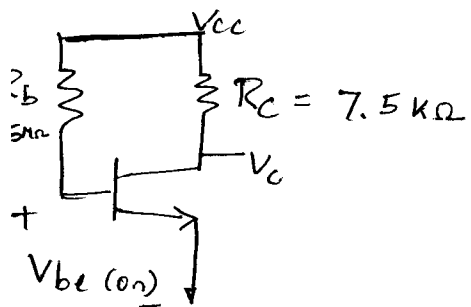

Here β is increased to 200
Now, applying KVL to input side
we get

$$V_{cc} - I_b R_b - V_{be(on)} = 0$$

$$\Rightarrow I_b = \frac{V_{cc} - V_{be(on)}}{R_b} = \frac{(3 - 0.7)V}{1.15 M\Omega}$$

$$\Rightarrow I_b = 2 \mu A \text{ (Same as before)}$$

$$\text{Now, } I_c = \beta I_b = 200 (2 \mu A) = 400 \mu A$$

Using this value of I_c , apply KVL to output loop
We get,

$$V_{cc} - I_c R_c = V_c \Rightarrow V_c = 3 - (400 \mu A)(7.5 k\Omega) \\ = 3 - 3 = 0 \text{ Volts}$$

$V_c = 0 \text{ Volts}$ is not practically possible as the minimum V_{CE} is $V_{CE(sat)} = 0.5 \text{ Volts}$.

In practical situation, as the β increases, the collector current increases (as long as the collector-base junction is reverse biased.)


In our case, $V_b = V_{be(on)} = 0.7 \text{ Volts}$.

Hence, when the collector voltage drops below

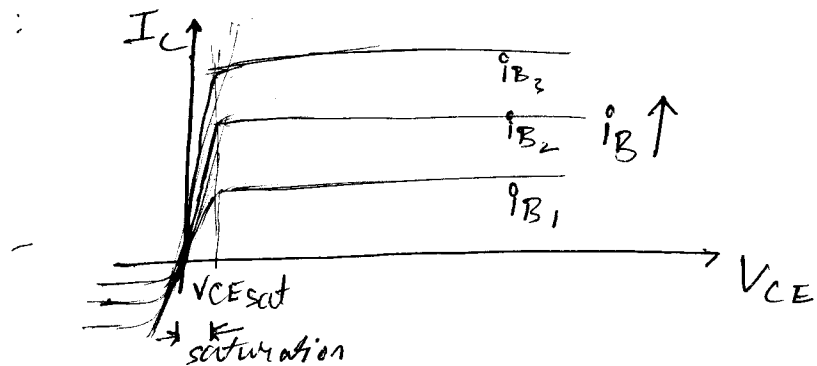0.7 Volts , $V_{cb} = V_c - V_b$ becomes negative and the

collector base junction becomes forward biased $\Rightarrow$ and the transistor enters saturation wherein both the P-N junctions are now forward biased.

Under saturation, the minimum V_{CE} is $V_{CE(sat)}$ as this graph shows:




Thus, in saturation,

$$I_C = \frac{V_{CC} - V_{CE(sat)}}{R_C}$$

$$= \frac{(3 - 0.5)V}{7.5k} = 333 \mu A$$

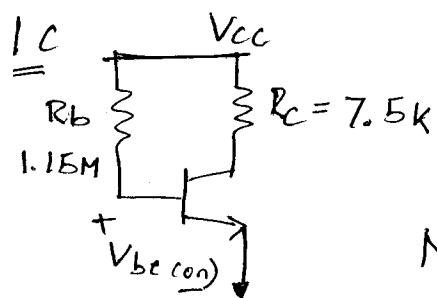And $V_C = V_{CE(sat)} = 0.5 \text{ Volts}$



$$\beta = 100 \quad \text{and} \quad V_{cc} = 3 + \left(\frac{\beta \times 10}{100} \right)$$

$$\underline{V_{cc} = 3.3 \text{ Volts}}$$

Now, apply KVL to the input loop

$$V_{cc} - I_b R_b - V_{be(con)} = 0$$

$$\Rightarrow I_b = \frac{V_{cc} - V_{be(con)}}{R_b} = \frac{(3.3 - 0.7) \text{ Volts}}{1.15 \text{ M}\Omega}$$

$$\Rightarrow I_b = \left(\frac{2.6 \text{ V}}{1.15 \text{ M}\Omega} \right) = \underline{2.26 \mu\text{A}}$$

$$\text{Now, } I_c = \beta I_b = 100 (2.26 \mu\text{A}) = \underline{226 \mu\text{A}}$$


Now, apply KVL to output loop :

$$\begin{aligned} V_{cc} - I_c R_c - V_c &= 0 \Rightarrow V_c = V_{cc} - I_c R_c \\ &= 3.3 \text{ V} - (226 \mu\text{A})(7.5 \text{ k}\Omega) \\ &= 3.3 \text{ V} - 1.695 \text{ V} \\ &= \underline{1.605 \text{ Volts}} \end{aligned}$$

As a check :

$$\begin{aligned} V_c > V_b (= 0.7 \text{ Volts}) &\Rightarrow \text{CB Junction is reverse biased} \\ &\Rightarrow \text{Transistor is still in active region} \end{aligned}$$

1d.

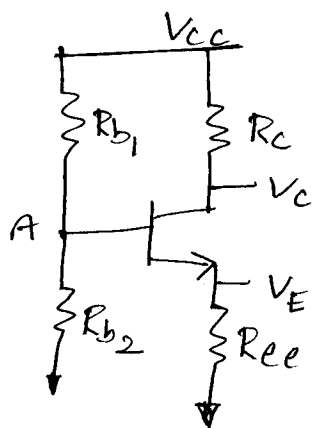

$$\beta = 100$$

$$V_{CC} = 3.3 \text{ Volts}$$

$$V_C = 2 \text{ Volts}$$

$$V_E = 1 \text{ Volts}$$

$$I_{R_{b2}} = 200 \mu\text{A}$$

$$I_C = 2 \text{ mA}$$

$$\beta = 100$$

$$\Rightarrow \alpha = \frac{\beta}{\beta + 1} = \frac{100}{101} = 0.99$$

$$\text{Now, } I_E = \frac{I_C}{\alpha} = \frac{2 \text{ mA}}{0.99}$$

$$\Rightarrow I_E = 2.02 \text{ mA}$$

$$V_E = I_E R_E \quad I_B = \frac{I_C}{\beta}$$

$$\Rightarrow I_B = 0.02 \text{ mA}$$

$$I_B = 20 \mu\text{A}$$

Now, apply KCL at node A to get

$$I_{R_{b1}} = I_{R_{b2}} + I_B = 200 \mu\text{A} + 20 \mu\text{A} = \underline{220 \mu\text{A}}$$

Now, apply Now, $V_{be(\text{on})} = V_B - V_E = 0.7 \text{ Volts}$

$$\Rightarrow V_B = 0.7 + V_E = 0.7 + 1 = 1.7 \text{ Volts}$$

Apply KVL to the input loop and we get

$$V_{CC} - I_{R_{b1}} R_{b1} = V_B \Rightarrow R_{b1} = \frac{V_{CC} - V_B}{I_{R_{b1}}}$$

$$\Rightarrow R_{b1} = \left(\frac{3.3 - 1.7}{220 \mu\text{A}} \right) = \underline{7.27 \text{ k}\Omega}$$

Also, $V_B = I_{R_{b2}} R_{b2} \Rightarrow R_{b2} = \left(\frac{1.7 \text{ V}}{200 \mu\text{A}} \right) = \underline{\underline{8.5 \text{ k}\Omega}}$

Also, $V_E = I_E R_{EE} \Rightarrow R_{EE} = \frac{V_E}{I_E} = \left(\frac{1V}{2.02mA} \right) = \underline{495\Omega}$

And, $V_C = V_{CC} - I_C R_C = 3.3 - (2mA) R_C = 2 \text{ Volts}$


$$\Rightarrow R_C = \frac{-2 + 3.3}{2mA} = \underline{650\Omega}$$

Thus, $R_{b1} = 7.27 k\Omega$

$R_{b2} = 8.5 k\Omega$

$R_C = 650\Omega$

$R_E = 495\Omega$

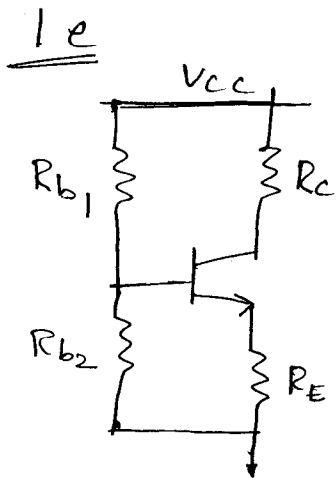


$\beta = 200$

$V_{CC} = 3.3 \text{ Volts}$

To make an approximate analysis, we can neglect I_B to find V_B as

$$V_B = \frac{V_{CC} \cdot R_{b2}}{R_{b2} + R_{b1}} =$$

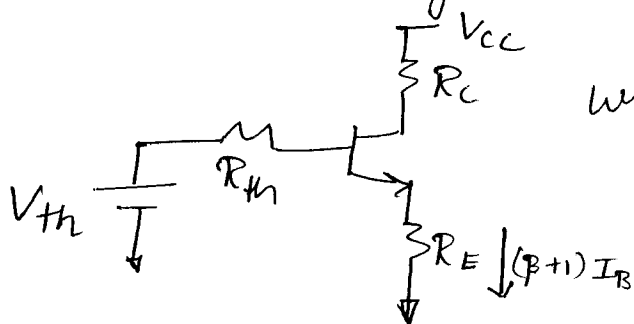The input to the circuit can be represented using a Thevenin Equivalent as:



where

$$V_{th} = \frac{V_{CC} \cdot R_{b2}}{R_{b2} + R_{b1}} = \underline{1.778 \text{ Volts}}$$

$$R_{th} = R_{b1} \parallel R_{b2} = \underline{3.91 k\Omega}$$

Now, we apply KVL to the input loop to get

$$V_{th} - I_B R_{th} - V_{be(on)} - (\beta + 1) I_B \cdot R_E = 0$$

$$\Rightarrow I_B = \frac{V_{th} - V_{be(on)}}{R_{th} + (\beta + 1) R_E} = \frac{1.778 - 0.7}{(3.91k) + (201)(495)}$$
$$= \frac{1.078}{\frac{95.585k}{103.405k}} = \frac{11.2\mu A}{10.4\mu A}$$

$$\text{Now, } I_C = \beta I_B = (200)(10.4\mu A)$$
$$= 2.08mA$$

Apply KVL to the output loop.


$$V_C = V_{CC} - I_C R_C = 3.3V - (2.08mA)(650\Omega)$$
$$= 1.948 \text{ Volts}$$

As a check,

$$V_B = V_{th} - I_B R_{th} = 1.77 - (10.4\mu A)(3.91k\Omega)$$
$$= \underline{1.73 \text{ Volts}}$$

As $V_C > V_B$, CB junction is reverse biased and the transistor is in the active region.

1e

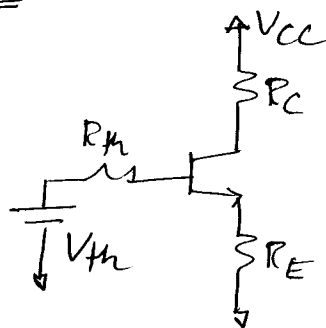

$$\beta = 100$$

$$V_{CC} = 3.3 + \frac{3.3 \times 10}{100} = \underline{3.63 \text{ Volts}}$$

$$V_{th} = \frac{V_{CC} \cdot R_{b2}}{R_{b2} + R_{b1}} = 1.956 \text{ Volts}$$

$$R_{th} = R_{b1} \parallel R_{b2} = 3.91 \text{ k}\Omega$$

Apply KVL to the input loop:

$$V_{th} - I_B R_{th} - V_{be(on)} - I_E R_E = 0 \quad \rightarrow (\beta+1)I_B$$

$$\Rightarrow I_B = \frac{V_{th} - V_{be(on)}}{R_{th} + (\beta+1)R_E} = \frac{1.956 - 0.7}{(3.91 \text{ k}) + (101)(495)}$$

$$I_B = \frac{1.256}{53905} = \underline{\underline{23.3 \mu\text{A}}}$$

$$\text{Now, } I_C = \beta I_B = 100 \cdot (23.3 \mu\text{A}) = \underline{2.33 \text{ mA}}$$

Apply KVL to the output loop and we get

$$V_{CC} - I_C R_C = V_C = 3.63 \text{V} - (2.33 \text{ mA})(650)$$


$$V_C = \underline{2.12 \text{ Volts}}$$

As a check,

$$V_B = V_{th} - I_B R_{th} = 1.956 \text{V} - (23.3 \mu\text{A})(3.91 \text{ k}) = 1.865$$

$\Rightarrow$ The transistor is in the active region.

$< V_C$

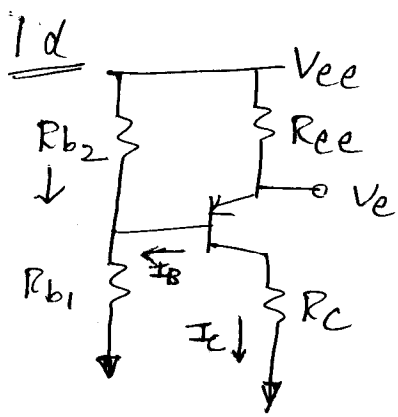

$$\beta = 300$$

$$V_{EE} = 3.3 \text{ Volts}$$

$$V_C = 1 \text{ Volts}$$

$$V_E = 2 \text{ Volts}$$

$$I_C = 2 \text{ mA}$$

$$I_{R_{b2}} = 200 \mu\text{A}$$

$$I_C = 2 \text{ mA}$$

$$\Rightarrow I_B = \frac{I_C}{\beta} = \frac{2 \text{ mA}}{300} = 6.6 \mu\text{A}$$

$$I_E = I_B + I_C = 2.006 \text{ mA}$$

$$I_{R_{b2}} + I_B = I_{R_{b1}} \quad (\text{KCL at Base})$$

$$\Rightarrow I_{R_{b1}} = \underline{206.6 \mu\text{A}}$$

$$\text{Now, } V_C = I_C R_C \Rightarrow \underline{R_C} = \frac{V_C}{I_C} = \frac{1}{2 \text{ mA}} = \underline{500 \Omega}$$

$$V_E = V_{EE} - I_E R_{EE} = 3.3 - (2.006 \text{ mA})(R_{EE}) = 2$$

$$\Rightarrow R_{EE} = \frac{3.3 - 2}{(2.006 \text{ mA})} = \underline{648 \Omega}$$

$$V_{BE(\text{on})} = V_B - V_E = -0.7 \quad (\text{PNP transistor})$$

$$\Rightarrow V_B = V_E - 0.7 = 2 - 0.7 = 1.3 \text{ Volts}$$


Now, apply KVL on input loop to get

$$V_{EE} - I_{R_{b2}} R_{b2} = V_B \Rightarrow R_{b2} = \frac{V_{EE} - V_B}{I_{R_{b2}}}$$

$$\Rightarrow R_{b2} = \frac{3.3 - 1.3}{200 \mu\text{A}} = \underline{10 \text{ k}\Omega}$$

$$\text{Also, } I_{R_{b1}} R_{b1} = V_B \Rightarrow R_{b1} = \frac{V_B}{I_{R_{b1}}} = \frac{1.3 \text{ V}}{206.6 \mu\text{A}}$$
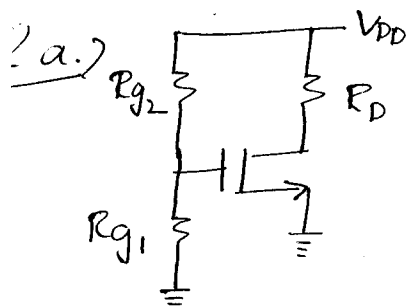
$$\Rightarrow R_{b1} = \underline{6.29 \text{ k}\Omega}$$



$$V_{th} = 0.3 \text{ Volt}$$

$$V_{sat} C_{ox} W_g = 1 \text{ mA/V}$$

$$R_{g1} = 200 \text{ k}\Omega$$

$$V_{DD} = 2.0 \text{ Volts}$$

$$I_D = 1 \text{ mA}$$

$$V_{DS} = 1.5 \text{ Volts}$$

Apply KVL at the output loop: $V_{DD} - I_D R_D = V_D$

Now, $V_{DS} = V_D - V_S = 1.5 \text{ Volts} \Rightarrow V_D = 1.5 \text{ Volts}$ ($\because V_S = 0$)

$$\Rightarrow R_D = \frac{V_{DD} - V_D}{I_D} = \frac{2 - 1.5}{1 \text{ mA}} = \underline{\underline{500 \Omega}}$$

Also, $V_{sat} \cdot C_{ox} \cdot W_g \cdot (V_{gs} - V_{th}) = I_D$


$$\Rightarrow V_g = \frac{I_D}{V_{sat} C_{ox} \cdot W_g} + V_{th} \quad (\because V_S = 0)$$

$$= \frac{1 \text{ mA}}{1 \text{ mA/V}} + 0.3 \text{ V} = 1.3 \text{ Volts}$$

Now, $V_g = \frac{V_{DD} \cdot R_{g1}}{R_{g1} + R_{g2}} = 1.3 \text{ V}$

$$\Rightarrow R_{g2} = \frac{V_{DD} \cdot R_{g1}}{1.3} - R_{g1} = \underline{\underline{107.7 \text{ k}\Omega}}$$

2b.)

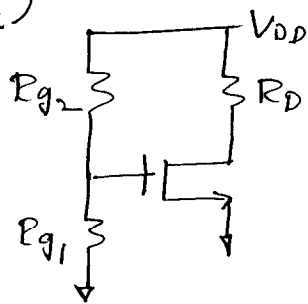

$$V_{DD} = 2 \text{ Volts}$$

$$V_{th} = 0.3 \text{ Volts}$$

$$R_D = 500 \Omega$$

$$R_{g1} = 200 \text{ k}\Omega$$

$$R_{g2} = 107.7 \text{ k}\Omega$$

$$V_{sat} C_{ox} W_g = 1 \text{ mA/V} + 0.1 \text{ mA/V} = 1.1 \text{ mA/V}$$

$$V_g = \frac{V_{DD} \cdot R_{g1}}{R_{g1} + R_{g2}} = \frac{2 (200 \text{ k})}{200 \text{ k} + 107.7 \text{ k}} = 1.3 \text{ Volts}$$

$$I_D = V_{sat} C_{ox} W_g (V_{gs} - V_{th}) = (1.1 \frac{\text{mA}}{\text{V}}) (1.3 - 0.3)$$

$$I_D = 1.1 \text{ mA}$$

$$V_D = V_{DD} - I_D R_D = 2 - (1.1 \text{ mA})(500 \Omega) = 1.45 \text{ V}$$

$$V_{DS} = 1.45 \text{ V} > V_{gs} - V_{th} = 1.3 - 0.3 = 1 \text{ Volt}$$

$\Rightarrow$ The device is in saturation (Normal mode of operation for MOSFET).

2b.) $V_{DD} = 2 \text{ V} + 0.2 \text{ V} = 2.2 \text{ Volts}$

$$V_{th} = 0.3 \text{ V}$$

$$V_{sat} C_{ox} W_g = 1 \text{ mA/V}$$


$$\text{Now, } V_g = \frac{V_{DD} \cdot R_{g1}}{R_{g1} + R_{g2}} = \frac{(2.2 \text{ V})(200 \text{ k})}{200 \text{ k} + 107.7 \text{ k}} = 1.429$$

$$I_D = V_{sat} C_{ox} W_g (V_{gs} - V_{th}) = (1 \text{ mA/V})(1.129) = 1.129 \text{ mA}$$

$$V_D = V_{DD} - I_D \cdot R_D = 2 \text{ V} - (1.129 \text{ mA})(500 \Omega) = 1.436 \text{ Volts}$$

$$V_{DS} = 1.436 > (V_{gs} - V_{th}) = (1.3 - 0.3) \text{ V}$$

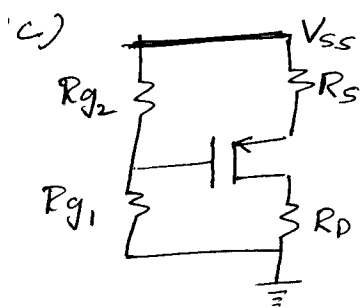$\Rightarrow$ The device operates in saturation.



$$V_{th} = -0.3 \text{ Volts}$$

$$V_{ss} = 3.3 \text{ Volts}$$

$$V_{sat} C_{ox} W_g = 2 \text{ mA/V}$$

$$I_{R_{g1}} = 1 \mu\text{A}$$

$$I_D = 1 \text{ mA}$$

$$V_s = 2.25 \text{ Volts}$$

$$V_D = 0.5 \text{ Volts}$$

Now,

$$V_D = I_D R_D = (1 \text{ mA})(R_D) \Rightarrow R_D = \frac{V_D}{I_D} = \frac{0.5 \text{ V}}{1 \text{ mA}} = \underline{500 \Omega}$$

Also,

$$V_{ss} - I_D R_s = V_s \quad (\because I_D = I_s)$$

$$\Rightarrow R_s = \frac{V_{ss} - V_s}{I_D} = \frac{3.3 - 2.25}{1 \text{ mA}} = \underline{1.05 \text{ k}\Omega}$$

Now,

$$V_{sat} C_{ox} W_g (-V_{gs} + V_{th}) = I_D$$

$$\Rightarrow -V_{gs} = \frac{I_D}{V_{sat} C_{ox} W_g} - V_{th} = 0.8 \text{ Volts} = -V_g + V_s$$


$$\Rightarrow V_g = V_s - 0.8 \text{ V} = 1.45 \text{ Volts}$$

$$\text{Now, } V_g = I_{R_{g1}} \cdot R_{g1} \Rightarrow R_{g1} = \frac{V_g}{I_{R_{g1}}} = \frac{1.45}{1 \mu\text{A}} = \underline{1.45 \text{ M}\Omega}$$

$$\text{Also, } \frac{V_{ss}}{R_{g1} + R_{g2}} = I_{R_{g1}} \Rightarrow R_{g2} = \frac{V_{ss}}{I_{R_{g1}}} - R_{g1}$$

$$= \frac{3.3 \text{ V}}{1 \mu\text{A}} - 1.45 \text{ M}\Omega$$
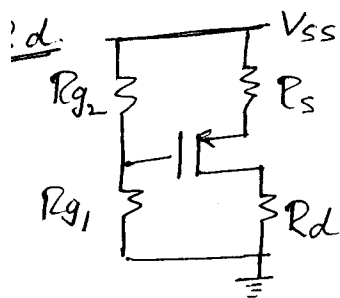
$$R_{g2} = \underline{1.85 \text{ M}\Omega}$$



$$\begin{aligned}
 R_D &= 500\Omega \\
 R_S &= 1.05\text{ k}\Omega \\
 R_{g1} &= 1.45\text{ M}\Omega \\
 R_{g2} &= 1.85\text{ M}\Omega
 \end{aligned}$$

$$\begin{aligned}
 V_{SS} &= 3.3\text{ V} \\
 V_{th} &= -0.3\text{ V}
 \end{aligned}$$

$$V_{sat} C_{ox} W_g = 2\text{ mA/V} + 0.2\text{ mA/V} = 2.2\text{ mA/V}$$

$$\text{Now, } V_g = \frac{V_{SS} \cdot R_{g1}}{R_{g1} + R_{g2}} = \frac{3.3\text{ V} (1.45\text{ M})}{(3.3\text{ M})} = \underline{1.45\text{ V}}$$

$$I_D = V_{sat} C_{ox} W_g (-V_{gs} + V_{th}) = (2.2\frac{\text{mA}}{\text{V}})(-V_{gs} - 0.3)$$

$$\begin{aligned}
 \therefore I_D &= (2.2\frac{\text{mA}}{\text{V}})[-V_g + V_{SS} - I_D R_S - 0.3] \\
 &= (2.2\frac{\text{mA}}{\text{V}})[-1.45 + V_{SS} - I_D R_S - 0.3] \\
 &= (2.2\frac{\text{mA}}{\text{V}})[1.55 - I_D R_S]
 \end{aligned}$$

$$\Rightarrow I_D = 3.41\text{ mA} - 2.31 I_D \Rightarrow I_D = \frac{3.41\text{ mA}}{3.31} = 1.03\text{ mA}$$

$$V_D = I_D R_D = (1.03\text{ mA})(500) = 0.515\text{ Volts}$$

$$V_S = V_{SS} - I_D R_S = 3.3 - (1.03\text{ mA})(1.05\text{ k}\Omega)$$

$$V_S = 2.22\text{ Volts}$$

$$V_{SD} = 1.705\text{ Volts}$$

$$-V_{gs} + V_{th}$$

$$V_{dg} = -0.935 < 0.3 (-V_{th})$$

$\Rightarrow$ The MOSFET is in constant current regime.

2d (contd.)

$$R_D = 500\Omega$$

$$R_S = 1.05\text{ k}\Omega$$

$$R_{g1} = 1.45\text{ M}\Omega$$

$$R_{g2} = 1.85\text{ M}\Omega$$

$$V_{SS} = 3.3 + 0.33 = 3.63\text{ Volts}$$

$$V_{th} = -0.3\text{ Volts}$$

$$V_{sat} \text{ Cox } W_g = 2\text{ mA/V}$$

$$V_g = \frac{V_{SS} \cdot R_{g1}}{R_{g1} + R_{g2}} = \frac{3.63 \times 1.45\text{ M}}{(1.45\text{ M} + 1.85\text{ M})} = 1.58\text{ Volts}$$

$$I_D = V_{sat} \text{ Cox } W_g (-V_{gs} + V_{th}) = \left(\frac{2\text{ mA}}{\text{V}}\right)(-V_{gs} - 0.3)$$

$$I_D = \left(\frac{2\text{ mA}}{\text{V}}\right)(-V_g + V_S - 0.3)$$

$$= \left(\frac{2\text{ mA}}{\text{V}}\right)(-1.58 + V_{SS} - I_D R_S - 0.3)$$

$$= \left(\frac{2\text{ mA}}{\text{V}}\right)(-1.58 + 3.63 - I_D(1.05\text{ k}) - 0.3)$$

$$= \left(\frac{2\text{ mA}}{\text{V}}\right)(1.75 - I_D(1.05\text{ k}))$$

$$I_D = 3.5\text{ mA} - 2.1 I_D \Rightarrow I_D = \frac{3.5\text{ mA}}{3.1} = 1.129\text{ mA}$$

Now, $V_D = I_D R_D = (1.129\text{ mA})(500\Omega) = 0.564\text{ Volts}.$

$$V_S = V_{SS} - I_D R_S = 3.63 - (1.129\text{ mA})(1.05\text{ k}\Omega) = 2.445\text{ Volts}.$$

Now, $V_{Dm} = -1.016 < -V_{th} (= 0.3)$

$\Rightarrow$ The device is in constant current regime.