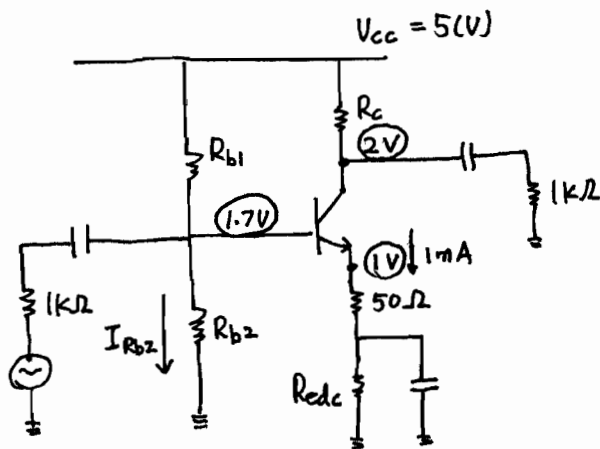


Solutions

P1.

$$V_a = 50, \beta = 100$$



a) Resistor Value.

$$R_c = \frac{V_{cc} - V_c}{I_c} = \frac{5 - 2}{1 \text{ mA}} = \boxed{3 \text{ k}\Omega}$$

since $I_c \approx I_E$


$$V_c = I_c (50 + R_{dc}) \Rightarrow 1 \text{ V} = 1 \text{ mA} (50 + R_{dc})$$

$$\Rightarrow \boxed{R_{dc} = 950 \Omega}$$


$$I_B = \frac{1}{\beta} I_c = \frac{1 \text{ mA}}{100} = 10 \mu\text{A}, \quad I_{Rb2} = 20 I_B = 200 \mu\text{A}, \quad V_B = 1.7.$$

$$R_{b2} = \frac{1.7}{0.2 \text{ mA}} = \boxed{8.5 \text{ k}\Omega}, \quad R_{b1} = \frac{V_{cc} - V_B}{I_{Rb2} + I_B} = \frac{5 - 1.7}{21 I_B} = \boxed{15.7 \text{ k}\Omega}$$

b) small signal

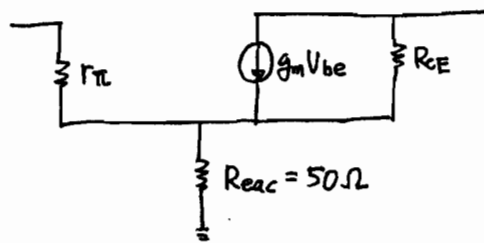

⇒
Emitter
Degeneration

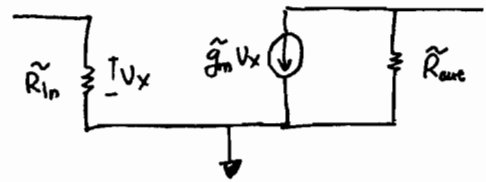

$$r_e = \frac{V_T}{I_E} = \frac{26 \text{ mV}}{1 \text{ mA}} = 26 \Omega$$

$$R_{CE} = \frac{V_A + V_{CE}}{I_C} = \frac{51}{1 \text{ mA}} = 51 \text{ k}\Omega$$


with

$$\begin{aligned} \tilde{R}_{in} &= (1 + \beta)(r_e + R_{EAC}) \\ \tilde{R}_{out} &= R_{CE} \left[1 + \frac{R_{EAC}}{r_e} \right] \\ \tilde{r}_e &= \frac{1}{\tilde{g}_m} = r_e + R_{EAC} \end{aligned}$$

$$\therefore \tilde{R}_{in} = 101 \cdot (26 + 50) = 7.68 \text{ k}\Omega$$

$$\tilde{R}_{out} = 51 \text{ k} \left(1 + \frac{50}{26} \right) = 149 \text{ k}\Omega$$
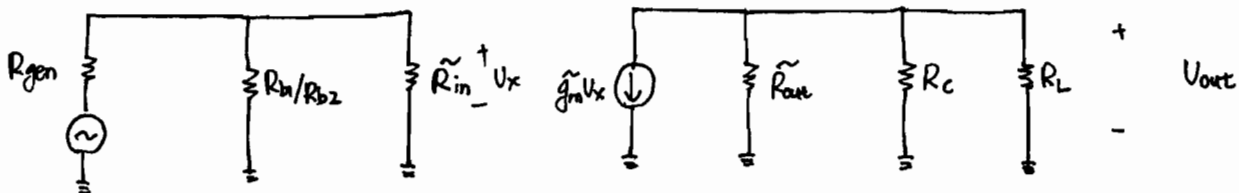
$$\tilde{r}_e = 76 \Omega, \quad \tilde{g}_m = 0.013$$



$$\frac{V_{out}}{V_{in}} = -\tilde{g}_m (\tilde{R}_{out} \parallel R_C \parallel R_L) = -0.013 \cdot 746 = \boxed{-9.7}$$

$$\frac{V_{in}}{V_{gen}} = \frac{(R_{B1} \parallel R_{B2} \parallel \tilde{R}_{in})}{R_{gen} + (R_{B1} \parallel R_{B2} \parallel \tilde{R}_{in})} = \frac{3.2 \text{ k}}{1 \text{ k} + 3.2 \text{ k}} = \boxed{0.76}$$

$$\frac{V_{out}}{V_{gen}} = \frac{V_{in}}{V_{gen}} \cdot \frac{V_{out}}{V_{in}} = \boxed{-7.4}$$

(3)

$$c) \quad R_{in} = R_{b1} // R_{b2} // \tilde{R}_{in} = \boxed{3.2 \text{ k}\Omega}$$

$$R_{out} = \tilde{R}_{out} // R_c = \boxed{2.95 \text{ k}\Omega}$$

d) saturation.


$$V_{CE} = 1 \text{ (V)}$$

$$\therefore \Delta V_{out} \downarrow = (1 - V_{CE(sat)}) = 1 - 0.5 = \boxed{0.5 \text{ (V)}}$$

cutoff

$$\Delta V_{out} \uparrow = I_c (R_c // R_L) = 1 \text{ mA } (0.75 \text{ k}\Omega) = \boxed{0.75 \text{ (V)}}$$

P2.

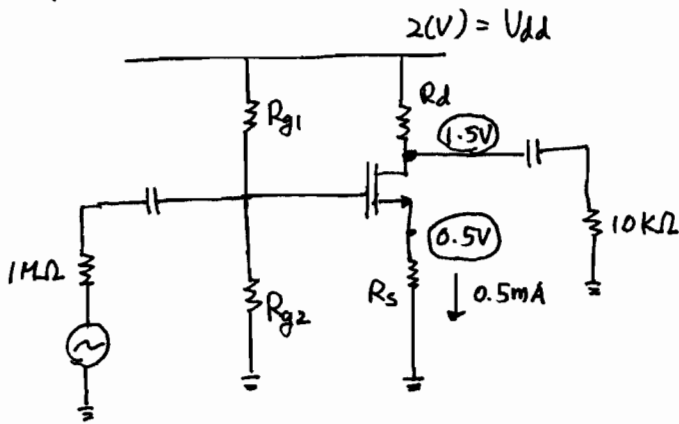

$$U_{th} = 0.3(V)$$

$$U_{sat} C_{ox} W_g = 1 \text{ mA/V}$$

$$\lambda = \frac{1}{50}$$

a) Resistor Value.

$$R_d = \frac{U_{DD} - U_D}{I_D} = \frac{0.5}{0.5 \text{ mA}} = \boxed{1 \text{ k}\Omega}$$

$$R_s = \frac{U_s}{I_D} = \frac{0.5}{0.5 \text{ mA}} = \boxed{1 \text{ k}\Omega}$$

$$I_D = U_{sat} W_g C_{ox} (U_g - U_s - U_{th}) (1 + \lambda U_{DS})$$

$$0.5 \text{ mA} = 1 \text{ mA/V} (U_g - 0.5 - 0.3) (1 + \frac{1}{50}) \Rightarrow U_g = 1.29(V)$$

$$R_{in} = R_{g1} \parallel R_{g2} = \frac{R_{g1} R_{g2}}{R_{g1} + R_{g2}} = 1 \text{ M}\Omega \quad - \text{①}$$

$$U_g = U_{DD} \frac{R_{g2}}{R_{g1} + R_{g2}} \Rightarrow \frac{R_{g2}}{R_{g1} + R_{g2}} = 0.645 \quad - \text{②}$$

$$R_{g1} = \frac{\text{①}}{\text{②}} = \boxed{1.55 \text{ M}\Omega} \quad - \text{③}$$

plugging ③ into ②, then

$$\boxed{R_{g2} = 2.81 \text{ M}\Omega}$$

(5)

b. small signal

$$\frac{V_{out}}{V_{in}} = \frac{-R_{Leq}}{R_s + 1/g_m}$$

$$\text{where } R_{Leq} = R_{in, drain} // R_d // R_L$$

$$\text{and } R_{in, drain} = r_{ds} (1 + g_m R_{ss})$$

$$r_{ds} = \left(\frac{1}{\lambda} + V_{DS} \right) / I_D$$

$$= \frac{-0.9K}{1K + 1K}$$

$$= \boxed{-0.45}$$

$$\Rightarrow r_{ds} = (50 + 1) / 0.5mA = 102K\Omega$$

$$R_{in, drain} = 102K (1 + (1m)(1K)) = 204K\Omega$$

$$R_{Leq} = 204K\Omega // 1K\Omega // 10K\Omega = 0.9K\Omega$$

$$\frac{V_{in}}{V_{gen}} = \frac{R_{g1} // R_{g2}}{R_{gen} + R_{g1} // R_{g2}} = \boxed{\frac{1}{2}}$$

= 1M Ω (from the problem condition)

$$\boxed{\frac{V_{out}}{V_{gen}} = -0.23}$$


c. input / output impedance.

$$R_{in} = R_{g1} // R_{g2} = \boxed{1M\Omega}$$

$$R_{out} = R_d // R_{in, drain} = \boxed{995\Omega}$$

(6)

3.

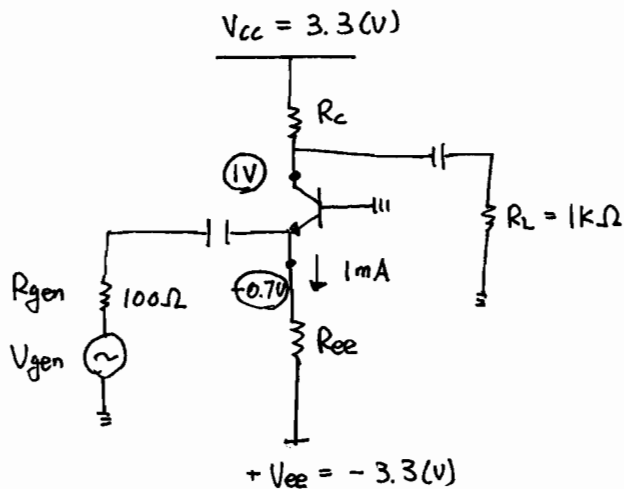

$$\beta = 50, V_A = 100$$

a) Resistor.

$$R_{ee} = \frac{-0.7 - (-3.3)}{1 \text{ mA}} = \boxed{2.6 \text{ k}\Omega}$$

$$I_c = \frac{\beta}{\beta + 1} I_E = 0.98 \text{ mA}$$

$$R_c = \frac{3.3 - 1}{0.98 \text{ mA}} = \boxed{2.35 \text{ k}\Omega}$$

b) small signal

*. Note that $R_{leq} \ll R_{ce}$
so $R_{in, emitter} \approx r_e + R_b/\beta$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{R_{leq}}{R_{in, emitter}} = \frac{R_c \parallel R_L}{r_e + \frac{R_b}{\beta + 1}} \quad \text{where } r_e = \frac{26 \text{ mV}}{I_E} = 26 \Omega$$

$$= \frac{2.35 \text{ k} \parallel 1 \text{ k}}{26} = \boxed{27.0}$$

$$\frac{V_{in}}{V_{gen}} = \frac{R_{ee} \parallel R_{in, emitter}}{R_{gen} + R_{ee} \parallel R_{in, emitter}} = \frac{25.7}{100 + 25.7} = \boxed{0.2}$$

$$\frac{V_{out}}{V_{gen}} = \boxed{5.4}$$

6

c) input, output impedance.

$$R_{in} = R_{ee} \parallel R_{in, emitter} = \boxed{25.7 \Omega}$$


$$R_{out} = R_c \parallel R_{in, collector}$$

$$\text{where } R_{in, collector} = r_{ce} \left(1 + \frac{R_{gen} \parallel R_{ee}}{r_e} \right)$$

$$\left. \begin{aligned} r_{ce} &= \frac{V_a + V_{ce}}{I_c} = 104 \text{ k}\Omega \\ r_e &= 26(\Omega) \end{aligned} \right\} \Rightarrow R_{in, collector} = 10 \text{ M}\Omega$$

$$\therefore R_{out} = 10 \text{ M} \parallel 2.35 \text{ k} = \boxed{2.35 \text{ k}\Omega}$$

4.

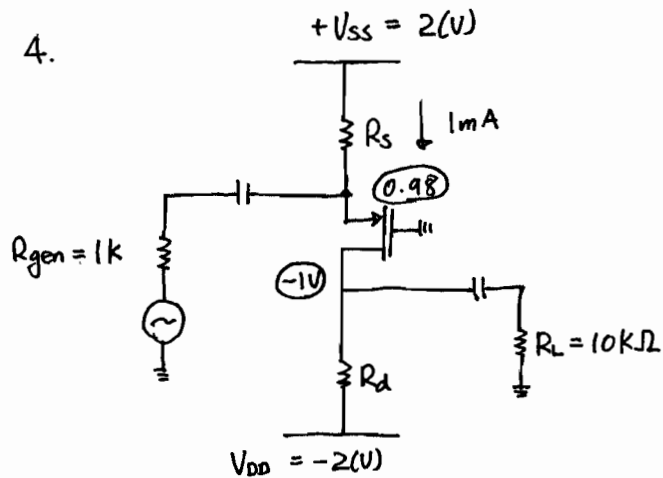

$$V_{th} = -0.5(V), \quad \lambda = \frac{1}{50}, \quad V_{sat} C_{ox} W_g = 2 \text{ mA/V}$$

a) Resistor.

$$R_d = \frac{-1 - (-2)}{1 \text{ mA}} = \boxed{1 \text{ k}\Omega}$$

$$I_D = V_{sat} W_g C_{ox} \left(-(V_{gs} - V_{th}) \right) \left(1 + \lambda V_{SD} \right)$$

$$\Rightarrow 1 \text{ mA} = 2 \text{ mA/V} \left(- \left(\underset{0}{V_g} - V_s + 0.5 \right) \left(1 + \frac{1}{50} (V_s - V_D) \right) \right)$$

$$0.5 = (V_s - 0.5) \left(1 + \frac{1}{50} (V_s + 1) \right)$$

solving equation : $V_s = \begin{pmatrix} 0.98 \\ -51.5 \end{pmatrix}$
second order

$$R_s = \frac{2 - 0.98}{1 \text{ mA}} = \boxed{1.02 \text{ k}\Omega} \approx \boxed{1 \text{ k}\Omega}$$

(9)

b) small signal.

$$\frac{V_{out}}{V_{in}} = \frac{R_{eq}}{R_{in, source}} = \frac{R_D // R_L}{(1/g_m)} = \boxed{1.82} \quad R_{in, source} = \frac{1}{g_m} = 0.5 k\Omega$$

$$\frac{V_{in}}{V_{gen}} = \frac{R_S // R_{in, source}}{R_S // R_{in, source} + R_{gen}} = \frac{330}{330 + 1000} = \boxed{0.25}$$

$$\boxed{\frac{V_{out}}{V_{gen}} = 0.46}$$

c) input/output impedance.

$$R_{in} = R_S // R_{in, source} = \boxed{330 \Omega}$$

$$R_{out} = R_D // R_{in, drain}$$



$$\text{where } R_{in, drain} = r_{ds} \left(1 + \frac{R_S // R_{gen}}{1/g_m} \right)$$

$$r_{ds} = (1/\lambda + V_{DS}) / I_D = (50 + 1.98) / 1mA = 52 k\Omega$$

$$\therefore R_{in, drain} = 52k \left(1 + g_{mA} (1k\Omega // 1k\Omega) \right) = 104 k\Omega$$

$$\therefore R_{out} = 1k\Omega // 104k\Omega \approx \boxed{1k\Omega}$$

5.

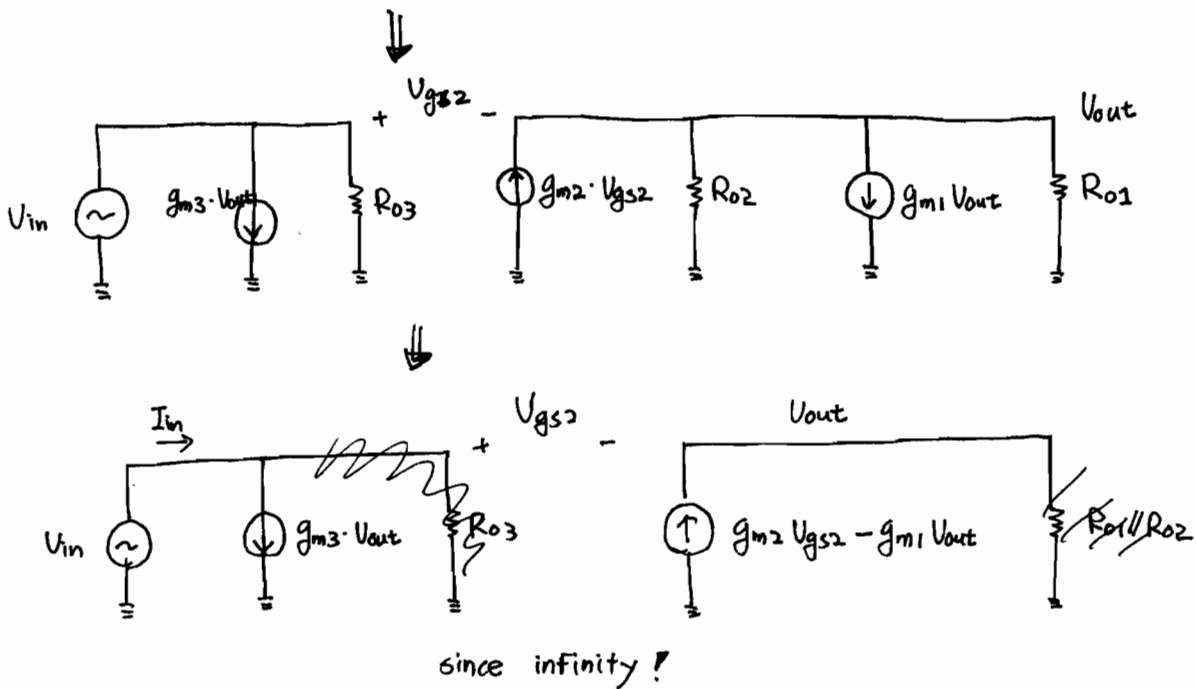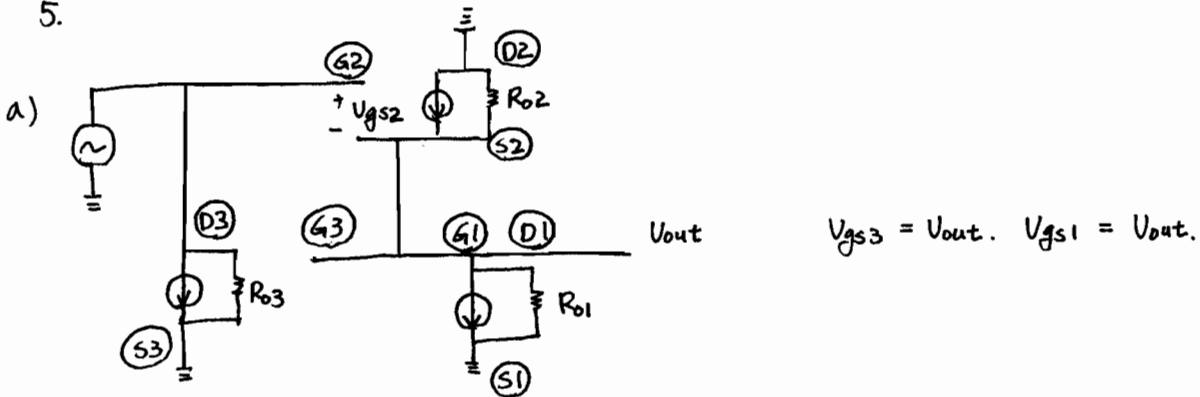

b) ① $g_{m2} V_{gs2} - g_{m1} V_{out} = 0$, $V_{gs2} = V_{in} - V_{out}$

$$g_{m2} (V_{in} - V_{out}) - g_{m1} V_{out} = 0$$

$$g_{m2} V_{in} = (g_{m1} + g_{m2}) V_{out}$$

 $\Rightarrow$

$$\boxed{\frac{V_{out}}{V_{in}} = \frac{g_{m2}}{g_{m1} + g_{m2}}}$$

② $I_{in} = g_{m3} V_{out}$, $V_{out} = \frac{g_{m2}}{g_{m1} + g_{m2}} \cdot V_{in}$

$$I_{in} = \frac{g_{m2} g_{m3}}{g_{m1} + g_{m2}} V_{in}$$

 $\Rightarrow$

$$\boxed{\frac{V_{in}}{I_{in}} = \frac{g_{m1} + g_{m2}}{g_{m2} g_{m3}}}$$

(11)

c) numerical

$$\frac{V_{out}}{V_{in}} = \frac{20m}{10m + 20m} = \boxed{\frac{2}{3}}$$

$$\frac{V_{in}}{I_{in}} = R_{in} = \frac{10m + 20m}{(20m)(30m)} = \boxed{50 \Omega}$$