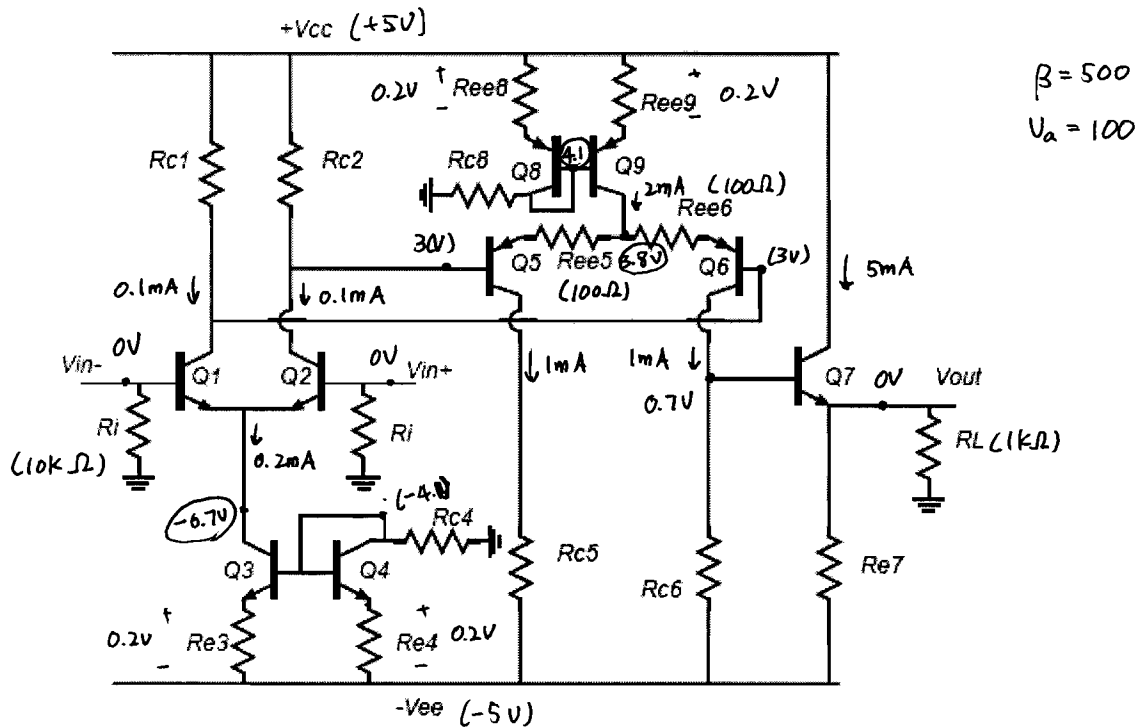


HW #6 solutions

1.



$$\beta = 500$$

$$V_a = 100$$

a) all resistor value

$$R_{e7} = \frac{5}{5\text{mA}} = 1\text{k}\Omega \quad // \quad R_{c6} = \frac{5.7}{I_{c6} - I_{B7}} = 5.7\text{k}\Omega \quad // \quad R_{c5} = R_{c6} = 5.7\text{k}\Omega \quad (\text{symmetric differential amp})$$

$$R_{ee9} = \frac{0.2}{2\text{mA}} = 100\Omega \quad // \quad \text{Let } I_{Rc8} = I_{Rc9} = 2\text{mA} \quad // \quad R_{EE8} = \frac{0.2\text{V}}{I_{Rc8} - I_{B9}} = 100\Omega$$

$$R_{c2} = \frac{5-3}{0.1\text{mA}} = 20\text{k}\Omega \quad // \quad R_{c1} = R_{c2} = 20\text{k}\Omega$$

$$R_{E3} = \frac{0.2}{0.2\text{mA}} = 1\text{k}\Omega \quad // \quad \text{Let } I_{Re4} = I_{E3} \quad // \quad \text{Let } I_{Rc4} = I_{c3} \quad // \quad R_{E4} = R_{E3} = 1\text{k}\Omega \quad // \quad R_{c4} = \frac{4.1}{0.2\text{mA}} = 20.5\text{k}\Omega$$

(2)

stage 3 : emitter follower.

$$A_{U3} = \frac{R_{Le3}}{R_{Le3} + r_e} = \boxed{0.99}$$

$\downarrow$ (1k//1k) $\rightarrow \frac{26}{5}$

$$R_{in7} = (\beta + 1)(R_{Le3} + r_e) = \boxed{253.1 \text{ k}\Omega}$$

Stage 2 : Diff. Amp.

$$A_{v2} = \frac{(R_{C6} \parallel R_{in7})}{2(R_{Ee6} + r_e)} = \frac{5.6 \text{ k}\Omega}{252} = \boxed{22.2}$$

$\uparrow$ 5.7k Ω $\uparrow$ 253.1k Ω
 $\downarrow$ 100 Ω $\rightarrow \frac{26 \text{ mV}}{1 \text{ mA}}$

$$R_{in, diff2} = (\beta + 1)2(r_e + R_{Ee5}) = \boxed{126 \text{ k}\Omega}$$

common mode.

$$A_{cm2} = \frac{(R_{C6} \parallel R_{in7})}{\underbrace{r_e + R_{Ee6}}_{126} + 2R_{out9}} = \boxed{0.013}$$

$\uparrow$ 5.6k $\downarrow$ 100 $\downarrow$ 1
 where $R_{out9} = \frac{(V_A + V_{CE})}{I_C} \left[1 + \frac{R_{Ee9}}{r_e} \right] = \boxed{439 \text{ k}\Omega}$
 $\uparrow$ 2mA $\uparrow$ 26/2 $\rightarrow$ 100

$$R_{in2, cm} = (\beta + 1)(r_e + R_{Ee6} + R_{out9}) = \boxed{219 \text{ M}\Omega}$$

Stage 1 : Diff. Amp.

$$A_{v1} = \frac{(R_{C1} \parallel R_{in, diff2})}{2 \cdot r_e} = \frac{17.3 \text{ k}\Omega}{2 \cdot 260} = \boxed{33.27}$$

$$A_{cm1} = \frac{(R_{C1} \parallel R_{in, cm2})}{r_e + 2R_{out3}} \approx \frac{R_{C1}}{2R_{out3}} = 2 \times 10^{-3}$$

$\uparrow$ (20k Ω) $\uparrow$ 219M Ω

$$\text{where } R_{out3} = \frac{(V_A + V_{CE})}{I_C} \left[1 + \frac{R_{E3}}{r_e} \right] = \boxed{4.5 \text{ M}\Omega}$$

$\downarrow$ 100 $\uparrow$ 4.8 - 0.7 = 4.1 $\downarrow$ 1k Ω
 $\uparrow$ 0.2mA $\uparrow$ 130

Thus,

$$A_{diff} = A_{v1} \cdot A_{v2} \cdot A_{v3} = (33.27)(22.2)(0.99) = 731.2$$

$$A_{cm} = A_{cm1} \cdot A_{cm2} \cdot A_{v3} = (2 \cdot 10^{-3})(0.013)(0.99) = 2.6 \times 10^{-5}$$

$$CMRR = \frac{A_{diff}}{A_{cm}} = \frac{731.2}{2.6 \times 10^{-5}} = 2.8 \times 10^7 = \boxed{149.1 \text{ dB}}$$

Finally

$$R_{out,amp} = R_{in,emitter7} \parallel R_{e7}$$

$$R_{in,emitter7} = \left(r_e + \frac{R_{B7}}{\beta + 1} \right) = \overset{\frac{26}{5}}{\downarrow} r_e + \overset{5.7 \text{ k}\Omega}{\downarrow} \frac{R_{C6} \parallel R_{out6}}{\beta + 1}$$

$$\text{where } R_{out6} = \frac{\overset{3}{\downarrow} V_A + V_{CE}}{\overset{\uparrow}{I_C}} \left(1 + \frac{R_{E6}}{\overset{\uparrow}{r_e}} \right)^{\overset{100}{\leftarrow}} = 500 \text{ k}\Omega$$


$\uparrow 1 \text{ mA}$
 $\uparrow \frac{26 \text{ mV}}{1 \text{ m}}$

$$\therefore R_{in,emitter7} = 11 \Omega$$

$$\therefore R_{out,amp} = R_{in,emitter7} \parallel R_{e7} = \boxed{10.9 \Omega}$$

prob 2.

4

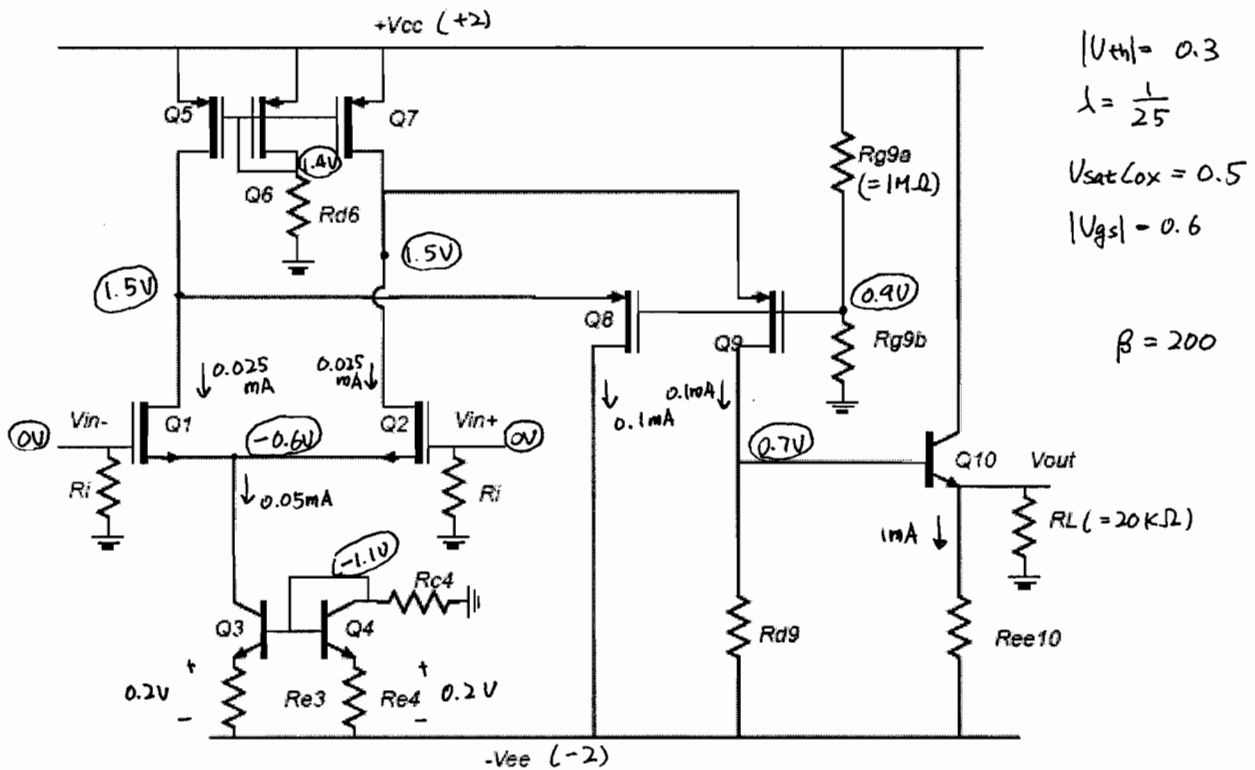

FET width

for Q_1, Q_2 (n-channel)

$$I_D = (V_{sat} \cdot C_{ox}) \cdot W_g (V_{gs} - V_{th}) (1 + \lambda V_{DS}) \Rightarrow W_g = \frac{I_D}{(V_{sat} \cdot C_{ox}) (0.3) (1 + \frac{1}{25} 2.1)}$$

$$W_{g1} = W_{g2} = \boxed{0.15 \mu m}$$

for Q_5, Q_6, Q_7, Q_8, Q_9 (p-channel)

$$I_D = (V_{sat} \cdot C_{ox}) W_g (- (V_{gs} - V_{th})) (1 + \lambda V_{SD}) \Rightarrow W_g = \frac{I_D}{0.5 (0.3) (1 + \lambda V_{SD})}$$

$\downarrow$ -0.6 $\uparrow$ -0.3

$$W_{g5} = W_{g7} \Big|_{\substack{I_D = 0.025 \text{ mA} \\ V_{SD} = 0.5 \text{ V}}} = \boxed{0.163 \mu m}$$

$$W_{g6} = \boxed{0.163 \mu m} \Big|_{\substack{I_D = 0.025 \text{ mA} \\ V_{SD} = 0.6}}$$

$$W_{g8} \Big|_{\substack{I_D = 0.1 \text{ mA} \\ V_{SD} = 3.5 \text{ V}}} = \boxed{0.585 \mu m}$$

$$W_{g9} \Big|_{\substack{I_D = 0.1 \text{ mA} \\ V_{SD} = 0.8 \text{ V}}} = \boxed{0.646 \mu m}$$

Resistor Value.

$$R_{d9} = \frac{2.7V}{0.1mA} = \boxed{27k\Omega}, \quad R_{ee10} = \frac{2}{1mA} = \boxed{2k\Omega}$$

$$2. \frac{R_{g9b}}{R_{g9b} + R_{g9a}} = 0.9(V) \Rightarrow R_{g9b} = \boxed{818.2k\Omega}$$

$$R_{d6} = \frac{1.4}{0.025mA} = \boxed{56k\Omega}$$

$$R_{e3} = \frac{0.2}{0.05mA} = \boxed{4k\Omega} = R_{e4}, \quad R_{c4} = \frac{1.1(V)}{0.05mA} = \boxed{22k\Omega}$$

(b) small signal analysis.

$$Q_{10}: \quad A_{v10} = \frac{R_{ee10} \parallel R_L}{R_{ee10} \parallel R_L + r_e} = \boxed{0.99}$$

$\swarrow 1.82k$
 $\downarrow 26$

$$R_{in10} = (\beta+1)(r_e + R_{ee10} \parallel R_L) = \boxed{370.6k\Omega}$$

$$Q_9: \quad A_{v9} = \underbrace{g_m}_{0.323mA} (R_{d9} \parallel R_{in10}) = \boxed{8.13}$$

$$R_{in9} = 1/g_m = \boxed{3.1k\Omega}$$

Q_2, Q_1 : Diff. stage.

$$A_{d1} = \frac{R_{out7} \parallel R_{in9}}{2} \cdot \underbrace{g_m}_{0.075} = \boxed{0.11}$$

$\swarrow \text{huge}$
 $\downarrow 0.075$

$$R_{in,D} = \infty$$

$$A_{CM1} = \frac{R_{out7} \parallel R_{in9} \parallel R_{out,dm2}}{1/g_m + 2R_{out3}} \approx \frac{R_{in9}}{1/g_m + 2R_{out3}} = \boxed{7.2 \times 10^{-3}}$$

$\swarrow \text{huge}$
 $\downarrow 0.075$

$$\text{where } R_{out3} = \frac{(V_A + V_{CE})}{I_{c3}} \left(1 + \frac{R_{e3}}{g_{m3}} \right) = 208k\Omega$$

$\swarrow 1.2V$
 $\uparrow 0.05$
 $\swarrow 4k\Omega$
 $\uparrow \frac{26}{0.05} = 520$

(6)

(c) output impedance.

$$R_{out,amp} = R_{e10} \parallel R_{in,emitter10}$$

$$\text{where } R_{in,emitter10} = r_e + \frac{R_{d9} \parallel R_{out,drain9}}{\beta+1}$$

$$\text{where } R_{out,drain9} = \frac{[1/\lambda + V_{os}]}{I_D} (1 + g_m (R_{in07} \parallel R_{in02}))$$

..... = large. (huge)

$$\therefore R_{in,emitter10} = 26 + \frac{27k}{201} = \boxed{39.4\Omega}$$

$$\therefore R_{out,amp} = 39.4\Omega \parallel 2k = \boxed{38.6\Omega}$$

(d) Signal Swing

$$Q10) \Delta V_{CE} = V_{CE} - V_{sat} = 2 - 0.5 = 1.5(V) \uparrow \text{ (sat)}$$

$$\Delta V_{cutoff} = 1mA (2k \parallel 20k) = 1.82 \downarrow \text{ (cutoff)}$$

$$Q9) V_{sat, knee} = V_G + |V_{th}| = 0.9 + 0.6 = 1.5(V)$$

$$\therefore \Delta V_D = 1.5 - 0.7 = 0.8(V) \uparrow$$

$$\Delta V_{out} \downarrow = 0.1mA (R_{d9} \parallel R_{in10}) = -2.51(V) \downarrow$$

$\uparrow \qquad \qquad \uparrow$
 $27k \qquad \qquad 370k$

pinchoff Q2) biased @ 0.025mA. Decreasing this to zero

$$\text{will increase } I_{s9} \text{ by } 0.025mA \times \frac{R_{in07}}{R_{in07} + R_{in9}} \approx 0.025.$$

$\downarrow$
 huge

$$\text{This will increase output voltage by } 0.025mA \times R_{d9} = 0.68(V) \uparrow \text{ (} V_{D10} \text{)}$$

pinchoff Q1) biased @ 0.025mA.

Decreasing this to zero will increase the current in Q2 by 0.025mA

$$\text{which will decrease the current in Q9 by } 0.025mA \cdot \frac{R_{in05}}{R_{in05} + R_{in9}} \approx 0.025mA$$

which will decrease the output voltage (V_{D10})

$$= -0.68(V) \downarrow$$

$$\therefore \text{Overall : } \boxed{\pm 0.68(V)}$$