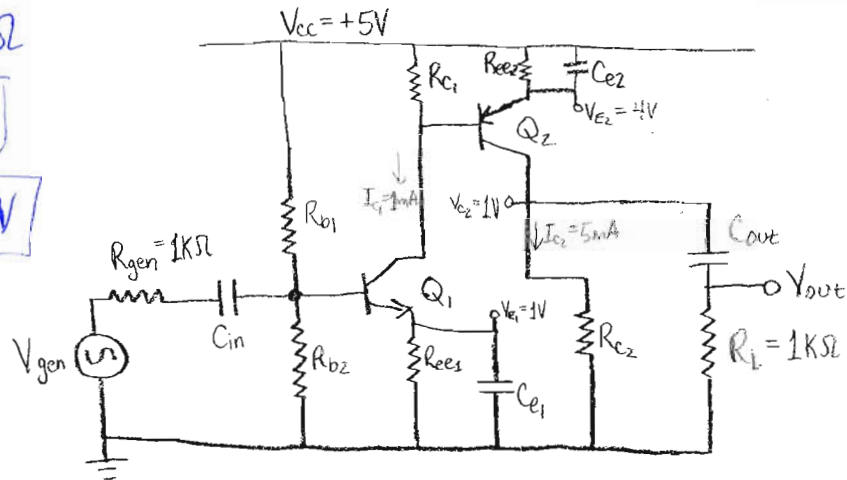


① $\beta = 50$, $V_A = 50V$, $V_{CC} = +5V$, $R_{gen} = 1K\Omega$, $R_L = 1K\Omega$,
 $I_{C1} = 1mA$, $I_{C2} = 5mA$, $V_{E2} = 4V$, $V_{C2} = 1V$, $V_{E1} = 1V$,

$R_{b1} \parallel R_{b2} = 10K\Omega$

* $V_{b1} = V_{E1} + V_{BE} = 1.7V$

* $V_{b2} = V_{C1} = V_{E2} - V_{BE} = 3.3V$



a) Find R_{b1} , R_{b2} , R_{C1} , R_{C2} , R_{ee1} , & R_{ee2} ?

$\Rightarrow$ Assume that I_B is negligible... So, $V_{b1} = \frac{R_{b2}}{R_{b1} + R_{b2}} \cdot V_{CC}$ & $\frac{R_{b1} \cdot R_{b2}}{R_{b1} + R_{b2}} = 10K\Omega$
Solving Equations gives $R_{b1} = 29.412 K\Omega$ & $R_{b2} = 15.152 K\Omega$

$\rightarrow R_{ee1} = \frac{V_{E1}}{I_E} = \frac{1V}{1.02mA} = 980\Omega$

$R_{C1} = \frac{V_{CC} - V_{C1}}{I_{C1} - I_{b2}} = \frac{5V - 3.3V}{1mA - 0.1mA} = 1889\Omega$

$\rightarrow R_{C2} = \frac{V_{C2}}{I_{C2}} = \frac{1V}{5mA} = 200\Omega$

$R_{ee2} = \frac{V_{CC} - V_{E2}}{I_{E2}} = \frac{5V - 4V}{5.1mA} = 196\Omega$

b) $g_{m2} = \frac{I_{C2}}{V_{th}} \approx 0.193 S$

$R_{CE2} = \frac{V_{EE2} + V_A}{I_{C2}} = \frac{3V + 50V}{5mA} = 10.6 K\Omega$

$\frac{V_{C2}}{V_{b2}} = g_{m2} \cdot (R_{CE2} \parallel R_{C2} \parallel R_L) = 31.67 \frac{V}{V}$

$R_{in2} = (\beta + 1) \cdot r_e \approx 259\Omega$ (264 Ω ok also)

c) $R_{CE1} \approx \infty$ & $g_{m1} = \frac{I_{C1}}{V_{th}} = \frac{1mA}{V_{th}} \approx 0.0387 S$

$\Rightarrow \frac{V_{C1}}{V_{b1}} = -g_{m1} \cdot (R_{C1} \parallel R_{in2}) \approx -8.81 \frac{V}{V}$

$R_{in,Q1} = (\beta + 1) \cdot r_e \approx 51 \cdot \frac{V_{th}}{I_{E1}} \approx 1.293 K\Omega$

$R_{in1} = R_{b1} \parallel R_{b2} \parallel R_{in,Q1} = 1.145 K\Omega$

$$\rightarrow \frac{V_{out}}{V_{gen}} = \frac{V_{out}}{V_{in}} \cdot \frac{V_{in}}{V_{gen}} = -279 \frac{V}{V} \cdot 0.534 \approx \boxed{-149 \frac{V}{V}}$$

pg 2

2) con'd

ECE 137A
Winter '07 - HW #5

b) $Q_1 \Rightarrow I_{D1} = 0.5 \text{ mA}, V_{D1} = +V_{DD} = 3 \text{ V},$

$\rightarrow V_{S1} = V_{S2} = -V_{GS2} \quad \& \quad V_{GS2} = \frac{I_{D2}}{V_{sat} \cdot C_{ox} \cdot W_g} + V_t = 0.8 \text{ V} \Rightarrow V_{S1} = -0.8 \text{ V}$

$V_{G1} = V_{G2} = 0 \text{ V}$ (for same current)

$Q_2 \Rightarrow I_{D2} = 0.5 \text{ mA}, V_{D2} = V_{S5} = 2 \text{ V}, V_{G2} = 0 \text{ V}, V_{S2} = V_{S1} = -0.8 \text{ V}$


$Q_3 \Rightarrow I_{D3} = I_{D1} + I_{D2} = 1 \text{ mA}, V_{D3} = V_{S1} = V_{S2} = -0.8 \text{ V}, V_{G3} = -I_{D4} \cdot R_{d4} = -1.7 \text{ V}, V_{S3} = -V_{S5} = -3 \text{ V}$

$Q_4 \Rightarrow I_{D4} = I_{D3} = 1 \text{ mA}, V_{D4} = V_{G3} = V_{G4} = -1.7 \text{ V}, V_{S4} = -V_{S5} = -3 \text{ V}$

$Q_5 \Rightarrow I_{D5} = 0.5 \text{ mA}, V_{D5} = 0 \text{ V}, V_{G5} = V_{GS5} + V_{S5} = 1.45 \text{ V}, V_{S5} = 2 \text{ V}$

c) $R_{in5} = \frac{1}{g_{m5}} \parallel R_{d2} = \frac{1}{0.25 \frac{\text{mA}}{\text{V}} \cdot 8 \mu\text{m}} \parallel 1 \text{ k}\Omega \approx 333 \Omega$


Find $\frac{V_{D5}}{V_{S5}}$

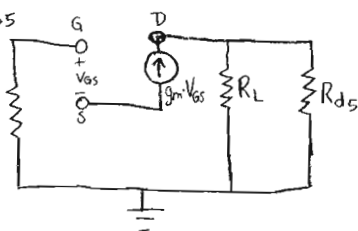

$V_{D5} = g_{m5} \cdot V_{GS5} \cdot (R_L \parallel R_{d5}) \quad \& \quad V_{DS5} = -V_{GS5}$

$\Rightarrow \frac{V_{D5}}{V_{S5}} = -g_{m5} (R_L \parallel R_{d5}) \approx -11.93 \frac{\text{V}}{\text{V}}$

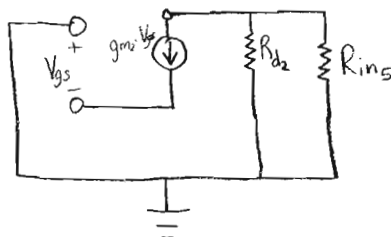
d) $R_{in2} = \frac{1}{g_{m2}} = \frac{1}{0.25 \text{ mA/V} \cdot 4 \mu\text{m}} \approx 1 \text{ k}\Omega$



$V_{D2} = -g_{m2} \cdot V_{GS2} \cdot (R_{d2} \parallel R_{in5}) \quad \& \quad V_{S2} = -V_{GS2}$

$\Rightarrow \frac{V_{D2}}{V_{S2}} = g_{m2} \cdot (R_{d2} \parallel R_{in5}) \approx 0.25 \frac{\text{V}}{\text{V}}$

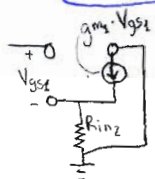e) $R_{in1} = \infty \quad g_{m1} = g_{m2} \quad \& \quad V_{S1} = g_{m1} \cdot V_{GS1} \cdot R_{in2} = g_{m1} \cdot R_{in2} \cdot (V_{G1} - V_{S1}) = \frac{g_{m1} \cdot R_{in2} \cdot V_{G1}}{1 + g_{m1} \cdot R_{in2}}$



$\Rightarrow \frac{V_{S1}}{V_{G1}} = \frac{g_{m1} \cdot R_{in2}}{1 + g_{m1} \cdot R_{in2}} = \frac{R_{in2}}{\frac{1}{g_{m1}} + R_{in2}} \approx 0.5 \frac{\text{V}}{\text{V}}$

② con'd

ECE 137A

Winter '07 - HW#5


f) Find $\frac{V_{in}}{V_{gen}}, \frac{V_{out}}{V_{in}}, \frac{V_{out}}{V_{gen}} \dots ?$

$$\rightarrow V_{in} = \frac{R_{g1}}{R_{g1} + R_{gen}} \cdot V_{gen} \Rightarrow \frac{V_{in}}{V_{gen}} = \frac{R_{g1}}{R_{g1} + R_{gen}} \approx \boxed{0.909 \frac{V}{V}}$$

$$\rightarrow \frac{V_{out}}{V_{in}} = \frac{V_{d5}}{V_{s5}} \cdot \frac{V_{d2}}{V_{s2}} \cdot \frac{V_{s1}}{V_{g1}} \approx \boxed{-1.49 \frac{V}{V}}$$

$$\rightarrow \frac{V_{out}}{V_{gen}} = \frac{V_{in}}{V_{gen}} \cdot \frac{V_{out}}{V_{in}} \approx \boxed{-1.36 \frac{V}{V}}$$

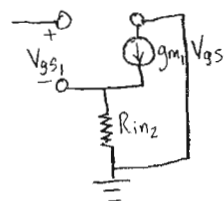g) Find max signal swing of ~~the~~ amp...?



• Clipping for Q_1 :

$\Delta V_{out} \downarrow \max$ occurs when $I_D = 0 \text{ mA}$

$$\Delta V_{out} \downarrow \max = I_{DQ} \cdot R_{in2} = 0.5 \text{ mA} \cdot 1 \text{ k}\Omega = \underline{0.5 \text{ V}}$$

$$\Delta V_{out} \uparrow \max \text{ occurs when } V_{dg} = -V_t = -0.3 \text{ V}, V_{dgQ} = 3 \text{ V} - 0 \text{ V} = 3 \text{ V}$$

$$\& V_{ds} = V_{dg} + V_{gs} \Rightarrow V_{ds} = V_{dg} + V_g - V_s \Rightarrow V_g = V_d - V_{dg}$$

$$\Delta V_{out} \downarrow \max = (V_d - V_{dgQ} - V_{gs}) - (V_d - V_{dg} - V_{gs}) = V_{dg} - V_{dgQ} = -0.3 \text{ V} - 3 \text{ V} = \underline{-3.3 \text{ V}}$$

Q_1 is limited by current...

• Clipping for Q_2 : when $I_D = 0 \text{ mA} \rightarrow \Delta V_{out} \downarrow \max = I_D \cdot (R_{in5} \parallel R_{d2}) = \underline{0.125 \text{ V}}$

$$\text{when } V_{dg} = -V_t, V_{ds} = V_{dg} + V_{gs} = -0.3 \text{ V} + 0.8 \text{ V} = 0.5 \text{ V}$$

$$\Delta V_{out} \downarrow \max = V_{dsQ} - V_{ds} = 2.8 \text{ V} - 0.5 \text{ V} = \underline{2.3 \text{ V}} \Rightarrow \text{Current is the limiting factor}$$

$$\text{Now } \Delta V_{out} \downarrow \max_1 \cdot \frac{V_{d2}}{V_{s2}} = 0.5 \text{ V} \cdot 0.25 = \underline{0.125 \text{ V}} \Rightarrow Q_1 \text{ is limiting up to this point}$$


• Clipping for Q_5 : when $I_D = 0 \text{ mA}, V_{out} = \frac{-3 \text{ V} \cdot R_L}{R_{d5} + R_L} \approx \underline{-2.98 \text{ V}}, V_{outQ} = 0 \text{ V}$

$$\Delta V_{out} \downarrow \max = -2.98 \text{ V} \text{ (Current limiting)}$$


$$\Delta V_{out} \downarrow \max = V_{dgQ} - V_t = -1.45 \text{ V} - 0.3 \text{ V} = \underline{-1.75 \text{ V}}$$

$$\Rightarrow \Delta V_{out} \downarrow \max \cdot \frac{V_{d5}}{V_{s5}} = 0.125 \text{ V} \cdot -11.93 \approx \underline{-1.49 \text{ V}}$$

$$\Rightarrow V_{out \max} = 1.49 \text{ V} \cdot 2 = \underline{2.98 \text{ V}_{p-p}} \quad Q_1 \text{ limits the output voltage swing} \quad \text{Pg. 4}$$

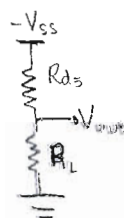

ECE 137A
Winter '07 - HW#5

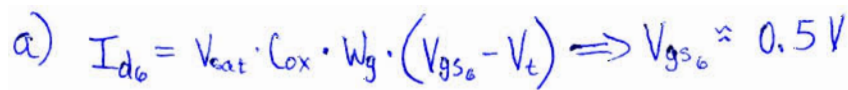

$$R_{cs} = \frac{V_{dd} + V_{gs7} - V_{gs6} + V_{ss}}{I_{D7}} = \frac{1.5V - 0.5V - 0.5V + 1.5V}{0.2mA} = 10K\Omega$$

$$R_{d1} = \frac{V_{dd} - V_{d1}}{I_{d1}} = \frac{1.5V - 0.5V}{0.1mA} = 10K\Omega$$

$$R_{d2} = R_{d1} = 10K\Omega$$

$Q_2 \Rightarrow I_{d_2} = 0.4 \text{ mA}, V_{D_2} = 0.5 \text{ V}, V_{g_2} = 0 \text{ V}, V_{s_2} = -0.4 \text{ V}$

Q4 $\Rightarrow I_{D4} = 0.1 \text{ mA}, V_{D4} = 0 \text{ V}, V_{G4} = V_{D2} = 0.5 \text{ V}, V_{S4} = V_{S3} = 0.9 \text{ V}$

Q6 $\Rightarrow I_{d6} = 0.2 \text{ mA}, V_{d6} = V_{g6} = -1 \text{ V}, V_{s6} = -V_{ss} = -1.5 \text{ V}$

③ con'd... b) con'd...

$$Q_7 \Rightarrow I_{d7} = 0.2\text{mA}, V_{d7} = V_{g7} = V_{gs7} + V_{dd} = +1\text{V}, V_{s7} = V_{dd} = 1.5\text{V}$$

$$Q_8 \Rightarrow I_{d8} = 0.2\text{mA}, V_{d8} = V_{s8} = 0.9\text{V}, V_{g8} = V_{g7} = 1\text{V}, V_{s8} = V_{dd} = 1.5\text{V}$$

ECE 137A

Winter '07 - HW#5

c) Find A_v of $\frac{Q_3}{Q_4} \dots ? \rightarrow A_v = \frac{g_m \cdot R_{Leq}}{2}$ & $R_{Leq} = R_{d4} \parallel R_L \approx 13.636\text{K}\Omega$

$$\Rightarrow A_v = \frac{1\text{mS} \cdot 13.636\text{K}\Omega}{2} \approx \boxed{6.81}$$

d) Find A_v of $\frac{Q_1}{Q_2} \dots ? \quad A_v = \frac{g_m \cdot R_{d1}}{2} + \frac{g_m \cdot R_{d2}}{2} \approx \boxed{10}$

e) Find $\frac{V_{in}}{V_{gen}}, \frac{V_{out}}{V_{in}}, \& \frac{V_{out}}{V_{gen}} \dots ?$

$$\frac{V_{in}}{V_{gen}} = 1 \frac{\text{V}}{\text{V}}$$

$$\frac{V_{out}}{V_{in}} = A_{v1,2} \cdot A_{v3,4} = 68.18 \frac{\text{V}}{\text{V}}$$

$$\frac{V_{out}}{V_{gen}} = 68.18 \frac{\text{V}}{\text{V}}$$