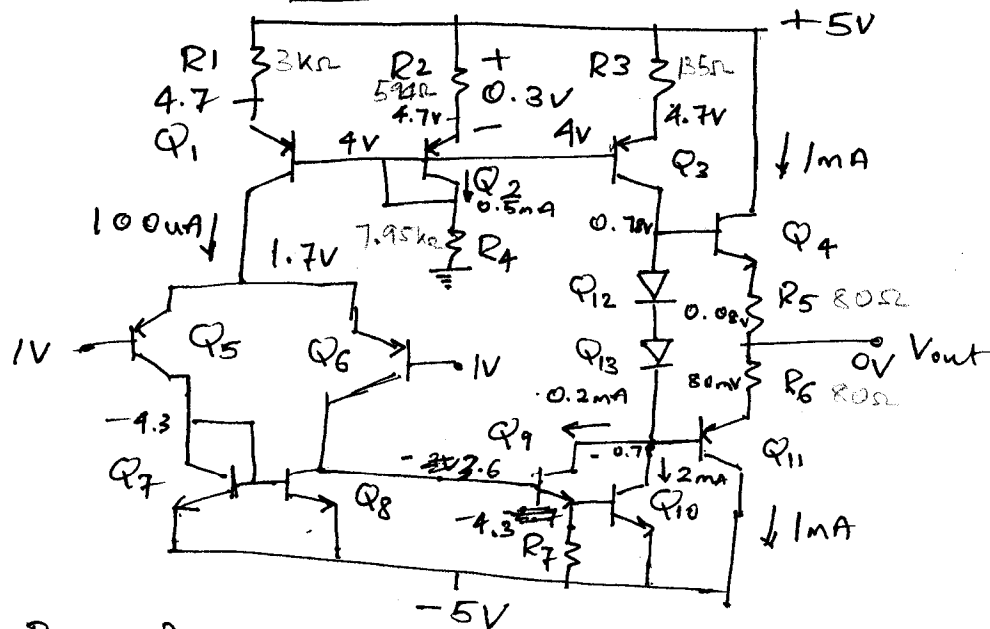


2.)

HW #7 SOLUTIONS

DC BIAS DESIGN:

For the O/P stage: $-V_{beQ12} - V_{beQ13} + V_{beQ11} + 2(I_{C4} R_5) + V_{beQ4} = 0$

$$\Rightarrow I_{C4} R_5 = V_{beQ12} - V_{beQ4} = V_T \ln \left[\frac{I_{C12}}{I_{S12}} \right] - V_T \ln \left[\frac{I_{C4}}{I_{S4}} \right]$$

$$= V_T \ln \left[\frac{I_{C12}}{I_{C4}} \cdot \frac{I_{S4}}{I_{S12}} \right]$$

Take $I_{S12} = \frac{1}{10} I_{S4}$ to get: $I_{C4} R_5 = V_T \ln \left[10 \cdot \frac{I_{C12}}{I_{C4}} \right]$

(O/P power transistors are typically larger and have a larger I_S)

Now, $I_{C12} = I_{CQ9} + I_{CQ10} - I_{BQ11}$

$$= 2.2\text{mA} - 5\mu\text{A} = 2.19\text{mA}$$

$$\Rightarrow I_{C4} R_5 = (26\text{mV}) \ln \left[10 \cdot \frac{2.19\text{mA}}{1\text{mA}} \right] = \underline{\underline{80\text{mV}}}$$

$$\Rightarrow \boxed{R_5 = 80\Omega}$$

$$\text{Now, } R_1 = \frac{V_{CC} - V_{E_{Q1}}}{I_{E_{Q1}}} = \frac{(5 - 4.7)\text{V}}{100\mu\text{A} \cdot (0.99)} = \boxed{3.03\text{k}\Omega}$$

$$R_2 = \frac{0.3\text{V}}{I_{E_{Q2}}} = \frac{0.3\text{V}}{(0.5\text{mA}) \cdot (0.99)} = \boxed{594\Omega}$$


$$R_3 = \frac{V_{CC} - V_{EQ_3}}{I_{EQ_3}} = \frac{(5 - 4.7)V}{2.2mA \cdot \left(\frac{1}{0.99}\right)} = \underline{\underline{135\Omega}}$$

$$R_4 = \frac{4V}{I_{CQ_2} + I_{BQ_2} + I_{BQ_1}} = \frac{4V}{0.5mA + 2.5\mu A + 0.5\mu A} = \boxed{7.952k\Omega}$$

$$R_5 = \frac{80mV}{1mA} = \boxed{80\Omega = R_6}$$

$$R_7 = \frac{V_{EQ_9} - V_{EE}}{I_{EQ_9}} = \frac{-4.3 + 5}{0.2mA \cdot \left(\frac{1}{0.99}\right)} = \boxed{-3.5\Omega}$$


AC Small Signal Analysis:

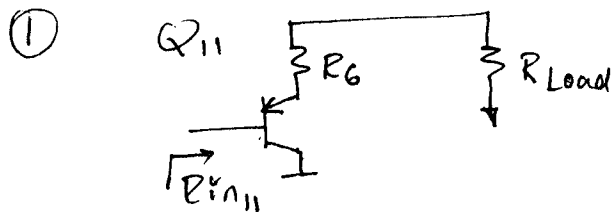

$$A_{V_{11}} = \frac{R_{Load}}{R_{Load} + R_6 + \mu_e} = \frac{5k\Omega}{5k\Omega + 80\Omega + 26\Omega}$$

$$\boxed{A_{V_{11}} = 0.979}$$
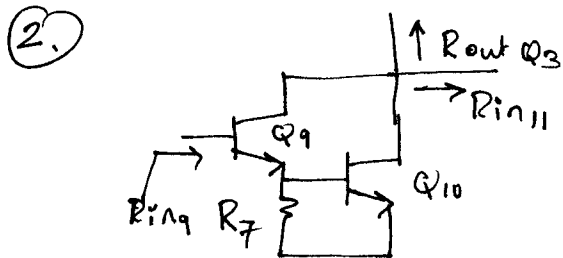
$$R_{in_{11}} = (\beta + 1)(\mu_e + R_6 + R_{Load}) = (201)(5106) = \boxed{1.02M\Omega}$$



$$A_{V_{9-10}} = - \left[A_{V_9} \cdot \frac{(R_{out_3} || R_{in_{11}})}{\mu_{e_{10}}} + \frac{(R_{out_2} || R_{in_{11}})}{R_7 + \mu_{e_9}} \right]$$

$$= - \left(0.94 \cdot \frac{363k\Omega}{13} + \frac{363k\Omega}{11k + 130} \right)$$

$$= -26280$$

$$\mu_{e_{10}} = \frac{V_A}{I_{C_{10}}} = \frac{100V}{2mA} \cdot \underline{50k\Omega}$$

$$R_{out_{Q_3}} = \mu_{e_9} (1 + g_m \cdot R_{ee})$$


$$= (50k\Omega) \left(1 + \frac{135}{13} \right)$$

$$= 570k$$

$$R_{inq} = (\beta + 1) (M_e + R_7 \parallel (\beta + 1) (M_{e10}))$$

$$= (201) (130 + (11.4k) \parallel (201)(13)) = \boxed{453 k\Omega}$$

3.)

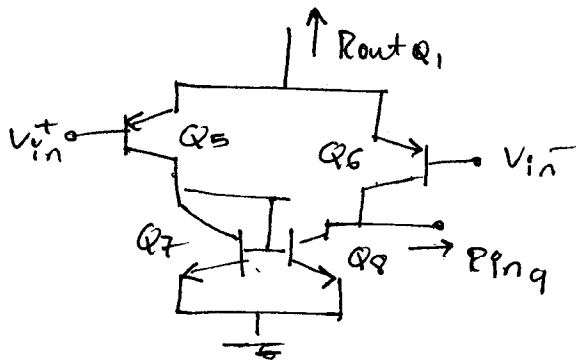

$$A_{v8} = \frac{R_{inq} \parallel M_{ce8} \parallel M_{ce6}}{M_{ce6}}$$

$$= \frac{453k \parallel 2M}{520}$$


$$= \underline{710.27}$$

$$M_{ce8} M_{out6} = M_{ce6} (1 + g_m R_{ce6})$$

$$= \left(\frac{100V}{50\mu A} \right) \left(1 + \left(\frac{100V}{.1mA} \right) \left(1 + \frac{3000}{260} \right) \right) = \underline{4.8 \times 10^{10}}$$

$$\text{Total gain} = A_{11} \cdot A_{vq} \cdot A_{v10} \cdot A_{v8} = \boxed{2.8 \times 10^6}$$

Common Mode Gain: (Differential Stage):

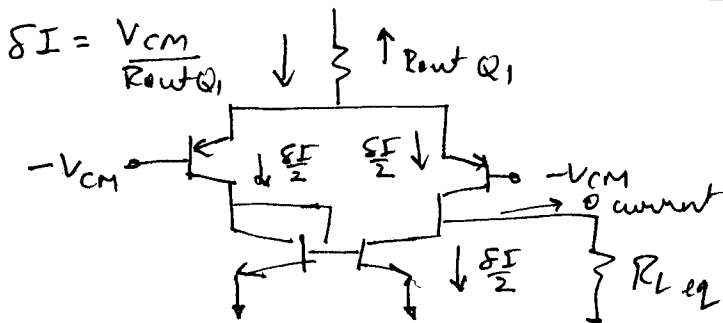

For ideal matched transistors, we see that $A_{cm} = 0 \Rightarrow \underline{CMRR = \infty}$

However in practise there are mismatches in the transistors $Q_5 - Q_6$ & Q_7 & Q_8 giving a finite Common Mode Gain.

Signal swings: (Dominant Factors)

Saturation of Q_{10} : $V_{CEQ} = 4.22V$ $V_{CEsat} = 0.2V$
 $\Delta V_{C_{10}} \downarrow = 4.02V$

$\Delta V_{out} \downarrow = (0.979) (4.02V) = 3.93V$


Saturation of Q_3 : Q_3 saturation causes it to stop being an ideal current source and it won't be able to give the required drive currents for o/p stage

$\Delta V_{C_3} \uparrow = (3.3 - 0.78)V = 2.52V$

$\Delta V_{out} \uparrow = 2.46V$

The maximum circuit can peak to peak swing which this deliver will be 4.9V ($\pm 2.46V$)

3)

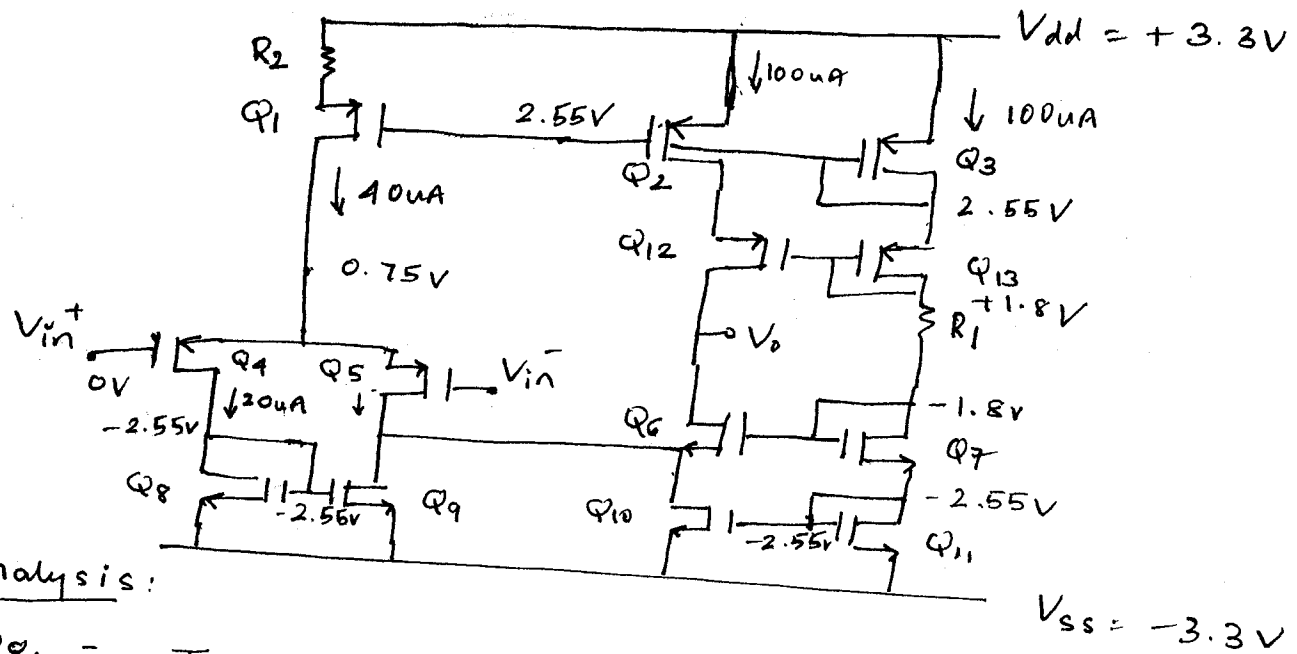

DC Analysis:

$$I_{DQ4} = I_{DQ5} = I_{DQ8} = I_{DQ9} = 20\mu A = g_m \cdot |V_{GS} - V_t|$$

$$\Rightarrow g_m = 6 \times 10^{-5} = V_{sat} \cdot C_{ox} \cdot W_g = g_m (0.25V)$$

$$\Rightarrow W_g = \left(\frac{8 \times 10^{-5}}{0.5 \times 10^{-3}} \right) \mu m = \boxed{0.16 \mu m}$$

$$\therefore W_{g4} = W_{g5} = W_{g8} = W_{g9} = 0.16 \mu m$$

$$I_{DQ2} = I_{DQ12} = I_{DQ6} = I_{DQ10} = 100\mu A = g_m |V_{GS} - V_t|$$

$$\Rightarrow g_m = 4 \times 10^{-4} = V_{sat} \cdot C_{ox} \cdot W_g \Rightarrow \boxed{W_g = 0.8 \mu m}$$

Also, since Q_3 , Q_{13} , Q_7 & Q_{11} form a current mirror with Q_2 , Q_{12} , Q_6 & Q_{10} respectively their currents are the same and hence the widths too.

$$\therefore \boxed{W_{g3,13,7,11} = 0.8 \mu m}$$

1 (contd.)

$$\text{Now, } (V_{gsQ_1} - V_{th}) g_{mQ_1} = 40 \mu A \quad \& \quad \underline{W_{Q_1} = W_{Q_2} = 0.8 \mu m}$$

$$\Rightarrow V_{gsQ_1} = \frac{40 \mu A}{g_{mQ_1}} + V_{thQ_1} = \frac{40 \mu A}{4 \times 10^{-4}} + (-0.5) = -0.5$$

$$\text{Now, } V_{gQ_1} = 2.55 V \Rightarrow \underline{V_{sQ_1} = 2.95 V}$$


$$\text{Also, } R_2 = \frac{V_{DD} - V_{sQ_1}}{I_{DQ_1}} = \frac{(3.3 - 2.95) V}{40 \mu A} = \underline{\underline{8.75 k\Omega}}$$

$$\text{Also, } R_1 = \frac{V_{DQ_{13}} - V_{DQ_7}}{I_{D_{13}}} = \frac{3.6 V}{100 \mu A} = \underline{\underline{36 k\Omega}}$$

→ The DC node voltages & currents have been labelled on the schematic. Also note that the DC voltage at the output node V_o is not very well defined and can be assumed to be 0V.

AC Small Signal Analysis

1)

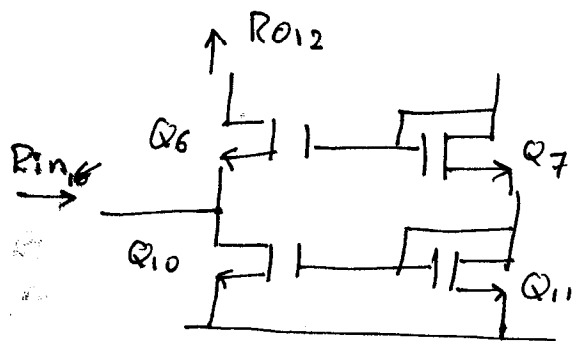

$$A_{V6} = \frac{R_{out12}}{1/g_{m6}}$$

$$= \frac{\mu_{ds12} (1 + g_m \mu_{in12})}{2.5k}$$

$$A_{V6} = 8190$$

$$R_{in6} = R_{in6} \parallel R_{DS10}$$

$$= \left(\frac{1}{g_{m6}} \right) \parallel \left(\frac{V_{DS10} + V_A}{I_D} \right)$$


$$= \left(\frac{1}{4 \times 10^{-4}} \right) \parallel \left(\frac{2.55 + 20V}{100 \mu A} \right)$$

$$= 2500 \parallel 225.5 \times 10^3$$

$$R_{in6} = 2472 \Omega$$

$$= \left(\frac{2.55 + 20V}{100 \mu A} \right) (1 + g_m (\mu_{ds})) / 2.5$$
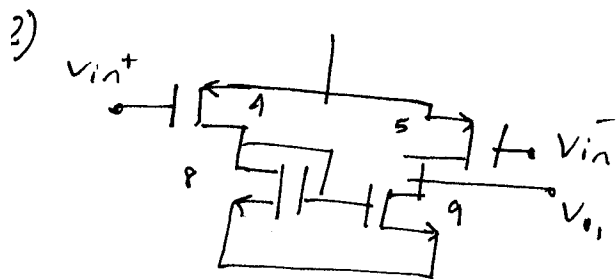
$$= \left(\frac{225k}{2.5k} \right) (1 + (4 \times 10^{-4}) (225k))$$



$$A_D = \frac{R_{in6}}{(1/g_m)} = g_m (R_{in6} \parallel R_{DS10} \parallel R_{OL12})$$

$$= (8 \times 10^{-5}) (2.4k \parallel 225k \parallel 20M)$$

$$= 0.1899$$

$$\text{Total Differential gain} = 1555$$

As was explained in the previous example, the Common Mode Gain for a Differential Pair with Current Mirror Load is ideally 0 & we need to consider mismatches in the transistors to ~~near~~ calculate it.

Peak Signal Swings:

1) Knuc voltage on Q_6 :

$$V_{DQ} > V_{th}$$

$$\Rightarrow V_D > V_G - V_{th} = -1.8 - 0.5 = -2.3V$$

$$\therefore \boxed{\Delta V_{out} \downarrow = 2.3V}$$

2) Pinch off on Q_5 :

$$\Delta I_0 = 20\mu A$$

$$\Delta V = \Delta I_0 \cdot R_{L_M} = (20\mu A)(2.4k\Omega)$$

$$\Delta V_{out} \uparrow = A_{V_1} \cdot 0.048V = > 6.6V = 0.048V$$

↳ This doesn't limit the signal swing

3) Knuc voltage on Q_{12} :

$$V_{DQ_{12}} < V_{th_{12}}$$


$$\therefore \boxed{\Delta V_{out} \uparrow = 1.3V}$$

$$\Rightarrow V_G \cdot V_{D2} < V_{th_{12}} + V_{G_{12}}$$

$$\Rightarrow V_{D_{12}} < -0.5 + 1.8 = 1.3V$$

⇒ Peak swing possible is 2.6V_{p-p}

4.1

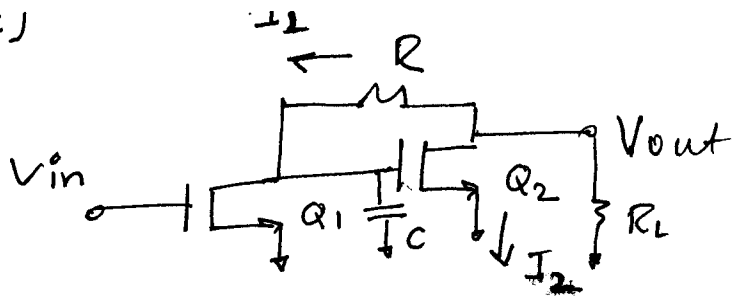

$$V_{out} = - (I_1 + I_2) R_L \quad \text{where}$$

$$I_1 = g_{m1} V_{in}$$

$$I_2 = g_{m2} (V_{gs2}) = g_{m2} (V_{out} - I_1 R)$$

$$= g_{m2} (V_{out} - g_{m1} V_{in} R)$$

$$\therefore V_{out} = - (g_{m1} V_{in} + g_{m2} (V_{out} - g_{m1} V_{in} R)) R_L$$

$$= - [(g_{m1} - g_{m1} g_{m2} R) V_{in} + g_{m2} V_{out}] R_L$$

$$\therefore V_{out} (1 + g_{m2} R_L) = - V_{in} \cdot R_L (g_{m1} - g_{m1} g_{m2} R)$$

$$\therefore \frac{V_{out}}{V_{in}} = - \frac{R_L (g_{m1} - g_{m1} g_{m2} R)}{1 + g_{m2} R_L}$$


$$= - R_L \cdot g_{m1} \cdot \frac{(1 - g_{m2} R)}{(1 + g_{m2} R_L)}$$

As R_L becomes very large, we get

$$\frac{V_{out}}{V_{in}} = - \frac{g_{m1}}{g_{m2}} (1 - g_{m2} R) = - \frac{20}{10} (1 - (10 \text{ mS})(1 \text{ k}\Omega))$$

$$\underline{A_v = 18 \text{ V/V}}$$

①

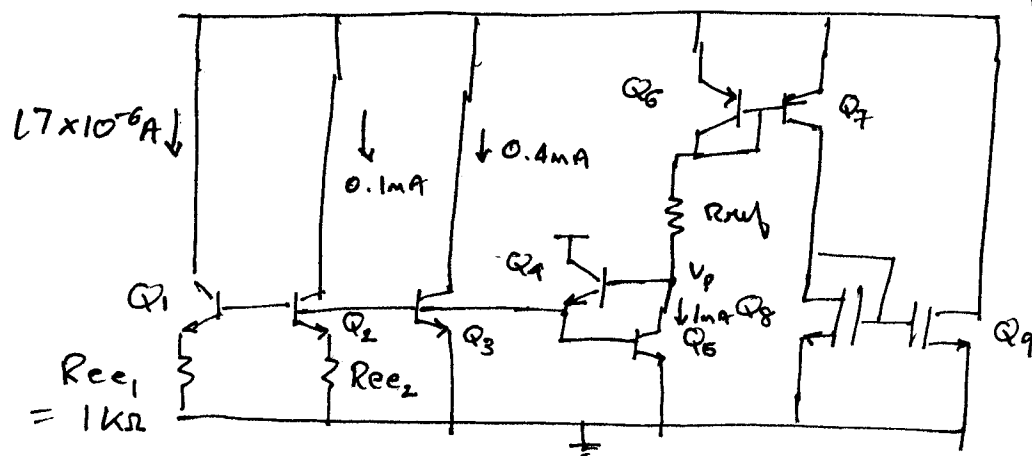

$$V_{CC} = 10V$$

$$\beta_{NPN} = 200$$

$$\beta_{PNP} = 10$$

$$V_T = 0.3V$$

$$V_{sat} C_{ox} W_g = 2mA/V$$

$$\lambda = 1/100 V$$

$$I_{C5} = 1mA$$

$$I_{C2} = 0.1mA$$

$$I_{S6} = 2 I_{S7}$$

$$I_{S5} = I_{S4}/3 = I_{S3}/4 = I_{S2} = 3 I_{S1}$$

Now, $V_{be3} = V_{be2} + I_{C2} R_2$

$$\Rightarrow V_T \ln \left[\frac{I_{C3}}{I_{S3}} \right] = V_T \ln \left[\frac{I_{C2}}{I_{S2}} \right] + I_{C2} R_2$$

$$\Rightarrow V_T \ln \left[\frac{I_{C3}}{I_{C2}} \cdot \frac{I_{S2}}{I_{S3}} \right] = I_{C2} R_2$$

Now, $\frac{I_{S3}}{I_{S2}} = 4 \Rightarrow V_T \cdot \ln \left[\frac{1}{4} \cdot \frac{I_{C3}}{0.1mA} \right] = (0.1mA) R_{ee2}$

If we assume $I_{C3} = 0.4mA$ ($4 \cdot I_{C2}$) we get $R_{ee} \approx 0$ - ①

Also, $V_{be3} = V_{be1} + I_{C1} R_{ee1}$

$$\Rightarrow V_T \ln \left[\frac{I_{C3}}{I_{S3}} \right] = V_T \ln \left[\frac{I_{C1}}{I_{S1}} \right] + I_{C1} \cdot R_{ee1}$$

$$\Rightarrow V_T \ln \left[\frac{0.4mA}{I_{C1}} \cdot \frac{1}{12} \right] = I_{C1} \cdot R_{ee1}$$

$$\Rightarrow 26mV \ln \left[\frac{0.033mA}{I_{C1}} \right] = I_{C1} \cdot (1k\Omega)$$

→ This is not a closed form solution

→ We need to use an iterative

~~appro~~

approach to find the solution.

Alternatively we can also use the Newton's Method to find roots of non-linear closed form equations like these.

$$I_{S1} \approx 10^{-7}$$

Using which we get $I_{C1} = \underline{17 \times 10^{-6} \text{ A}}$

$$\Rightarrow V_{B1} = I_{C1} R_{E1} + V_T \ln \left[\frac{I_{C1}}{I_{S1}} \right] = \underline{0.15 \text{ V}}$$

$\Rightarrow$

$$\begin{aligned} \text{Now, } I_{C4} &= I_{B1} + I_{B2} + I_{B3} + I_{B5} + I_{B4} \\ &= \frac{17 \mu\text{A} + 0.1 \text{ mA} + 0.4 \text{ mA} + 1 \text{ mA} + I_{C4}}{200} \end{aligned}$$

$$\therefore = \frac{1.4 \text{ mA} + I_{C4}}{200}$$

$$\Rightarrow \boxed{I_{C4} = 7 \mu\text{A}}$$

$$I_{C6} = I_{B4} + I_{C5} = \underline{1 \text{ mA}}$$

$$V_{BE4} = V_T \ln \left[\frac{I_{C4}}{I_{S4}} \right] = 26 \text{ mV} \cdot \ln \left[\frac{7 \mu\text{A}}{9 \times 10^{-7}} \right] \approx 53 \text{ mV}$$

$$\Rightarrow \underline{V_P = 200 \text{ mV}}$$

$$V_{BE6} = V_T \ln \left[\frac{I_{C6}}{I_{S6}} \right] \approx 0.210 \text{ V}$$

(Assuming $I_{S6} \approx 3 \cdot I_{S1} = I_{S5}$)

$$\Rightarrow R_{\text{ref}} = \frac{9.78 - 0.2}{0.1 \text{ mA}} = \underline{95 \text{ k}\Omega}$$

Now since $V_{beQ6} = V_{beQ7}$ & $I_{S7} = \frac{I_{S6}}{2}$

$$\Rightarrow I_{C7} = \frac{I_{C6}}{2} = 0.05 \text{ mA} = I_{D8}$$

$$I_{D8} = g_m (V_{gs} - V_t) (1 + \lambda V_{ds})$$

$$\frac{0.05 \text{ mA}}{2 \text{ mA/V}} = (V_{gs} - 0.3) \left(1 + \frac{V_{gs}}{100}\right) \quad (\because V_{gs} = V_{ds})$$

$$0.025 = V_{gs} - 0.003 V_{gs} + \frac{V_{gs}^2}{100} - 0.3$$

$$0 = 0.997 V_{gs} + \frac{V_{gs}^2}{100} - 0.325$$

$$\Rightarrow \boxed{V_{gs} = 0.3249 \text{ V}} = V_{gs9}$$

$$I_{D9} = g_m (V_{gs} - V_t) (1 + \lambda V_{ds9})$$

$$= \left(\frac{2 \text{ mA}}{\text{V}}\right) (0.0249) (1 + 0.1)$$

$$\boxed{I_{D9} = 0.0547 \text{ mA}}$$