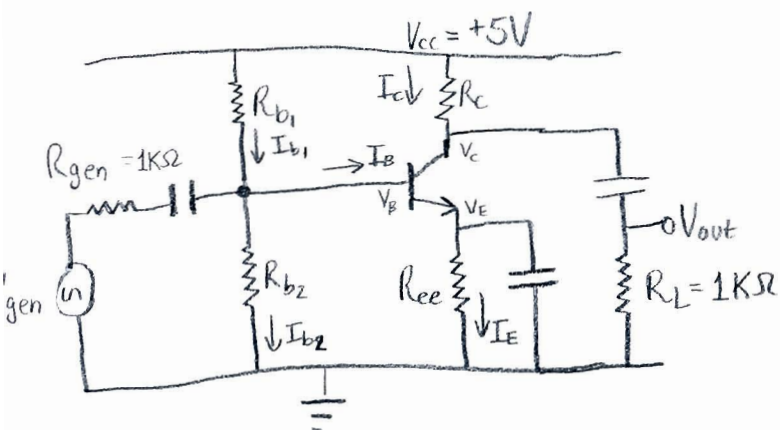


①  $\beta = 100$ ,  $V_{CC} = +5V$ ,  $R_L = 1K\Omega$ ,  $R_{gen} = 1K\Omega$   
 $V_A = 100V$ ,  $V_{CE_{sat}} = 0.5V$ ,  $V_E = 1V$ ,  $V_C = 3V$ ,

ECE 137A Homework #2  
 Winter '07



$I_C = 1mA$ ,  $I_{B2} = 0.1mA$ ,  $V_{BE} = 0.7V(on)$

a) Find  $R_{b1}$ ,  $R_{b2}$ ,  $R_C$ ,  $R_{EE}$ ?

$I_C = \frac{V_{CC} - V_C}{R_C} \Rightarrow \frac{5V - 3V}{R_C} = 1mA \Rightarrow R_C = 2K\Omega$

$I_{B2} = \frac{V_B}{R_{b2}} \dots V_B - V_E = 0.7V \rightsquigarrow V_B = 1.7V$

$0.1mA = \frac{1.7V}{R_{b2}} \Rightarrow R_{b2} = 17K\Omega$

$I_E = \frac{V_E}{R_{EE}}$  w/  $\frac{I_C}{I_E} = \frac{\beta}{\beta + 1} \Rightarrow \frac{100}{101} = \frac{1mA}{I_E}$

$1.01mA = \frac{1V}{R_{EE}} \Rightarrow R_{EE} = 990.1\Omega$

$I_{B1} = \frac{V_{CC} - V_B}{R_{b1}}$  &  $I_{B1} = I_{B2} + I_B \Rightarrow I_{B1} = 0.1mA + I_B$  w/  $I_B = \frac{I_C}{\beta} = 0.01mA$

$\rightsquigarrow I_{B1} = 0.11mA = \frac{5V - 1.7V}{R_{b1}} \Rightarrow R_{b1} = 30K\Omega$


b)  $g_m = \frac{I_C}{V_t} = \frac{1mA}{25.8mV} \approx 0.03876S$

$r_e = \frac{V_t}{I_E} = \frac{25.8mV}{1.01mA} \approx 25.5\Omega$

$r_o = \frac{V_{CE} + V_A}{I_C} = \frac{3V - 1V + 100V}{1mA} \approx 102K\Omega$

$r_{\pi} = \frac{\beta}{g_m} \approx 2.58K\Omega$

c)

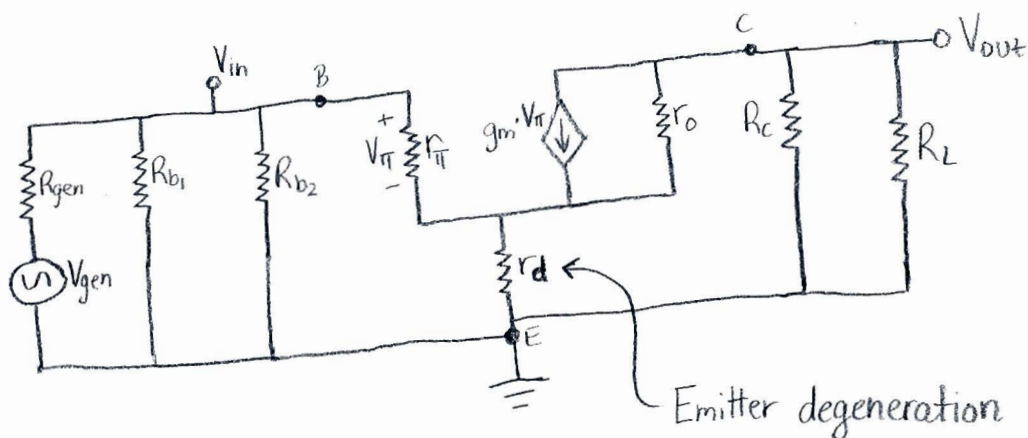

① d)  $R_{in} = R_{b1} \parallel R_{b2} \parallel (\beta+1) \cdot r_e$   
 $\Rightarrow R_{in} \approx 2.08 \text{ k}\Omega$


ECE 137A Homework #2  
 Winter '07

$V_{in} = V_{\pi} \quad \& \quad V_{out} = -g_m \cdot V_{\pi} \cdot (r_o \parallel R_c \parallel R_L)$

$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{-g_m \cdot V_{\pi} \cdot (r_o \parallel R_c \parallel R_L)}{V_{\pi}} \approx -25.7$

$V_{in} = V_{gen} \cdot \frac{R_{in}}{R_{in} + R_{gen}} \Rightarrow \frac{V_{in}}{V_{gen}} = \frac{R_{in}}{R_{in} + R_{gen}} \approx 0.675$

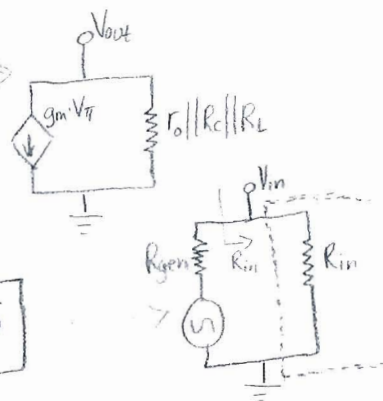$\frac{V_{out}}{V_{gen}} = \frac{V_{out}}{V_{in}} \cdot \frac{V_{in}}{V_{gen}} = -25.7 \cdot 0.675 \approx -17.36$



e)  $I_{CQ} = 1 \text{ mA}$ ,  $I_{Cmin} = 0 \text{ mA}$ ,  $\Rightarrow \Delta I_{Cmax} = 1 \text{ mA}$ ,  $\& \Delta V_{outmax} = \Delta I_{Cmax} \cdot (r_o \parallel R_c \parallel R_L) \approx 0.66 \text{ V}$

$V_{CEQ} = 2 \text{ V}$ ,  $V_{CEmin} = V_{CEsat} = 0.5 \text{ V}$ ,  $\Delta V_{CEmax} = 1.5 \text{ V}$ ,  $\Rightarrow \Delta V_{outmax} = 1.5 \text{ V}$

So, for  $\Delta V_{outmax}$  smaller than cutoff  $\Rightarrow V_{P-Pmax} = 2 \cdot \Delta V_{outmax} = 2 \cdot 0.66 \text{ V} \approx 1.32 \text{ V}_{P-P}$

②  $V_{sat} \cdot C_{ox} \cdot W_g = 10 \text{ mA/V}$ ,  $V_{th} = 0.3 \text{ V}$ ,  $\lambda = 0.04 \text{ V}$ ,  $V_{dd} = 2 \text{ V}$ ,  $R_{gen} = 50 \text{ k}\Omega$ ,  $R_L = 10 \text{ k}\Omega$ ,  
 $V_D = 1 \text{ V}$ ,  $I_D = 2 \text{ mA}$ ,  $R_{in} = 1 \text{ M}\Omega$


a) Find  $R_{g1}$ ,  $R_{g2}$ ,  $\& R_d$ ?

$I_D = \frac{V_{dd} - V_D}{R_d} \Rightarrow R_d = \frac{2 \text{ V} - 1 \text{ V}}{2 \text{ mA}} \approx 500 \Omega$

$I_D = V_{sat} \cdot C_{ox} \cdot W_g \cdot (V_g - V_{th})$

$\Rightarrow 2 \text{ mA} = 10 \text{ mA/V} \cdot (V_g - 0.3 \text{ V}) \Rightarrow V_g \approx 0.5 \text{ V}$

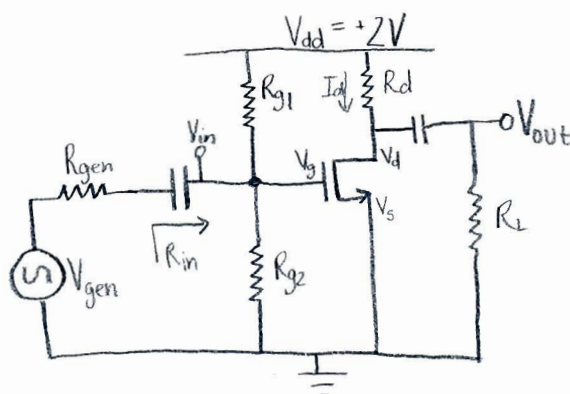$\Rightarrow R_{g1} = 4 \text{ M}\Omega \quad \& \quad R_{g2} = 1.3 \text{ M}\Omega$




b) Find  $g_m$   $\& r_{ds}$ ?

$g_m = V_{sat} \cdot C_{ox} \cdot W_g \Rightarrow g_m = 10 \text{ mS}$

$r_{ds} = \frac{1}{\lambda \cdot I_D} \Rightarrow r_{ds} = 12.5 \text{ k}\Omega$

2) c)

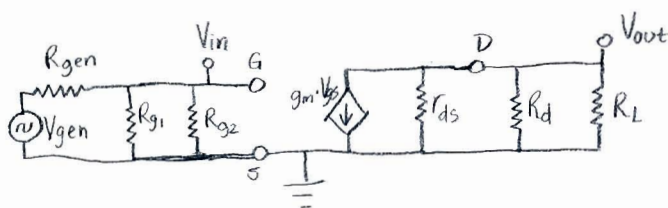

ECE 137A Homework #2  
Winter '07

d)  $R_{in}$  is given as  $1M\Omega$

$$V_{in} = V_g \quad \& \quad V_{out} = -g_m \cdot V_g \cdot (r_{ds} \parallel R_d \parallel R_L) \Rightarrow \frac{V_{out}}{V_{in}} = -g_m \cdot (r_{ds} \parallel R_d \parallel R_L) \approx \boxed{-4.587}$$

$$V_{in} = V_{gen} \cdot \left( \frac{R_{in}}{R_{gen} + R_{in}} \right) \Rightarrow \frac{V_{in}}{V_{gen}} = \frac{R_{in}}{R_{gen} + R_{in}} \approx \boxed{0.952}$$


$$\frac{V_{out}}{V_{gen}} = \frac{V_{out}}{V_{in}} \cdot \frac{V_{in}}{V_{gen}} = -4.587 \cdot 0.952 \approx \boxed{-4.369}$$

e) Max -ve swing  $\rightarrow V_{ds} = V_g - V_{th} = 0.5V - 0.3V = 0.2V \quad \dots \Delta V_{out_{max}} = V_{ds_{Q}} - V_{ds} = 1V - 0.2V = 0.8V$

Max +ve swing  $\rightarrow \Delta I_{D_{max}} = 2mA \quad \rightarrow \Delta V_{out_{max}} = \Delta I_{D_{max}} \cdot (r_{ds} \parallel R_d \parallel R_L) \approx 0.917V$

$\Rightarrow$  Using -ve swing (b/c it's smallest)  $\dots V_{p-p_{max}} = 2 \cdot 0.8V = \boxed{1.6V}$

3)

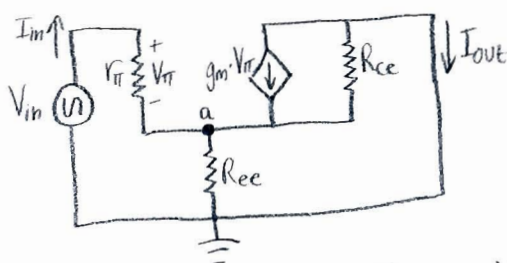

a)  $V_{\pi} = I_{in} \cdot r_{\pi}$

$$V_{in} = V_{\pi} + V_a \rightarrow V_{in} - V_{\pi} = V_a \rightarrow V_a = V_{in} - I_{in} \cdot r_{\pi}$$

$$I_{in} = \frac{V_a}{R_{ce} \parallel R_{ce}} - g_m \cdot V_{\pi} \rightarrow I_{in} = \frac{V_{in} - I_{in} \cdot r_{\pi}}{R_{ce} \parallel R_{ce}} - g_m \cdot I_{in} \cdot r_{\pi}$$

$$\Rightarrow I_{in} \cdot \left[ \frac{r_{\pi}}{R_{ce} \parallel R_{ce}} + g_m \cdot r_{\pi} + 1 \right] = \frac{V_{in}}{R_{ce} \parallel R_{ce}} \Rightarrow \frac{V_{in}}{I_{in}} = r_{\pi} + (R_{ce} \parallel R_{ce}) \cdot (g_m \cdot r_{\pi} + 1) = \boxed{r_{\pi} + (R_{ce} \parallel R_{ce}) (\beta + 1)}$$

$$I_{out} = -g_m \cdot V_{\pi} + \frac{V_a}{R_{ce}} = -g_m \cdot I_{in} \cdot r_{\pi} + \frac{V_{in} - I_{in} \cdot r_{\pi}}{R_{ce}} \Rightarrow I_{out} \cdot R_{ce} = V_{in} - I_{in} \cdot r_{\pi} \cdot [g_m R_{ce} + 1]$$

$$\rightarrow I_{out} \cdot R_{ce} = V_{in} - \frac{V_{in} \cdot r_{\pi}}{R_{in}} \cdot [g_m \cdot R_{ce} + 1] \Rightarrow I_{out} \cdot R_{ce} = V_{in} - \frac{V_{in} \cdot r_{\pi} \cdot [g_m \cdot R_{ce} + 1]}{r_{\pi} + (R_{ce} \parallel R_{ce}) (\beta + 1)}$$

$$\rightarrow I_{out} \cdot R_{ce} \cdot [r_{\pi} + (R_{ce} \parallel R_{ce}) (\beta + 1)] = V_{in} \cdot [r_{\pi} + (R_{ce} \parallel R_{ce}) (\beta + 1) - r_{\pi} \cdot (g_m \cdot R_{ce} + 1)]$$

$$\rightarrow I_{out} \cdot R_{ce} \cdot [r_{\pi} + (R_{ce} \parallel R_{ce}) (\beta + 1)] = V_{in} \cdot \left[ r_{\pi} + \frac{R_{ce} \cdot R_{ce} \cdot (\beta + 1)}{R_{ce} + R_{ce}} - \beta \cdot R_{ce} \cdot r_{\pi} \right]$$

$$\rightarrow I_{out} \cdot R_{ce} \cdot [r_{\pi} + (R_{ce} \parallel R_{ce}) (\beta + 1)] = V_{in} \cdot \left[ \frac{R_{ce} \cdot R_{ce} \cdot (\beta + 1) - \beta \cdot R_{ce} (R_{ce} + R_{ce})}{R_{ce} + R_{ce}} \right]$$


$$\rightarrow \frac{I_{out}}{V_{in}} = \left[ \frac{R_{ce} \cdot \beta + R_{ce} - \beta \cdot R_{ce} - \beta \cdot R_{ce}}{R_{ce} + R_{ce}} \right] \cdot \left[ \frac{r_{\pi} \cdot (R_{ce} + R_{ce}) + R_{ce} \cdot R_{ce} \cdot (\beta + 1)}{R_{ce} + R_{ce}} \right]^{-1}$$

3) con'd...

$$\rightarrow \frac{I_{out}}{V_{in}} = \frac{R_{ee} - \beta \cdot R_{ce}}{r_{\pi} \cdot (R_{ee} + R_{ce}) + R_{ee} \cdot R_{ce} \cdot (\beta + 1)}$$

ECE 137A Homework #2  
Winter '07

b)

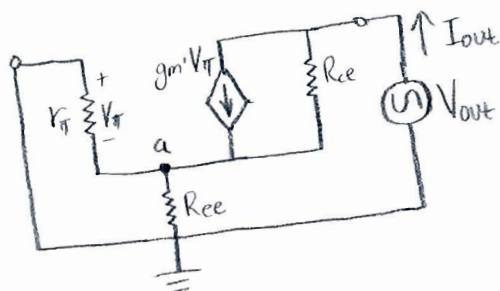

$$V_{\pi} = -V_a \quad V_a = I_{out} \cdot (R_{ee} \parallel r_{\pi})$$

$$I_{out} = \frac{V_{out} - V_a}{R_{ce}} + g_m \cdot V_{\pi}$$

$$\rightarrow I_{out} = \frac{V_{out}}{R_{ce}} - \frac{I_{out} \cdot (R_{ee} \parallel r_{\pi})}{R_{ce}} - g_m \cdot I_{out} \cdot (R_{ee} \parallel r_{\pi})$$

$$\rightarrow I_{out} \cdot [R_{ce} + (R_{ee} \parallel r_{\pi}) \cdot (1 + g_m \cdot R_{ce})] = V_{out}$$

$$\Rightarrow \frac{V_{out}}{I_{out}} = R_{ce} + (R_{ee} \parallel r_{\pi}) \cdot (1 + g_m \cdot R_{ce})$$