
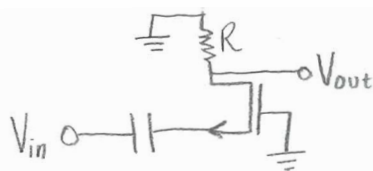


1) $R_{DS} = \infty$

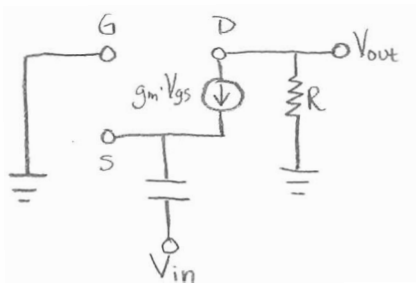

ECE 137A-HW#8
Winter '07

a)



b) $g_m = 200 \text{ mS}$, $C = 100 \text{ pF}$, $R = 1 \text{ k}\Omega$

Find $\frac{V_{out}(s)}{V_{in}(s)} \dots ?$

$V_{out} = -g_m \cdot V_{gs} \cdot R$

& $V_{gs} = 0 - (V_{in} + g_m \cdot V_{gs} \cdot \frac{1}{s \cdot C})$

$\Rightarrow V_{gs} = \frac{-V_{in}}{1 + \frac{g_m}{s \cdot C}}$

$\Rightarrow V_{out} = (-g_m \cdot R) \cdot \frac{-V_{in}}{1 + \frac{g_m}{s \cdot C}}$

$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{g_m \cdot R}{1 + \frac{g_m}{s \cdot C}} \text{ or } \frac{s \cdot g_m \cdot R}{s + \frac{g_m}{C}} \text{ or } \frac{s \cdot C \cdot R}{1 + s \cdot \frac{C}{g_m}}$

c) Find all zero & pole frequencies...


d) see page 2

$\rightarrow$ 1 zero at $s=0$ or $f=0 \text{ Hz}$


$\rightarrow$ 1 pole at $s = \frac{g_m}{C}$ or $f = 318.31 \text{ MHz}$

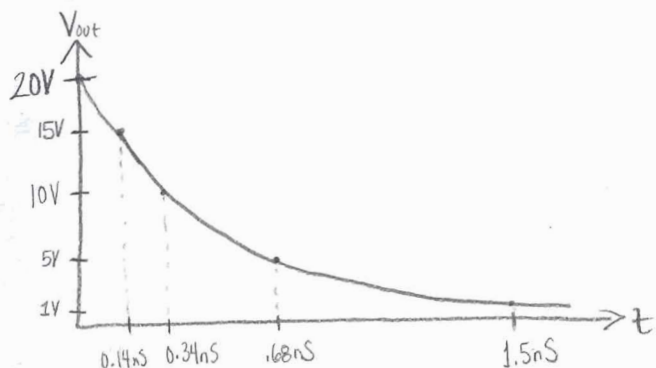e) $V_{in} = 100 \text{ mV} \cdot u(t) \Rightarrow V_{out}(s) = \frac{s \cdot g_m \cdot R}{s + \frac{g_m}{C}} \cdot \frac{0.1 \text{ V}}{s} = \frac{20 \text{ V}}{s + 2 \times 10^9 \text{ Hz}}$

$V_{out}(t) = 20 \text{ V} \cdot e^{-2 \times 10^9 \text{ Hz} \cdot t}$





Problem 1 (d)

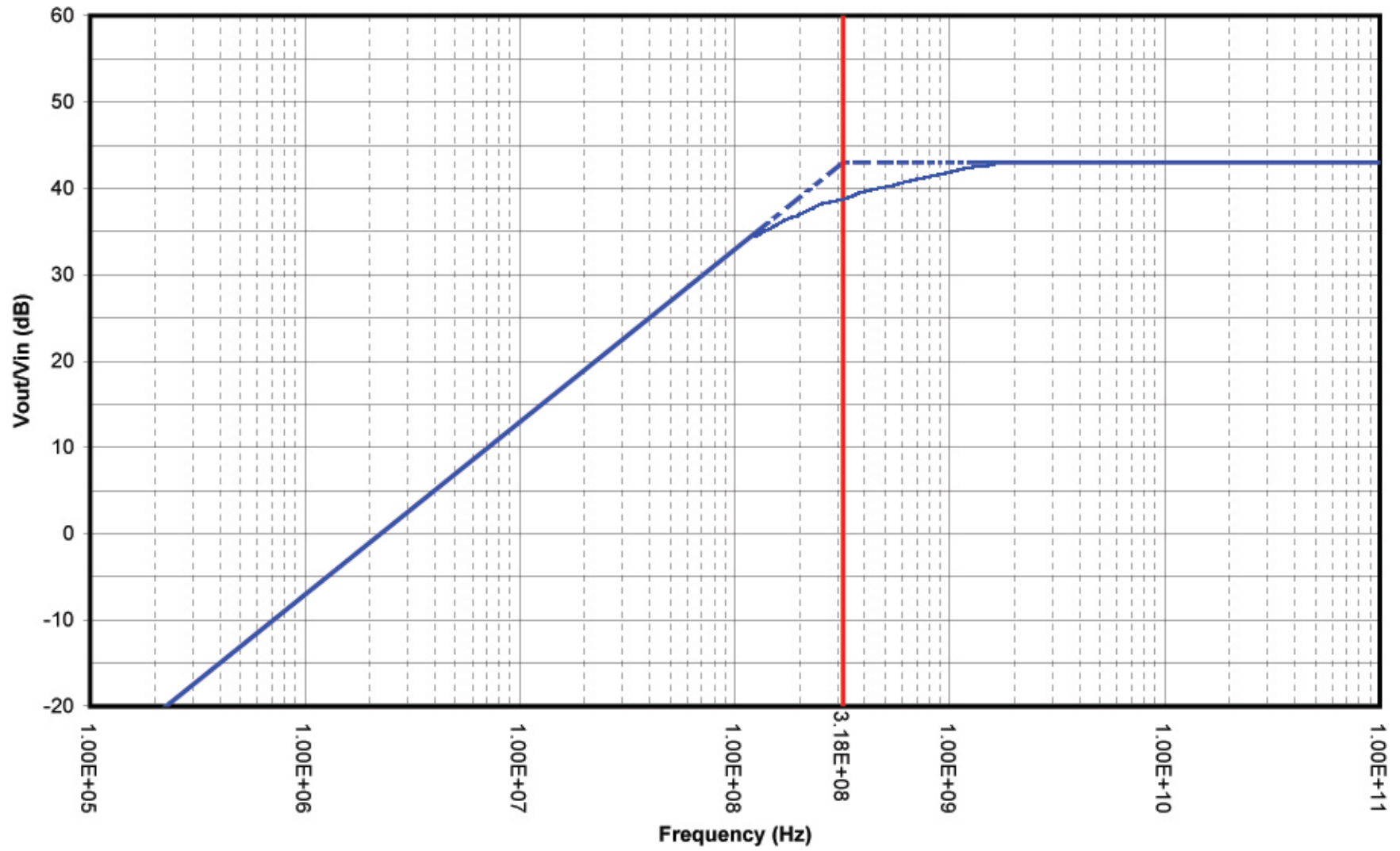

2) For Q_1 & $Q_2 \dots C_{gs} = C_{gd} = 0F$ & $R_{ds} = \infty$
 $g_{m1} = 20 \text{ mS}$, $g_{m2} = 50 \text{ mS}$, $R = 1 \text{ K}\Omega$, $C = 10 \text{ pF}$

ECE 137A - HW#8
 Winter '07

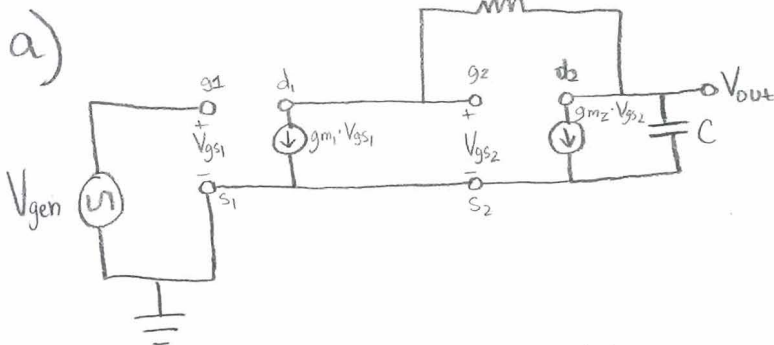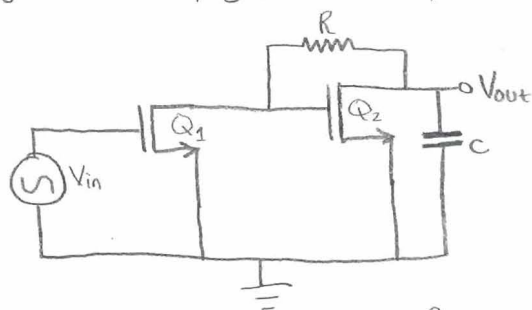

b) $V_{gs1} = V_{gen}$

$$\rightarrow \frac{V_{out} - V_{gs2}}{R} = g_{m1} \cdot V_{gen}$$

$$\Rightarrow V_{out} = g_{m1} \cdot R \cdot V_{gen} + V_{gs2}$$

$$\Rightarrow V_{gs2} \cdot g_{m2} + g_{m1} \cdot V_{gen} + V_{out} \cdot s \cdot C = 0$$

$$\Rightarrow V_{gs2} = \frac{-g_{m1} \cdot V_{gen}}{g_{m2}} - \frac{s \cdot C \cdot V_{out}}{g_{m2}} \Rightarrow V_{out} \cdot \left(1 + \frac{s \cdot C}{g_{m2}}\right) = V_{gen} \cdot \left(g_{m1} \cdot R - \frac{g_{m1}}{g_{m2}}\right)$$


$$\Rightarrow \frac{V_{out}(s)}{V_{gen}(s)} = \frac{\frac{g_{m1}}{C} \cdot (g_{m2} \cdot R - 1)}{s + \frac{g_{m2}}{C}} \quad \text{or} \quad \frac{g_{m1} \cdot R - \frac{g_{m1}}{g_{m2}}}{1 + \frac{s \cdot C}{g_{m2}}}$$

c) 1 pole @ $s = \frac{g_{m2}}{C} \Rightarrow f_p = 795.775 \text{ MHz}$

d) See page 4...

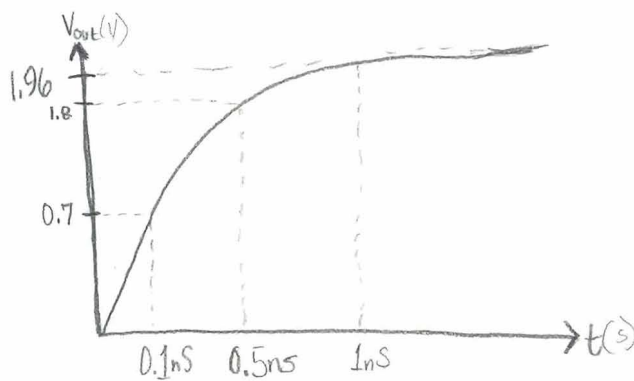e) $V_{out}(s) = \frac{g_{m1} \cdot R - \frac{g_{m1}}{g_{m2}}}{1 + \frac{s \cdot C}{g_{m2}}} \cdot \frac{0.1 \text{ V}}{s} = \frac{19.6}{1 + s \cdot 0.2 \text{ ns}} \cdot \frac{0.1 \text{ V}}{s} = \frac{9.8 \text{ E } 9}{s \cdot (s + 5 \text{ E } 9)} = \frac{-1.96}{s + 5 \text{ E } 9} + \frac{1.96}{s}$

$$\Rightarrow V_{out}(t) = 1.96 \cdot u(t) \cdot [1 - e^{-5 \text{ GHz} \cdot t}]$$



Problem 2 (d)

