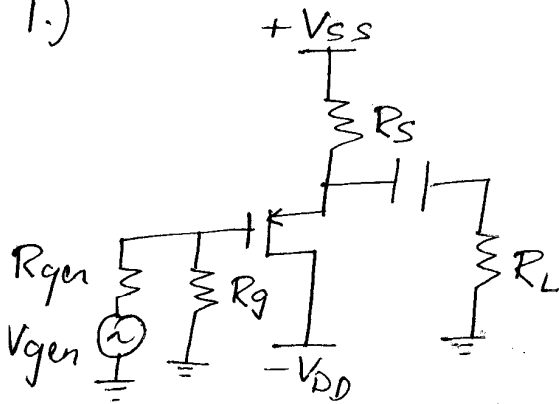


HW #4 SOLUTIONS

1.)



$$V_t = -0.5 \text{ Volt}$$

$$V_{\text{sat}} C_{ox} W_g = 10 \text{ mA/V}$$


$$V_{SS} = -V_{DD} = 2 \text{ V}$$

$$I_s = 5 \text{ mA}$$

$$R_g = 10 \text{ M}\Omega$$

$$R_{gen} = 1 \text{ M}\Omega$$

$$R_L = 100 \Omega$$

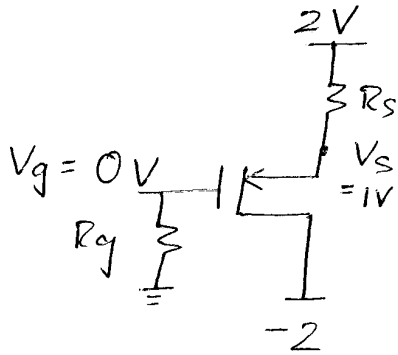DC Analysis:

$$I_s = V_{\text{sat}} C_{ox} W_g [- (V_{gs} - V_t)]$$

$$\Rightarrow 5 \text{ mA} = (10 \text{ mA/V}) (-V_{gs} + V_t)$$

$$\Rightarrow V_{gs} = -0.5 + V_t$$

$$\Rightarrow V_{gs} = -0.5 - 0.5 = \underline{\underline{-1 \text{ V}}}$$


$$\text{Now, } V_g = 0 \text{ V} \Rightarrow \underline{\underline{V_s = +1 \text{ V}}}$$

$$I_s = 5 \text{ mA} \Rightarrow \frac{V_{SS} - V_s}{R_s} = 5 \text{ mA} \Rightarrow R_s = \left(\frac{V_{SS} - V_s}{5 \text{ mA}} \right)$$

$$\Rightarrow R_s = \frac{2 - (+1)}{5 \text{ mA}} = \frac{1 \text{ V}}{5 \text{ mA}} = \boxed{200 \Omega}$$

AC Small Signal Analysis

2

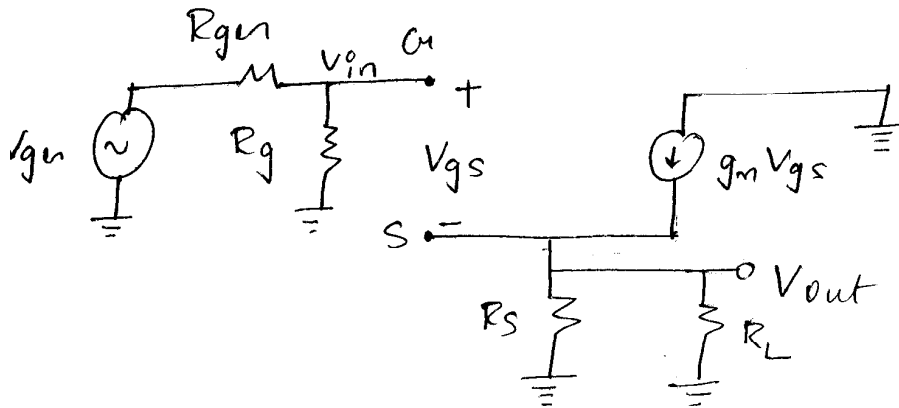

From the small signal model,
 $-V_{gs} = (V_{out} - V_{in})$

$$V_{out} = g_m V_{gs} (R_s \parallel R_L)$$
$$= g_m (V_{in} - V_{out}) (R_s \parallel R_L)$$

$$V_{out} (1 + g_m (R_s \parallel R_L)) = g_m V_{in} (R_s \parallel R_L)$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{g_m (R_s \parallel R_L)}{1 + g_m (R_s \parallel R_L)} = \frac{R_s \parallel R_L}{\frac{1}{g_m} + R_s \parallel R_L}$$

Now, $g_m = 10 \text{ mA/V}$

$$R_s \parallel R_L = 200 \Omega \parallel 100 \Omega$$
$$= 66.67$$

$$A_v = \frac{66.67}{100 + 66.6} = \underline{\underline{0.399}}$$

$$\begin{aligned}
 \text{Now, } V_{in} &= V_{gen} \left(\frac{R_g}{R_g + R_{gen}} \right) \\
 &= V_{gen} \left(\frac{10e6}{10e6 + 1e6} \right) \\
 &= V_{gen} (0.909)
 \end{aligned}$$


$$\Rightarrow \frac{V_{in}}{V_{gen}} = 0.909$$

$$\text{Now, } \frac{V_{out}}{V_{gen}} = \frac{V_{out}}{V_{in}} \cdot \frac{V_{in}}{V_{gen}} = (0.399)(0.909)$$

$$\therefore \boxed{\frac{V_{out}}{V_{gen}} = 0.362}$$

$$\text{Input impedance } Z_{in} = R_g = 10M\Omega$$

Output impedance:

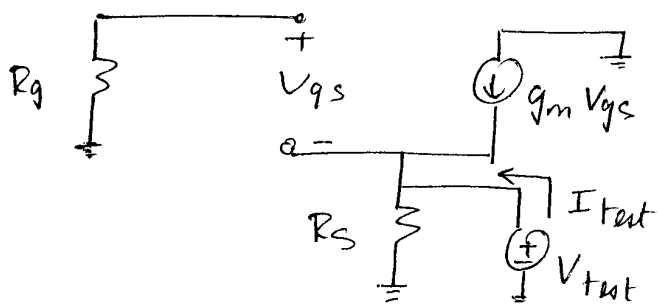

$$\text{here, } V_{gs} = -V_{test}$$

By applying KCL at output node we get


$$g_m V_{gs} + I_{test} - \frac{V_{test}}{R_s} = 0$$

$$\text{i.e. } \left(-g_m + \frac{1}{R_s} \right) V_{test} + I_{test} = 0 \Rightarrow \frac{V_{test}}{I_{test}} = \frac{1}{g_m + \frac{1}{R_s}}$$

$$Z_{out} = \frac{R_s / g_m}{R_s + \frac{1}{g_m}} = R_s \parallel \frac{1}{g_m} = 200 \parallel 100 = \underline{\underline{66.67\Omega}}$$

4)

4

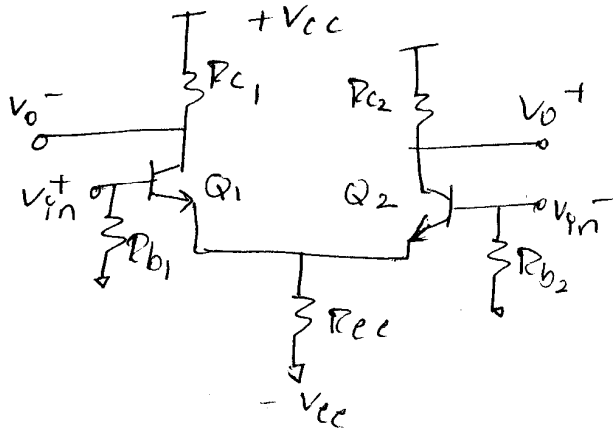

$$V_{CC} = 10V$$

$$V_{EE} = -10V$$

From datasheet

For 2N3904 BJT,

$$\beta = 130$$

$$R_{CE} = 66.6 k\Omega$$


$$I_{E1} = I_{E2} = 1mA$$

$$V_{C1} = V_{C2} = 5V$$

$$R_{B1} = R_{B2} = 10 k\Omega$$

$$R_{L1} = R_{L2} = 10 k\Omega$$

DC Analysis:

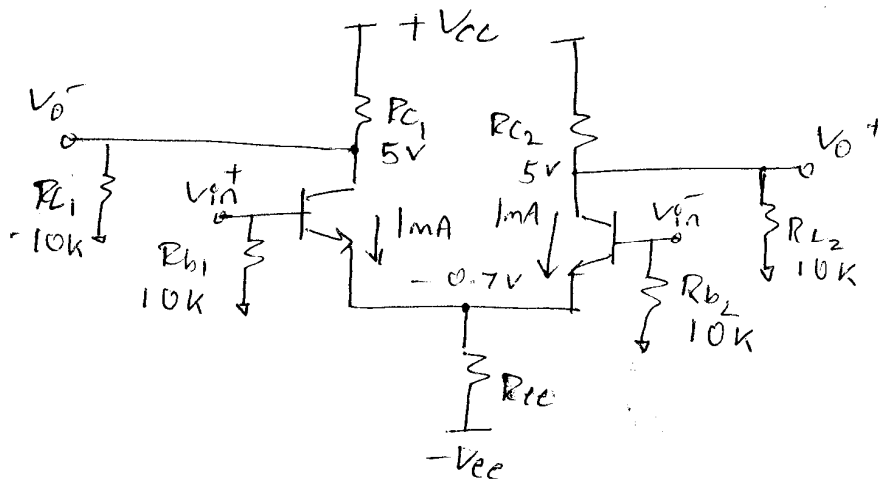

$$I_C = \alpha I_E \text{ where}$$

$$\alpha = \frac{\beta}{\beta + 1} = 0.99$$

$$\Rightarrow I_C = 0.992mA$$

$$\text{Now, } I_{RC1} = I_{C1} + \frac{V_C}{R_L}$$

$$I_{RC1} = 0.992mA + 0.5mA$$

$$I_{RC1} = 1.49mA$$

$$R_{C1} = \frac{V_{CC} - V_C}{I_{RC1}} = \left(\frac{10 - 5V}{1.49mA} \right) = \underline{\underline{3.351 k\Omega}}$$

Also,

$$V_E - 2I_{E0} R_{EE} = V_{EE}$$

$$\Rightarrow R_{EE} = \frac{V_E - V_{EE}}{2I_E} = \frac{-0.7 + 10}{2(1mA)} \Rightarrow \boxed{R_{EE} = 4.65 k\Omega}$$

AC Small Signal Analysis:


5

Differential input impedance: $\left(\frac{V_{d1/2}}{I_{in}}\right) = (\beta+1)r_e \parallel R_{b1}$

here $r_e = \frac{1}{g_m} = 26 \Omega$

$$R_{in(d)} = 2 [131(26) \parallel 10k]$$
$$= 5.08 k\Omega$$
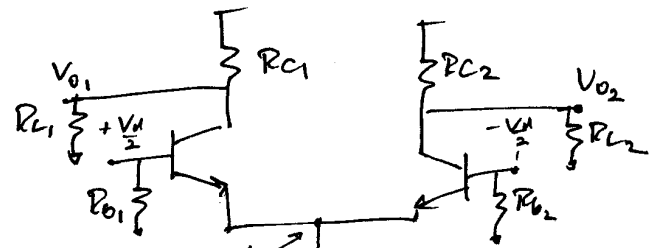
$$A_D = \frac{V_{out_L}}{V_d} = \frac{2}{2} \left(\frac{R_{L_{eq}}}{r_e} \right) \quad \text{where}$$
$$= \frac{2.4k}{2 \times 26} = \underline{\underline{46.6}}$$



This point is small signal ground.

$$R_{L_{eq}} = R_{c1} \parallel R_L \parallel R_{ee} = \frac{3.4k}{2.4k}$$


$$CMRR = \frac{R_{ee}}{r_e} = \frac{4.65k}{26} = 179.5$$

$$20 \log(CMRR) = \underline{\underline{45.08 dB}}$$

$$CMRR = \frac{A_d}{A_{cm}} \quad \text{where}$$

$$A_{cm} = \text{Common Mode Gain} = \frac{-R_{L_{eq}}}{2R_{ee} + r_e} \approx \frac{-R_{L_{eq}}}{2R_{ee}}$$

3.)

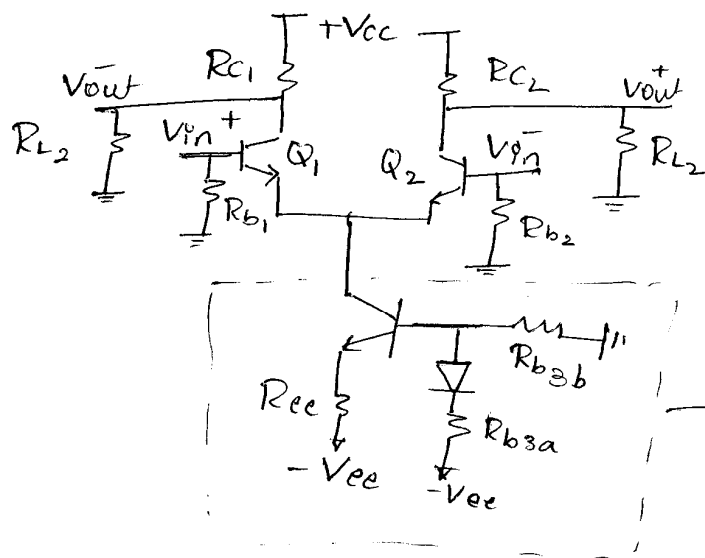

The bias currents and bias voltages on the differential pair are the same as before.

Design of the Biasing circuit is done as follows:

$$R_{C1} = R_{C2} = \frac{V_{CC} - V_C}{I_C} = 5.05 k\Omega$$

Using the values for the 2n3904 BJT's:

$$\beta_3 = 130 \Rightarrow \alpha = 0.99$$

$$I_E = \frac{I_C}{\alpha} = \underline{\underline{2.02 \text{ mA}}}$$

$$I_{E3} \cdot R_{ee3} = 0.2 \text{ V}$$

$$\Rightarrow R_{ee3} = \frac{0.2 \text{ V}}{2.02 \text{ mA}} = \underline{\underline{99 \Omega}}$$

Now, assuming drop across the diode to be 0.7 we get

$$V_{E3} = (-10 + 0.2) \text{ V} = -9.8 \text{ V}$$

$$V_{b3} = (-9.8 + 0.7) \text{ V} = -9.1 \text{ V}$$

$$V_{b3a} = (-9.1 - 0.7) \text{ V} = -9.8 \text{ V}$$

$$\Rightarrow (R_{b3a}) \cdot \left[\frac{1}{10} I_{E3} \right] = (+10 + (-9.8))$$

$$\Rightarrow R_{b3a} = \frac{0.2 \times 10}{2.02 \text{ mA}} = \underline{\underline{990 \Omega}}$$

Now, ~~low collector~~ $Q_3 =$

$$R_{b3b} = \frac{-V_{b3}}{I_{b3} + I_{R_{b3a}}} = \frac{9.1}{0.215 \text{ mA}} = \underline{\underline{41.8 \text{ k}\Omega}}$$

Now, $R_{in \text{ collector } Q_3} = \mu_{ce3} \left(1 + g_{m3} R_{EE3} \left(\frac{\mu_{be}}{\mu_{be} + R_B + R_{EE3}} \right) \right)$

where $\mu_{ce3} = 66.6 \text{ k}\Omega$ $R_{EE3} = 99 \Omega$

$$g_{m3} = \frac{I_E}{V_T} = \frac{2.02 \text{ mA}}{26 \text{ mV}} = 0.077 \text{ V}^{-1}$$


$$\mu_{be} = \beta \mu_e = 1688 \Omega$$

$$\begin{aligned} R_B &= (R_{b3a} + R_{b3b}) \parallel R_{EE3} \\ &= \left(\frac{26 \text{ mV}}{0.202 \text{ mA}} + 990 \right) \parallel 41.8 \text{ k}\Omega \\ &= 1089 \Omega \end{aligned}$$

$$\begin{aligned} R_{in \text{ collector } Q_3} &= (66.6 \text{ k}\Omega) \left(1 + 0.077(99) \left(\frac{1688}{1688 + 1089 + 99} \right) \right) \\ &= \underline{\underline{364.6 \text{ k}\Omega}} \end{aligned}$$

Now, $CMRR = \frac{R_{in \text{ collector } Q_3}}{\mu_e} = \frac{364.6 \text{ k}\Omega}{26} = \underline{\underline{14 \times 10^3}}$

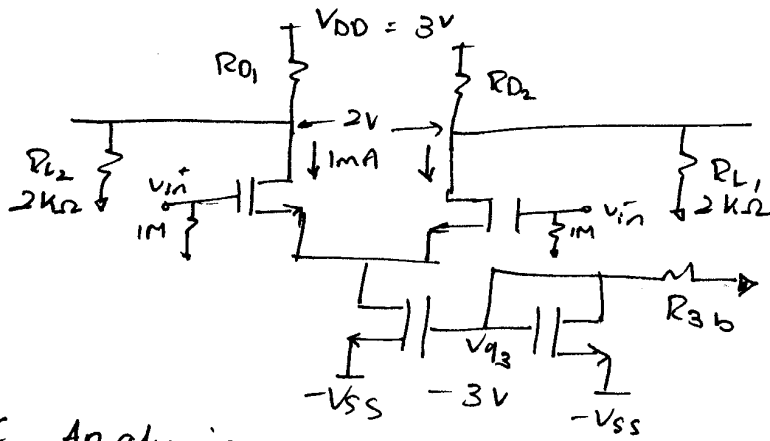We thus see that constant current biasing helps to give a higher CMRR on the differential pair.



$$V_T = 0.3V$$

$$V_{sat} C_{ox} W_g = 2mA/V$$

$$I_{D1} = I_{D2} = 1mA$$

$$R_{L1} = R_{L2} = 2k\Omega$$

$$R_{g1} = R_{g2} = 1M\Omega$$

DC Analysis:

$$I_{RD1} = I_{D1} + \frac{V_D}{R_{L1}} = 1mA + \frac{2V}{2k\Omega} = 2mA$$

$$\text{Now, } R_{D1} = \frac{V_{DD} - V_D}{I_{RD1}} = \frac{3 - 2}{2mA} = \boxed{500\Omega} = R_{D2}$$

$$\text{Now, } I_{DQ3} = V_{sat} C_{ox} W_g (V_{gs3} - V_t) = 2mA$$

$$\Rightarrow V_{gs3} - V_t = 1V \Rightarrow V_{gs3} = 1.3V$$

$$\text{Now, } V_{s3} = -3V \Rightarrow V_{g3} = 1.3V + V_s = -1.7V$$

$$\text{Now, } I_{R3b} = 2mA \Rightarrow R_{3b} = \frac{1.7V}{2mA} = \boxed{850\Omega}$$

CMRR calculation:

$$V_{s1} = V_{s2} = \frac{-I_{D1}}{V_{sat} C_{ox} W_g} + V_g - V_t = -0.5 + 0 - 0.3 = -0.8V$$

$$\text{Now, } V_{s1} = V_{D3} = -0.8V \Rightarrow V_{DS3} = +2.2V$$

$$R_{DSQ3} = \frac{\frac{1}{\lambda} + V_{DSQ3}}{I_{D3}} (1 + g_m R_{ss}) = \frac{10 + 2.2}{2mA} = 6100\Omega$$

$$CMRR = \frac{R_{ee}}{(1/g_m)} = \frac{6100}{1/(2mA/V)} = \underline{\underline{12.2}}$$

$$\text{Differential input impedance} = Z_{in(d)} = \frac{V_d}{I_d} = 2R_g = \underline{\underline{2M\Omega}}$$

$$\text{Differential gain} = A_D = -\frac{g_m}{2} (R_D || R_L || R_{DS})$$


$$\text{Now, } R_{DS} = \left(\frac{1}{\lambda} + \frac{V_{DS}}{I_D} \right) (1 + g_m R_{SS})$$

$$= \left(\frac{1 \text{ } 0\text{V} + 2.8\text{V}}{1\text{mA}} \right) (1 + 2 \frac{\text{mA}}{\text{V}} \cdot 6.1\text{k} \cdot 2)$$


$$= (12.8\text{k}) (1 + 24.4) = \underline{\underline{325.1\text{k}}}$$

$$A_D = -\frac{g_m}{2} (R_D || R_L || R_{SS}) = -\frac{2\text{m}}{2} (2\text{k} || 500 || 325.1\text{k})$$

$$= \underline{\underline{-0.4}}$$

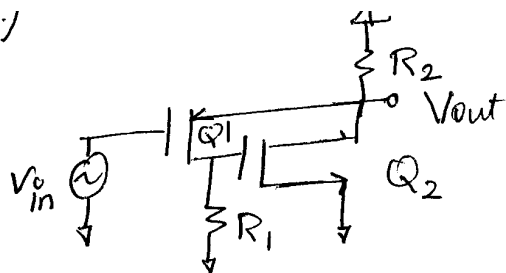

Small signal Model:

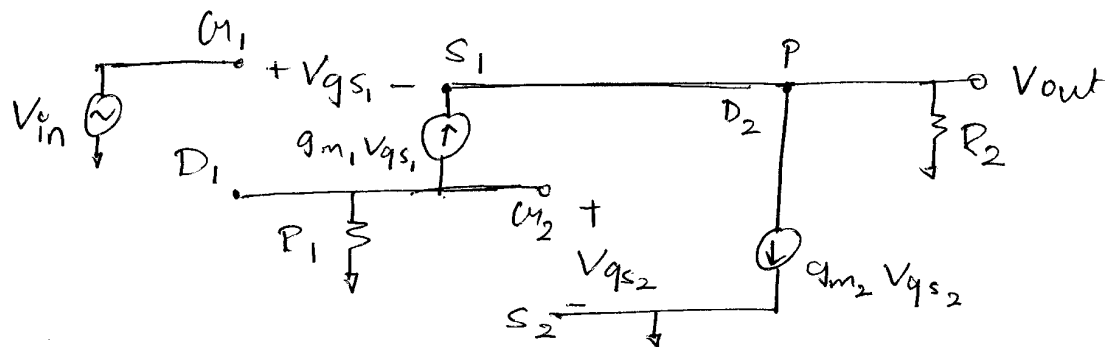

$$V_{gs1} = V_{in} - V_{out}$$

$$V_{gs2} = (g_{m1} V_{gs1}) R_1 = g_{m1} R_1 (V_{in} - V_{out})$$

Apply KCL at node P:

$$\frac{V_{out}}{R_2} + g_{m2} V_{gs2} - g_{m1} V_{gs1} = 0$$

$$\therefore \frac{V_{out}}{R_2} + g_{m2} (g_{m1} R_1) (V_{in} - V_{out}) - g_{m1} (V_{in} - V_{out}) = 0$$

$$\therefore V_{out} \left(\frac{1}{R_2} + g_{m1} g_{m2} R_1 + g_{m1} \right) + V_{in} (g_{m1} g_{m2} R_1 - g_{m1}) = 0$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{g_{m1} - g_{m1} g_{m2} R_1}{\frac{1}{R_2} + g_{m1} + g_{m1} g_{m2} R_1}$$

Substituting

$$g_{m1} = 10 \text{ mS}$$

$$g_{m2} = 100 \text{ mS}$$

$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 500 \Omega$$

$$\text{we get } \frac{V_{out}}{V_{in}} = 1.00$$