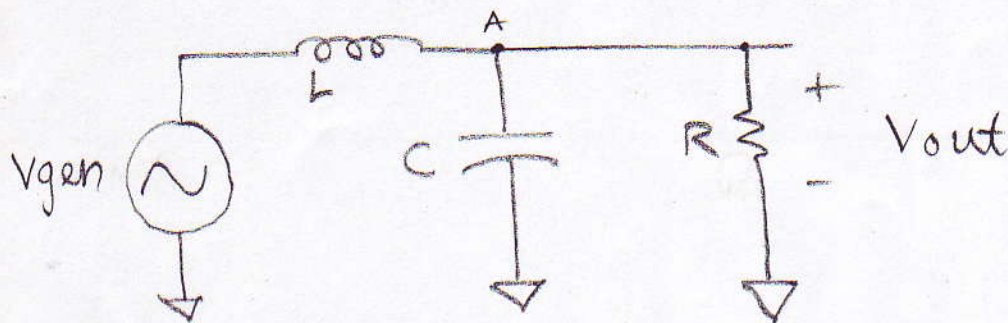


(1)



(a) Considering Node A we have $V_A = V_{out}$

$$\frac{V_{out} - V_{gen}}{Ls} + V_{out} \times sC + \frac{V_{out}}{R} = 0$$

(Equating the sum of the currents at node A to 0)

$$V_{out} \left(\frac{1}{Ls} + sC + \frac{1}{R} \right) = \frac{V_{gen}}{Ls}$$

$$V_{out} \left(\frac{R + s^2 LRC + Ls}{RLs} \right) = \frac{V_{in}}{Ls} \quad (\text{since } V_{gen} = V_{in})$$

$$\frac{V_{out}}{V_{in}} = \frac{R}{s^2 LRC + sL + R} = \frac{R}{R \left(s^2 LC + s \frac{L}{R} + 1 \right)}$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{s^2 LC + s \left(\frac{L}{R} \right) + 1} \rightarrow \textcircled{1}$$

Note that the denominator has no units because LC has units secs^2 and $\frac{L}{R}$ has a unit of secs.

(b) $R = 1000 \Omega$

$f_n = 20 \text{ GHz}$

$\zeta = 0.2$

Comparing equation ① with that of the standard form of the denominator which is $s^2 \left(\frac{1}{\omega_n^2} \right) + s \left(\frac{2\zeta}{\omega_n} \right) + 1$ we have

$$LC = \left(\frac{1}{\omega_n^2} \right) (\text{sec})^2 \rightarrow \textcircled{2}$$

$$\frac{L}{R} = \left(\frac{2\zeta}{\omega_n} \right) \text{sec} \rightarrow \textcircled{3}$$

From ③ we have $L = R \left(\frac{2\zeta}{\omega_n} \right)$

$$L = \frac{1000 \times \cancel{2} \times 0.2}{\cancel{2} \times \pi \times 20 \times 10^9} \frac{\Omega}{\text{rad/sec}}$$

$$= 1000 \times 0.159 \times \frac{2}{10^{11}} \Omega \text{ sec}$$

$$L = 3.18 \times 10^{-9} \text{ H} \quad \left(\because \Omega \text{ sec} = \text{H} \right)$$

From (2)

$$\begin{aligned} \text{units} \left\{ \begin{array}{l} IR = L \times \frac{di}{dt} \\ \frac{\text{C}}{\text{s}} \Omega = L \times \frac{\text{C}}{\text{s}^2} \end{array} \right. ; \text{C} - \text{Coulomb} \\ \text{s} - \text{second} \end{aligned}$$

$$C = \frac{1}{\omega^2 \times L} \left(\frac{\text{sec}^2}{\text{H}} \right) = \frac{1}{(2\pi(20 \times 10^9))^2 (3.18 \times 10^{-9})} \text{ F}$$

$$C = \frac{1}{4\pi^2 \times 400 \times 10^{18} \times \frac{1}{\pi} \times 10^{-8}} \text{ F}$$

$$= \frac{1}{2\pi} \times \frac{1}{2\pi} \times \frac{10^{-10}}{400 \times \frac{1}{\pi}} \text{ F} \quad \left(\because 0.318 = \frac{1}{\pi} \right)$$

$$C = \frac{0.159}{800} \times 10^{-10} \text{ F} \quad (F \rightarrow \text{Farad})$$

$$C = 1.9875 \times 10^{-14} \text{ F} = 19.87 \times 10^{-15} \text{ F} \approx 20 \text{ fF}$$

$$L = 3.18 \times 10^{-9} \text{ H} = 3.18 \text{ nH} \quad (\text{f - femto})$$

- (c) The Bode plot and the phase of the frequency response are shown in the next page. The poles are complex and hence there is a single roll off of 40 dB/dec.
- (d) The root locus is shown next

Note that in the transfer function there is no zero. The poles are given by

$$(\omega_n \zeta, \omega_n \sqrt{1-\zeta^2}) \text{ and } (-\omega_n \zeta, -\omega_n \sqrt{1-\zeta^2})$$

$$\omega_n \zeta = 2\pi \times 20 \times 10^9 \times 0.2 \frac{\text{rad}}{\text{sec}}$$

$$= 8\pi \times 10^9 \frac{\text{rad}}{\text{sec}}$$

$$\omega_n \zeta = 2.51327 \times 10^{10} \frac{\text{rad}}{\text{sec}} ; f_n \zeta = 4 \text{ GHz}$$

$$\omega_n \sqrt{1-\zeta^2} = 2\pi \times 20 \times 10^9 \times \sqrt{1-0.04} \frac{\text{rad}}{\text{sec}}$$

$$= 1.23125 \times 10^{11} \text{ rad/sec}$$

$$f_n \sqrt{1-\zeta^2} = 19.6 \text{ GHz}$$

The step response is shown on page-9
corresponding to $V_{in}(t) = 2.5 u(t)$

$$V_{out}(s) = V_{in}(s) \times \frac{1}{s^2 \left(\frac{1}{\omega_n^2} \right) + s \left(\frac{2\zeta}{\omega_n} \right) + 1}$$

$$V_{out}(s) = 2.5 \times \frac{1}{s} \times \frac{1}{s^2 \left(\frac{1}{\omega_n^2} \right) + s \left(\frac{2\zeta}{\omega_n} \right) + 1}$$

$$V_{out}(t) = 2.5 \left[1 - e^{-\sigma t} \left(\cos \omega_d t + \frac{\sigma}{\omega_d} \sin(\omega_d t) \right) \right]$$

$$\text{where } \sigma = \omega_n \zeta = 2.5 / 327 \times 10^{10} \text{ rad/sec}$$


$$\omega_d = \omega_n \sqrt{1 - \zeta^2} = 1.23 / 25 \times 10^{11} \text{ rad/sec}$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{\omega_n^2}{(s + \sigma)^2 + \omega_d^2}$$


$$f_n \zeta = 4 \text{ GHz}$$

$$f_n \sqrt{1 - \zeta^2} = 19.6 \text{ GHz}$$

Problem 1 - Magnitude response

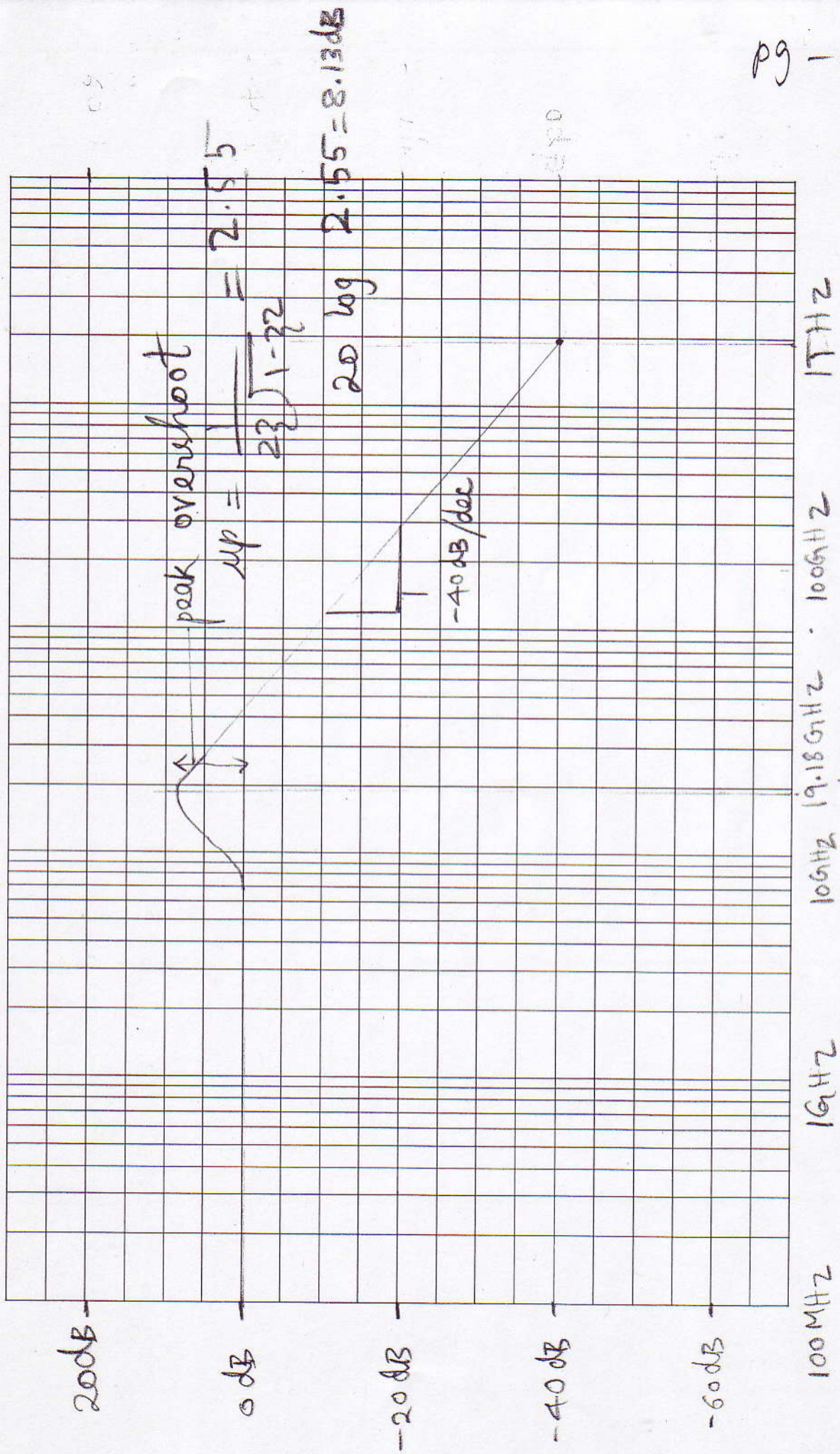


Problem 1 - Phase Response.

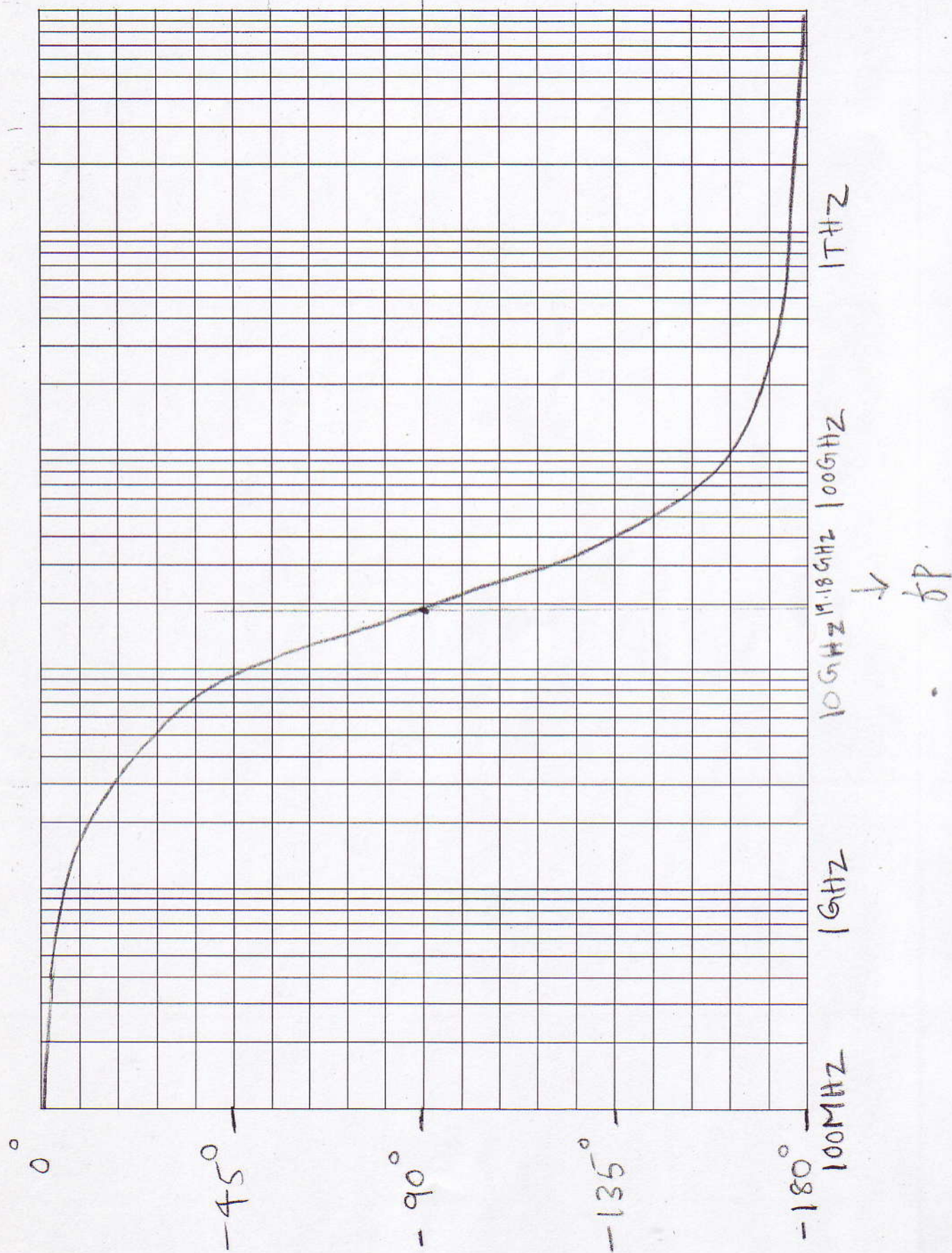


Problem 1 - Root locus

pg-8

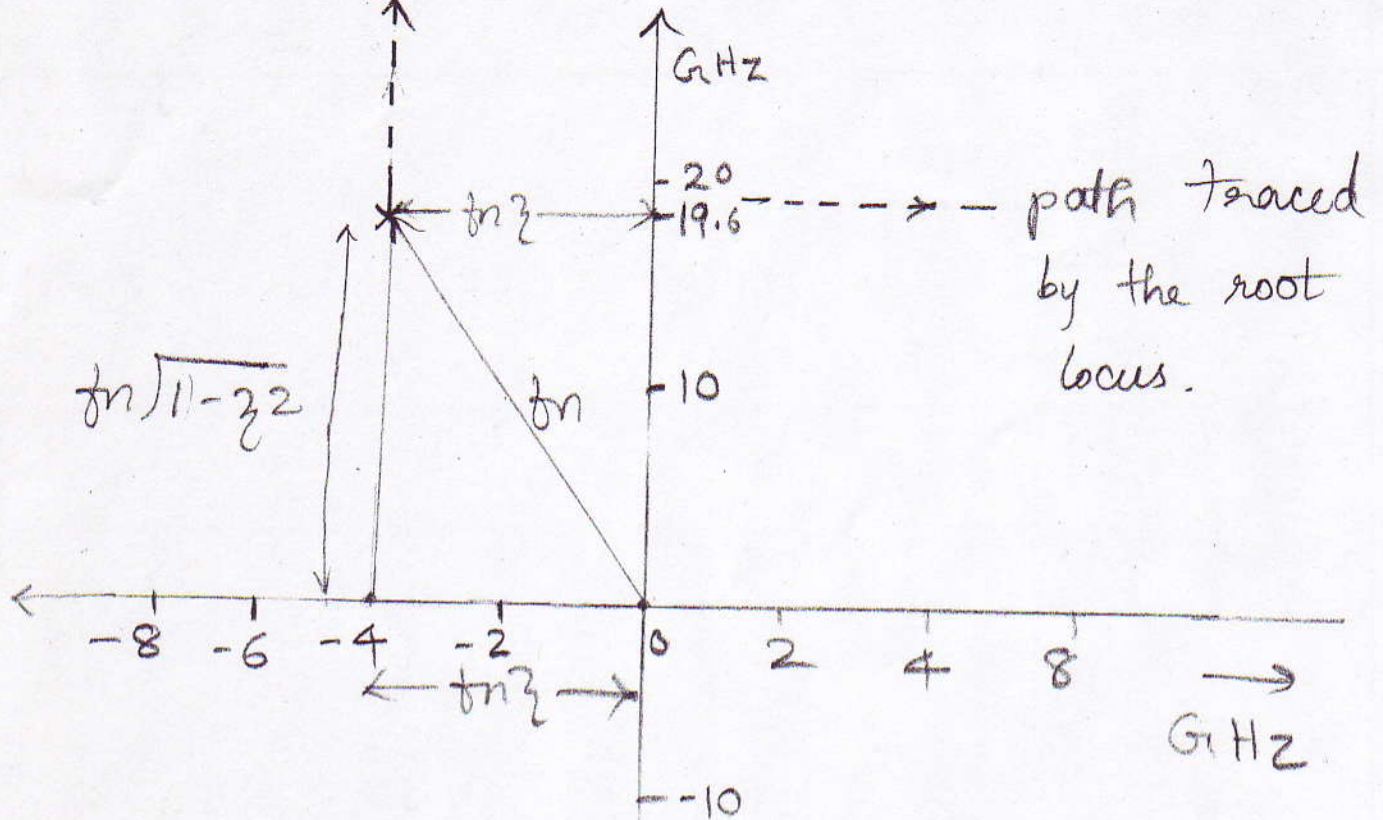

$$\begin{aligned} \zeta n &= 4 \text{ GHz} \\ \zeta n &= 20 \text{ GHz} \\ \zeta n \sqrt{1-\zeta^2} &= 19.6 \text{ GHz} \end{aligned}$$

Problem 1 - Step response

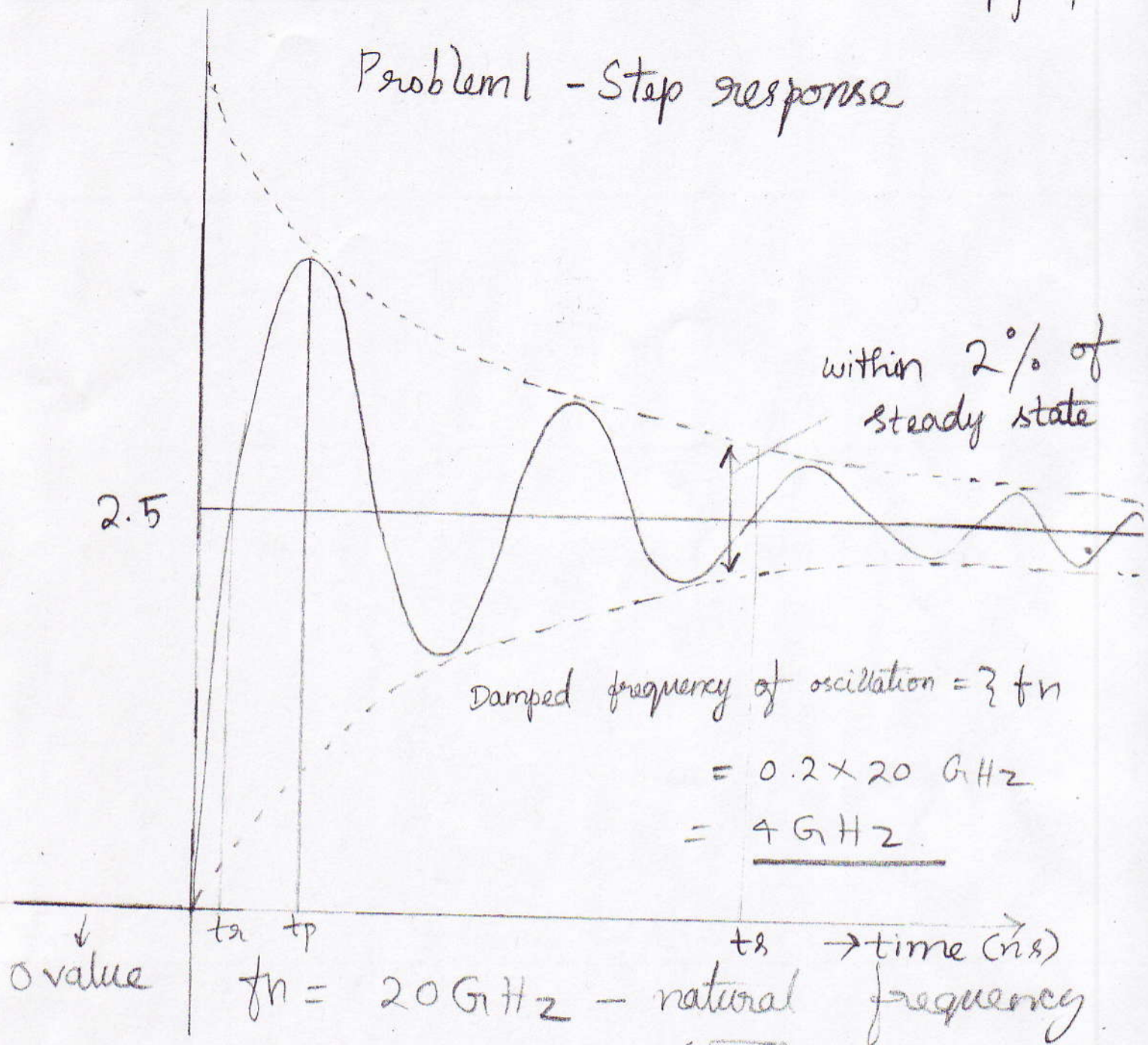

$$\text{Rise time } t_r = \left(\frac{\pi - \theta}{\omega_d} \right) s = \left(\frac{\pi - \tan^{-1}\left(\frac{\sqrt{1-\zeta^2}}{\zeta}\right)}{\omega_d} \right) s = \left(\frac{3.14 - 1.37}{1.23 \times 10^{11}} \right) s = \underline{0.014 \text{ ns}}$$


$$\text{Peak time } t_p = \left(\frac{\pi}{\omega_n \sqrt{1-\zeta^2}} \right) s = \frac{\pi}{\omega_d} s = \frac{3.14}{1.23 \times 10^{11}} = 2.55 \times 10^{-11} s = \underline{0.025 \text{ ns}}$$

$$\text{Settling time} = \left(\frac{4}{3 \omega_n} \right) s = \left(\frac{4}{2.5 \times 10^{10}} \right) s = 1.59 \times 10^{-10} s = \underline{1.59 \text{ ns}}$$

Bode plot

$$\omega_p = \frac{1}{2\sqrt{1-\zeta^2}} = 2.55$$

peak overshoot ≈ 8.1 dB

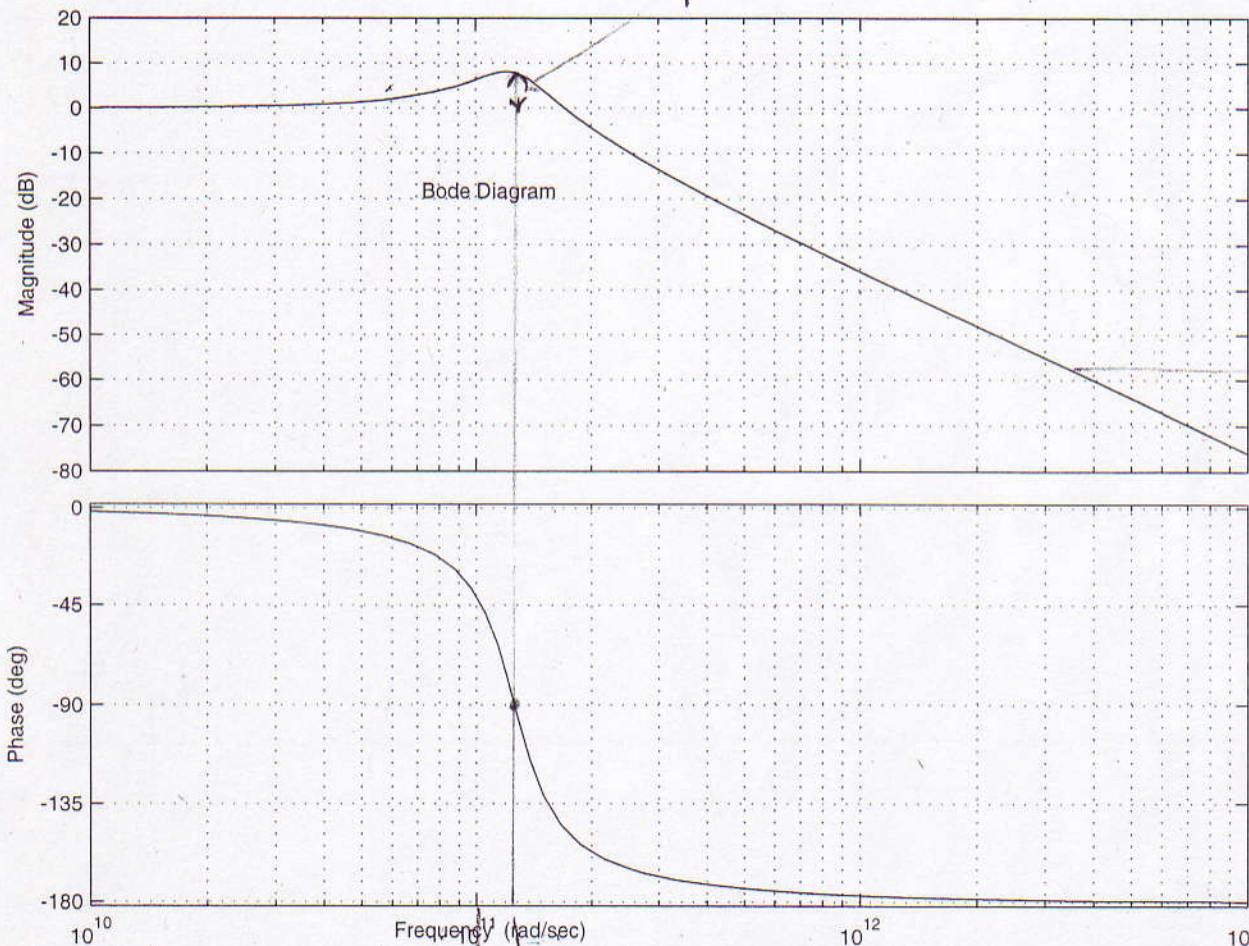

$\rightarrow 40 \text{ dB}$
decade

1) Phase at $\omega_p = -90^\circ$ $\rightarrow 1.20532 \times 10^{11} \frac{\text{rad}}{\text{sec}}$


2) There is a single roll off at ω_p

$$3) \omega_p = \omega_n \sqrt{1-\zeta^2} = 2\pi \times 20 \times 10^9 \times \sqrt{1-0.08}$$

$$= 12.0532 \times 10^{11}$$


$$\omega_p = 1.20532 \times 10^{11} \text{ rad/sec}$$

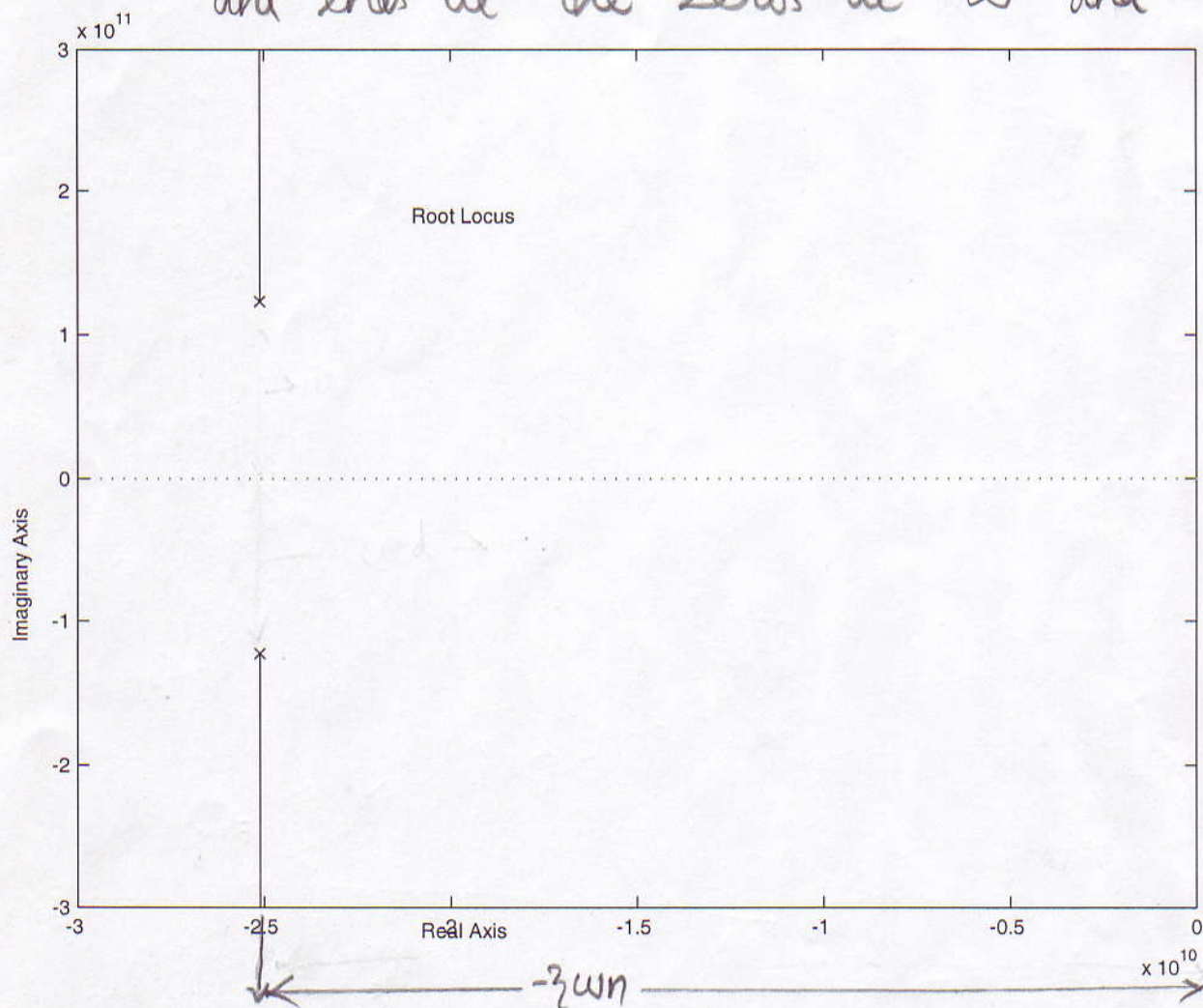
Root locus - starts at the poles and ends at the zeros at ∞ and $-\infty$.




$\times$ - poles
 distand of poles from x axis = $\omega_n \sqrt{1 - \zeta^2}$
 $= 1.23125 \times 10^{11} \frac{\text{rad}}{\text{sec}}$

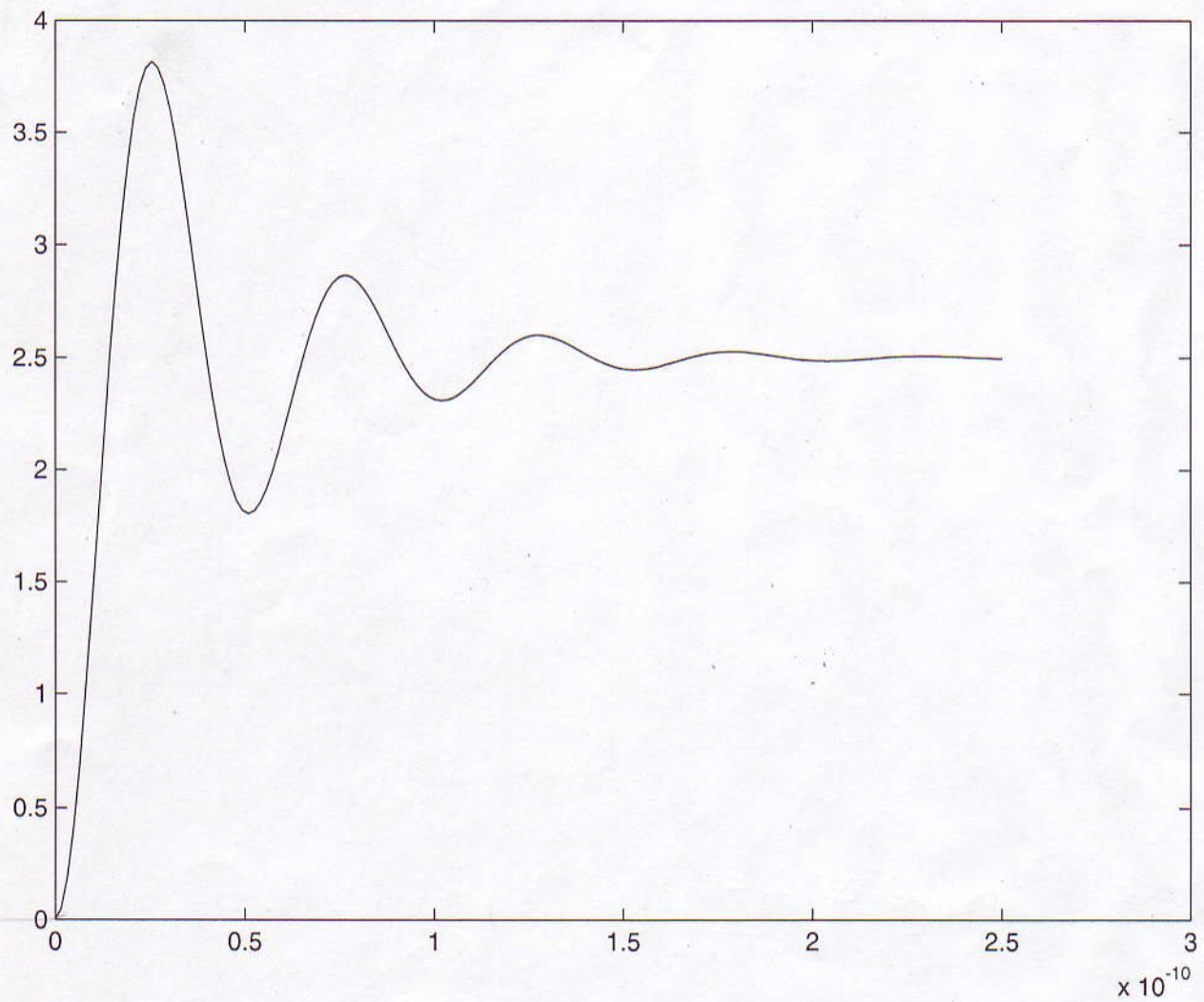Step response corresponding to $v_{in} = 2.5 u(t)$



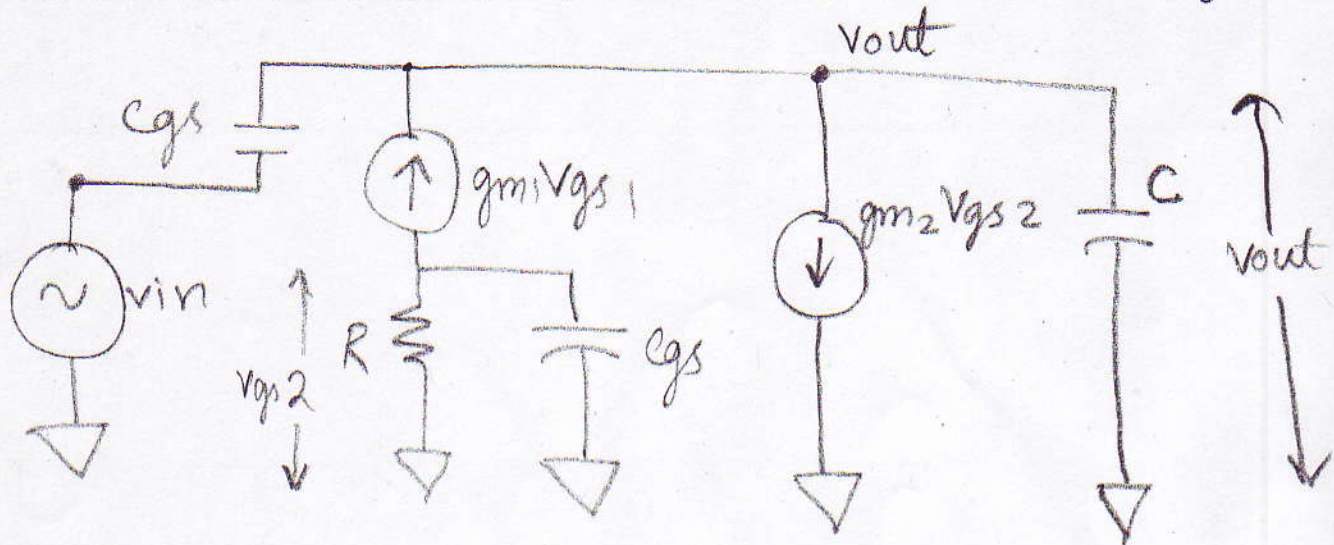

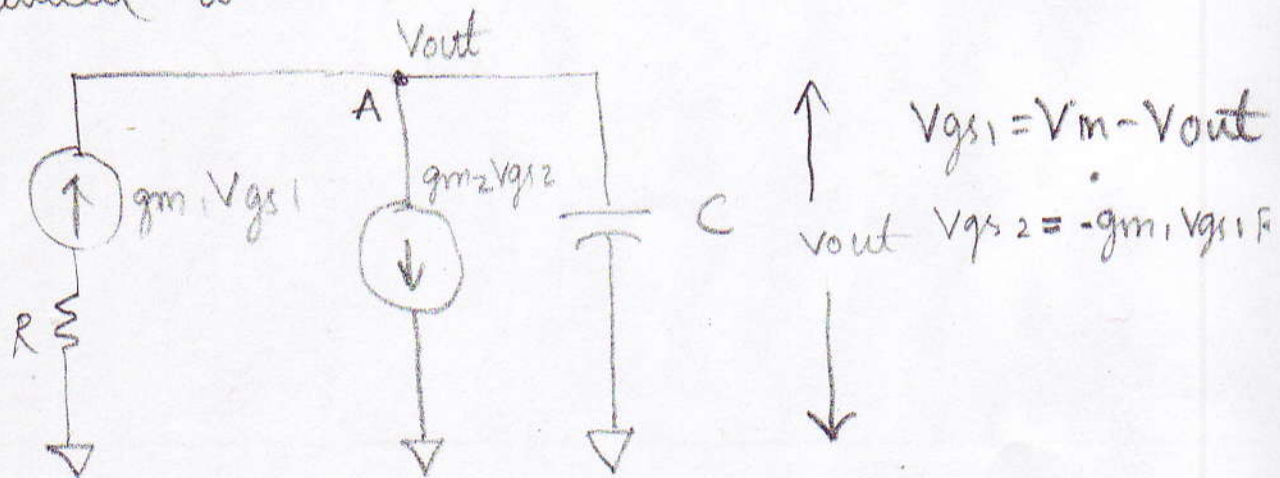Since $C_{gs} = 0$ we have the circuit reduced to



Applying Nodal analysis at node A and equating the currents to 0 we have

$$v_{out}(sC) + g_{m2}V_{gs2} - g_{m1}V_{gs1} = 0$$

$$v_{out} = \frac{V_{gs1} g_{m1} - V_{gs2} g_{m2}}{sC} \rightarrow \textcircled{1}$$

From the circuit it can be seen that

$$V_{gs1} = V_{in} - V_{out}$$

and

$$V_{gs2} = -g_{m1} V_{gs1} \times R = -g_{m1} R (V_{in} - V_{out})$$

From equation (1)

$$V_{out} = \frac{1}{sC} \left((V_{in} - V_{out}) g_{m1} + g_{m1} R (V_{in} - V_{out}) \times g_{m2} \right)$$

$$V_{out} \left(\frac{1}{sC} (g_{m1} + g_{m1} g_{m2} R) + 1 \right) = \frac{1}{sC} (g_{m1} + g_{m1} g_{m2} R) V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{g_{m1}}{sC} (1 + g_{m2} R)}{1 + \frac{g_{m1}}{sC} (1 + g_{m2} R)} \quad \text{no units}$$

$$g_{m1} = g_{m2} = 100 \text{ mS}$$

$$R = 10 \text{ k}\Omega$$

$$C = 1 \text{ pF} = 10^{-12} \text{ F}$$

It can be seen that the transfer function is that of a buffer.

$$\begin{aligned}
 \frac{V_{out}(s)}{V_{in}(s)} &= \frac{100 \times 10^{-3}}{10^{-12} \times s} \left(1 + \underbrace{100 \times 10^{-3} \times 10 \times 10^3}_{\text{no units}} \right) \\
 &= \frac{1 + \frac{100 \times 10^{-3}}{10^{-12} \times s} \left(1 + \underbrace{100 \times 10^{-3} \times 10 \times 10^3}_{\text{no units}} \right)}{s} \\
 &= \frac{10^{14} (1001) \times 10^{-3}}{s (1 + 10^{14} (1001) \times 10^{-3})} \quad \text{no units} \\
 &= \frac{10^{14} (1.001)}{s + 10^{14} (1.001)} \quad \text{no units}
 \end{aligned}$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{10^{14}}{s + 10^{14}}$$

note: $g_m \times R$ - No units
 $\frac{g_m}{C_s} = \frac{1}{RC_s}$ - No units
 ($RC \rightarrow \text{units} - \text{secs}$
 $s \rightarrow \text{units} - \frac{1}{\text{secs}}$)

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{1 + \frac{s}{10^{14}}} \rightarrow \textcircled{2}$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{1 + j \times \left(\frac{\omega}{\omega_0} \right)} \rightarrow \textcircled{3}$$

Comparing (2) and (3) we have

$$\omega_o = 10^{14} \text{ rad/sec} ; f_o = 16 \times 10^{12} \text{ Hz}$$

$$f_o = 16 \text{ THz}$$


$$\omega_p = 10^{14} \text{ rad/sec} ; f_p = 16 \text{ THz}$$

(c) The root locus is shown in the next page followed by (d) the Bode plot.

The pole is present at -10^{14} rad/sec .
There is no finite zero in the transfer function.

Problem 2 - Magnitude response

pg - 157

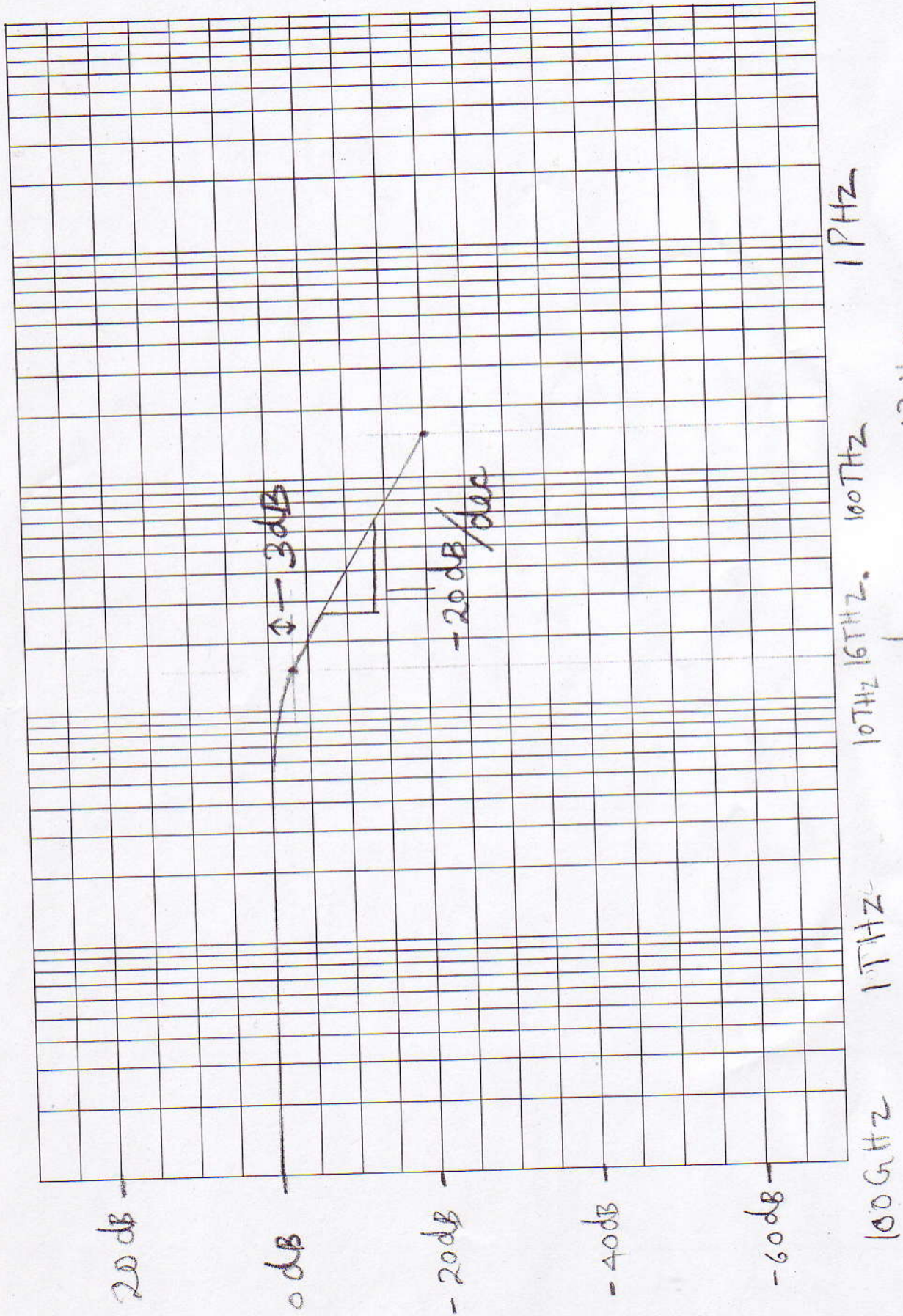


$$f_p = 16 \times 10^{12} \text{ Hz}$$

$$f_0 = 16 \text{ THz}$$

Problem 2 - Phase response

pg-18

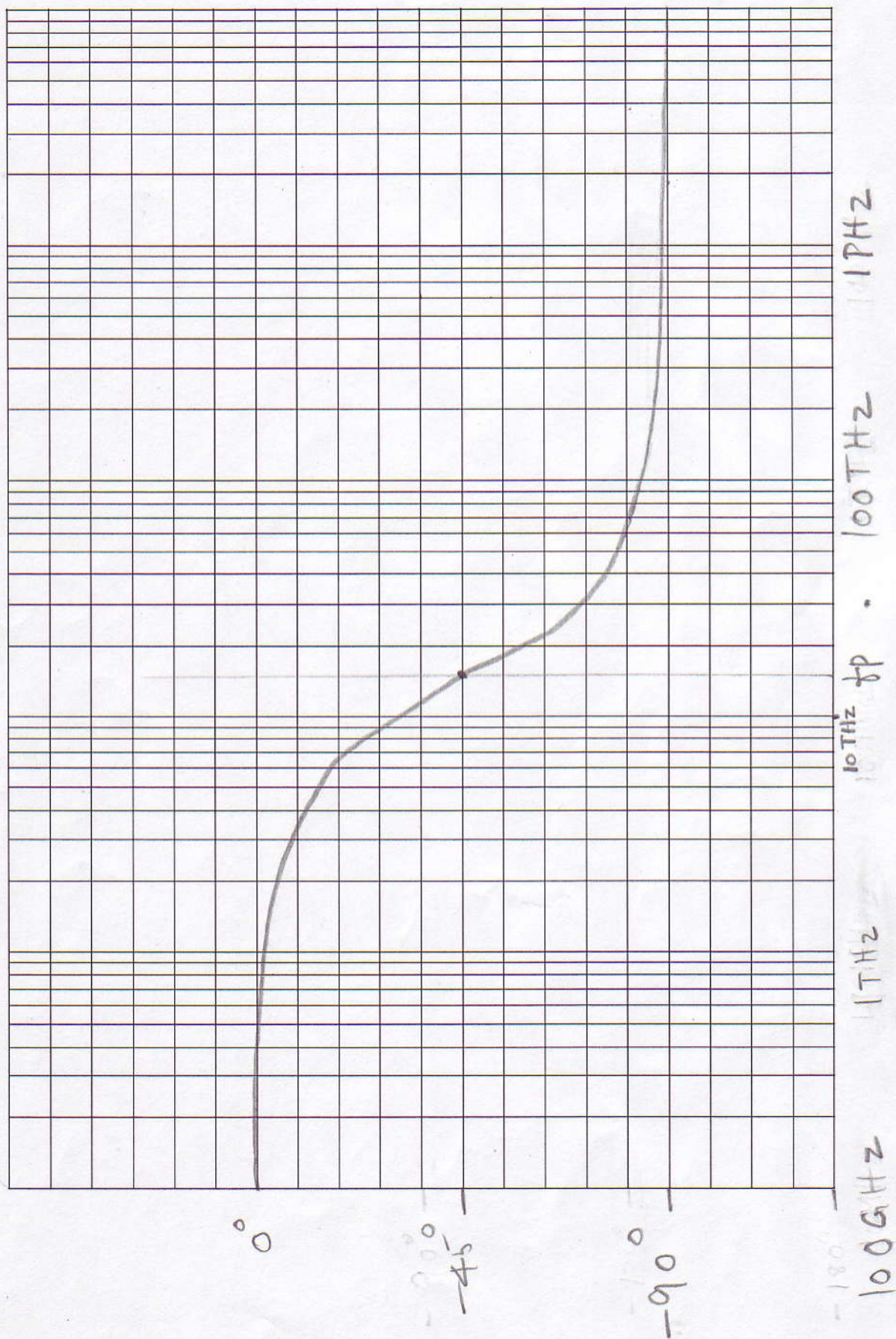


$$f_p = 1.6 \times 10^{13} \text{ Hz} = 16 \times 10^{12} \text{ Hz} = 16 \text{ THz}$$

Problem 2

pg-19

Root locus


--- ← --- root locus

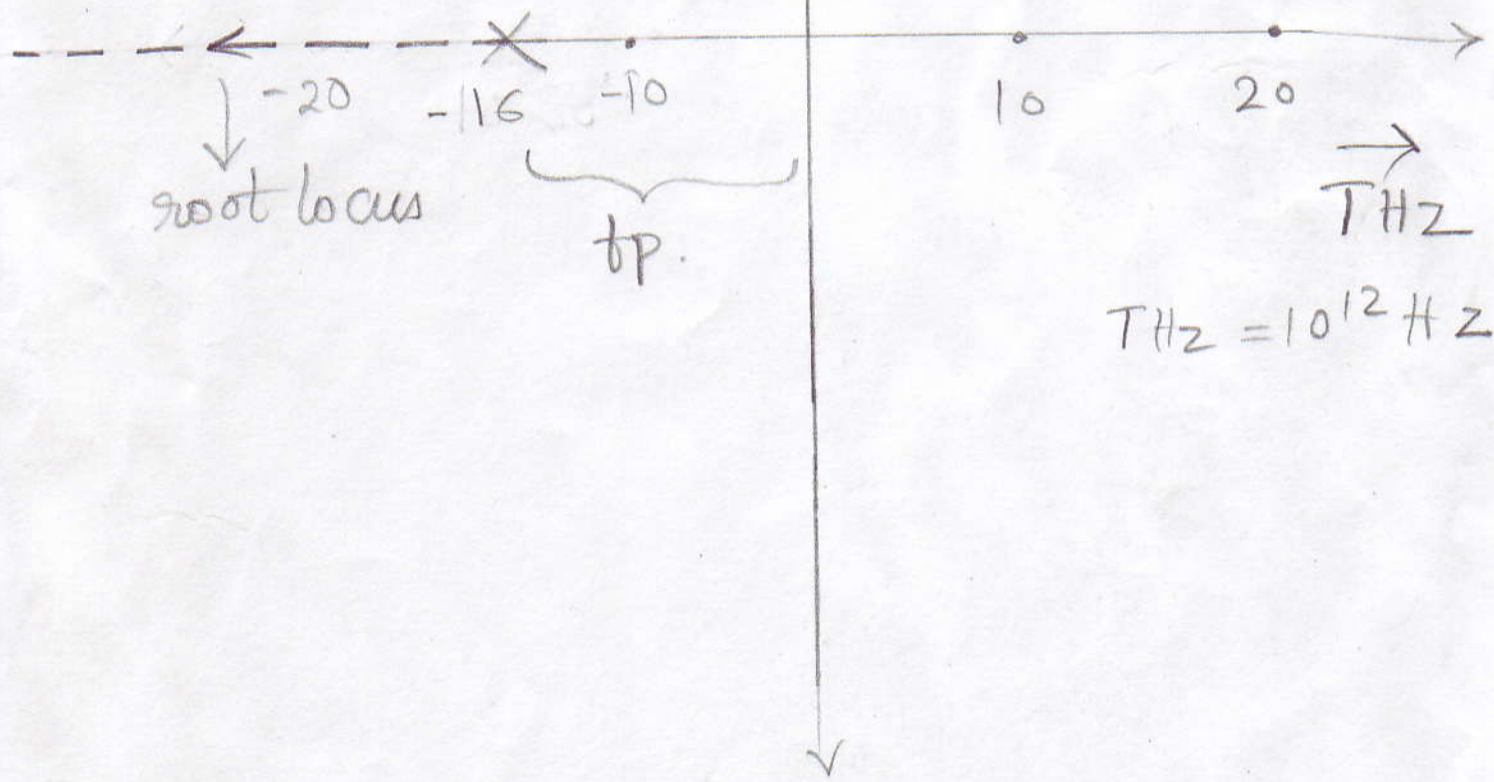

→ THz

$$THz = 10^{12} Hz$$

Problem 2 Step response

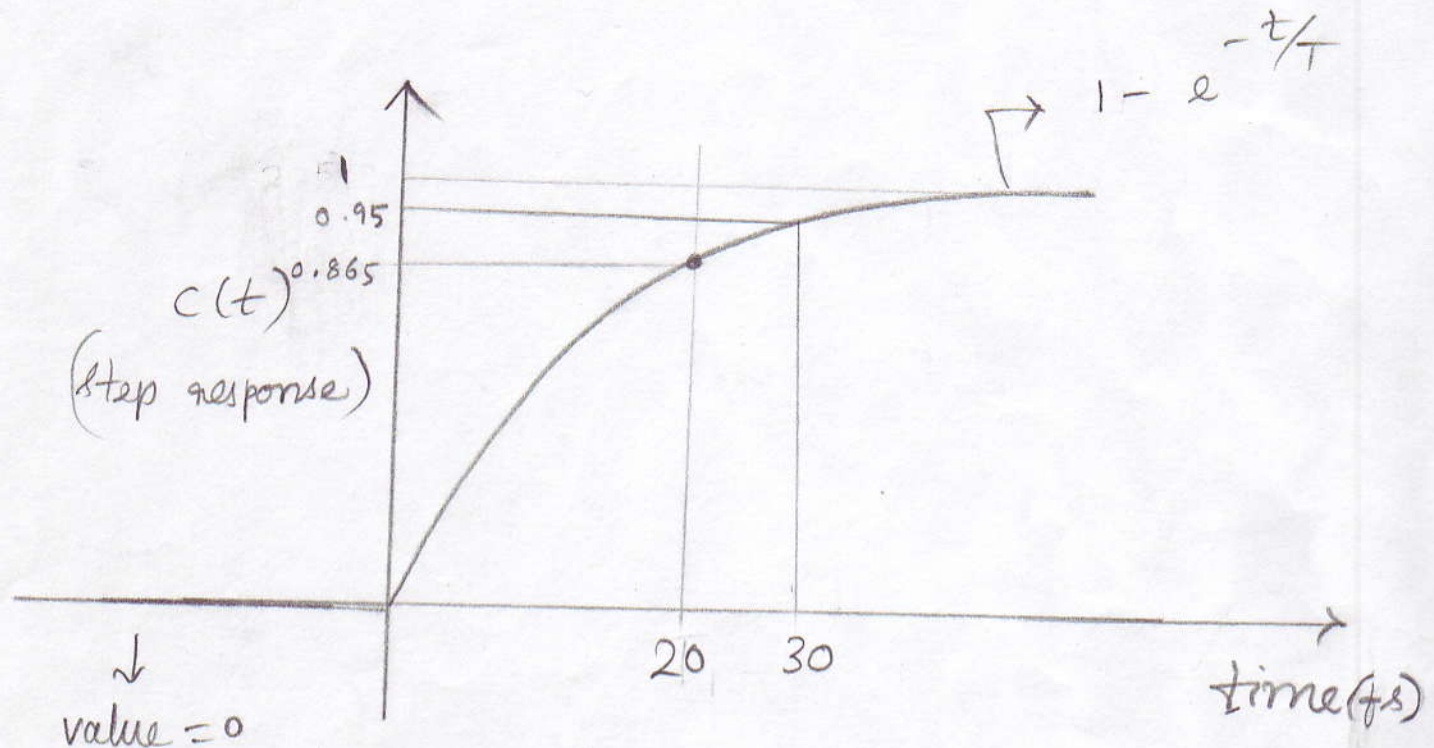

$$T = \frac{1}{10^{14}} \text{ secs}$$

$$T = 1 \times 10^{-14} \text{ secs.}$$

$$T = 10 \times 10^{-15} \text{ secs} = 10 \text{ f secs}$$

$$f = \text{fermto} = 10^{-15}$$


when $t = T$, $c(t) = 1 - e^{-1} = 0.632$

$t = 2T$, $c(t) = 1 - e^{-2} = 0.865$

$t = 3T$, $c(t) = 1 - e^{-3} = 0.95$

$t = \infty$, $c(t) = 1 - e^{-\infty} = 1$


Bode plot

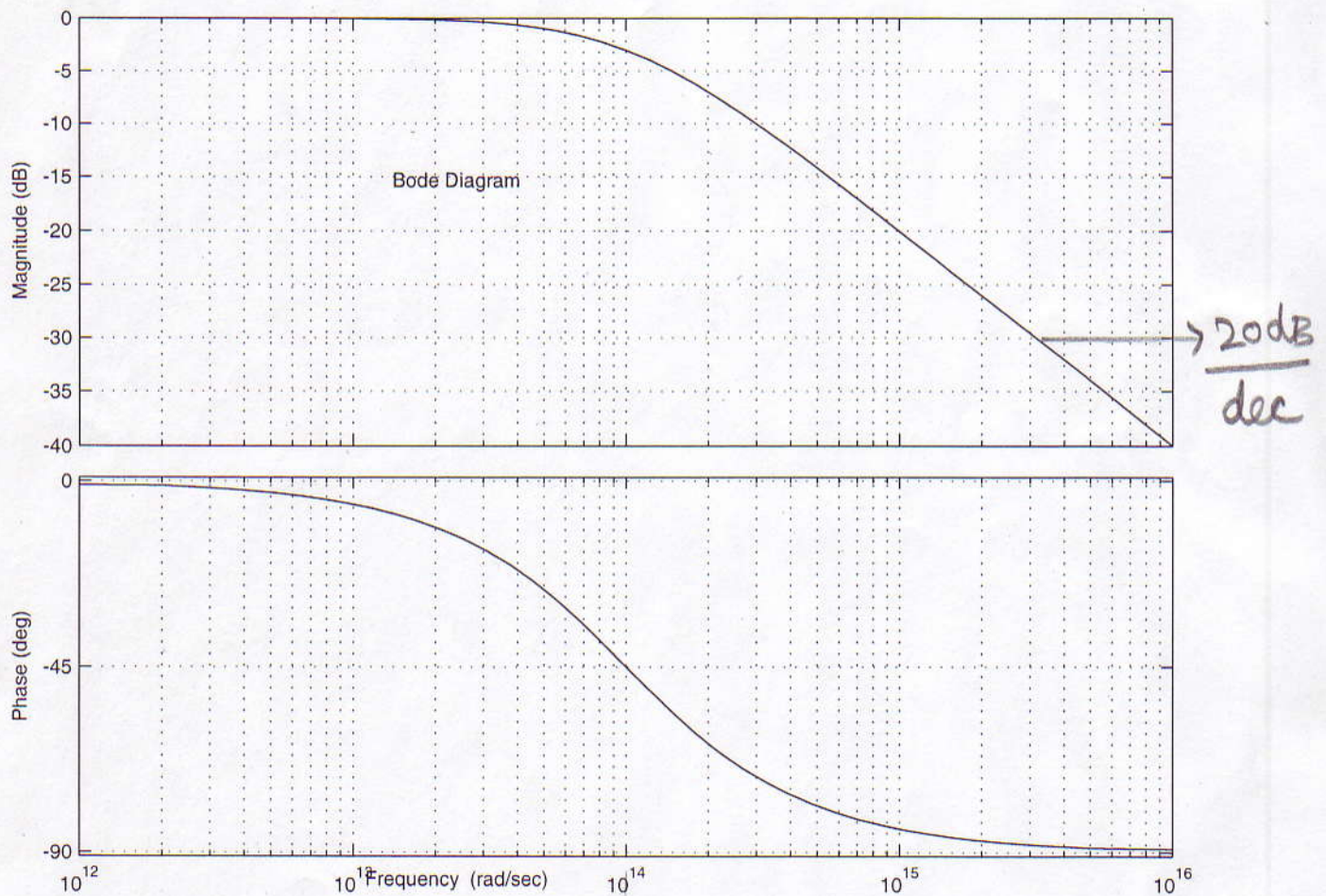

$\downarrow$ pole
 $\text{pole} = 10^{14} \text{ rad/sec} = \omega_p$


Note the phase at $\omega_p = -45^\circ$
 corresponding to $\phi = \tan^{-1}\left(\frac{\omega}{\omega_p}\right)$

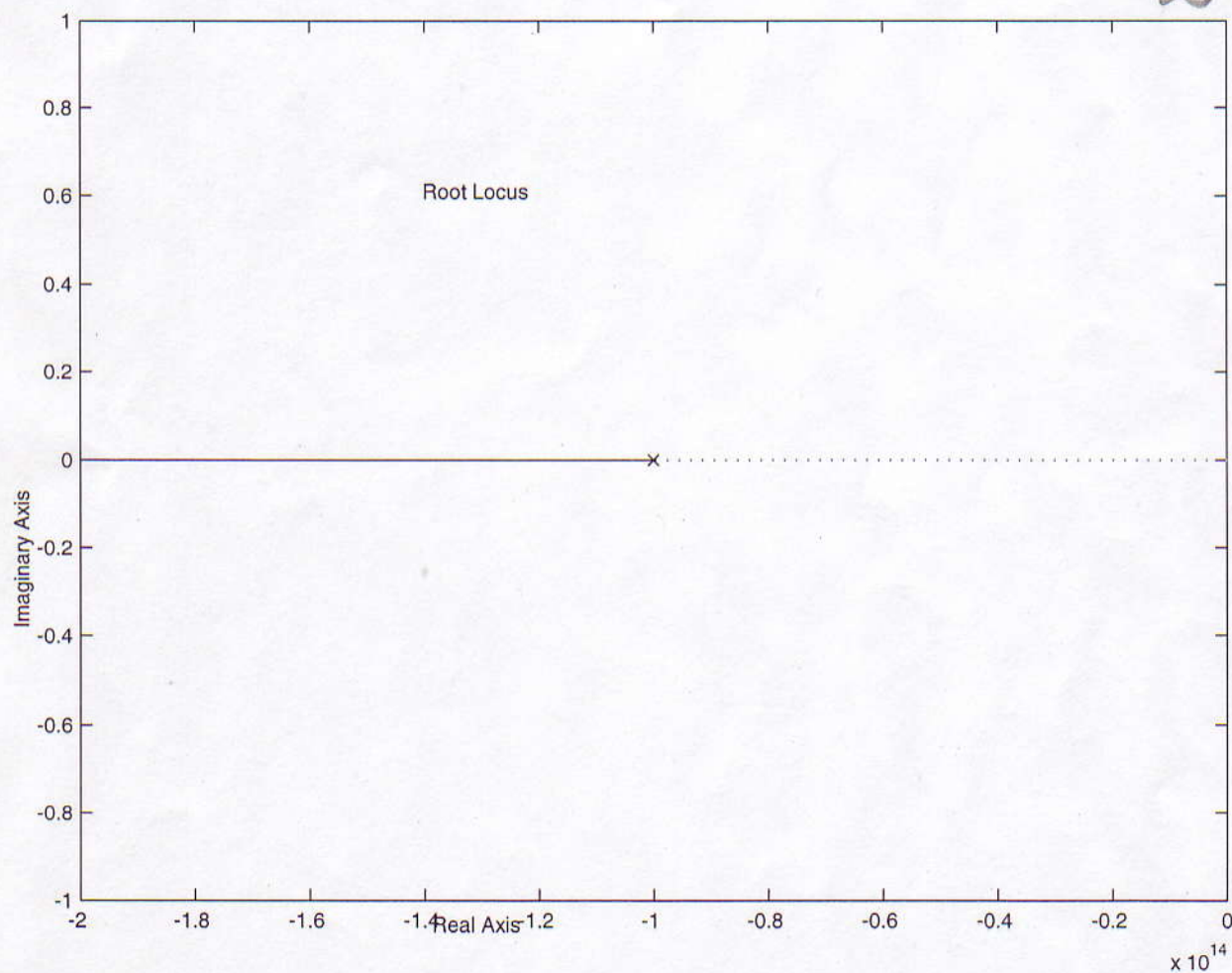Root locus
starts at the pole and ends at the zero at $-\infty$.



pole is at -10^{14} rad/sec.

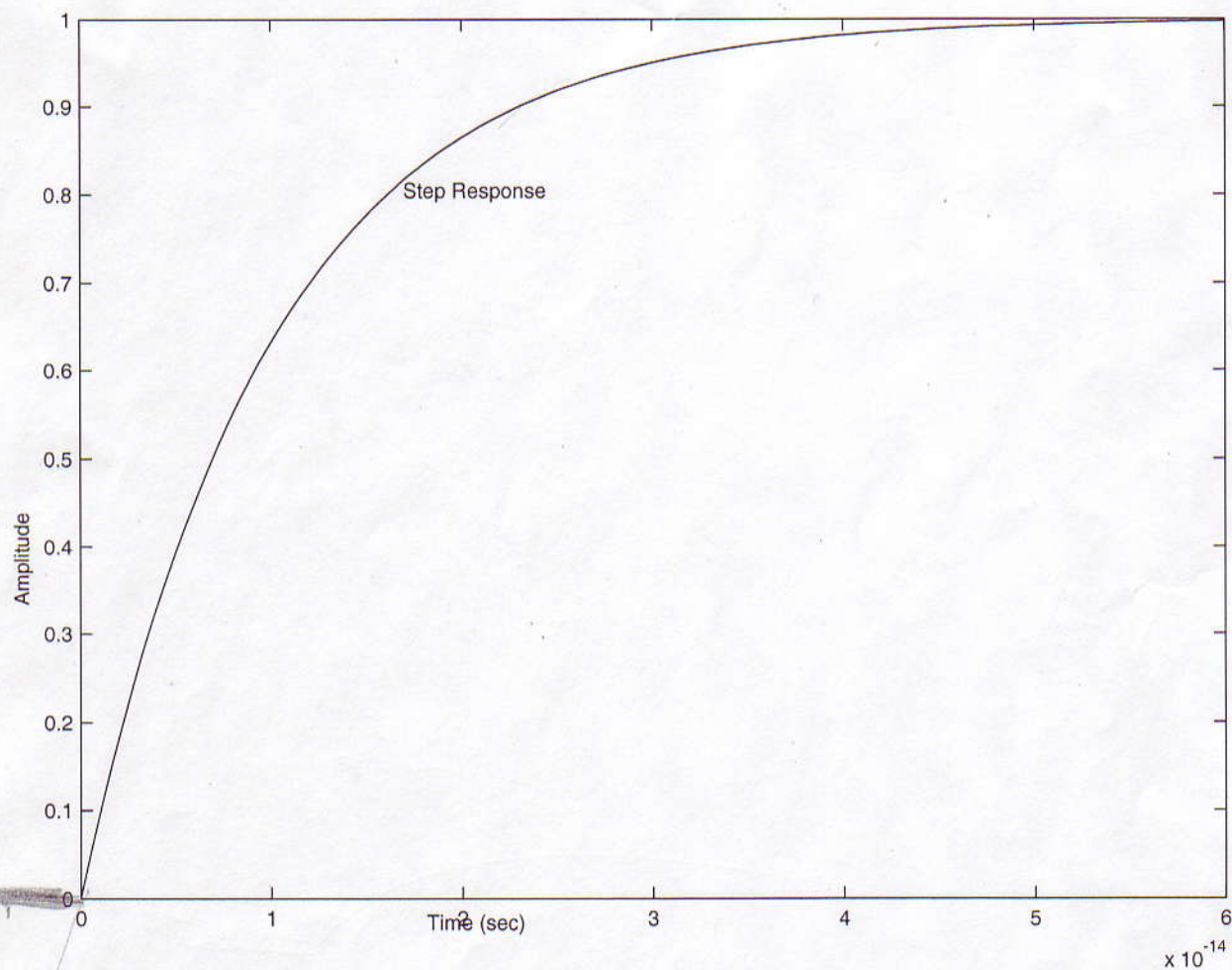Step response corresponding to $V_{in} = u(t)$



$$C = \frac{1}{\omega n^2 \times L} \frac{\text{sec}^2}{H} \quad (H - \text{Henry})$$

$$\frac{\text{sec}^2}{H} = \frac{\text{sec}^2}{\Omega \text{ sec}}$$

$$\frac{\text{sec}^2}{H} = \frac{\text{sec}}{\Omega}$$

$$i = C \times \frac{dv}{dt} \rightarrow \text{capacitance}$$

$$C = \frac{i}{\frac{dv}{dt}} = \frac{i}{R \times \frac{di}{dt}} \xrightarrow{\text{units}} \frac{\cancel{C}/s}{\Omega \times \frac{\cancel{C}}{s}} \quad (\text{here } C - \text{coulomb})$$

$$F = \frac{\text{sec}}{\Omega}$$

$$\text{Hence } \frac{\text{sec}^2}{H} = F.$$