

Q1

Sol

(a)

$$\frac{U_o}{U_{in}}(s) = C \cdot \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots}$$

By MOTC, we can redraw the schematic as following


$$C_1 = 1 \text{ (fF)}$$

$$C_2 = 2 \text{ (fF)}$$

$$R_1 = 3 \text{ (k}\Omega\text{)}$$

$$R_2 = 2 \text{ (k}\Omega\text{)}$$

$$R_3 = 1 \text{ (k}\Omega\text{)}$$

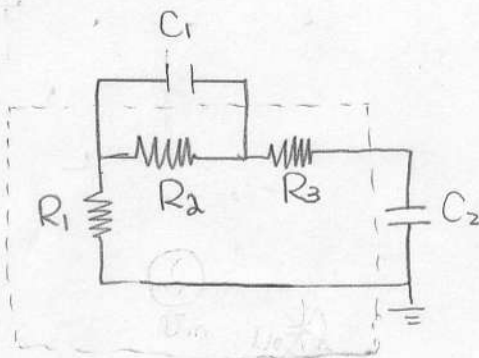

$$R_{11}^0 = R_2$$

$$R_{22}^0 = R_1 + R_2 + R_3$$

$$R_{11}^2 = R_2 \parallel (R_1 + R_3)$$

$$R_{22}^1 = (R_1 + R_3)$$

$$\therefore a_1 = C_1 R_{11}^0 + C_2 R_{22}^0$$

$$= C_1 R_2 + C_2 (R_1 + R_2 + R_3) = 1 \text{ (fF)} \cdot 2 \text{ (k}\Omega\text{)} + 2 \text{ (fF)} \cdot 6 \text{ (k}\Omega\text{)}$$

$$= 14 \text{ (ps)}$$

$$a_2 = C_1 C_2 (R_{11}^0 R_{22}^1)$$

$$= C_1 C_2 (R_2 \cdot (R_1 + R_3)) = 1 \text{ (fF)} \cdot 2 \text{ (fF)} \{ 2 \text{ (k}\Omega\text{)} \cdot (3 \text{ (k}\Omega\text{)} + 1 \text{ (k}\Omega\text{)}) \}$$


$$= 16 \text{ (ps)}^2$$

$$(b) \frac{a_2}{a_1} = 1.14 \text{ (ps)} \gg 1 \text{ ps} \therefore a_1 \gg \frac{a_2}{a_1}$$

$\Rightarrow$ we may use separate pole approximation

$$\therefore f_{p1} = \frac{0.159}{14 \text{ (ps)}} = 11.36 \text{ (GHz)}$$
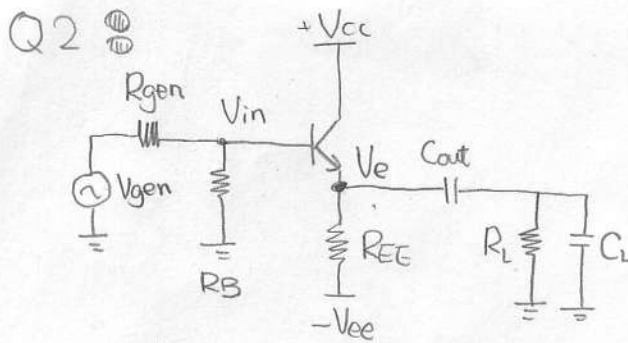
$$f_{p2} = \frac{0.159}{1.07 \text{ (ps)}} = 139.5 \text{ (GHz)}$$



$$\tau_f = 1 \text{ (ps)}, C_{je} = C_{cb} = 20 \text{ (fF)}$$

$$\beta = 100, R_B = 10 \cdot R_{gen} = 10 \text{ (k}\Omega\text{)}$$

$$V_{cc} = +3.3 \text{ (V)}, -V_{ee} = -3.3 \text{ (V)}$$

$$R_{gen} = 1 \text{ (k}\Omega\text{)}, C_L = 50 \text{ (fF)}$$

$$R_L = 100 \text{ (}\Omega\text{)}, I_E \approx I_C = 5 \text{ (mA)}$$

• Parameter Calculation

$$\begin{cases} g_m \approx \frac{1}{r_e} = \frac{I_E}{V_T} = \frac{5 \text{ (mA)}}{26 \text{ (mV)}} = 192 \text{ (mS)} \\ C_{be} = g_m \tau_f + C_{je} = 192 \text{ (mS)} \cdot 1 \times 10^{-12} \text{ (sec)} + 20 \times 10^{-15} \text{ (F)} = 212 \text{ (fF)} \\ f_T = \frac{g_m}{2\pi (C_{cb} + C_{be})} = \frac{192 \text{ (mS)} \cdot 0.159}{20 \text{ (fF)} + 212 \text{ (fF)}} = 131.6 \text{ (GHz)} \end{cases}$$

(a) • Bias Condition

$$\text{assume } V_{be(on)} = 0.7 \text{ (V)}$$

$$I_B = \frac{I_C}{\beta} = 50 \text{ (}\mu\text{A)}, V_{in(DC)} = 0 - I_B \cdot (R_{gen} \parallel R_B) = -46 \text{ (mV)}$$

$$V_{be} = V_{in} - V_e$$

$$\Rightarrow V_e = V_{in} - V_{be} = -0.746 \text{ (V)}$$

$$\therefore R_{EE} = \frac{V_e - V_{ee}}{I_E} = \frac{-0.746 \text{ (V)} - (-3.3 \text{ (V)})}{5 \text{ (mA)}} = 511 \text{ (}\Omega\text{)}$$

• Calculate Mid-band $\frac{V_{out}}{V_{in}}$, $\frac{V_{in}}{V_{gen}}$, R_{out_amp} , R_{in_amp}

$$r_e = \frac{V_T}{I_E} = \frac{26 \text{ (mV)}}{5 \text{ (mA)}} = 5.2 \text{ (}\Omega\text{)}$$

$$R_{L,eq} = R_{EE} \parallel R_L = 511 \text{ (}\Omega\text{)} \parallel 100 \text{ (}\Omega\text{)} = 83.6 \text{ (}\Omega\text{)} \quad (\text{assume } R_{ce} = \infty \text{ (}\Omega\text{)})$$

$$\left. \frac{V_{out}}{V_{in}} \right|_{MB} = \frac{R_{L,eq}}{r_e + R_{L,eq}} = 0.942$$

$$R_{in,T} = (1+\beta)(R_{L,eq} + r_e) = (101) \cdot (83.6(\Omega) + 5.2(\Omega)) \approx 8.97 \text{ (k}\Omega\text{)}$$


$$\therefore R_{in_amp} = R_B \parallel R_{in,T} = \frac{10(\text{k}\Omega) \cdot 8.97(\text{k}\Omega)}{10(\text{k}\Omega) + 8.97(\text{k}\Omega)} \approx \underline{4.73 \text{ (k}\Omega\text{)}}$$

$$\therefore \left. \frac{V_{in}}{V_{gen}} \right|_{MB} = \frac{4.73(\text{k}\Omega)}{1(\text{k}\Omega) + 4.73(\text{k}\Omega)} = \underline{0.825}$$

$$R_{out,T} = \frac{(R_{gen} \parallel R_B)}{1+\beta} + r_e = \frac{1(\text{k}\Omega) \parallel 10(\text{k}\Omega)}{101} + 5.2(\Omega) = 14.2(\Omega)$$

$$\therefore R_{out_amp} = R_{out,T} \parallel R_{EE} = \underline{13.82(\Omega)}$$

(b) MOTC

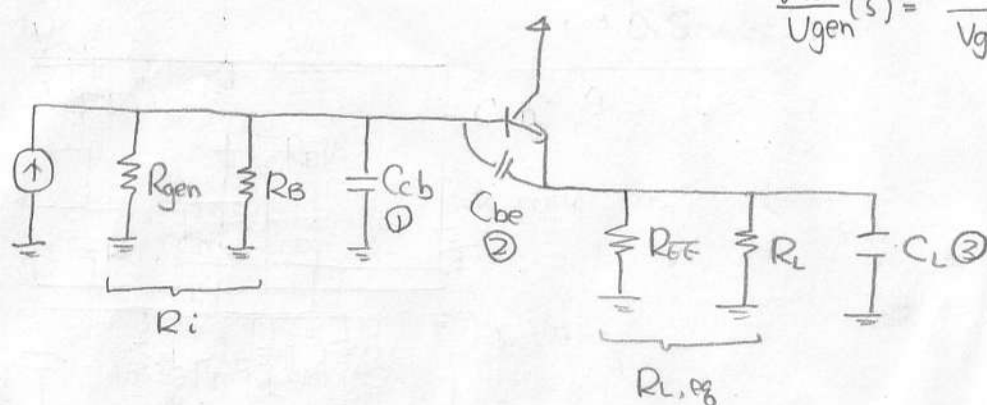

$$\frac{V_{out}}{V_{gen}}(s) = \left. \frac{V_{out}}{V_{gen}} \right|_{MB} \cdot \frac{1 + b_1 s}{1 + a_1 s + a_2 s^2}$$

$$R_{ii}^0 = R_i \parallel R_{in,T} = 1(\text{k}\Omega) \parallel 10(\text{k}\Omega) \parallel 8.97(\text{k}\Omega) \approx 825(\Omega)$$

$$R_{33}^0 = R_{L,eq} \parallel R_{out,T} = 83.6(\Omega) \parallel 14.2(\Omega) = 12.14(\Omega)$$

$$R_{22}^0 = \frac{(1+\beta)}{g_m} \parallel \left[R_i \left(1 - \frac{R_{L,eq}}{R_{L,eq} + r_e} \right) + r_e \parallel R_{L,eq} \right] = 5.23(\Omega)$$

$$a_1 = C_{cb} \cdot R_{ii}^0 + C_{be} \cdot R_{22}^0 + C_L \cdot R_{33}^0$$

$$= 20(\text{fF}) \cdot 825(\Omega) + 212(\text{fF}) \cdot 5.23(\Omega) + 50(\text{fF}) \cdot 12.14(\Omega)$$

$$= 18.22(\text{ps})$$

$$a_2 = (R_i \parallel R_{in,T}) \left(\frac{1}{g_m} \parallel R_{L,eq} \right) \cdot (C_{cb} \cdot C_{be} + C_{cb} \cdot C_L + C_{be} \cdot C_L)$$

$$= 825(\Omega) \cdot 14.9(\Omega) \cdot (20(\text{fF}) \cdot 212(\text{fF}) + 20(\text{fF}) \cdot 50(\text{fF}) + 212(\text{fF}) \cdot 50(\text{fF}))$$

$$= 4.64(\text{ps})^2$$

$$\frac{a_2}{a_1} = 3.153 \text{ (pS)}$$

$\therefore a_1$ is only 5.78 times bigger than $\frac{a_2}{a_1}$

$\therefore$ Separate pole approximate is invalid here

$$\Rightarrow \text{solve } a_2 \cdot s^2 + a_1 s + 1 = 0$$

$$\Rightarrow f_{p1}, f_{p2} = 0.159 \cdot \left[\frac{-a_1 \pm \sqrt{a_1^2 - 4a_2}}{2a_2} \right] = 11.8 \text{ (GHz)}, 33.5 \text{ (GHz)}$$

$$\therefore f_{p1} = 11.8 \text{ (GHz)}, f_{p2} = 33.5 \text{ (GHz)}, f_{3dB} \approx f_{p1} = 11.8 \text{ (GHz)}$$

two real poles

(c) Bode Plot

$$\left. \frac{V_{out}}{V_{gen}} \right|_{MB} = 0.826 \cdot 0.942 = 0.777 = -2.19 \text{ (dB)}$$

the transfer function has a zero at

$$f_z = 0.159 \cdot \frac{g_m}{C_{be}} = 144 \text{ (GHz)}$$

$\therefore$ Total Transfer function is


$$\frac{V_{out}}{V_{gen}}(s) = 0.777 \cdot \frac{1 + j \frac{f}{144 \text{ (GHz)}}}{\left(1 + j \frac{f}{11.8 \text{ (GHz)}}\right) \left(1 + j \frac{f}{33.5 \text{ (GHz)}}\right)}$$

bode plot is in next page


$$\left| \frac{V_{out}}{V_{in}} \right|_{dB}$$

Question 2.

3dB frequency $\approx 11.8 \text{ GHz}$

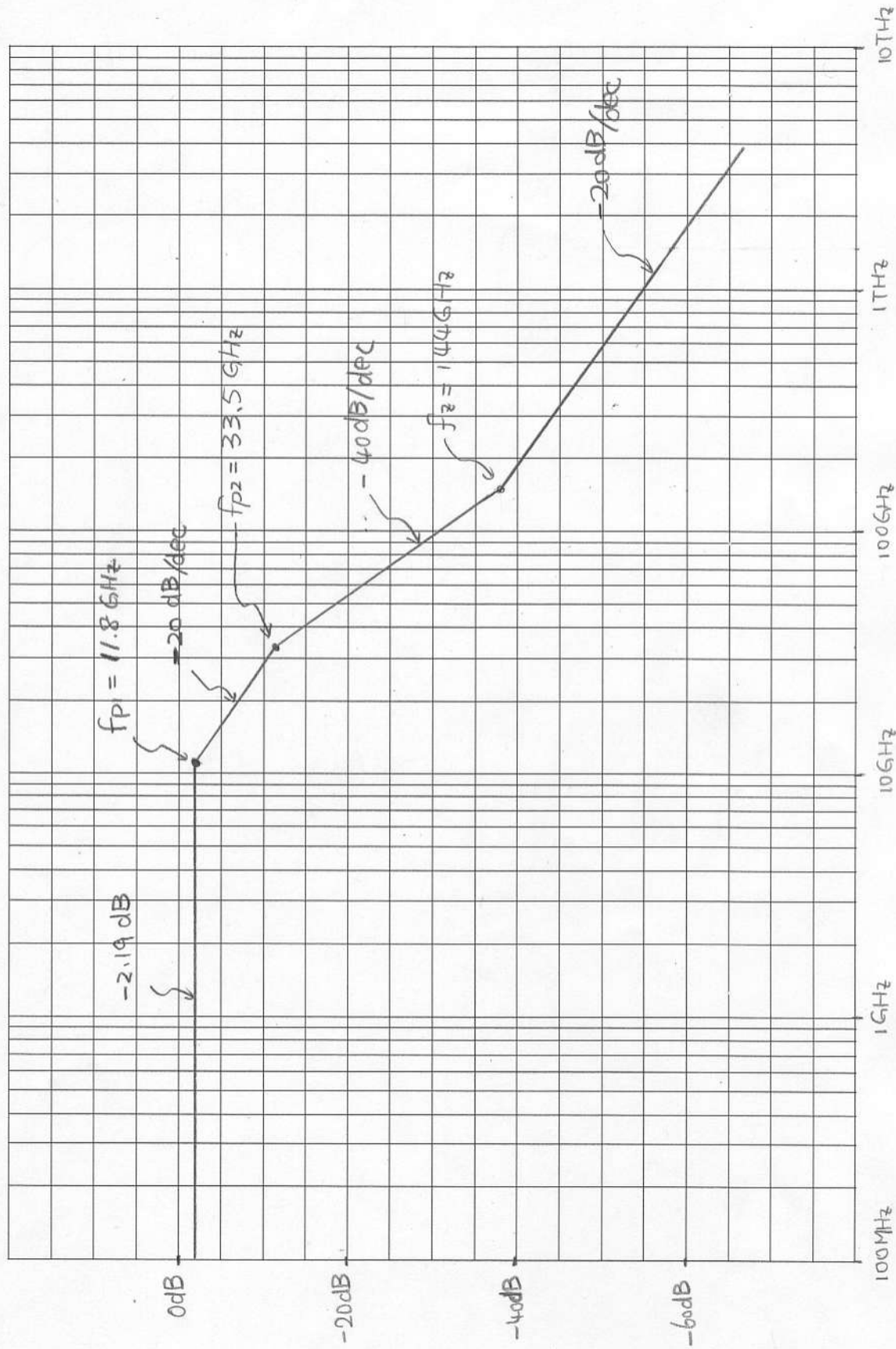

frequency, log (Hz)

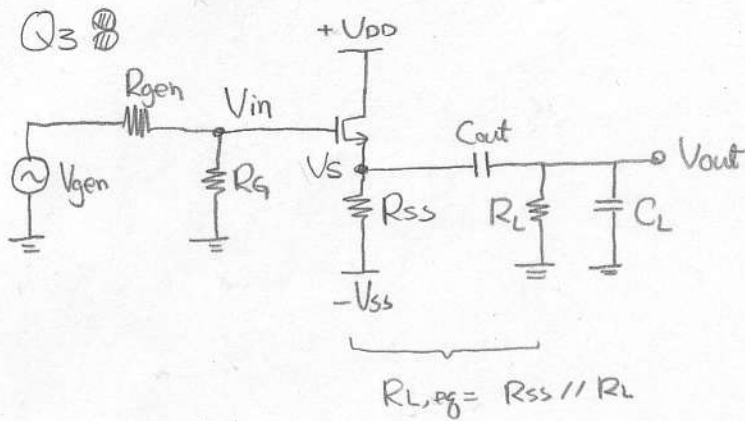

$$g_m = 10 \text{ (mS)}, \lambda = 0, L_g = 90 \text{ (nm)}$$

$$I_D = I_S = 2 \text{ mA}, V_{sat} = 10^5 \left(\frac{\text{m}}{\text{s}} \right)$$

$$V_{DD} = +1 \text{ (V)}, -V_{SS} = -1 \text{ (V)}$$

$$V_{th} = 0.3 \text{ (V)}, \lambda = 0$$

$$\epsilon_r = 3.8, R_L = 2 \text{ (k}\Omega\text{)}, C_L = 200 \text{ (fF)}$$

$$R_g = 20 \text{ (k}\Omega\text{)}, R_{gen} = 2 \text{ (k}\Omega\text{)}$$

$$T_{ox} = 1.6 \text{ (nm)}$$

• Parameter calculation

$$C_{ox} = \frac{\epsilon_r \cdot \epsilon_0}{T_{ox}} = \frac{3.8 \times 8.854 \times 10^{-12} \left(\frac{\text{F}}{\text{m}} \right)}{1.6 \times 10^{-9} \text{ (m)}} = 2.1 \times 10^{-2} \left(\frac{\text{F}}{\text{m}^2} \right)$$

$$W_g = \frac{g_m}{V_{sat} \cdot C_{ox}} = \frac{10 \times 10^{-3} \left(\frac{\text{A}}{\text{V}} \right)}{10^5 \left(\frac{\text{m}}{\text{s}} \right) \cdot 2.1 \times 10^{-2} \left(\frac{\text{F}}{\text{m}^2} \right)} = 4.76 \text{ }\mu\text{m}$$

$$C_{gs} = C_{ox} \cdot L_g \cdot W_g = 9 \text{ (fF)}$$

$$C_{gd} = \frac{C_{gs}}{10} = 0.9 \text{ (fF)}$$

(a). Bias Condition

$$I_G = 0, V_G = 0$$

$\therefore L_g = 90 \text{ (nm)} \therefore$ Velocity model is applied

$$\therefore I_D = g_m (V_{GS} - V_{th}) (1 + \lambda V_{DS}) \quad \text{when } V_{GS} \geq V_{th}$$

$$\Rightarrow V_{GS} = \frac{I_D}{g_m} + V_{th} = 0.5 \text{ (V)}$$

$$\therefore V_S = V_G - V_{GS} = -0.5 \text{ (V)}$$

$$\therefore R_{SS} = \frac{V_S - V_{SS}}{I_D} = \frac{-0.5 \text{ (V)} + 1 \text{ (V)}}{2 \text{ (mA)}} = \underline{250 \text{ (}\Omega\text{)}}$$

$$\therefore R_{L,eq} = R_{SS} \parallel R_L = 250 \text{ (}\Omega\text{)} \parallel 2 \text{ (k}\Omega\text{)} = 222 \text{ (}\Omega\text{)}$$

$$\therefore \left. \frac{V_{out}}{V_{in}} \right|_{MB} = \frac{R_{L,eq}}{\frac{1}{g_m} + R_{L,eq}} = \underline{0.689}$$


$$R_{in_amp} = R_G // R_{in,T} = 20(k\Omega) // \infty(\Omega) = \underline{20(k\Omega)}$$

$$\therefore \frac{V_{in}}{V_{gen}} \Big|_{MB} = \frac{R_{in_amp}}{R_{gen} + R_{in_amp}} = \underline{0.909}$$

$$R_{out,T} = \frac{1}{g_m} = 100\Omega$$

$$\therefore R_{out_amp} = R_{ss} // R_{out,T} = 71.43(\Omega)$$

(b) MOTC

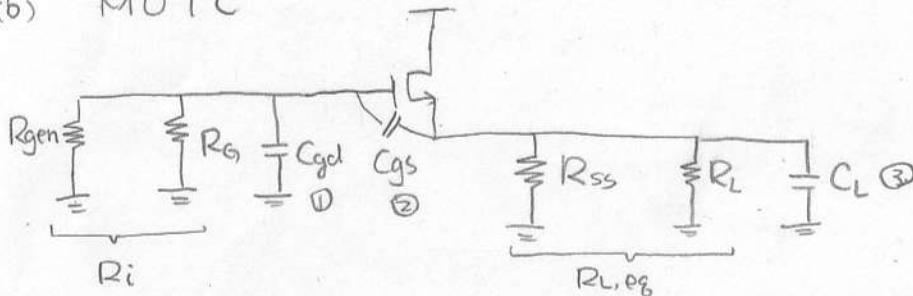

$$R_{ii}^o = R_{gen} // R_G = 1.82(k\Omega)$$

$$R_{22}^o = \frac{1}{g_m} // R_{L,eq} + R_i (1 - A_{v|MB}) = 634.4(\Omega)$$

$$R_{33}^o = R_{L,eq} // \frac{1}{g_m} = 68.94(\Omega)$$

$$\therefore A_1 = C_{gd} \cdot R_{ii}^o + C_{gs} \cdot R_{22}^o + C_L \cdot R_{33}^o = 0.9(fF) \cdot 1.82(k\Omega) + 9(fF) \cdot 634.4(\Omega) + 200(fF) \cdot 68.94(\Omega)$$

$$= 0.9(fF) \cdot 1.82(k\Omega) + 9(fF) \cdot 634.4(\Omega) + 200(fF) \cdot 68.94(\Omega)$$

$$= 21.03(pS)$$

$$A_2 = R_i \cdot (R_{L,eq} // \frac{1}{g_m}) \cdot (C_{gd} \cdot C_{gs} + C_{gd} \cdot C_L + C_{gs} \cdot C_L)$$

$$= 1.82(k\Omega) \cdot 68.94(\Omega) \cdot (0.9(fF) \cdot 9(fF) + 0.9(fF) \cdot 200(fF) + 9(fF) \cdot 200(fF))$$

$$= 249.46(pS)^2$$

$$\text{examine } \frac{A_2}{A_1} = 11.86(pS)$$

$\therefore a_1$ is only 1.77 times bigger than $\frac{a_2}{a_1}$

$\therefore$ Separate pole approximation is invalid here

$$\text{solve } a_2 s^2 + a_1 s + 1 = 0$$

$$\Rightarrow f_{p1}, f_{p2} = 0.159 \cdot \left[\frac{-a_1 \pm \sqrt{a_1^2 - 4a_2}}{2a_2} \right] = -6.702 \pm j 7.512 \text{ (GHz)}$$

two complex poles

$$\bullet \quad a_2 s^2 + a_1 s + 1 = \left(\frac{1}{\omega_n}\right)^2 \cdot s^2 + \left(\frac{2\xi}{\omega_n}\right) \cdot s + 1$$

$$\therefore f_n = \frac{0.159}{\sqrt{a_2}} = 10 \text{ (GHz)} \quad (\text{natural frequency})$$

$$\xi = \frac{a_1}{2 \cdot \sqrt{a_2}} = 0.667$$

$$\therefore f_d = f_n \sqrt{1 - \xi^2} = 7.45 \text{ GHz} \quad (\text{peak frequency})$$

and 3dB BW is roughly at $f_n = 10 \text{ (GHz)}$.

(C)

The transfer function has a zero at

$$f_z = 0.159 \cdot \frac{g_m}{C_{gs}} = 176.67 \text{ (GHz)}$$

$$\frac{V_{out}}{V_{gen}} \Big|_{MB} = 0.909 \times 0.689 = 0.626 = -4.07 \text{ (dB)}$$

$$\text{Peak height} = -20 \log_{10} (2\xi \sqrt{1 - \xi^2}) = 5.31 \times 10^{-2} \text{ (dB)} \quad \text{small peak}$$


($\xi = 0.7071$ will give "zero peak")


the bode plot is in next page

Question 3

$$\left| \frac{V_{out}}{V_{in}} \right|_{dB}$$

3dB frequency $\approx 10 \text{ GHz}$

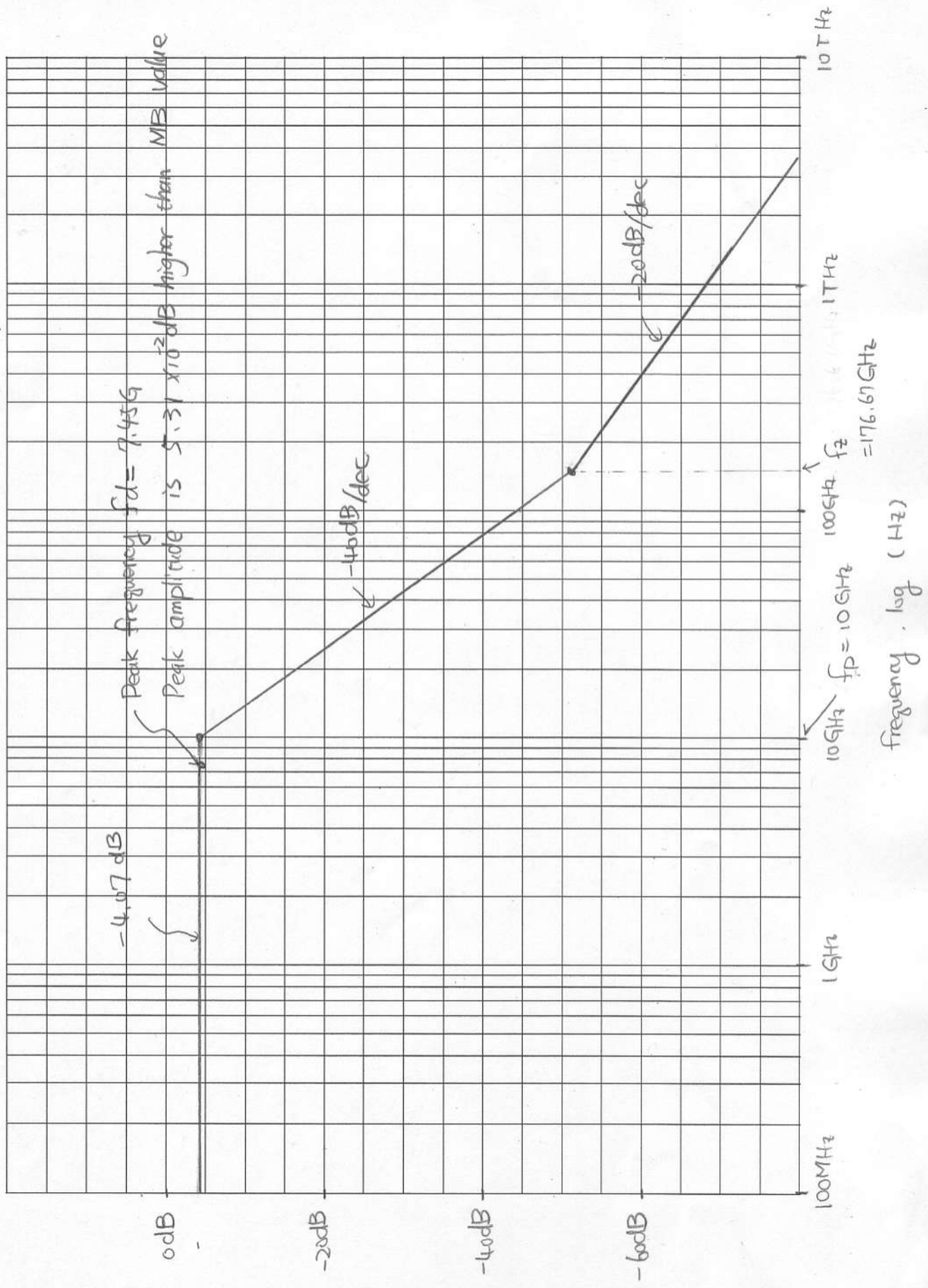

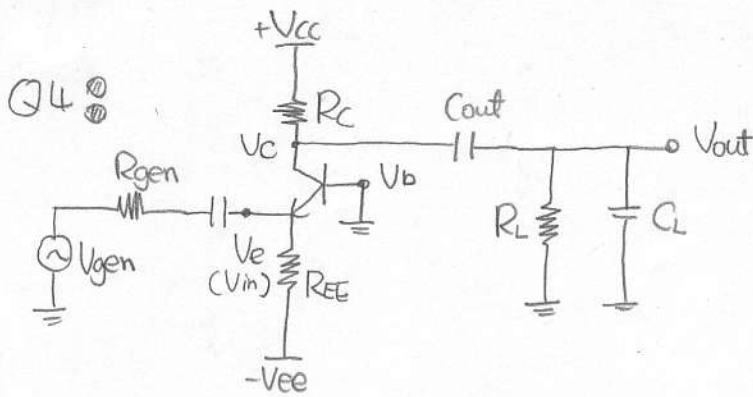

$$\tau_f = 1 \text{ (ps)}, C_{je} = 50 \text{ (fF)}$$

$$C_{cb} = 100 \text{ (fF)}, \beta = 50$$

$$V_{cc} = 5 \text{ (V)}, -V_{ee} = -5 \text{ (V)}$$

$$R_L = 1 \text{ (k}\Omega\text{)}, C_L = 200 \text{ (fF)}$$

$$R_{gen} = 50 \text{ (}\Omega\text{)}$$

$$I_E \approx I_C = 2 \text{ mA}, V_{CE} = 2 \text{ (V)}$$

• Parameter calculation

$$\begin{cases} g_m = \frac{1}{r_e} = \frac{I_E}{V_T} = 77 \text{ (mS)} \\ C_{be} = g_m \tau_f + C_{je} = 77 \text{ (mS)} \cdot 1 \text{ (ps)} + 50 \text{ (fF)} = 127 \text{ (fF)} \\ f_T = \frac{g_m}{2\pi(C_{cb} + C_{be})} = 53.9 \text{ (GHz)} \end{cases}$$

(a) • Bias Condition assume $V_{be(ON)} = 0.7 \text{ (V)}$

$$\begin{cases} V_e = V_b - V_{be(ON)} = -0.7 \text{ (V)} \\ V_c = V_e + 2 \text{ (V)} = 1.3 \text{ (V)} \\ R_{EE} = \frac{V_e + V_{ee}}{I_E} = \frac{-0.7 \text{ (V)} + 5 \text{ (V)}}{2 \text{ (mA)}} = 2.15 \text{ (k}\Omega\text{)} \\ R_c = \frac{V_{cc} - V_c}{I_C} = \frac{5 \text{ (V)} - 1.3 \text{ (V)}}{2 \text{ (mA)}} = 1.85 \text{ (k}\Omega\text{)} \end{cases}$$

• Calculate the Mid-band $\frac{V_{out}}{V_{in}}, \frac{V_{in}}{V_{out}}, R_{out_amp}, R_{in_amp}$

assume $R_{ce} = \infty \text{ (}\Omega\text{)}$

$$r_e = \frac{V_T}{I_E} = 13 \text{ (}\Omega\text{)}$$

$$\therefore R_{in,T} = r_e \text{ and } R_{out,T} = R_{ce}(1 + g_m R_{EE}) = \infty \text{ (}\Omega\text{)}$$

$$\therefore R_{in_amp} = r_e \parallel R_{EE} = 13 \text{ (}\Omega\text{)} \parallel 2.15 \text{ (k}\Omega\text{)} = \underline{12.92 \text{ (}\Omega\text{)}}$$

$$R_{L,eq} = R_c \parallel R_L = 649 \text{ (}\Omega\text{)}$$


$$R_{out_amp} = R_{L,eq} \parallel R_{out,T} = \underline{649 \text{ (}\Omega\text{)}}$$

$$\left. \frac{V_{out}}{V_{in}} \right|_{MB} = \frac{R_{L,eq}}{R_{in-amp}} = \frac{649(\Omega)}{12.92(\Omega)} = \underline{50.23}$$

$$\left. \frac{V_{in}}{V_{gen}} \right|_{MB} = \frac{R_{in-amp}}{R_{gen} + R_{in-amp}} = \frac{12.92(\Omega)}{50(\Omega) + 12.92(\Omega)} = \underline{0.205}$$

(b)

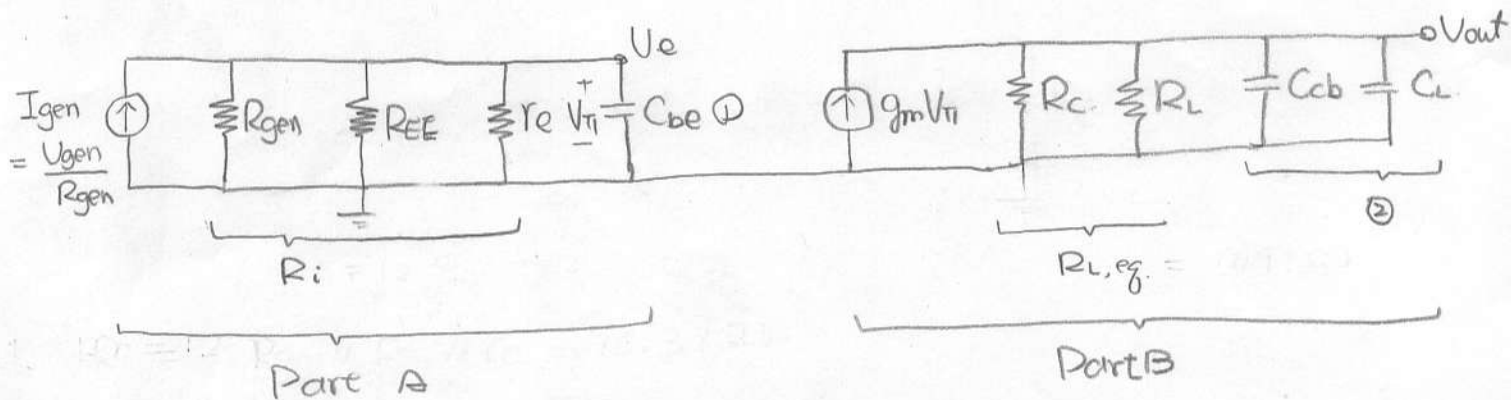• Small-signal circuit diagram is shown below



• Part A and B have no direct connections
 ∴ we may consider the whole transfer function as the product of transfer functions of part A and B. due to the dependent current source.

• Part A

$$\tau_A = R_i \cdot C_{be} = (R_{gen} \parallel R_{EE} \parallel r_e) \cdot C_{be} = 10.3(\Omega) \cdot 127(\text{pF}) = 1.31(\text{ps})$$

• Part B.

$$\tau_B = R_{L,eq} \cdot (C_L + C_{cb}) = 649(\Omega) \cdot (100(\text{pF}) + 200(\text{pF})) = 195(\text{ps})$$

$$\therefore a_1 = \tau_A + \tau_B = \underline{196.31 \text{ (ps)}}$$

$$a_2 = \tau_A \cdot \tau_B = \underline{255.45 \text{ (ps)}^2}$$

$$\text{and } \begin{cases} f_{pA} = \frac{0.159}{\tau_A} = \frac{0.159}{1.31 \text{ (ps)}} = \underline{121.4 \text{ (GHz)}} \\ f_{pB} = \frac{0.159}{\tau_B} = \underline{815.38 \text{ (MHz)}} \end{cases}$$

$\therefore$ Dominate pole frequency is 815.38 (MHz) $\approx f_{3dB}$ frequency

(c) Bode Plot

• There is no zero frequency in this system.

$$\bullet \left. \frac{V_{out}}{V_{gen}} \right|_{MB} = 50.23 \times 0.205 \approx 10.3 \approx 20.57 \text{ (dB)}$$

• The total transfer function


$$\frac{V_{out}}{V_{gen}}(s) = 10.3 \cdot \frac{1}{\left(1 + j \frac{f}{815.38 \text{ (MHz)}}\right) \cdot \left(1 + j \frac{f}{121.4 \text{ (GHz)}}\right)}$$

The bode plot is in next page.

Question 4

$\left| \frac{V_{out}}{V_{in}} \right|_{dB}$

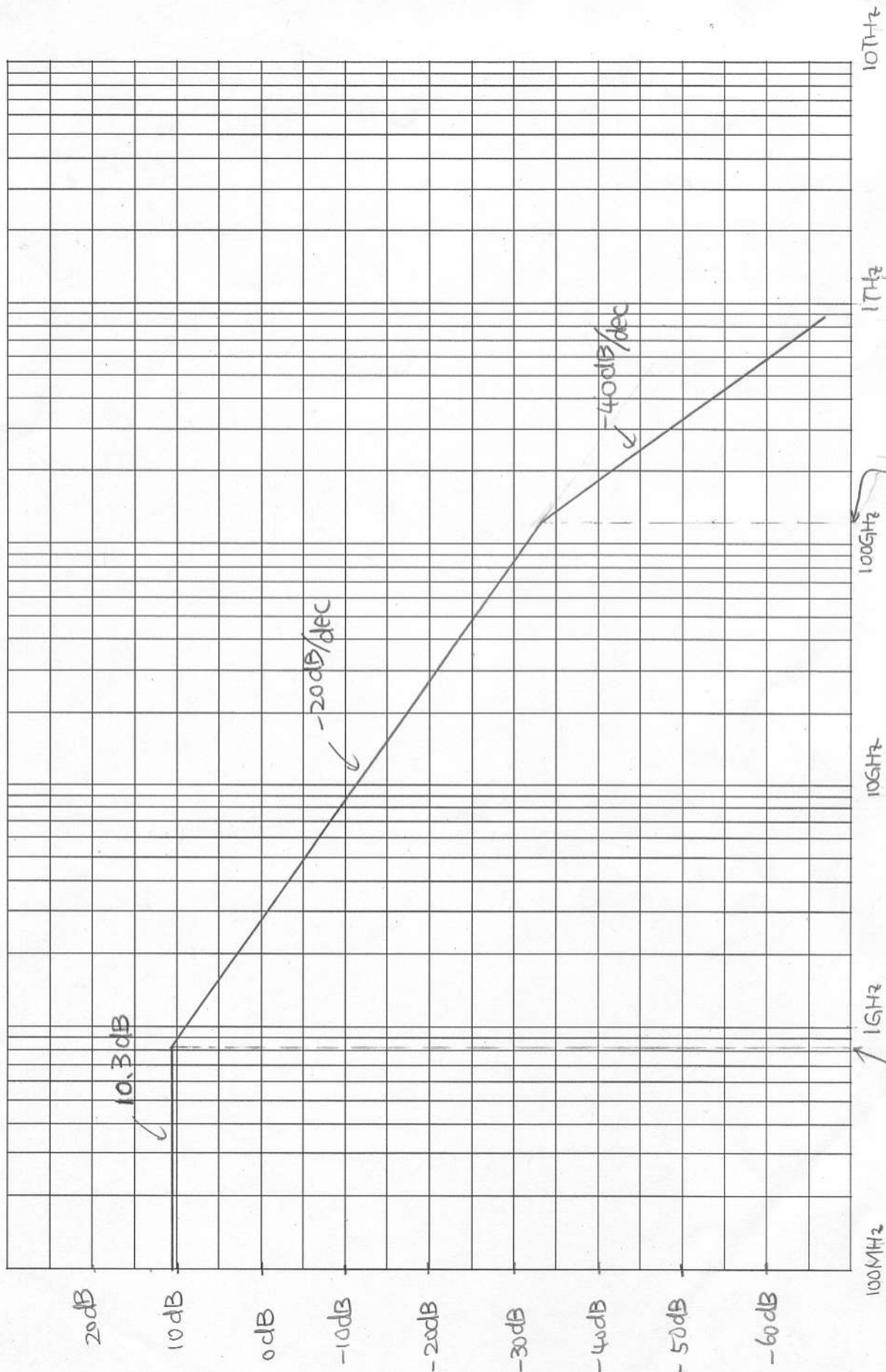3dB frequency $\approx 815.38 \text{ MHz}$



$f_{p,B} = 815.38 \text{ MHz}$

$f_{p,B} = 121.46 \text{ GHz}$

frequency, $\log (Hz)$