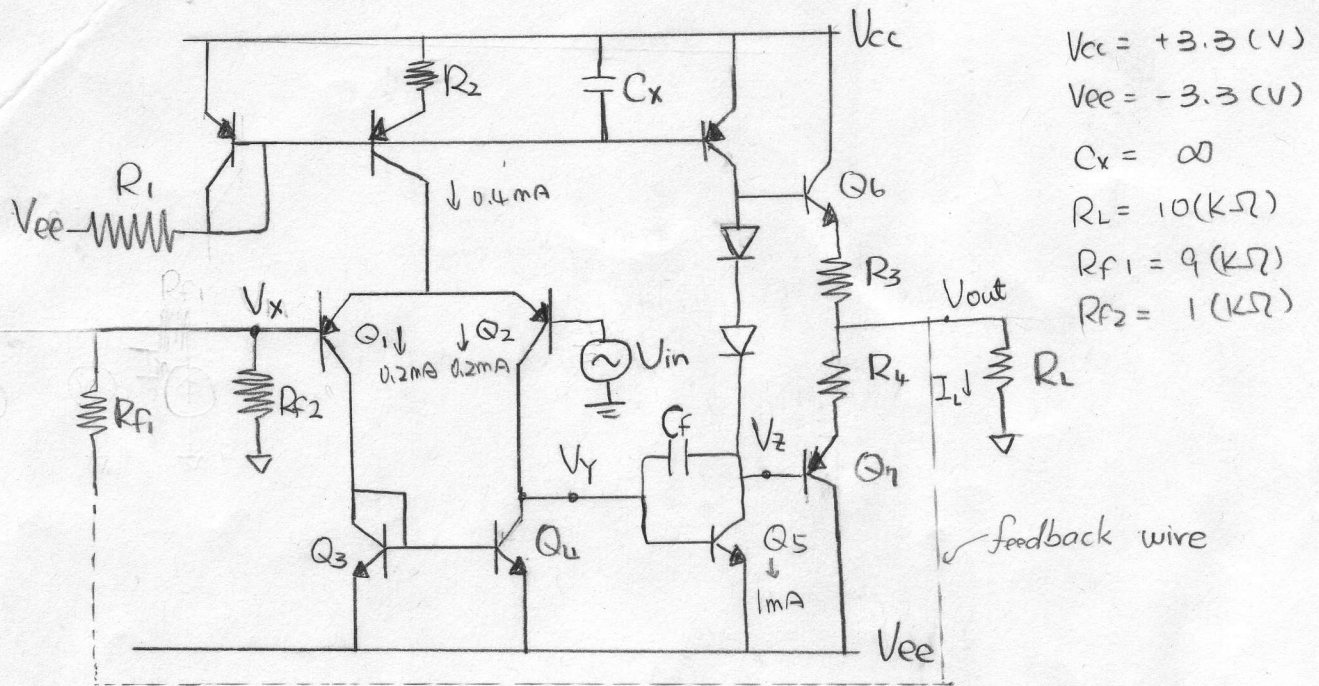


Q18



Transistor parameters are listed in the table below

	$I_C (mA)$	β	$V_A (V)$	$g_m (mS)$	$C_{cb} (pF)$	$\tau_f (ns)$	*1 $C_{be} (pF)$	*2 $f_T (MHz)$
Q1	0.2	∞	∞	7.7	3	0.5	3.85	178.65
Q2	0.2	∞	∞	7.7	3	0.5	3.85	178.65
Q3	0.2	∞	∞	7.7	3	0.5	3.85	178.65
Q4	0.2	∞	100	7.7	3	0.5	3.85	178.65
Q5	1	∞	100	38.5	3	0.5	19.25	275.09
Q6	0.2	∞	∞	7.7	100	20	154	4.82
Q7	0.2	∞	∞	7.7	100	20	154	4.82

*1 $C_{be} = g_m \tau_f + C_{je}$. Since C_{je} is not given, we assume $C_{je} = 0(F)$

*2 $f_T = \frac{0.159 \cdot g_m}{C_{be} + C_{cb}}$

⑩ Feedback Network Loading to the amplifier

Feedback network loaded on input node is $R_{f1} // R_{f2}$

Feedback network loaded on output node is $R_{f1} + R_{f2}$

(a) DC bias condition

① R_1

$$\therefore I_C @ Q_5 = 1 \text{ mA}$$

$\therefore$ Current following through R_1 is also 1 mA


$$\therefore 1 \text{ mA} = \frac{V_{CC} - V_{BE} - V_{EE}}{R_1}$$

$$\Rightarrow R_1 = \frac{3.3 \text{ (V)} - 0.7 \text{ (V)} - (-3.3 \text{ (V)})}{1 \text{ mA}} = \underline{5.9 \text{ (k}\Omega\text{)}}$$

② R_2

Consider the upper left 2 pnp (Current mirrors) drawn below
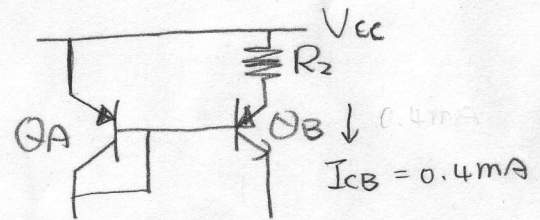
$$V_{BE} = \frac{KT}{q} \ln\left(\frac{I_C}{I_S}\right)$$



$$\therefore V_{BE,QA} = V_{BE,QB} + R_2 I_{CB}$$

$$\Rightarrow \frac{KT}{q} \ln \frac{I_{CA}}{I_S} = \frac{KT}{q} \ln \frac{I_{CB}}{I_S} + R_2 I_{CB} \quad [\text{all BJTs have the same } I_S]$$

$$\Rightarrow R_2 = \frac{KT}{q} \cdot \ln \frac{I_{CA}}{I_{CB}} / I_{CB} = 26 \text{ (mV)} \cdot \ln \left(\frac{1 \text{ (mA)}}{0.4 \text{ (mA)}} \right) / 0.4 \text{ (mA)}$$

$$\underline{\underline{\approx 60 (\Omega)}}$$


③ R_3, R_4

Consider the voltage drop across two diodes shown in the right figure.

$$V_D = V_{BE,Q6} + I_{C6} \cdot R_3$$

$$+ I_{C7} \cdot R_4 + V_{BE,Q7}$$

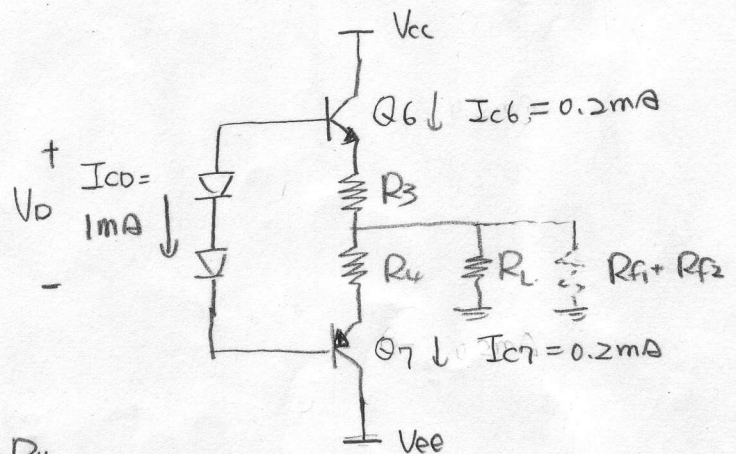assume $V_{BE,Q6} = V_{BE,Q7}$, and $R_3 = R_4$



$$\therefore 2 \cdot \left(\frac{KT}{q} \cdot \ln \left(\frac{I_{CD}}{I_S} \right) \right) = 2 \left(\frac{KT}{q} \cdot \ln \left(\frac{I_{C6}}{I_S} \right) \right) + 2 \cdot I_{C6} \cdot R_3$$

$$\Rightarrow R_3 = \frac{KT}{q} \ln \left(\frac{I_{CD}}{I_{C6}} \right) / I_{C6} = 26 \text{ (mV)} \cdot \ln \left(\frac{1 \text{ (mA)}}{0.2 \text{ (mA)}} \right) / 0.2 \text{ (mA)} = \underline{\underline{209 (\Omega)}}$$

(R_4)

④ R_{ce4} , R_{ce5}

$$R_{ce4} = \frac{V_{be,05} + V_A}{I_{c4}} = \frac{0.7(V) + 100(V)}{0.2(mA)} = \underline{503.5(k\Omega)}$$

at steady-state condition, $I_{c6} = I_{c7} = 0.2(mA)$

$$\therefore I_L = 0(mA) \Rightarrow V_{out} = 0(V)$$

$$\begin{aligned} \therefore V_{ce5} &= V_{out} - I_{c7} \cdot R_4 - V_{be,07} - V_{ee} \\ &= 0(V) - 0.2(mA) \cdot 209(\Omega) - 0.7(V) + 3.3(V) \\ &= 2.56(V) \end{aligned}$$

$$\therefore R_{ce5} = \frac{V_{ce5} + V_A}{I_{c5}} = \frac{2.56(V) + 100(V)}{1(mA)} = \underline{102.56(k\Omega)}$$

⑤ Open-loop Gain [mid-band]

refer to the notations in the schematic (page 1)

$$1. \frac{V_{out}}{V_z} = \frac{R_L \parallel (R_{f1} + R_{f2})}{1/g_{m1} + R_4 + R_L \parallel (R_{f1} + R_{f2})} = \frac{5(k\Omega)}{1/7.7 \times 10^{-3}(S) + 209(\Omega) + 5(k\Omega)} \approx 0.94$$

$$2. \frac{V_z}{V_Y} = -g_{m5} R_{ce5} \approx -38.5(mS) \cdot 102.56(k\Omega) = -3949$$

$$3. \frac{V_Y}{V_{in}} = -g_{m1} \cdot R_{ce4} = -7.7(mS) \cdot 503.5(k\Omega) \approx -3877$$

$$\text{The open-loop gain } \frac{V_{out}}{V_{in}} = 0.94 \cdot (-3949) \cdot (-3877) = 1.44 \times 10^7$$

The Total Voltage Gain $A_v = \frac{V_{out}}{V_{in}} = -g_{m1} g_{m5} R_{ce4} R_{ce5} = 1.44 \times 10^7$


$$= 1.44 \times 10^7$$

$$5. B = \frac{R_{f2}}{R_{f1} + R_{f2}} = \frac{1(k\Omega)}{9(k\Omega) + 1(k\Omega)} = 0.1$$

⑩ Closed-loop Gain.

$$\beta = \left. \frac{V_f}{V_{out}} \right|_{I_f=0} = \frac{R_{f2}}{R_{f1} + R_{f2}} = \frac{11}{910}$$

Feedback Network

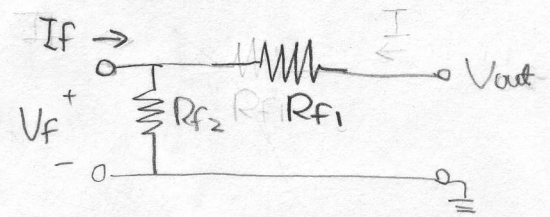

$$\therefore T = A\beta = (1.44 \times 10^7) \cdot \left(\frac{1}{10} \right) = 1.44 \times 10^6 = 1.44 \times 10^6$$


⑪ Cf

Assume the dominate pole is located at collector-base junction of Q5

By MOTC

$$a_1 = [C_1 R_{ii}^0] = (C_f + C_{cb5}) \cdot R_{ii}^0 \quad \text{--- ①}$$
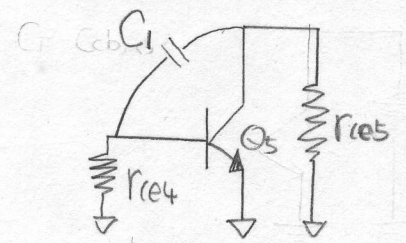
$$\begin{aligned} R_{ii}^0 &= r_{ce4} \cdot [1 - (-g_{m5} r_{ce5})] + r_{ce5} \\ &= 503.5 (\text{k}\Omega) \cdot [1 + 3949] + 102.56 (\text{k}\Omega) \\ &\approx \underline{1.984 (\text{G}\Omega)} \end{aligned}$$



$$C_1 = C_f + C_{cb5}$$

$$\text{also, } a_1 = \frac{0.159}{f_{p,OL}}, \quad f_{p,OL} = \frac{f_{p,CL}}{1+T}, \quad \begin{aligned} f_{p,OL} &: \text{open-loop BW.} \\ f_{p,CL} &: \text{closed-loop BW.} \end{aligned}$$


$$\therefore a_1 = \frac{0.159 \times (1+T)}{f_{p,CL}} \quad \text{--- ②}$$

by solving ① and ②

$$\begin{aligned} C_f &= \frac{0.159 \times (1+T)}{R_{ii}^0 \cdot f_{p,CL}} - C_{cb,05} \\ &= \frac{0.159 \times (1 + 1.44 \times 10^6)}{1.984 (\text{G}\Omega) \cdot 2 (\text{MHz})} - 3 (\text{pF}) \approx \underline{55 (\text{pF})} \end{aligned}$$


(b) High Frequency Analysis

Redraw the schematic as following.

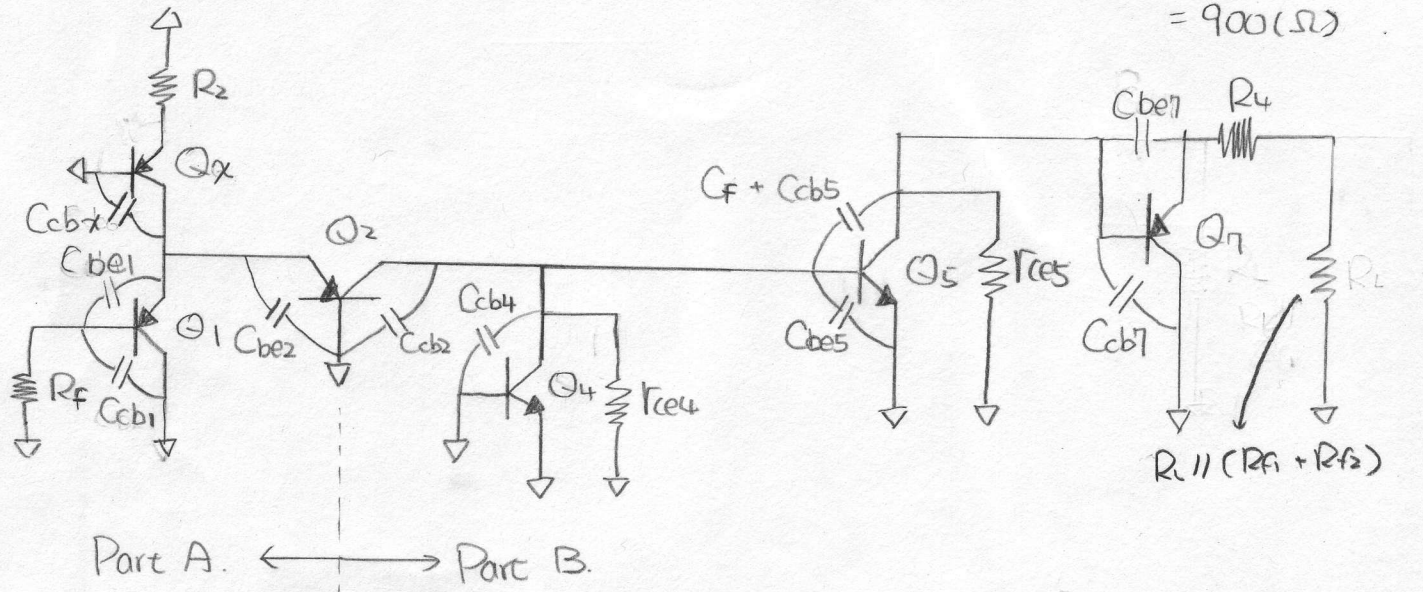

Due to the common-base stage (Q_2), we may separate the circuit into two parts to analyze. (Part A, Part B)

① Part A

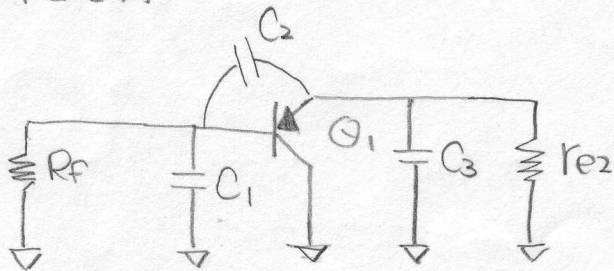

$$C_1 = C_{be1}$$

$$C_2 = C_{be1}$$

$$C_3 = C_{cbx} + C_{be2}$$

$$\theta_1 = C_1 R_{11}^0 + C_2 R_{22}^0 + C_3 R_{33}^0$$

$$= C_1 \cdot R_F + C_2 \cdot \left[R_F \cdot \left(1 - \frac{r_{e2}}{r_{e1} + r_{e2}} \right) + r_{e1} \parallel r_{e2} \right] + C_3 (r_{e1} \parallel r_{e2})$$

$$= 3(pF) \cdot 900(\Omega) + 3.85(pF) \cdot \left[900(\Omega) \left(1 - \frac{1}{2} \right) + \frac{0.5}{7.7(ms)} \right]$$

$$+ 6.85(pF) \cdot \frac{0.5}{7.7(ms)}$$

$$\approx \underline{\underline{5.45(nSec)}}$$

$$a_2 = R_{11}^0 C_1 C_2 R_{22}^1 + R_{11}^0 C_1 C_3 R_{33}^1 + R_{22}^0 C_2 C_3 R_{33}^2$$

$$= R_f \cdot (r_{e1} \parallel r_{e2}) \cdot [C_1 C_2 + C_1 C_3 + C_2 C_3]$$

$$= 900 (\Omega) \cdot \left(\frac{0.5}{7.7 (\text{mS})} \right) \cdot [3 (\text{pF}) \cdot 3.85 (\text{pF}) + 3 (\text{pF}) \cdot 6.85 (\text{pF}) + 3.85 (\text{pF}) \cdot 6.85 (\text{pF})]$$

$$= \underline{3.42 (\text{nSec})^2}$$

examine $\frac{a_2}{a_1} = 0.628 (\text{nSec}) \ll a_1 = 5.45 (\text{nSec})$ [


↪ 8 times

we may estimate the poles by separation pole approximation.

$$\therefore f_{p1} = \frac{0.159}{a_1} \approx \underline{29.2 (\text{MHz})}$$

$$f_{p2} = \frac{0.159}{a_2 / a_1} \approx \underline{253.2 (\text{MHz})}$$

⑩ Part B

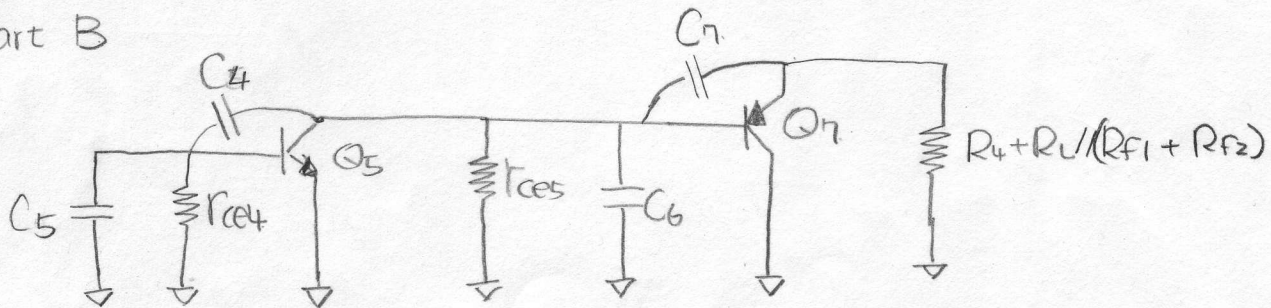

$$C_4 = C_f + C_{cb5} = 58 (\text{pF})$$

$$C_5 = C_{cb2} + C_{cb4} + C_{be5} = 25.25 (\text{pF})$$

$$C_6 = C_{cb7} = 3 (\text{pF})$$

$$C_7 = C_{be7} = 154 (\text{pF})$$

- From the description of the question, we know $C_4 R_{44}^0$ is very big.

$$a_1 = C_4 R_{44}^0 + C_5 R_{55}^0 + C_6 R_{66}^0 + C_7 R_{77}^0 \approx C_4 R_{44}^0$$

$$a_1 = 58 (\text{pF}) \cdot [503.5 (\text{k}\Omega) \cdot (1 + 3949) + 102.56 (\text{k}\Omega)] = 0.115 (\text{sec})$$

$$f_{p3} = \frac{0.159}{0.115} \approx 1.34 (\text{Hz})$$

Op-amp BW.

$$A_2 = \begin{bmatrix} C_4 R_{44}^0 & C_5 R_{55}^4 \\ C_4 R_{44}^0 & C_6 R_{66}^4 \\ C_4 R_{44}^0 & C_7 R_{77}^4 \end{bmatrix} + \begin{bmatrix} C_5 R_{55}^0 & C_6 R_{66}^5 \\ & + \\ C_5 R_{55}^0 & C_7 R_{77}^5 \end{bmatrix} + \begin{bmatrix} C_6 R_{66}^0 & C_7 R_{77}^6 \end{bmatrix}$$

too small

too small

$$\approx C_4 R_{44}^0 [C_5 R_{55}^4 + C_6 R_{66}^4 + C_7 R_{77}^4]$$

$$\begin{aligned} \therefore \frac{A_2}{A_1} &= C_5 R_{55}^4 + C_6 R_{66}^4 + C_7 R_{77}^4, & R_{55}^4 &= r_{ce4} // \frac{1}{g_{m5}} // r_{ce5} \approx 26(\Omega) \\ &= (25.25(\text{pF}) \cdot 26(\Omega)) + (25.25(\text{pF}) \cdot 26(\Omega)) \\ &+ 3(\text{pF}) \cdot 26(\Omega) & R_{66}^4 &= r_{ce5} // \frac{1}{g_{m5}} // r_{ce4} \approx 26(\Omega) \\ &+ 154(\text{pF}) \cdot 128(\Omega) & R_{77}^4 &= [(r_{ce5} // \frac{1}{g_{m5}} // r_{ce4}) \cdot (1 - A_v) \\ &= 20.4(\text{nSec}) & &+ \frac{1}{g_{m7}} // (R_4 + R_L // (R_{51} + R_{52})) \\ & & &= [26(\Omega) \cdot (1 - 0.94) + \frac{1}{7.7(\text{mS})} // (209(\Omega) \\ & & &= + 10(\text{k}\Omega) // 10(\text{k}\Omega)] \approx 128\Omega \end{aligned}$$

$$\therefore \frac{A_2}{A_1} = 20.4(\text{nSec}) \ll A_1 = 0.115(\text{Sec})$$

we may estimate the poles by separation pole approximation

$$\therefore f_{p3} = \frac{0.159}{A_1} \approx 1.38(\text{Hz})$$

$$f_{p4} = \frac{0.159}{A_2 / A_1} \approx 17.79(\text{MHz})$$

To summarize part A and B

There are four poles in the circuit.

$$\begin{array}{ccccccc} f_{p3} & < & f_{p4} & < & f_{p1} & < & f_{p2} \\ 1.38(\text{Hz}) & < & 17.79(\text{MHz}) & < & 29.2(\text{MHz}) & < & 253.2(\text{MHz}) \end{array}$$

f_{p3} is the dominant pole.

⊗ Bode plot.

$$20 \log |A_{OL}| = 20 \log |1.4 \times 10^7| = 143.2 \text{ dB} \quad (1)$$

$$20 \log \left| \frac{1}{\beta} \right| = 20 \log |10| = 20 \text{ dB} \quad (2)$$





The intercept point of $20 \log |A_{OL}|$ and $20 \log \left| \frac{1}{\beta} \right|$ is the 3dB closed-loop bandwidth.

$$\therefore \left\{ \begin{array}{l} f_{p, OL} = 1.38 \text{ Hz} \\ f_{p, CL} = 2 \text{ MHz} \\ \text{phase margin} = 72^\circ \\ \text{gain margin} = -24 \text{ dB} \end{array} \right\} \Rightarrow \text{This amplifier is stable.}$$

The plot is shown in next page.

$|A_{OL}(f)| \text{ dB}$

143.2 dB

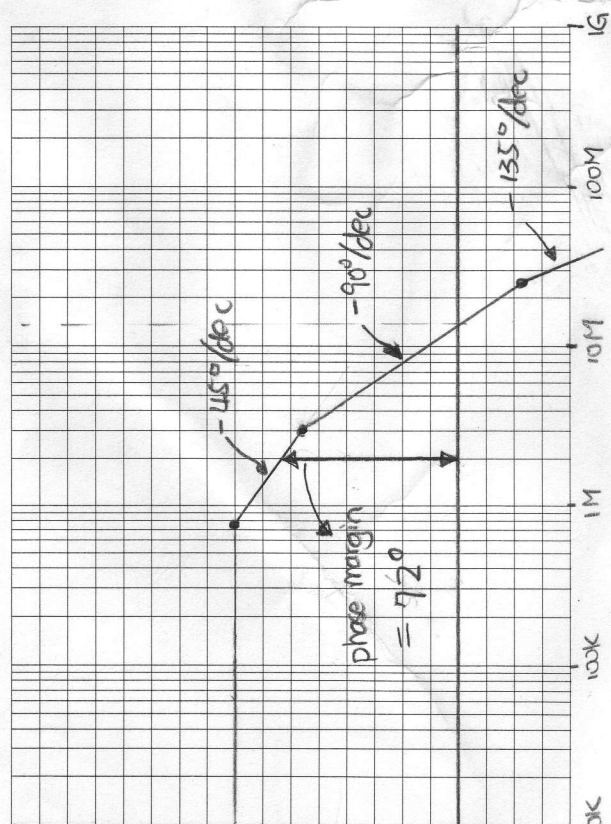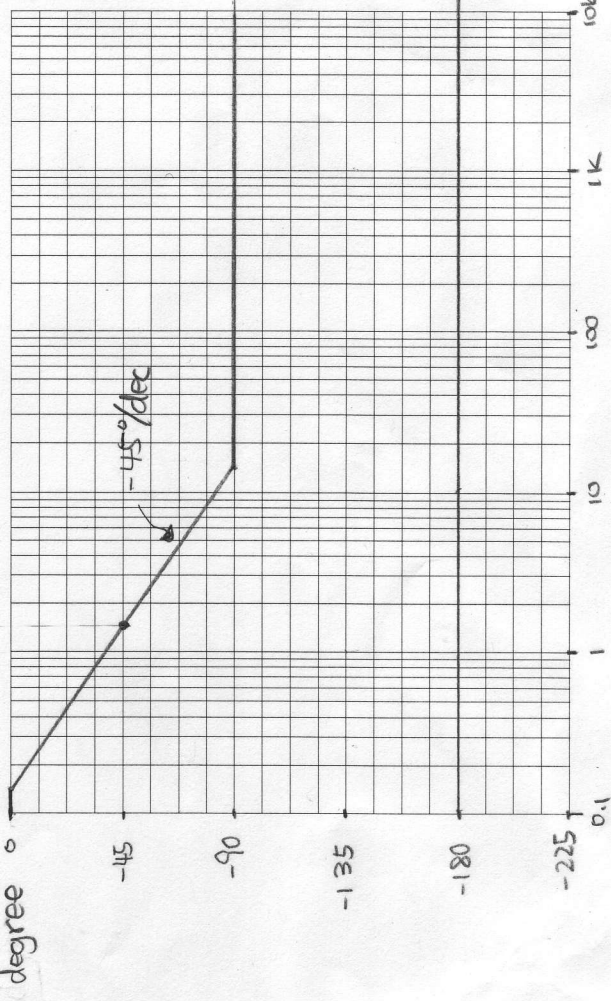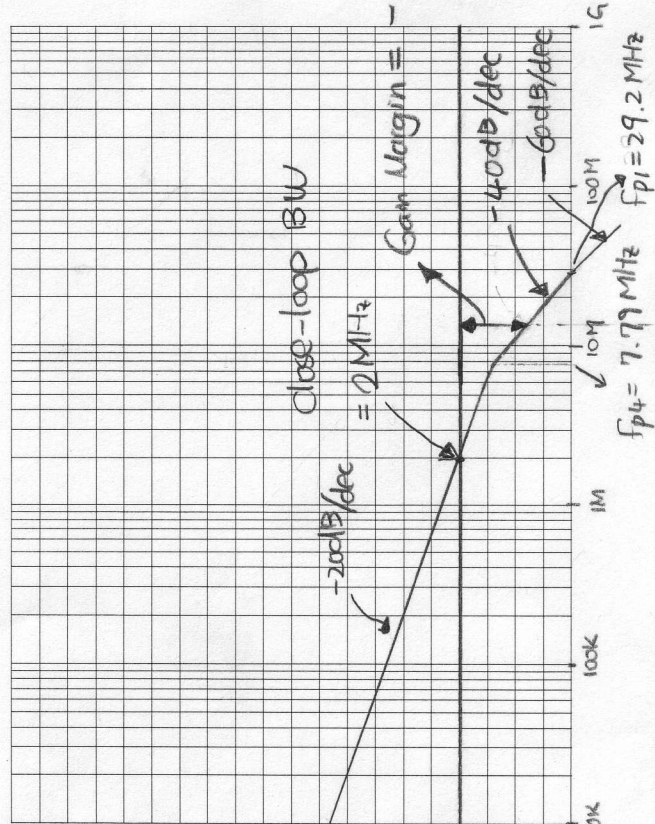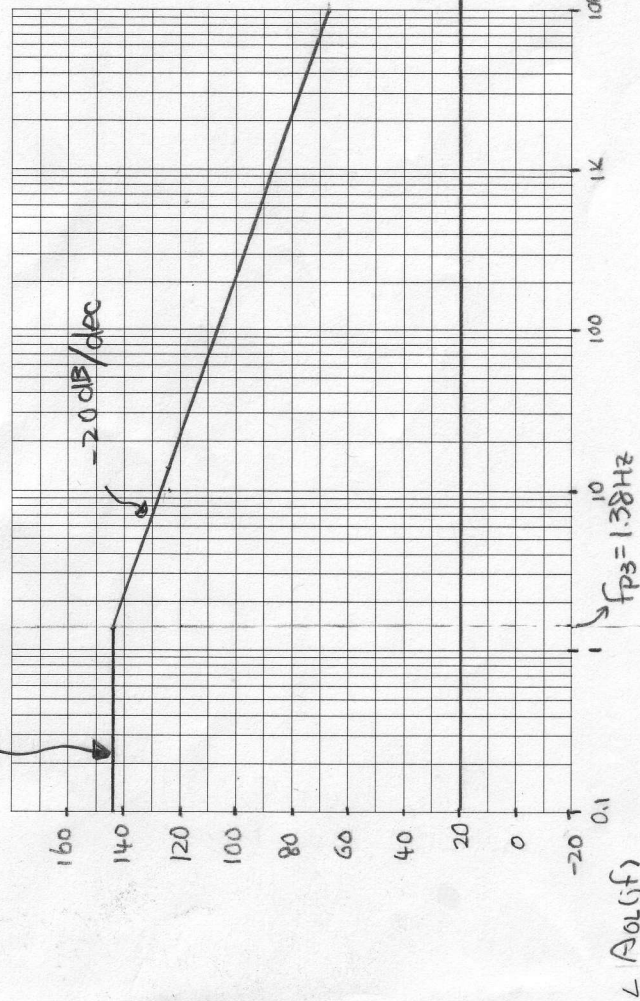

frequency, log (Hz)