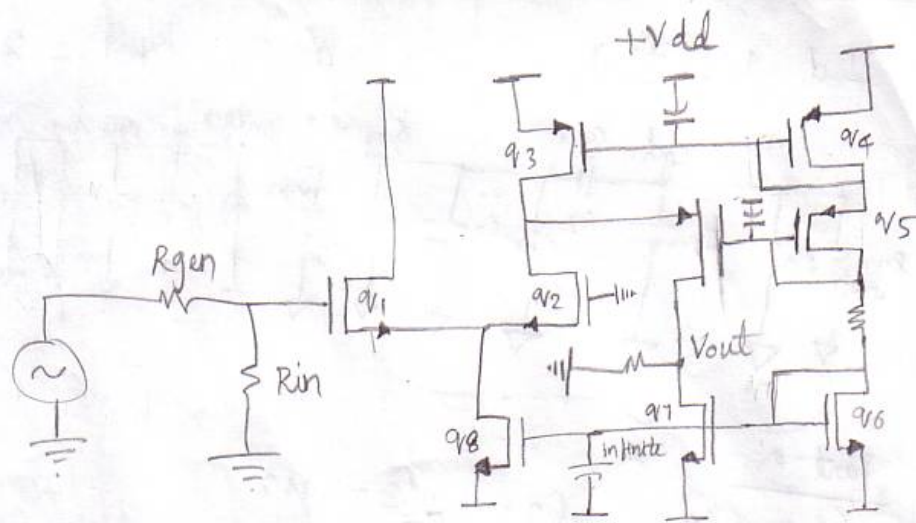




To find R_{bias} we need V_{gs} .

$$I_d = g_m (V_{gs} - V_{th})$$


$$V_{gs} = \frac{I_d}{g_m} + V_{th} = \frac{0.2 \text{ mA}}{1 \text{ mS}} + 0.3 \text{ V} = 0.5 \text{ V}$$

$$R_{bias} = \frac{[6 - 3(V_{gs})] \text{ V}}{0.2 \text{ mA}} = \frac{[6 - 4.5] \text{ V}}{0.2 \text{ mA}} = \underline{\underline{22.5 \text{ k}\Omega}}$$

To find W_g we have

$$\begin{aligned} I_{d,8} = 0.4 \text{ mA} = 2 \cdot I_{d,6} & \quad W_{g,8} = 2 \cdot W_{g,6} = 4 \mu\text{m} \\ I_{d,3} = 0.4 \text{ mA} = 2 \cdot I_{d,4} & \quad W_{g,3} = 2 \cdot W_{g,4} = 4 \mu\text{m} \\ I_{d,7} = I_{d,6} = 0.2 \text{ mA} & \rightarrow W_{g,7} = W_{g,6} = 2 \mu\text{m} \end{aligned}$$
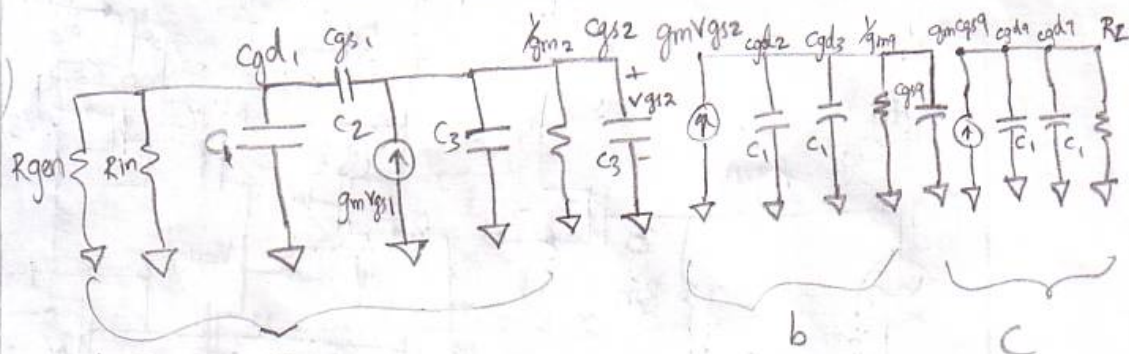
$$I_{d,1} = I_{d,5} = 0.2 \text{ mA}, \quad W_{g,1} = 2 \mu\text{m}$$



Part a

$$C_1 = c_{gd1}, \quad C_3 = c_{gd2} + c_{gs2}$$

$$C_2 = c_{gs1}$$

$$a_1 = (R_{11}^0 C_1 + R_{22}^0 C_2 + R_{33}^0 C_3) \text{ sec}$$

$$R_{11}^0 = R_{gen} \parallel R_{in} = 10 \text{ k} \parallel 9 \text{ k} = 909 \Omega$$

$$R_{22}^0 = R_i (1 - A_v) + r_{o1} \parallel R_{Leq} = R_i \left(1 - \frac{R_{Leq}}{R_{Leq} + \frac{1}{g_{m1}}} \right) + \frac{1}{g_{m1}} \parallel \frac{1}{g_{m2}}$$

$$\text{Here } R_{Leq} = r_{e2} = \frac{1}{g_{m2}}$$

$$R_{22}^0 = R_i \left(1 - \frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m2}} + \frac{1}{g_{m1}}} \right) + 1000 \Omega \parallel 1000 \Omega$$

$$R_{22}^0 = 909 \times \frac{1}{2} + 500 \approx 955 \Omega$$

$$R_{33}^0 = \frac{1}{\frac{1}{1000} + \frac{1}{1000}} = 500 \Omega$$

the above values we can calculate

$$a_1 = [R_{11}^0 C_{gd1} + R_{22}^0 C_{gs1} + R_{33}^0 (C_{gd8} + C_{gs2})] \text{ sec}$$

$$a_1 = 909 \Omega C_{gd1} F + 955 \Omega C_{gs1} F + 500 \Omega (C_{gd8} + C_{gs2}) F$$

$$C_{gd1} = 0.133 \text{ fF} \quad \text{from } f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

$$C_{gs1} = 0.663 \text{ fF}$$

$$C_{gd8} = 0.265 \text{ fF} \quad \left. \begin{array}{l} C_{gs2} = 1.22 \text{ fF} \\ C_{gd2} = 0.22 \text{ fF} \end{array} \right\} \text{ for } Q_3, Q_8.$$

$$a_1 = (909 \Omega)(0.133 \text{ fF}) + 955 \Omega(0.663 \text{ fF}) + 500 \Omega(0.265 + 0.663)$$

$$a_1 = 1.2 \text{ psec}$$

$$a_2 = (R_{11}^0 C_1 C_2 R_{22}^1 + R_{11}^0 C_1 C_3 R_{33}^1 + R_{22}^0 C_2 C_3 R_{33}^2) \text{ sec}$$

$R_{11}^0, R_{22}^1, R_{33}^1, R_{22}^0, R_{33}^2$ - units Ω , C_1, C_2, C_3 - units Fara

$$R_{22}^1 = \frac{1}{g_{m1}} \parallel \frac{1}{g_{m2}} = 500 \Omega \rightarrow \text{Resistance as seen from port 2 with } R_i$$

$R_{33}^1 = R_{33}^0$ with $R_i = 0$; $R_{22}^1 \rightarrow$ is simply R_{22}^0 with $R_i = 0$

$R_{33}^1 = 500 \Omega$; $R_{22}^3 = R_L = 909 \Omega$ (see next page)

$$a_2 = (909 \Omega)(0.133 \text{ fF})(0.663 \text{ fF})(500 \Omega) + (909 \Omega)(0.133 \text{ fF})(0.928 \text{ fF})(500 \Omega) + (500 \Omega)(0.663 \text{ fF})(0.928 \text{ fF})(909 \Omega)$$

$$a_2 = 3.75 \times 10^{-25} \text{ sec}^2$$

the above values we can calculate
 $[R_{11}^0 C_{gd1} + R_{22}^0 C_{gs1} + R_{33}^0 (C_{gd8} + C_{gs2})] \text{ sec}$

$$909 \Omega C_{gd1} F + 955 \Omega C_{gs1} F + 500 \Omega (C_{gd8} + C_{gs2}) F$$

$$= 0.133 \text{ fF} \quad \text{from } f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

$$1 = 0.663 \text{ fF}$$

$$8 = 0.265 \text{ fF}$$

$$.8 = 1.33 \text{ fF} \quad \left. \begin{array}{l} 1 \\ 8 \\ .8 \end{array} \right\} \text{ for } Q_7, Q_8.$$

$$1 = (909 \Omega)(0.133 \text{ fF}) + 955 \Omega(0.663 \text{ fF})$$

$$+ 500 \Omega(0.265 + 0.663) \text{ fF}$$

$$1 = 1.2 \text{ p sec}$$

$$x_2 = (R_{11}^0 C_1 C_2 R_{22}^1 + R_{11}^0 C_1 C_3 R_{33}^1 + R_{22}^0 C_2 C_3 R_{33}^{\frac{1}{2}}) \text{ sec}^2$$

$R_{11}^0, R_{22}^1, R_{33}^1, R_{22}^0, R_{33}^2$ - units Ω , C_1, C_2, C_3 - units Farad

$$R_{22}^1 = \frac{1}{g_{m1}} \parallel \frac{1}{g_{m2}} = 500 \Omega \rightarrow \text{Resistance as seen from port 2 with } R_i = 0$$

$$R_{33}^1 = R_{33}^0 \text{ with } R_i = 0; R_{22}^1 \rightarrow \text{is simply } R_{22}^0 \text{ with } R_i = 0$$

$$R_{33}^1 = 500 \Omega; R_{22}^3 = R_i = 909 \Omega \quad (\text{see next page})$$

$$a_2 = (909 \Omega)(0.133 \text{ fF})(0.663 \text{ fF})(500 \Omega) + (909 \Omega)(0.133 \text{ fF})(0.928 \text{ fF})(500 \Omega)$$

$$+ (500 \Omega)(0.663 \text{ fF})(0.928 \text{ fF})(909 \Omega)$$

$$a_2 = 3.75 \times 10^{-25} \text{ sec}^2$$

In the calculation of a_2 we had

the term $R_{22}^0 C_2 C_3 R_{33}^2$

We can equal this term as

$$R_{22}^0 C_2 C_3 R_{33}^2 = R_{22}^3 C_2 C_3 R_{33}^0$$

R_{22}^3 is the resistance at port 2 with port 3 shorted.

$$\text{Thus } R_{22}^3 = R_i = 909 \Omega$$

For capacitances

$$C_{gd1} = C_{gdq} = 0.133 \text{ fF}$$

$$C_{gd2} + C_{gd3} + C_{gsq} = 0.133 \text{ fF} + 0.265 \text{ fF} + 0.663 \text{ fF}$$

$$C_{gd2} + C_{gd3} + C_{gsq} = 1.06 \text{ fF}$$

$$\text{From } 1 + 1.22 \times 10^{-12} s + 3.75 \times 10^{-25} s^2 = 0$$

we have

$$s = (-1.62 \pm j0.1932) \times 10^{10}$$

Thus we have $\omega_n = \frac{1}{\tau_{a2}} \frac{\text{rad}}{\text{sec}} = \frac{1}{\sqrt{3.75 \times 10^{-28} \text{ sec}}} \frac{\text{rad}}{\text{sec}} = 1.63 \times 10^{12} \frac{\text{rad}}{\text{sec}}$

$$f_p = 2.6 \times 10^{11} \text{ Hz}$$

$f_p = 260 \text{ GHz}$ — natural frequency

Thus there is a -40 dB roll off at 260 GHz

Part b

$$C_1 = (c_{gd2} + c_{gd3} + c_{gs9})F, R_{11}^0 = \frac{1}{g_{m9}} = 1000 \Omega$$

$$C_1 = 1.06 \text{ fF}$$

$$\tau_1 = C_1 R_{11}^0 = 1.06 \text{ psec}$$

$$f_p = \frac{1}{2\pi \times 1.06 \text{ psec}} \approx 0.15 \times 10^{12} \text{ Hz}$$


$$f_p = 150 \text{ GHz}$$

Part c


$$C_1 = c_{gd9} + c_{gd7} = 0.13263 \text{ fF} + 0.13263 \text{ fF}$$

$$C_1 = 0.265 \text{ fF}$$

Problem 1 Part A - $f_p = 260 \text{ GHz}$, roll off = -40 dB/decade

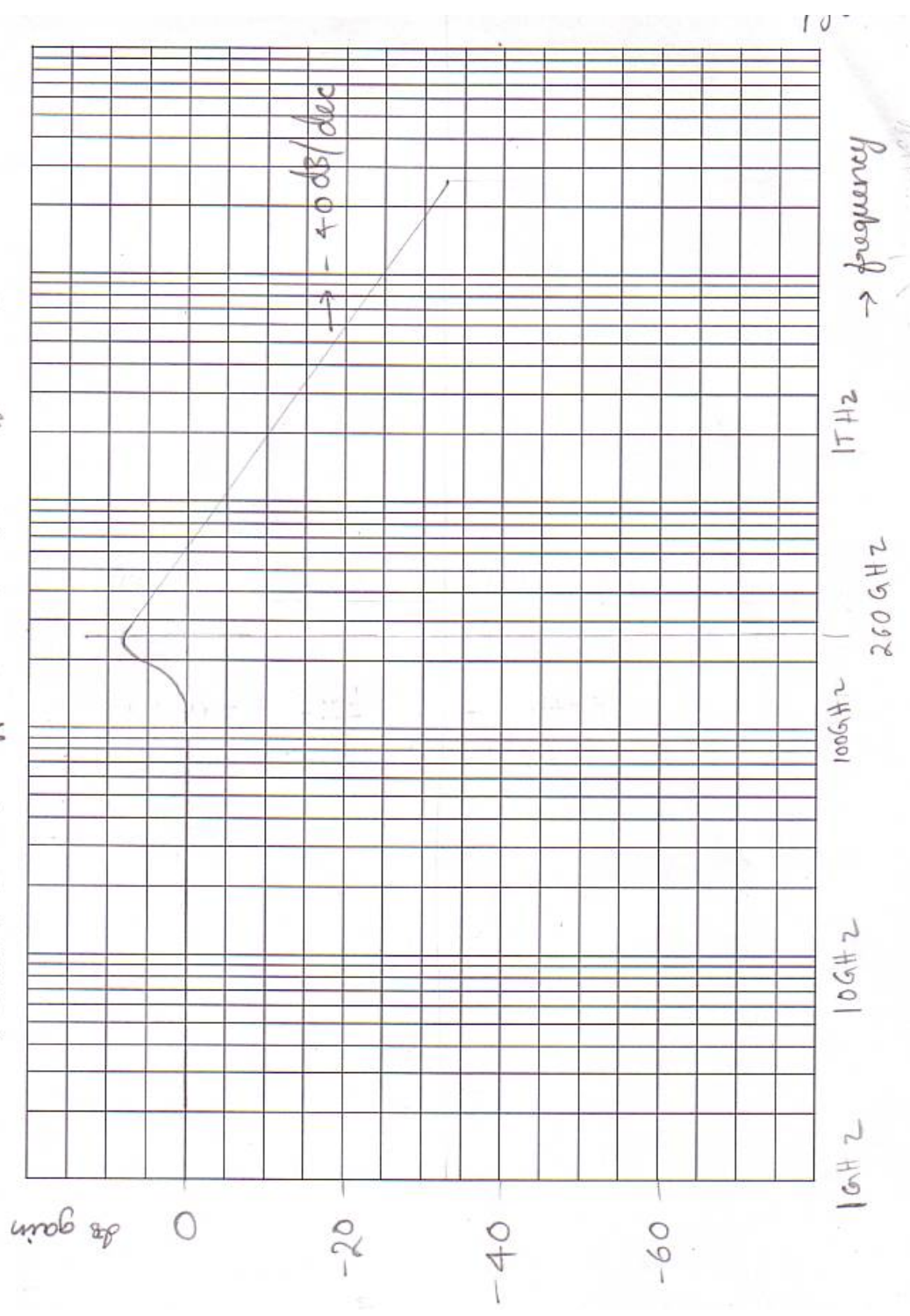

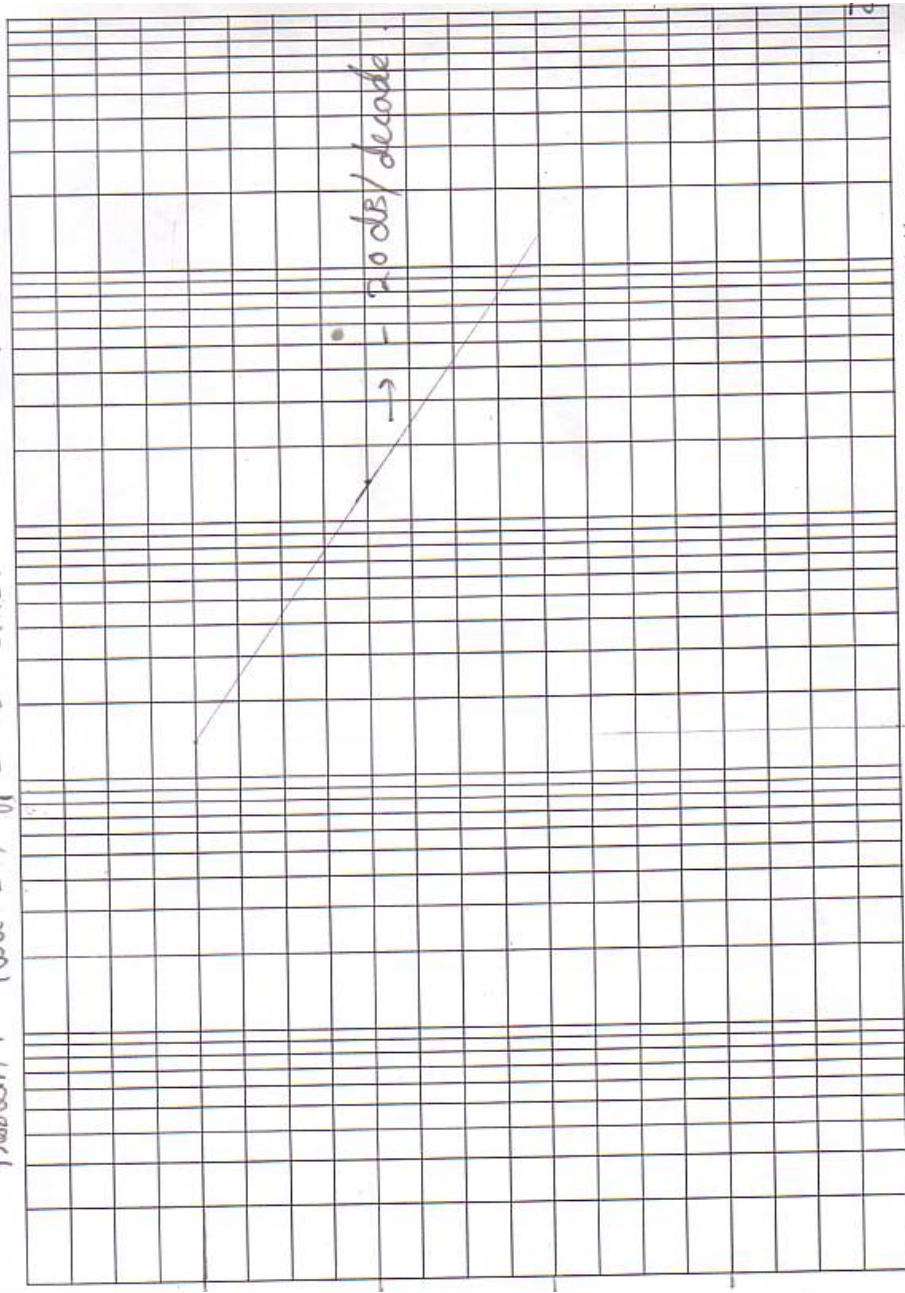Problem 1 - Port B $\rightarrow f_p = 150 \text{ GHz} \rightarrow -20 \text{ dB/decade}$ roll off



10 THz
 $\rightarrow$ frequency


1 THz

100 GHz
150 GHz

10 GHz

GHz

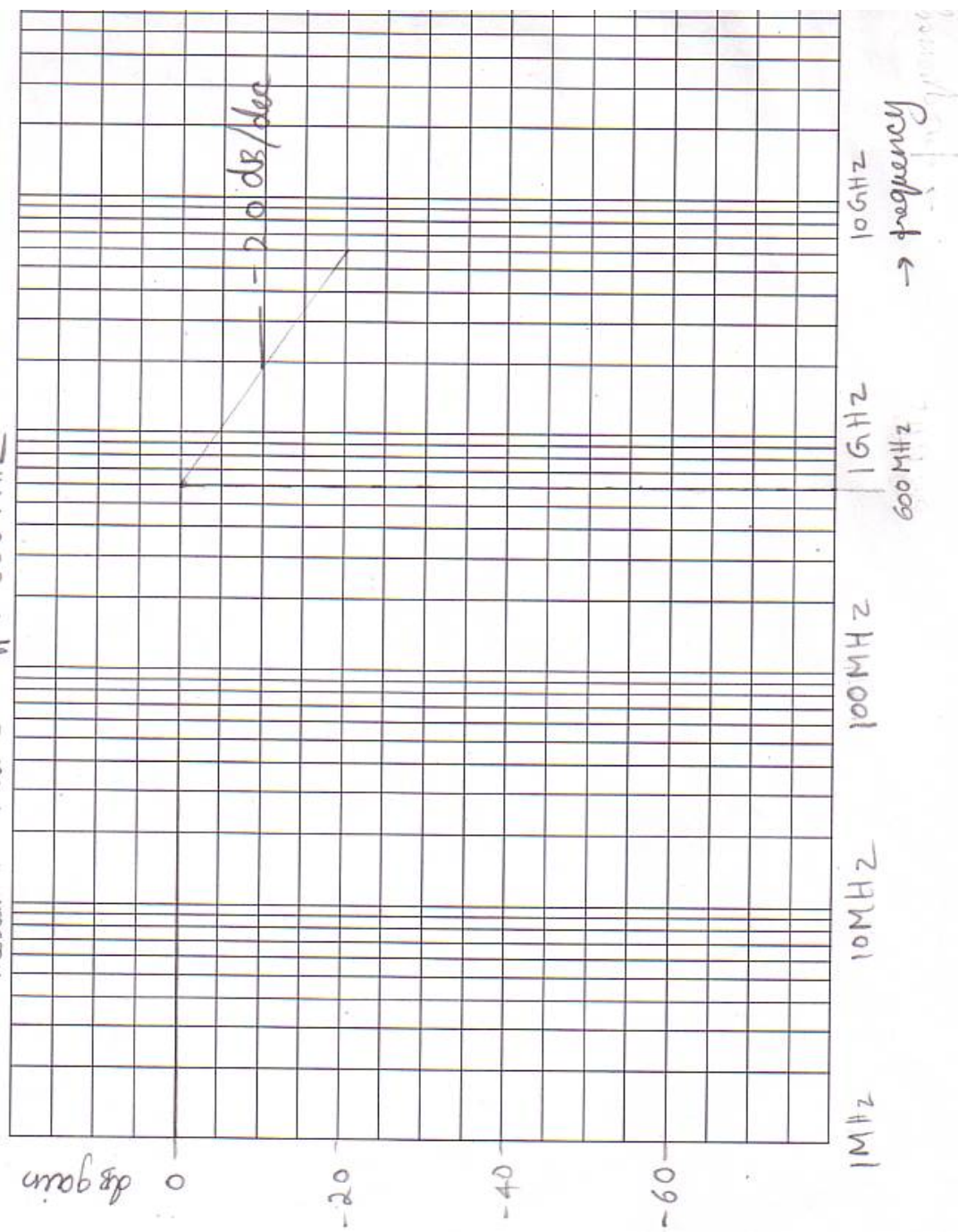Problem 1 - Part C - $f_p = 600 \text{ MHz}$



$$R_{ii}^0 = R_L = 1 \text{ M}\Omega$$


pg 9

$$a_1 = C_1 R_{ii}^0 = 0.26526 \text{ fF} \times 10^6 \Omega$$

$$a_1 = 0.26526 \text{ n s}$$

$$f_{pc} = \frac{0.159}{2.6 \times 10^{-10}} = \boxed{6 \times 10^8 \text{ Hz}} = 600 \text{ MHz}$$

Problem 2

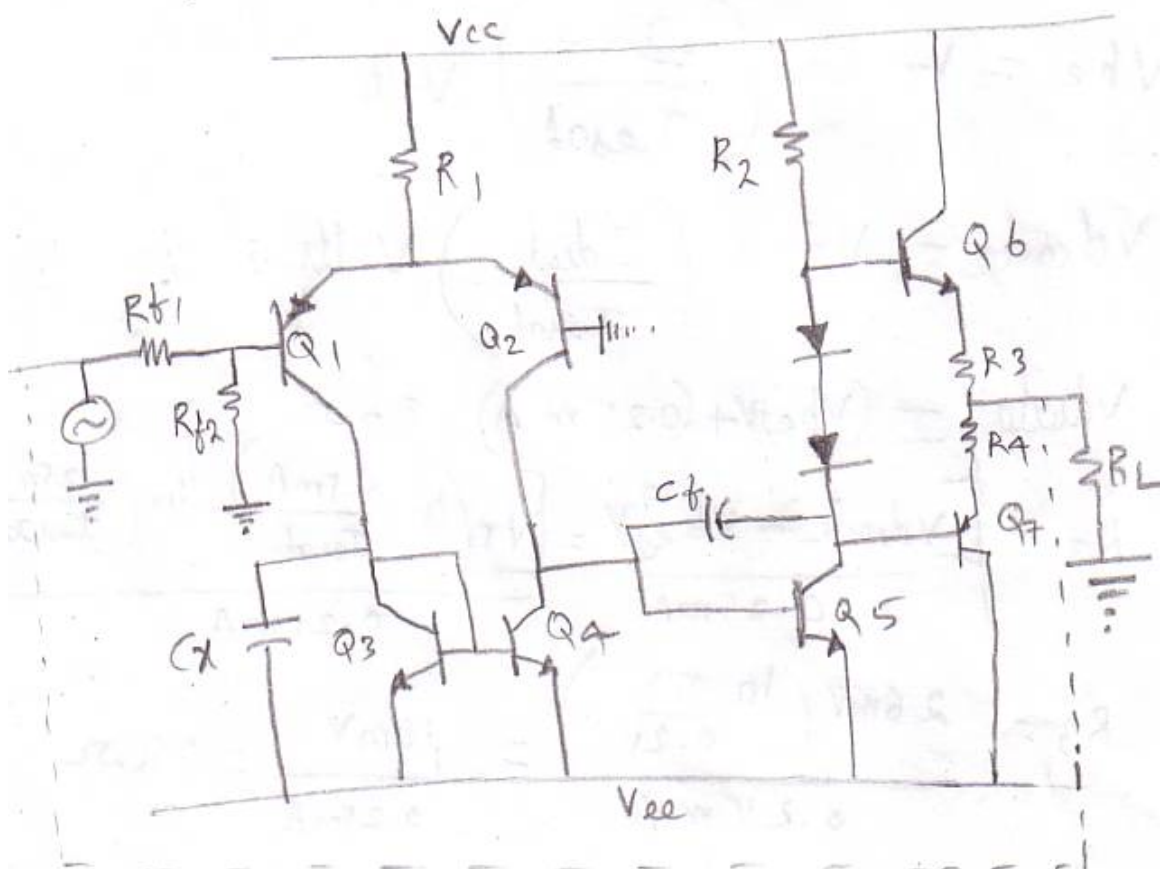

$$R_1 = \frac{[V_{CC} - 0.7] \text{ Volts}}{[2 I_E] \text{ A}} = \frac{(3 - 0.7) \text{ Volts}}{2 \cdot \left(0.2 \text{ mA} + \frac{0.2 \text{ mA}}{100}\right)}$$

$$R_1 = 5.7 \text{ k}\Omega$$

$$R_2 = \frac{(V_{CC} - 0.7) \text{ V}}{(I_{C5}) \text{ A}} = \frac{2.3 \text{ V}}{0.5 \text{ mA}} = 4.6 \text{ V}$$

$$I_C = \left(I_{E \text{ sat}} \times e^{\frac{V_{BE}}{V_T}} \right) \text{ A}$$

$$V_{BE} = V_T \ln \left(\frac{I_C}{I_{E \text{ sat}}} \right) \text{ Volts}$$



$$V_{\text{diode}} = V_T \ln \left(\frac{I_{\text{diode}}}{I_{E \text{ sat}}} \right) \text{ Volts}$$

$$V_{\text{diode}} = (V_{BE}) + (0.25 \text{ mA}) \cdot R_3 \Omega$$

$$R_3 = \frac{[V_{\text{diode}} - V_{BE}] \text{ V}}{0.25 \text{ mA}} = \frac{\left[V_T \left(\ln \left(\frac{0.5 \text{ mA}}{I_{E \text{ sat}}} \right) - \ln \left(\frac{0.25 \text{ mA}}{I_{E \text{ sat}}} \right) \right) \text{ V} \right]}{0.25 \text{ mA}}$$

$$R_3 = \frac{26 \text{ mV} \left(\ln \frac{0.5}{0.25} \right)}{0.25 \text{ mA}} = \frac{18 \text{ mV}}{0.25 \text{ mA}} = 72 \Omega$$

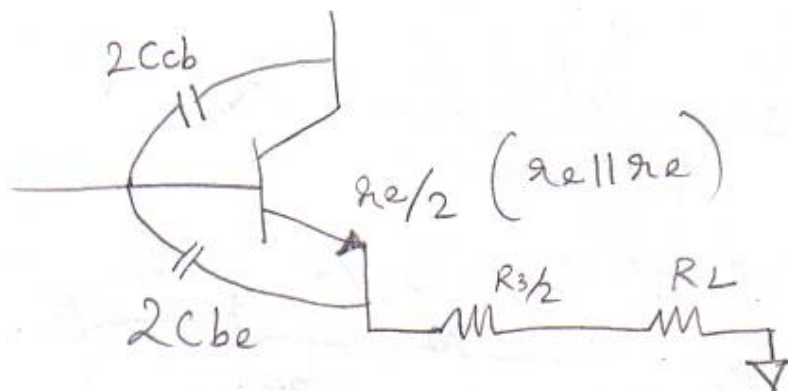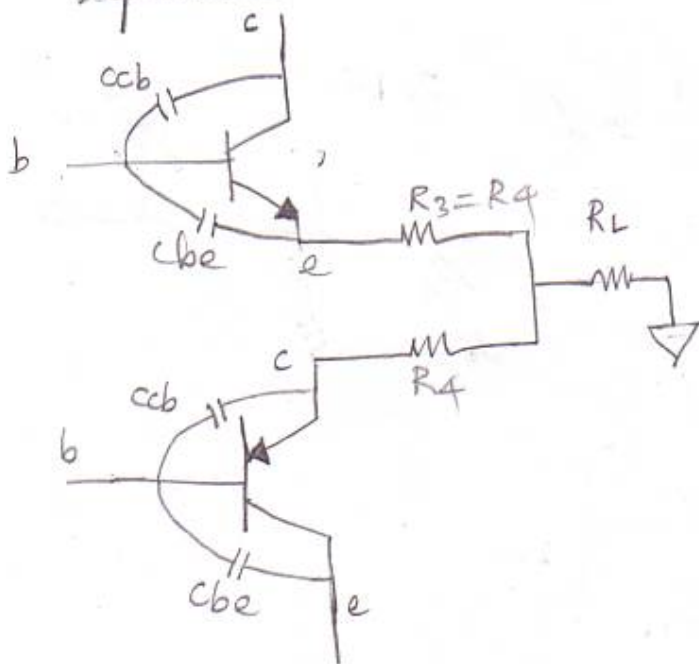
Q_6 and Q_7 can be equivalently (pg 11)
represented as



In order to calculate the gain around the feedback loop we should determine

A_{V1} , A_{V2} , A_{V5} , A_{V6} .

The AC equivalent circuit is as follows.

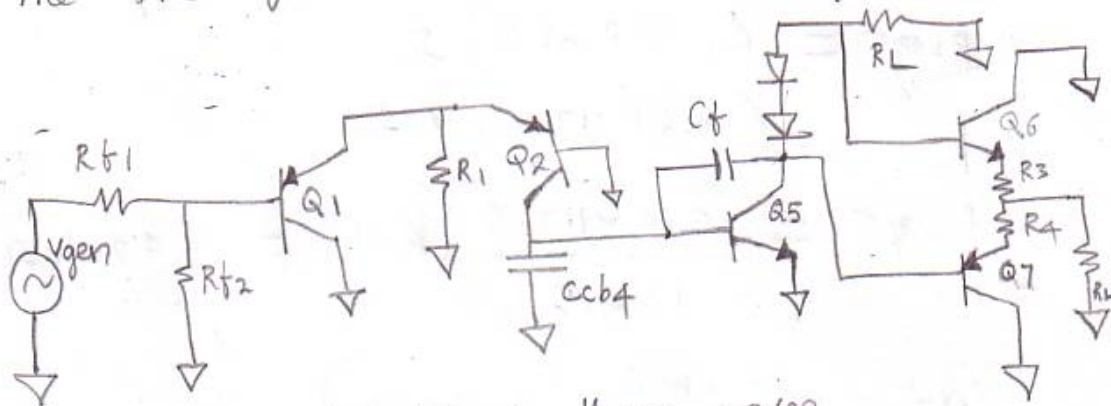

Let us consider the voltage gain from the output to the input

$$A_{V6} = \left(\frac{R_{Leq6} \Omega}{(r_{e6} + R_{Leq6}) \Omega} \times \frac{R_L \Omega}{(R_3 + R_4) \Omega} \right)$$

$$A_{V6} = 0.85$$

$$A_{V5} = -g_{m5} \left(\frac{1}{\Omega} \right) R_{Leq5} (\Omega)$$

$$g_{m5} = \frac{0.5 \text{ mA}}{26 \text{ mV}}$$

$$R_{Leq5} = (R_2 \parallel R_{int6}) \Omega$$

$$R_{Leq5} = [4.6 \text{ K} \Omega \parallel R_{int6} \Omega]$$

$$R_{int6} = [\beta (r_{e6} + R_3 + R_L)] \Omega$$

$$R_{int6} = \beta (r_{e6} + R_3 + R_L) \Omega$$

$$R_{int6} = 100(104 + 72 + 1000) \Omega$$

$$R_{int6} = 100(1176) = 117.6 \text{ k}\Omega$$

$$R_{Leq5} = (R_2 \parallel R_{int6}) \Omega$$

$$= (4.6 \parallel 117.6) \text{ k}\Omega$$

$$R_{Leq5} = \left(\frac{4.6 \times 117.6}{122.2} \right) \text{ k}\Omega = 4.426 \text{ k}\Omega$$

$$A_{V5} = - \frac{0.5 \text{ mA}}{26 \text{ mA}} (4.426 \text{ k})$$

$$A_{V5} = -85$$

$$A_{V2} = g_{m2} \left(\frac{1}{\Omega} \right) R_{in5} \Omega$$

$$R_{in5} = \beta r_{e5}$$

$$A_{V2} = \frac{0.2 \text{ mA}}{26 \text{ mV}} (100) \times \frac{26 \text{ mV}}{0.5 \text{ mA}} = 40$$

$$A_{V1} = \left(\frac{R_{f2} \parallel R_{int1} \Omega}{(R_{f1} + R_{f2} \parallel R_{int1}) \Omega} \times \frac{(R_{Leq1}) \Omega}{(r_{e1} + R_{Leq1}) \Omega} \right)$$

$$A_{V1} = 0.0969 \times 0.49 = 0.047$$

$$R_{f1} = 9k, R_{f2} = 1k, R_{inT1} = \beta (r_{e1} + R_{f1} \parallel r_{e2}) \Omega$$

$$R_{inT1} = 100 \left(\frac{26mV}{0.2mA} + 5.7k\Omega \parallel \frac{26mV}{0.2mA} \right) \Omega$$

$$R_{inT1} = 25.7k\Omega$$

$$R_{Leq1} = (R_{f1} \parallel \left(\frac{1}{g_{m2}} \right) \parallel \left(\frac{1}{g_{m1}} \right)) = 5.7k \parallel 130\Omega \approx 129\Omega$$

Thus, voltage gain A_V is given by

$$A_V = A_{V1} \cdot A_{V2} \cdot A_{V3} \cdot A_{V4}$$

$$= 0.047 \times 40 \times -85 \times 0.85$$

$$A_V = -140$$

The dominant poles
we have for PNP.

$$C_{be1} = C_{je} + \tau_f g_m$$
$$= 50 \text{ fF} + (5 \text{ ps}) \left(\frac{0.2 \text{ mA}}{26 \text{ mV}} \right)$$

$$C_{be1} = 88.5 \text{ fF} \quad ; \quad C_{be2} = 88.5 \text{ fF}$$

$$C_{be5} = C_{je} + \tau_f g_m$$

$$= 10 \text{ fF} + (1 \text{ ps}) \left(\frac{0.5 \text{ mA}}{26 \text{ mV}} \right)$$
$$C_{cb2} = 100 \text{ fF}$$

$$\frac{C_{be5}}{NPN} = 29.23 \text{ fF}$$

$$C_{be6} = C_{je} + \tau_f g_m$$


$$= 10 \text{ fF} + (1 \text{ ps}) \left(\frac{0.25 \text{ mA}}{26 \text{ mV}} \right)$$

$$C_{be6} = 19.62 \text{ fF}$$

$$C_{cb5} = 20 \text{ fF}$$

$$C_{cb6} = 20 \text{ fF}$$

$$C_{cb4} = 20 \text{ fF}$$

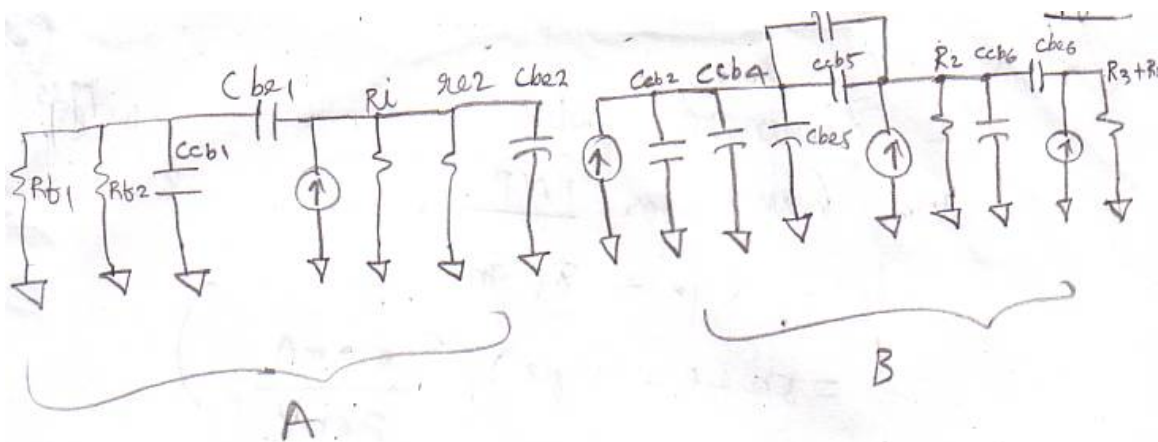

Part A

$$a_1 = C_{cb1} (R_i \parallel R_{int1}) + C_{be1} ((R_i(1-A_1) + R_{Leq1}) \parallel R_{be1}) + C_{be2} R_{Leq1} \rightarrow (1)$$

$$R_{int1} = (\beta + 1)(r_{e1} + R_i \parallel r_{e2})$$

$$\approx 100(130 + 127) \Omega$$

$$R_{Leq} = R_i \parallel r_{e2}$$

$$= 5.7k\Omega \parallel 130\Omega$$

$$R_{Leq} = 127\Omega$$

$$R_{int1} \approx 25.7k\Omega$$

$$R_{be1} = \beta r_{e1} \Omega$$

$$= 100(130) \Omega$$

$$= 13k\Omega$$

$$A_1 = \frac{R_{Leq1}}{R_{Leq1} + r_{e1}}$$

From the values of R and C and (1) we get

$$a_1 = 138 \mu\text{sec}$$

$$a_2 = (R_i \parallel R_{int1})(r_{e1} \parallel R_{Leq1})(C_{b1}C_{be1} + C_{b1}C_{be2} + C_{be1}C_{be2}) \rightarrow (2)$$

$$a_2 = 1.45 \times 10^{-21} \text{sec}^2$$

$$1 + a_1 s + a_2 s^2 = 0$$

$$s_1 = -9.616 \times 10^{10} ; s_2 = -7.292 \times 10^9 / s$$

$$f_{p2} = 15.304 \text{ GHz}$$

$$f_{p1} \approx 1.18 \text{ GHz}$$

Part b

$$C_1 = (C_{cb2} + C_{cb4} + C_{bes}) F = 100 \text{ fF} + 20 \text{ fF} + 29.23 \text{ fF}$$

$$C_1 = 149.23 \text{ fF}$$

$$C_2 = C_f + C_{cb5} = 10.02 \text{ pF}$$

$$C_3 = 20 \text{ fF}$$

$$C_4 = 1.96 \times 10^{-14} \text{ F}$$

$$a_1 = (R_{11}^0 C_1 + R_{22}^0 C_2 + R_{33}^0 C_3 + R_{44}^0 C_4) \text{ sec}$$



$R_{11}^0, R_{22}^0, R_{33}^0 \rightarrow \text{units } \Omega ; C_1, C_2, C_3 \rightarrow \text{units F}$

$$R_{11}^0 = \beta R_{e5} = 100 \cdot \frac{26 \text{ mV}}{0.5 \text{ mA}} = 5200 \Omega$$

$$R_{22}^0 = 5200 \Omega (1 - A_{v5}) + 4.6 \text{ k}\Omega \parallel (\beta (r_{e6} + 1072))$$

$$= 5200 \Omega (1 + 85.13) + 4426.84 \Omega$$
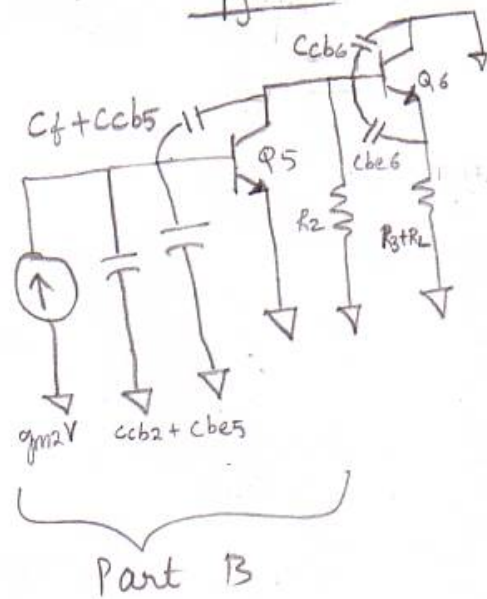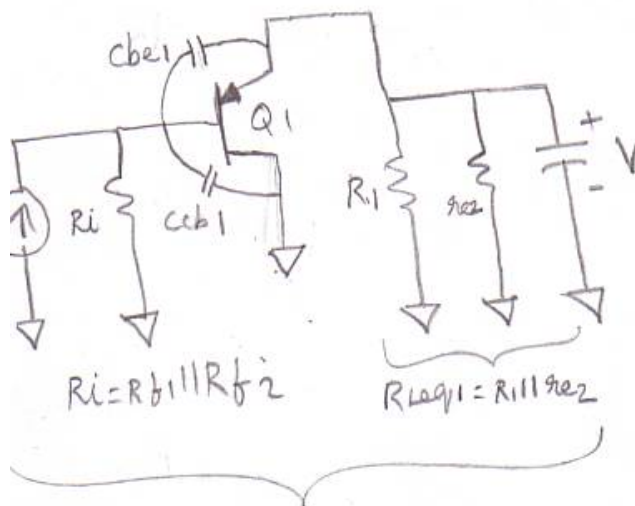
$$R_{22}^0 = 452 \text{ k}\Omega ; R_{22}^1 = R_{33}^1 = R_2 \parallel R_{inT6} = 4.426 \text{ k}\Omega$$



Part A
we also have

$$R_{33}^2 = R_2 \parallel r_{e5}$$

$$R_{33}^2 = 4.6k \parallel \left(\frac{26mV}{0.5mA} \right) = 51.42 \Omega$$

$$R_{44}^2 = R_{be6} \parallel r_{e5} \approx r_{e5} \approx 52 \Omega$$

$$R_{44}^3 = r_{e6} \parallel (R_3 + R_L)$$

$$= 104 \parallel 1072$$

$$R_{44}^3 = 94.8 \Omega ; R_{44}^1 = R_{44}^0 = 4k \Omega$$

$$R_{33}^{\circ} = (R_2 \Omega \parallel (\beta (r_{e6} + R_3 + R_L) \Omega))$$

$$R_{33}^{\circ} = 4.6 \text{ k}\Omega \parallel \beta (r_{e6} + 1072) \Omega = 4.6 \text{ k}\Omega \parallel (100(104 + 1072)) \Omega$$

$$R_{33}^{\circ} = 4426 \Omega ; R_{44}' = R_{44}^{\circ} = 462 \Omega$$

$$R_{44}^{\circ} = \left[R_{33}^{\circ} (1 - A_{v6}) \Omega + (1072 \parallel r_{e6}) \Omega \right] \parallel \beta r_{e2} \Omega$$

$$R_{44}^{\circ} = 46.2 \Omega$$

$$a_1 = (5200 \Omega) (149.23 \text{ fF}) + (452 \text{ k}\Omega) (10.02 \text{ pF}) + (4426 \Omega) (20 \text{ fF}) + (462 \Omega) (19.6 \text{ fF})$$

$$a_1 \approx 4.53 \mu \text{secs}$$


a_1 is in μsecs - It's likely that a_1 contributes to the dominant pole.

$$a_2 = (R_{11}^{\circ} C_1 C_2 R_{22}' + R_{11}^{\circ} C_1 C_3 R_{33}' + R_{11}^{\circ} C_1 C_4 R_{44}' + R_{22}^{\circ} C_2 C_3 R_{33}^2 + R_{22}^{\circ} C_2 C_4 R_{44}^2 + R_{33}^{\circ} C_3 C_4 R_{44}^3) \text{ sec}^2$$



$$a_2 = (5200 \Omega) (149.23 \text{ fF}) (10.02 \text{ pF}) (4426 \Omega) + (5200 \Omega) (149.23 \text{ fF}) (20 \text{ fF}) (4426 \Omega) + (5200 \Omega) (149.23 \text{ fF}) (19.6 \text{ fF}) (462 \Omega) + (452 \text{ k}\Omega) (149.23 \text{ fF}) (20 \text{ fF}) (51.42 \Omega) + (452 \text{ k}\Omega) (10.02 \text{ pF}) (19.6 \text{ fF}) (52 \Omega) + (4426 \Omega) (20 \text{ fF}) (19.6 \text{ fF}) (46.2 \Omega)$$

From the orders of magnitude of the terms in a_2 we can say that a_2 is of the order of 10^{-17} sec^2 .

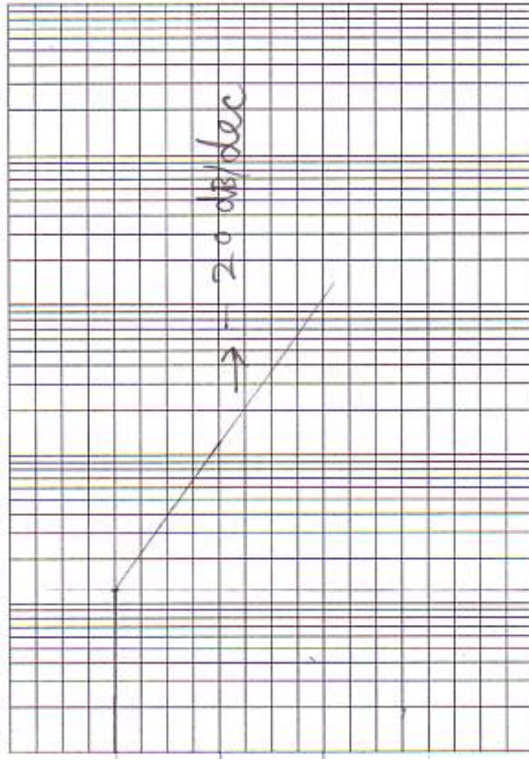
Then the dominant pole is $f_{p1} = \frac{0.159}{a_1} = 35 \text{ kHz}$
 ($\frac{a_2}{a_1}$ is in 10^{-11} sec which is $\ll a_1$, Hence SPA works here)



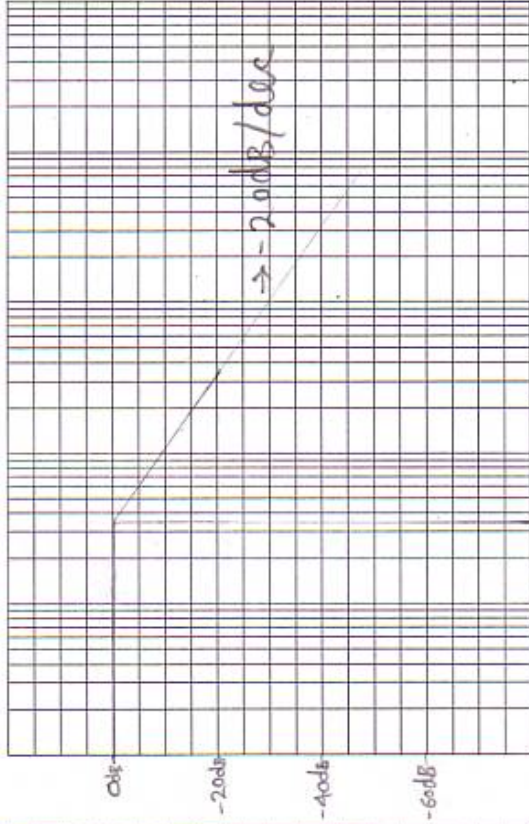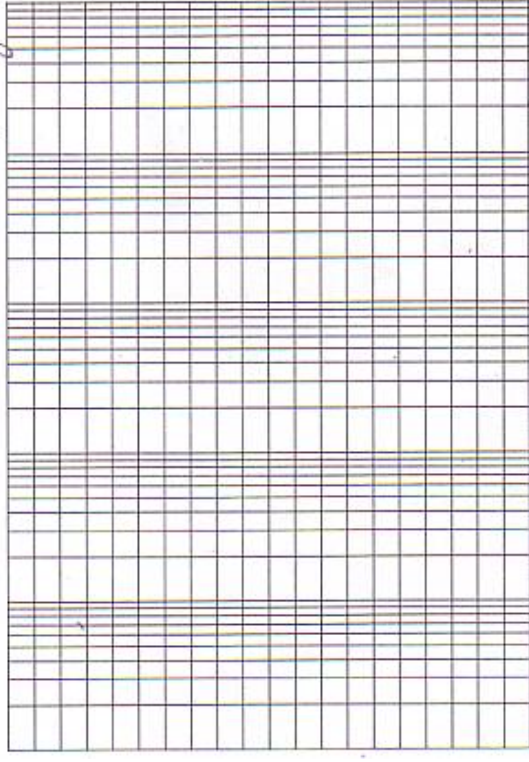1.06GHz 1.18GHz 1.27GHz
 $\rightarrow$ frequency




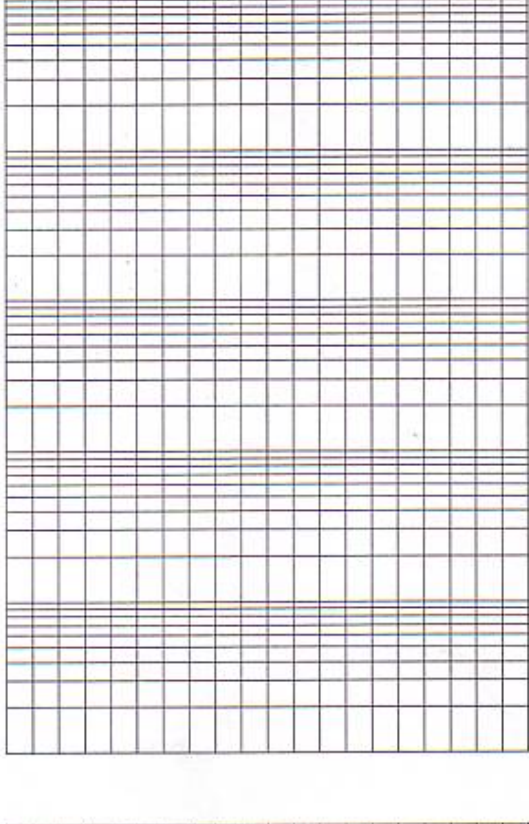1kHz 10kHz 35kHz 100kHz
 $\rightarrow$ frequency



Thus the 2 dominant poles are ^(pg 21)
 1.18 GHz and 35 kHz

Problem 3

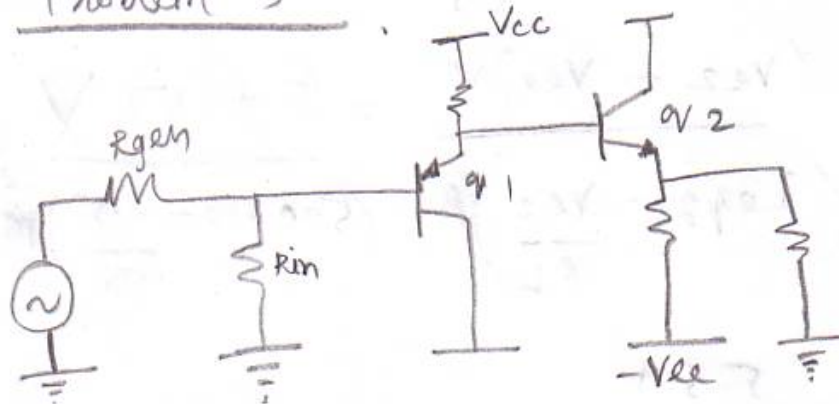

(a) DC bias

$$I_{BQ1} = \frac{(I_{CQ1})A}{\beta} = \frac{100 \text{ mA}}{50} = 2 \text{ mA}$$

$$V_{B1} = I_{BQ1} R_{gen} // R_{in} = 2 \text{ mA} \cdot 250 \Omega = 0.5 \text{ V}$$

$$V_{E1} = 0.5 + 0.7 = 1.2 \text{ V}$$

$$R_{E1} = \frac{(V_{CC} - V_{E1})V}{\left[(\beta + 1)I_{B1} + \frac{500}{50} \right] A} = \frac{(3.8)V}{102 \text{ mA} + 10 \text{ mA}} = 34 \Omega$$

$$V_{e2} = V_{e1} - 0.7 = 0.5 \text{ V}$$

$$R_{e1} = \frac{(V_{cc} - V_{e1}) \text{ V}}{\left((\beta + 1) I_{B1} + \frac{500}{50} \right) \text{ A}} = \frac{3.8 \text{ V}}{102 \text{ mA} + 10 \text{ mA}} = 34 \Omega$$

$$R_{e2} = \frac{(V_{e2} - V_{ee}) \text{ V}}{\left(I_{eq2} - \frac{V_{e2}}{R_L} \right) \text{ A}} = \frac{(5 + .5) \text{ V}}{\left(500 + 10 - \frac{0.5}{50} \right) \text{ mA}}$$

$$R_{e2} = \frac{5.5 \text{ V}}{(500 + 10 - 10) \text{ mA}} = 11 \Omega$$

Mid-Band Gain

$$\frac{V_{out}}{V_{gen}} = \frac{V_{in}}{V_{gen}} \cdot \frac{V_{out}}{V_{in}}$$

$$\frac{V_{out}}{V_{gen}} = \frac{(R_{in} \parallel R_{inQ1}) \Omega}{(R_{gen} + R_{in} \parallel R_{inQ1}) \Omega} \cdot A_{v1} \cdot A_{v2}$$

$$A_{v1} = \frac{(R_{e1} \parallel R_{inQ2}) \Omega}{\left(\frac{1}{g_{m1}} + R_{e1} \parallel R_{inQ2} \right) \Omega}$$

$$R_{in Q2} = \beta(r_{e2} + R_{Leq}) \Omega \approx 452 \Omega$$

$$R_{in Q1} = \beta(r_{e1} + R_{e1} \parallel R_{in Q2}) \Omega \approx 1.6 k\Omega$$

$$r_{e1} = \left(\frac{1}{g_{m1}} \right) \Omega = \left(\frac{V_T}{I_{e1}} \right) \frac{V}{A} = 0.26 \Omega$$

$$R_{e1} = 34 \Omega$$


$$R_{Leq} = (R_{e2} \parallel R_{Load}) \Omega$$

$$R_{Leq} = 11 \Omega \parallel 50 \Omega = 9 \Omega$$

$$\frac{V_{out}}{V_{gen}} = \underbrace{\frac{(381) \Omega}{(500 + 381) \Omega}}_{0.4324} \cdot \underbrace{\frac{(31.62) \Omega}{(0.26 + 31.62) \Omega}}_{0.9918} \cdot \underbrace{\frac{(9) \Omega}{(0.052 + 9) \Omega}}_{0.9942}$$

$$\frac{V_{out}}{V_{gen}} = 0.426$$

(b) MOTC to find poles

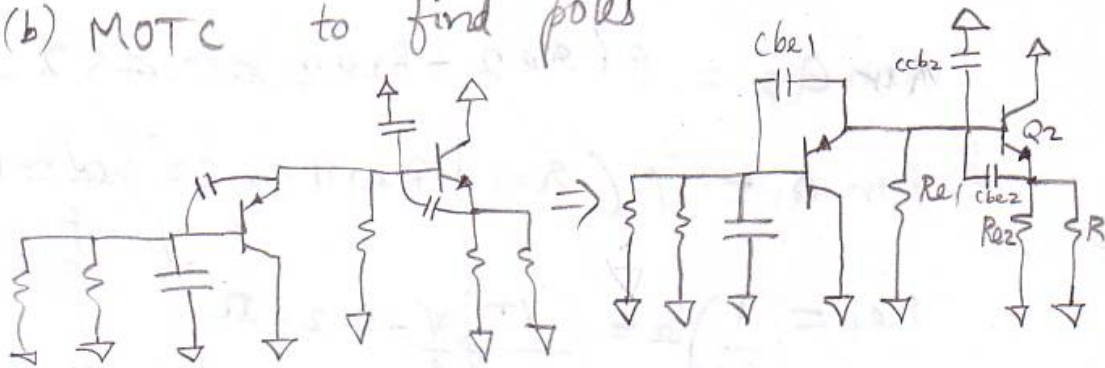

$$C_1 = C_{be1} = 100 \text{ fF}$$

$$C_2 = C_{be2} = C_{je} + g_{m1} \tau_f = 40 \text{ fF} + \frac{100}{26} \times 2 \text{ pF} = 7.723 \text{ pF}$$

$$C_4 = C_{be2} = C_{je} + g_{m2} \left(\frac{1}{\omega} \right) \text{ sec} = 40 \text{ fF} + \frac{500}{26} \cdot 2 \text{ pF}$$

$$= 38.5 \text{ pF} \quad (\text{Note: } \frac{1}{\omega} \text{ sec} = \text{Farad})$$

$$a_1 = [C_1 R_{11}^0 + C_2 R_{22}^0 + C_3 R_{33}^0 + C_4 R_{44}^0] \text{ s}$$

$$R_{11}^0 = (R_{B1} \parallel R_{inQ1}) \text{ s} \quad R_{22}^0 = \beta R_{E1} \parallel (R_{E1} (1 - A_{V1}) + R_{E1} \parallel R_{inQ2}) \text{ s}$$

$$= 250 \text{ s} \parallel 1.6 \text{ k s} \quad \approx 9.37 \text{ s}$$

$$R_{11}^0 = 216 \text{ s}$$

$$R_{33}^0 = R_{E1} \parallel \left(R_{E1} \parallel \left(R_{E1} + \frac{R_{B1}}{\beta} \right) \right) \parallel R_{inQ2} \text{ (s)} = 34 \text{ s} \parallel 445 \text{ s} \parallel (0.26 \text{ s})$$

$$R_{33}^0 = 4.5 \text{ s}$$

$$R_{44}^{\circ} = \left[R_{be2} \parallel \left(R_{e1} \parallel R_{out1} (1 - A_{v2}) + R_{Leq2} \right) \right] \Omega$$

$$R_{44}^{\circ} = 2 \Omega$$

$$a_1 = C_1 R_{11}^{\circ} + C_2 R_{22}^{\circ} + C_3 R_{33}^{\circ} + C_4 R_{44}^{\circ} \rightarrow (1)$$

$$a_1 = 21.6 \mu\text{sec} + 72.36 \mu\text{s} + 0.45 \mu\text{sec} + 77 \mu\text{sec}$$

Thus we have

$$a_1 = 171.41 \mu\text{sec}$$

$$a_2 = \left(R_{11}^{\circ} C_1 C_2 R_{22}^{\circ} + R_{11}^{\circ} C_1 C_3 R_{33}^{\circ} + R_{11}^{\circ} C_1 C_4 R_{44}^{\circ} + R_{22}^{\circ} C_2 C_3 R_{33}^{\circ} + R_{22}^{\circ} C_2 C_4 R_{44}^{\circ} + R_{33}^{\circ} C_3 C_4 R_{44}^{\circ} \right) \text{sec}^2 \rightarrow (2)$$

$R_{11}^{\circ}, R_{22}^{\circ}, R_{33}^{\circ}, R_{44}^{\circ}, R_{33}^2, R_{22}^{\circ}, R_{44}^2, R_{44}^3, R_{33}^{\circ} \rightarrow \text{units} - \Omega, C_1, C_2, C_3, C_4 \rightarrow \text{units}$

$$R_{22}^{\circ} = 3 \text{ } \Omega \parallel (R_{e1} \parallel R_{inQ2} \parallel R_{e1}) \Omega = 0.26 \Omega$$

$$R_{33}^{\circ} = R_{22}^{\circ} = 0.26 \Omega$$

$$R_{44}^{\circ} = \left(R_{e1} \parallel R_{e1} \right) \Omega (1 - A_{v2}) + \left(R_{Leq1} \parallel \frac{1}{g_{m2}} \right) \Omega \parallel R_{be2} \Omega \approx R_{e2} \approx 0.052$$

$$R_{33}^2 = (R_{e1} \parallel R_{i1} \parallel R_{inQ2}) \Omega = 30 \Omega$$

$$R_{44}^2 = \left[(R_{e1} \parallel R_i) \cdot (1 - A_{v2}) + \left(R_{L2} \parallel \frac{1}{g_{m2}} \right) \right] \parallel R_{b2}$$

$$R_{44}^2 \simeq r_{e2} = 0.052 \Omega$$

$$R_{44}^3 = 0.052 \Omega$$

From (2) and the above values
we get

$$a_2 = 4.610 \times 10^{-22} \text{ sec}^2$$

We have

$$a_1 \gg \frac{a_2}{-a_1}$$

so we can use separated pole approximation

$$f_{p1} = 159 \text{ GHz} \times \frac{1}{171.4} = 927 \text{ MHz}$$

$$f_{p2} = \frac{0.159}{(a_2/a_1)} = 159 \text{ GHz} \times \frac{1}{2.69} = 59.1 \text{ GHz}$$

For the Bode plot we have

$$20 \log \left(\frac{V_{out}}{V_{in}} \right) = 20 \log (0.426)$$

$$= -7.39 \text{ dB}$$

Problem 3 $f_{p1} = 900 \text{ MHz}$; $f_{p2} = 60 \text{ GHz}$

