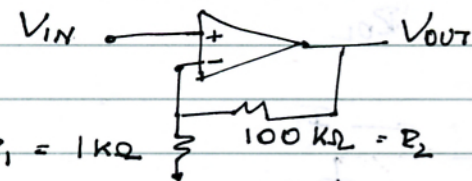


HW #6 SOLUTIONS

1.) V_{IN}  V_{OUT} $A_{DIFF} = 100,000$

$R_1 = 1k\Omega$ $100k\Omega = R_2$


$$V_{OUT} = (V^+ - V^-) A_{DIFF} = \left(V_{IN} - \frac{V_{OUT} \cdot R_1}{R_1 + R_2} \right) A_{DIFF}$$

$$V_{OUT} \left[1 + \frac{A_{DIFF} \cdot R_1}{R_1 + R_2} \right] = V_{IN} \cdot A_{DIFF}$$

a) $\Rightarrow \frac{V_{OUT}}{V_{IN}} = \frac{A_{DIFF} (R_1 + R_2)}{R_1 + R_2 + A_{DIFF} \cdot R_1} = \frac{A_{DIFF}}{1 + \left(A_{DIFF} \cdot \frac{R_1}{R_1 + R_2} \right)}$

$$= \frac{10^5}{1 + 10^5 \cdot \left[\frac{1k}{101k} \right]} = \boxed{100.891}$$

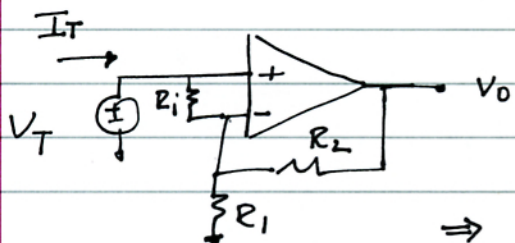b) $Z_{in \text{ open loop}} = 100k\Omega$



$$I_T = (V^+ - V^-) / R_i$$

$$\Rightarrow I_T = \left[V_T - V_O \left(\frac{R_1}{R_1 + R_2} \right) \right] / R_i$$

$$\Rightarrow I_T = \left(V_T - \left(\frac{A_D}{1 + A_D \beta} \right) V_T \cdot \beta \right) / R_i$$


After substituting $V_O = \left(V_T \cdot \frac{A}{1 + A\beta} \right)$ where $\beta = \frac{R_1}{R_1 + R_2}$

$$\Rightarrow I_T = \frac{\left(V_T - \left(\frac{T}{1+T} \right) V_T \right)}{R_i} \text{ where } T = A_D \beta$$

$$\Rightarrow I_T = \frac{V_T}{(1+T) R_i} \Rightarrow \boxed{\frac{V_T}{I_T} = R_i (1+T)}$$

$$\Rightarrow Z_{in(\text{close loop})} = (100k\Omega) (1 + 990.09) = \boxed{99M\Omega}$$

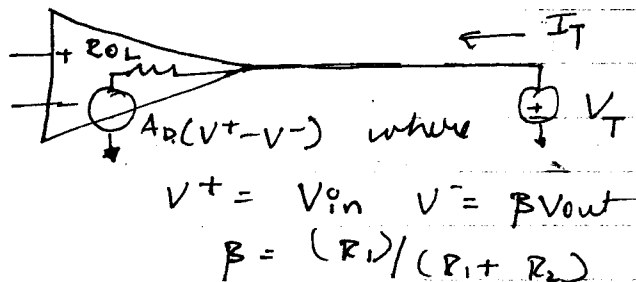c.) $Z_{OUT} \text{ open loop} = 10\Omega = R_{OL}$



Here we get:

$$I_T = \frac{V_T - A_D(V^+ - V^-)}{R_{OL}} = \frac{V_T - A_D(0 - \beta V_T)}{R_{OL}}$$


$$\Rightarrow I_T = \frac{(1 + A_D \beta) V_T}{R_{OL}}$$

$$\Rightarrow \boxed{\frac{V_T}{I_T} = \left(\frac{R_{OL}}{1 + A_D \beta} \right)} = R_{OUT, CL} = \frac{10}{1 + 990.1} = \underline{\underline{0.01\Omega}}$$

$R_{OUT, CL} = 0.01\Omega$

Note: This result can be obtained directly by using the formula $(A_{\infty} \frac{T}{1+T})$ where A_{∞} = Loop gain for infinite feedback gain

2.)

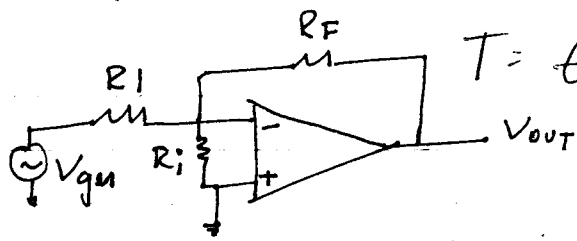

$T =$ ~~closed~~ loop gain with effect of loading included

$$A_{DIFF} = 1000$$

$$R_F = 1\text{M}\Omega$$

$$R_i = 10\text{k}\Omega$$

$$R_i = 2\text{k}\Omega$$

$$V_{OUT} = A_{DIFF} \cdot [V^+ - V^-] = -A_{DIFF} \cdot V^- \quad (\text{Since } V^+ = 0)$$

Now,

$$V^- = V_{gm} \left(\frac{R_i \parallel R_F}{R_i \parallel R_F + R_i} \right) + V_{OUT} \left(\frac{R_i \parallel R_i}{R_i \parallel R_i + R_F} \right)$$

$$V^- = V_{gm} \left[\frac{R_i \parallel R_F}{R_i \parallel R_F + R_i} \right] + V_{OUT} \left[\frac{R_i \parallel R_i}{R_i \parallel R_i + R_F} \right]$$


$$\therefore V_{OUT} = -A_{DIFF} \left[V_{gm} \left(\frac{R_i \parallel R_F}{R_i \parallel R_F + R_i} \right) + V_{OUT} \left(\frac{R_i \parallel R_i}{R_i \parallel R_i + R_F} \right) \right]$$

$$\therefore V_{OUT} \left[1 + A_{DIFF} \cdot \left(\frac{R_i \parallel R_i}{R_i \parallel R_i + R_F} \right) \right] = -A_{DIFF} \cdot V_{gm} \cdot \left(\frac{R_i \parallel R_F}{R_i \parallel R_F + R_i} \right)$$

$$\therefore \frac{V_{OUT}}{V_{gm}} = \frac{-A_{DIFF} \cdot \left[\frac{R_i \parallel R_F}{R_i \parallel R_F + R_i} \right]}{1 + A_{DIFF} \cdot \left(\frac{R_i \parallel R_i}{R_i \parallel R_i + R_F} \right)}$$

$$= \frac{-(1000) \left[\frac{1996}{1996 + 10\text{k}\Omega} \right]}{1 + 1000 \left[\frac{1666}{1666 + 10\text{k}\Omega} \right]} = -62.33$$

Ans: $\frac{V_{OUT}}{V_{gm}} = -62.33$

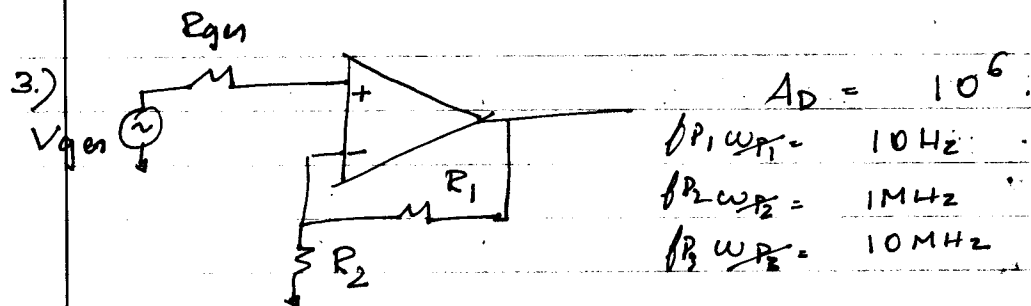

a) $R_1 = 0$ $R_2 = 1 \text{ k}\Omega \Rightarrow \beta = 1$
 b) $R_1 = 9 \text{ k}\Omega$ $R_2 = 1 \text{ k}\Omega \Rightarrow \beta = 0.9$

a) $\phi_m = 0^\circ$ $\text{GM} = 0^\circ$ Loop BW = 7.5 MHz

b) $\phi_m = 45^\circ$ $\text{GM} = < 5 \text{ dB}$ Loop BW = 1 MHz

$T(j\omega) = \frac{1 + (j\omega/\omega_{z_1})}{(1 + j\omega/\omega_{p_1})}$

$\angle T(j\omega) = \tan^{-1}(\omega/\omega_{z_1}) - \tan^{-1}(\omega/\omega_{p_1})$


This gives -45° phase at pole freq & $+45^\circ$ phase at zero freq.
 The tangent is well approximated by a linear fit from $\frac{\omega_p}{10}$ to $10\omega_p$

as by line whose is $-45^\circ/\text{dec}$ and similarly for a zero by a line of slope $+45^\circ/\text{dec}$.

The net phase response is obtained by summing individual responses. (Linear Superposition)


(dB)

Part a: $\beta = 1$

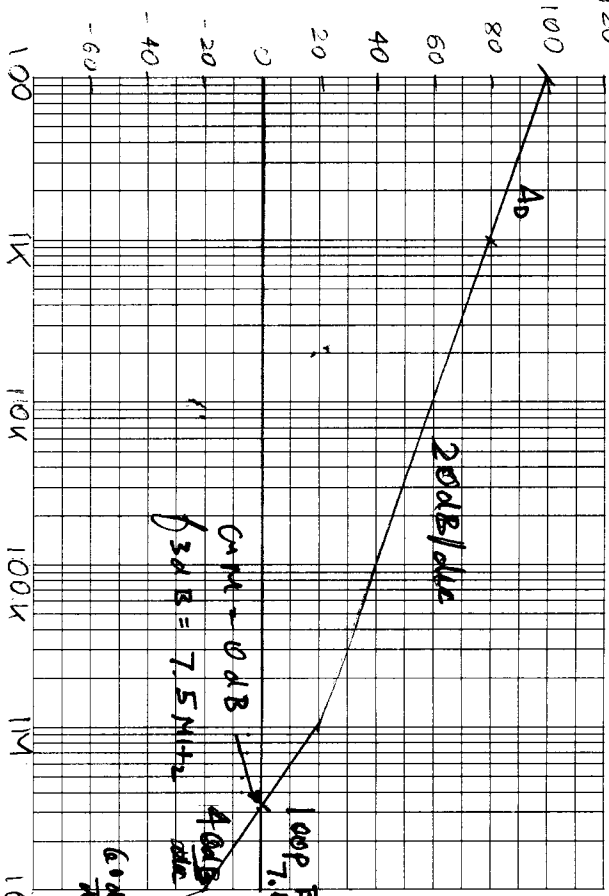


(dB)


Part b: $\beta = 0.9$

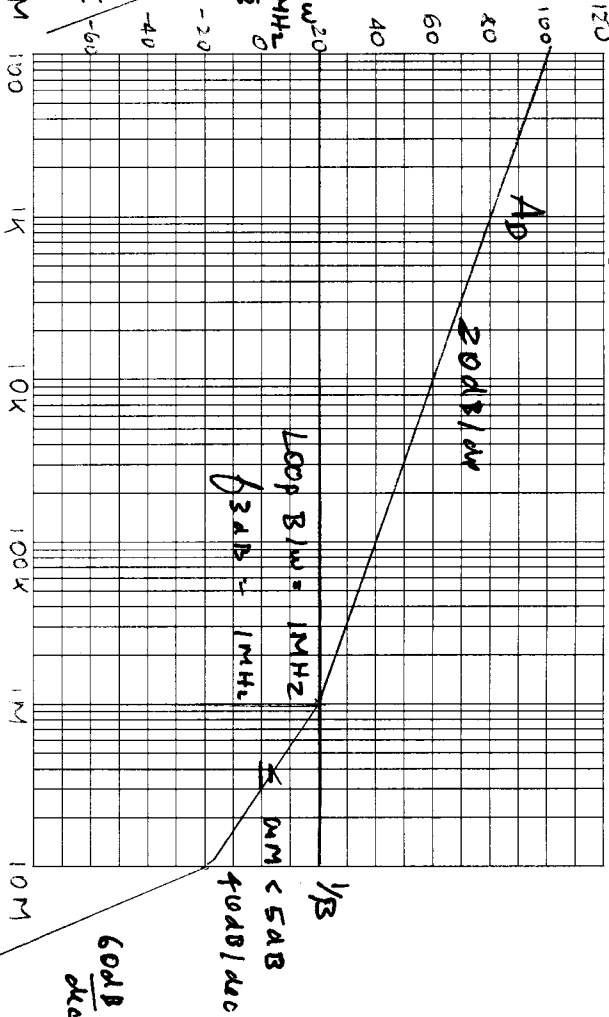


Phase (°)

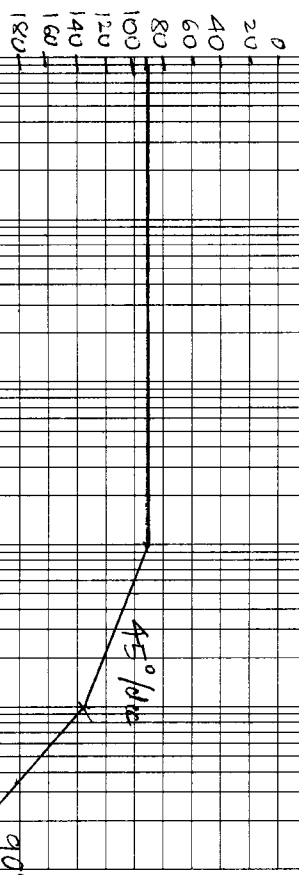

Phase (°)

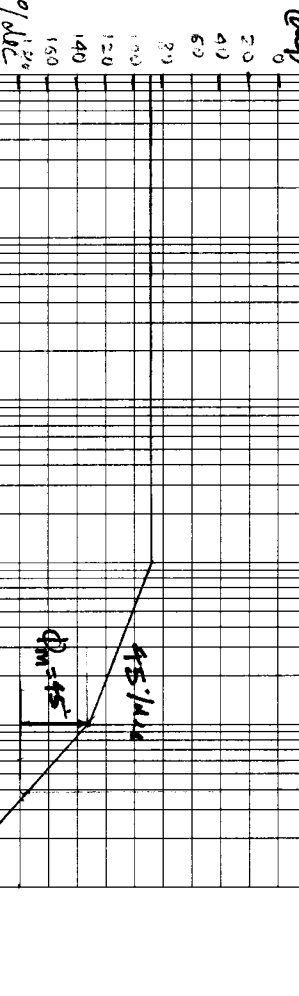

4.)

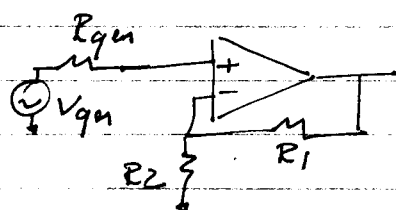

$$A_D = 10^6$$

$$f_{P_1} = 1 \text{ Hz}$$

$$f_{P_2} = 1 \text{ MHz}$$

$$R_{qn} = 0 \Omega$$

$$a) R_1 = 0 \quad R_2 = 1 \text{ k}\Omega$$

$$\beta = \frac{R_2}{R_2 + R_1} = 1$$

$$A_{OL}(s) = \frac{A_D}{(1 + \frac{s}{\omega_{P_1}})(1 + \frac{s}{\omega_{P_2}})} \quad \text{where } \omega_{P_1} = 2\pi f_{P_1}$$

$$\omega_{P_2} = 2\pi f_{P_2}$$

$$A_{CL}(s) = \frac{1}{\beta} \cdot \left[\frac{A_{OL}(s) \beta}{1 + A_{OL}(s) \beta} \right]$$

Put

$$A_{OL}(s) \cdot \beta = T(s) = A_{OL}(s) \cdot (1)$$

$$T(s) = \frac{N_T}{D_T} = \frac{A_D \cdot (1)}{(1 + \frac{s}{\omega_{P_1}})(1 + \frac{s}{\omega_{P_2}})} = \frac{A_D}{\frac{s^2}{\omega_{P_1} \omega_{P_2}} + s(\frac{1}{\omega_{P_1}} + \frac{1}{\omega_{P_2}}) + 1}$$

$$\Rightarrow A_{CL}(s) = \frac{1}{\beta} \left[\frac{T(s)}{1 + T(s)} \right] = \frac{1}{\beta} \left[\frac{N_T/D_T}{N_T/D_T + 1} \right] = \frac{1}{\beta} \left[\frac{N_T}{N_T + D_T} \right]$$

$$= \frac{1}{\beta} \left[\frac{A_D}{A_D + 1 + s(\frac{1}{\omega_{P_1}} + \frac{1}{\omega_{P_2}}) + s^2(\frac{1}{\omega_{P_1} \omega_{P_2}})} \right]$$

$$= \frac{1}{\beta} \left[\frac{T_0}{1 + T_0 + s(\frac{1}{\omega_{P_1}} + \frac{1}{\omega_{P_2}}) + s^2(\frac{1}{\omega_{P_1} \omega_{P_2}})} \right]$$

$$\text{where } T_0 = A_D \cdot \beta \quad \text{here } \beta = 1$$

$$\therefore A_{CL}(s) = \frac{1}{\beta} \cdot \frac{T_0}{1 + T_0} \left[\frac{1}{1 + s \left[\frac{1}{(1 + T_0) \omega_{P_1}} + \frac{1}{(1 + T_0) \omega_{P_2}} \right] + \frac{s^2}{(1 + T_0) \omega_{P_1} \omega_{P_2}}} \right]$$

$$= \frac{1}{\beta} \cdot \frac{T_0}{1 + T_0} \left[\frac{1}{1 + \frac{a_1}{1 + T_0} s + \frac{a_2}{(1 + T_0)^2} s^2} \right]$$

In general for $\beta \neq 1$

$$A_{CL}(s) = \frac{1}{\beta} \cdot \frac{T_0}{1+T_0} \cdot \frac{1}{1 + \left(\frac{a_1}{1+T_0}\right)s + \left(\frac{a_2}{1+T_0}\right)s^2}$$

For part a: $\beta = 1$

$$\begin{aligned} \omega_{P1} &= 1 \text{ Hz} \\ \omega_{P2} &= 1 \text{ MHz} \end{aligned}$$

$$a_1 = \frac{1}{\omega_{P1}} + \frac{1}{\omega_{P2}} = 0.159$$

$$a_2 = \frac{1}{\omega_{P1} \omega_{P2}} = 2.53 \times 10^{-8} \text{ s}^2$$

$$T_0 = A_D \cdot \beta = 10^6$$

$$\therefore A_{CL}(s) = \left(\frac{10^6}{1+10^6} \right) \cdot \frac{1}{1 + 1.58 \times 10^{-7} s + (2.53 \times 10^{-14}) s^2}$$

$$\therefore A_{CL}(s) = 0.9999 \cdot \frac{1}{1 + (1.58 \times 10^{-7} s) + (2.58 \times 10^{-14}) s^2}$$



$$D_A = \cancel{1 + (1.58 \times 10^{-7}) s + (2.58 \times 10^{-14}) s^2}$$

$$A_{CL}(s) = \frac{3.87 \times 10^{13}}{s^2 + (6.12 \times 10^6) s + 3.87 \times 10^{13}}$$


Comparing the denominator with $s^2 + 2\zeta\omega_n s + \omega_n^2$
we get

$$\begin{aligned} \omega_n &= 6.22 \times 10^6 \text{ Rad/s} \rightarrow \text{Natural freq} \\ \zeta &= 0.4915 \rightarrow \text{Damping Factor} \\ \omega_d &= \omega_n \sqrt{1-\zeta^2} = 4.71 \times 10^6 \text{ Rad/s} \rightarrow \text{Damped freq} \end{aligned}$$


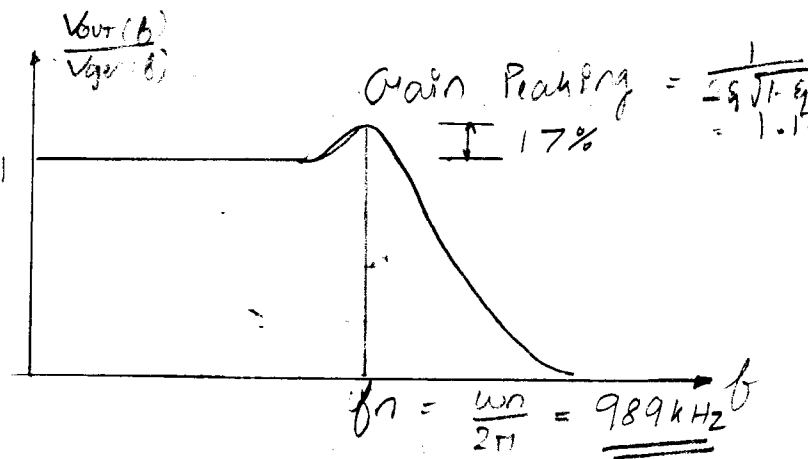
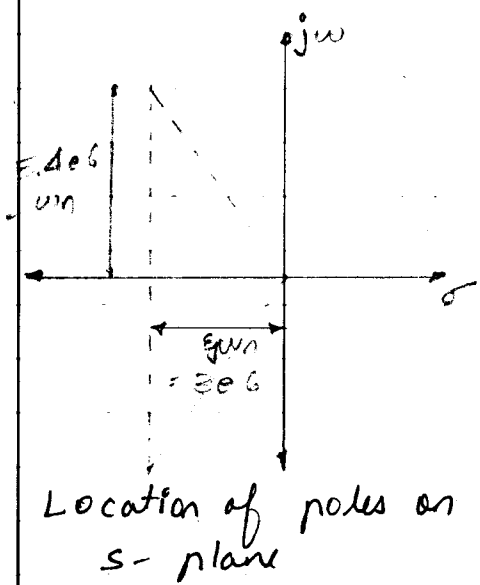
$$\text{Pole frequencies: } \omega_{P1} = -3e6 \pm (5.416e6)i$$



Plot of $V_{out}(f) / V_{gn}(f)$

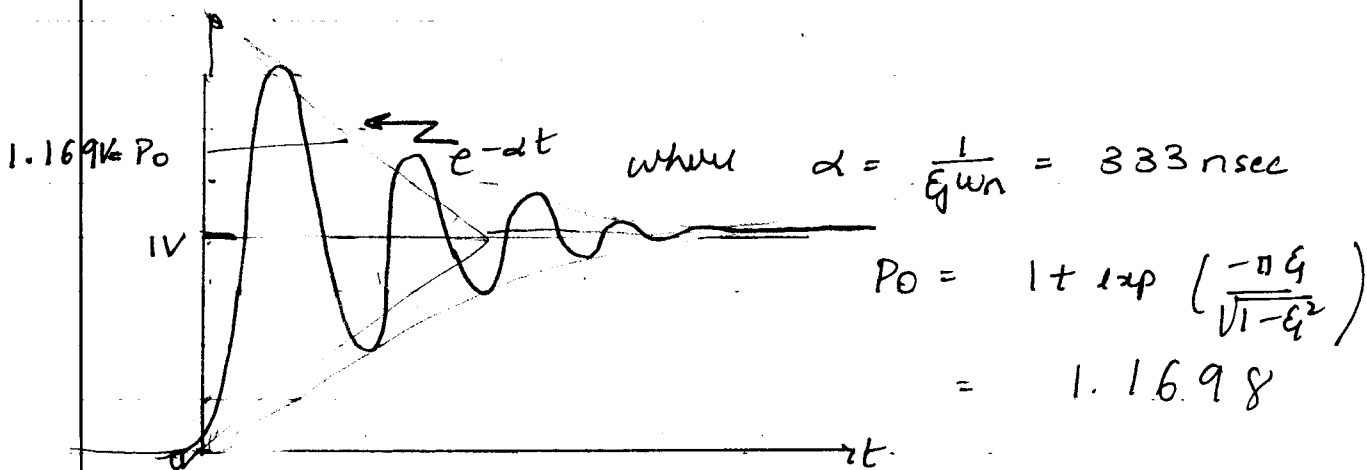

10.1 kHz
0.85 kHz

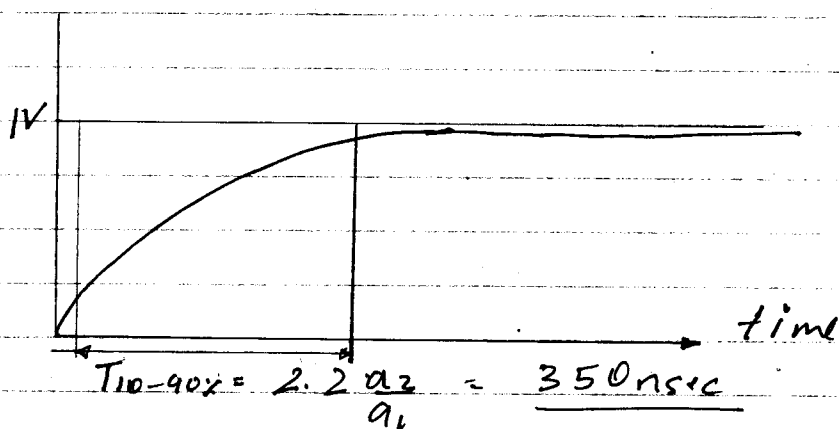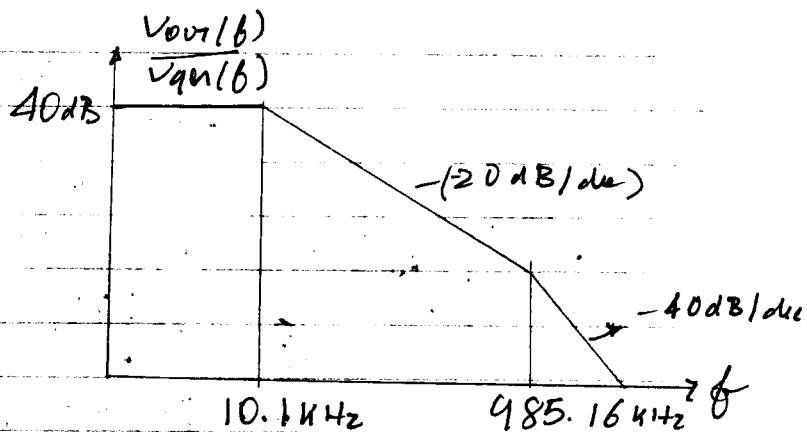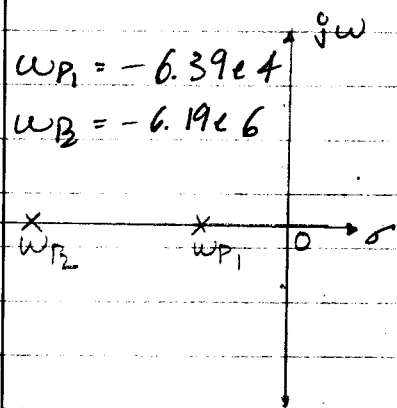

Step response to a 1V step

$$\begin{aligned} V_{TH} &= 0.3V \\ V_{DD} &= -V_{SS} = 3V \\ I &= 0 \end{aligned}$$

$$I_{D4} = I_{D5} = I_{D6} = 0.3 \text{ mA}$$

$$w_{g4} = w_{g5} = w_{g6} = 2 \mu m$$

Given: $I_{D4} = 0.3 \text{ mA}$ $V_{\text{sat}} C_{ox} W_4 = (1 \text{ mS}/\mu\text{m}) \times 2 \mu\text{m}$
 $V_{th} = 0.3 \text{ V}$ $= 2 \text{ mS}$

Now, $V_S = V_{DD} = 3V \Rightarrow V_g = V_S - 0.45 = 2.55V$

Now, $V_{gs5} = V_{gs4} = -0.45 \text{ V} \Rightarrow V_{g5} = 3 - 2(0.45)$
 $V_{g5} = 2.1 \text{ V}$

Also, $I_{D6} = 0.3 \text{ mA} \Rightarrow V_{g6} = (-3 + 0.45) \text{ V} = -2.55 \text{ V}$

$$R_{BIAS} = \frac{V_{G5} - V_{G6}}{(0.3mA)} = \frac{(2.1 + 2.55)}{0.3mA} = \underline{\underline{15.5 K\Omega}}$$

$$I_{DQ1} = I_{DQ2} = 0.3 \text{ mA} \Rightarrow I_{DQ8} = 0.6 \text{ mA}$$

$$I_{DQ8} = g_{m8} (V_{GS8} - V_{th})$$

$$V_{GS8} = V_{GS6} = 0.45 \text{ V}$$

$$\Rightarrow g_{m8} = \frac{I_{DQ8}}{(V_{GS8} - V_{th})} = 4 \text{ mS} \Rightarrow \boxed{W_{g8} = 4 \mu\text{m}}$$

$$I_{DQ3} = I_{DQ2} + I_{DQ9}$$


Now since R_{f1} & R_{f2} are very large we can neglect the current flowing through them

$$\text{So, } I_{DQ9} = I_{DQ7} = 0.3 \text{ mA}$$


$$\Rightarrow I_{DQ3} = 0.6 \text{ mA} = g_{m3} (V_{GS3} - V_{th})$$

$$\Rightarrow g_{m3} = \frac{0.6 \text{ mA}}{(0.45 - 0.3)} = 4 \text{ mS} \Rightarrow \boxed{W_{g3} = 4 \mu\text{m}}$$

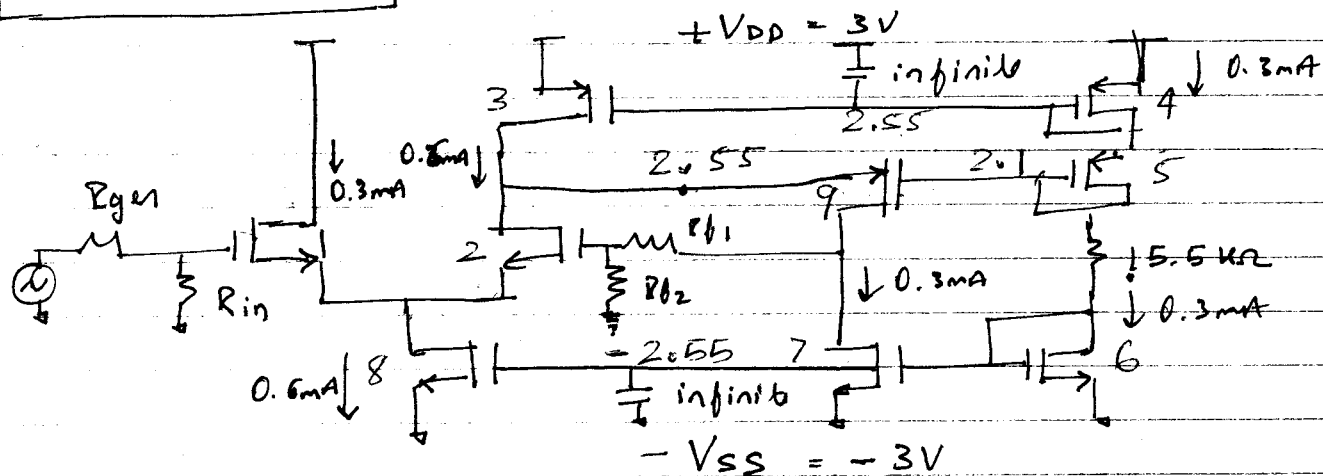
$$\boxed{W_{g7} = W_{g6} = 2 \mu\text{m}}$$




b.) Poles on loop transmission:

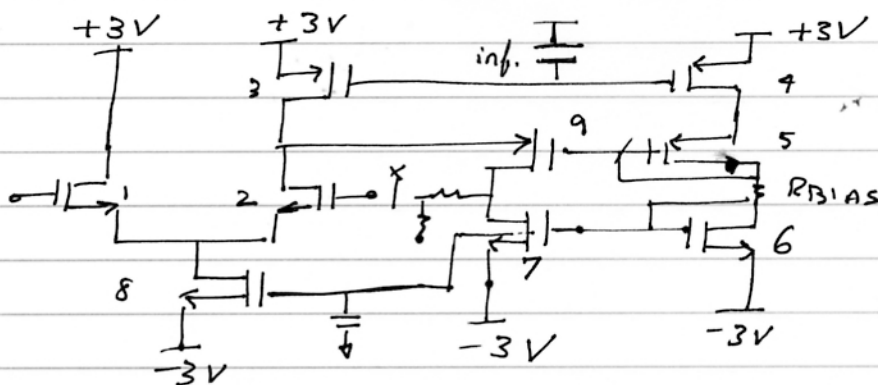

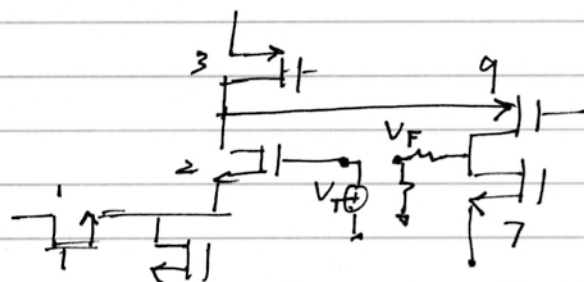Breaking the Feedback loop at point X we get:



$\frac{V_F}{V_T}$ is the negd. loop tx

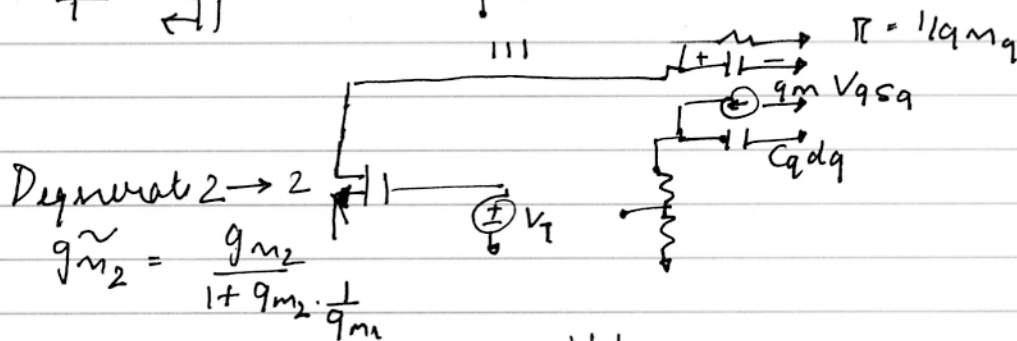


$$\tilde{g}_{m2} = \frac{g_{m2}}{1 + g_{m2} \cdot \frac{1}{g_{m1}}}$$

$$= (g_{m2}/2)$$

|||

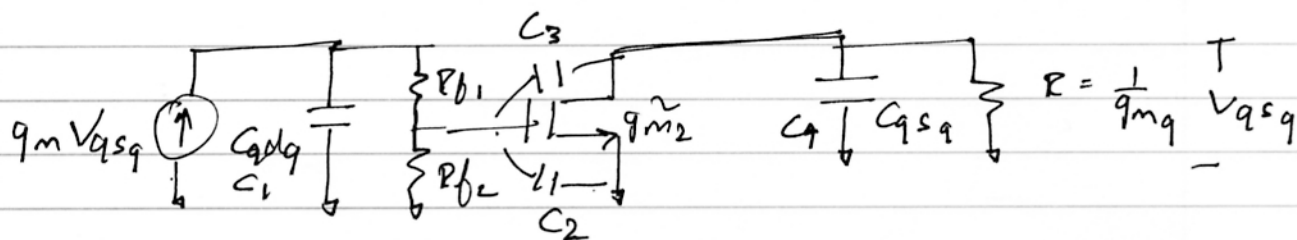Using the small signal equivalent circuits




$$C_1 = C_{qdq} \rightarrow R_{i1} = \left(\frac{1}{g_{m5}} \right) \parallel (P_{b1} + P_{b2}) + (A_{Va}) \left(\frac{1}{g_{m5}} \right)$$

Now.


$$R_{22}^1 = \left(\frac{1}{g_{m2}} \parallel \frac{1}{g_{m1}} \right) \left(\frac{1}{2} \right) + (R_{b2} \parallel R_{b1})$$

$$= \underline{91.5 \text{ k}\Omega}$$

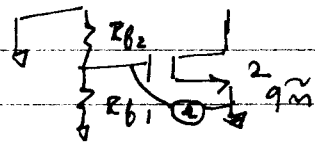


$$R_{33}^1 = (1 - A_{v2}) (R_{b1} \parallel R_{b2}) + \left(\frac{1}{g_{mq}} \right)$$

$$= \underline{180.5 \text{ k}\Omega}$$

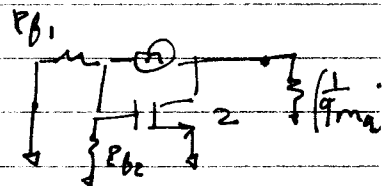

$$R_{44}^1 = \left(\frac{1}{g_{mq}} \right)$$

$$= \underline{500 \Omega}$$

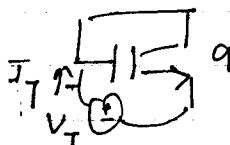

$$R_{33}^2 = (1 - A_{v2}) (0) + \frac{1}{g_{mq}} = \underline{500 \Omega}$$

$$R_{44}^2 = R_{44}^0 = \underline{500 \Omega}$$

$$R_{44}^3 = \left(\frac{1}{g_{mq}} \parallel \frac{1}{g_{m2}} \right) = \underline{250 \Omega}$$

$$a_1 = R_{11}^0 C_1 + R_{22}^0 C_2 + R_{33}^0 C_3 + R_{44}^0 C_4$$

$$= \underline{1.07 \text{ nsec}}$$

$$a_2 = R_{11}^0 C_1 C_2 R_{22}^1 + R_{11}^0 C_1 C_3 R_{33}^1 + R_{11}^0 C_1 C_4 R_{44}^1$$

$$+ R_{22}^0 C_2 C_3 R_{33}^2 + R_{22}^0 C_2 C_4 R_{44}^2$$

$$+ R_{33}^0 C_3 C_4 R_{44}^3$$

$$= \underline{2.54 \times 10^{-19} \text{ sec}^2}$$

$a_1 \nrightarrow a_2/a_1 \Rightarrow$ SPA doesn't hold.

Roots of $1 + a_1 s + a_2 s^2$: $s_1 = -137955421$

$s_2 = -2813049215$

$$\Rightarrow f_{P1} = 222 \text{ MHz}$$

$$f_{P2} = 447 \text{ MHz}$$

$$C_1 = C_{gdq}$$

$$= \underline{0.6 \text{ fF}}$$

$$R_{11}^0 = \left(\frac{1}{g_{m5}} \right) (1 - A_{Vq}) + (\beta \beta_1 + \beta \beta_2)$$

$$= \left(\frac{1}{2 \text{ mS}} \right) \left(1 - \frac{g_{m5} (\beta \beta_1 + \beta \beta_2)}{g_{m5} + R_{DS1} + R_{DS2}} \right) + (1.1 \text{ M}\Omega)$$

$$\approx \left(\frac{1}{2 \text{ mS}} \right) + 1.1 \text{ M}\Omega$$

$$\approx \underline{1.1 \text{ M}\Omega}$$

$$C_2 = C_{gs2}$$

$$= 3 \text{ fF}$$

$$R_{22}^0 = \left(\frac{1}{g_{m2}} \parallel \frac{1}{g_{m1}} \right) \left(1 - \frac{1}{2} \right) + (\beta \beta_1 + \beta \beta_2)$$

$$= (1 \text{ mS})^{-1} \left(\frac{1}{2} \right) + 100 \text{ k}\Omega$$

$$= \underline{101.5 \text{ k}\Omega}$$

$$C_3 = C_{gd2}$$

$$= 0.6 \text{ fF}$$

$$R_{33}^0 = (1 - A_{V2}) (\beta \beta_1 + \beta \beta_2) + \left(\frac{1}{g_{m1}} \right)$$

$$= \frac{\frac{1}{g_{m1}}}{\frac{1}{2} \left(\frac{1}{g_{m2}} \right)} \cdot (\beta \beta_1 + \beta \beta_2) + \left(\frac{1}{g_{m1}} \right)$$

$$= 2 (90 \text{ k}\Omega) + 500$$

$$= \underline{180.5 \text{ k}\Omega}$$

$$C_4 = C_{gsq}$$

$$= 3 \text{ fF}$$

$$R_{44}^0 = (1 - A_{Vq}) \left(\frac{1}{g_{m5}} \parallel R_{BIAS} + \frac{1}{g_{m6}} \right) + \frac{1}{g_{m1}}$$

$$\approx \frac{1}{g_{m1}} \quad \text{as } A_{Vq} \approx 1$$

$$= \underline{500 \Omega}$$

$$T(j\omega) = g_{n2} \cdot (P_{f1} + P_{f2}) = 90.9 \frac{\text{V}}{\text{V}} = 11$$

