

Closed-Book Exam

There are 2 problems on this exam , and you have 50 minutes.

1) show all work. Full credit will not be given for correct answers if supporting work is not shown.

2) please write answers in provided blanks

3) Don't Panic !

4) 137a, 137b crib sheets, and 2 pages personal sheets permitted.

Do not turn over the cover page until requested to do so.

Name:


→ MID TERM B SOLUTIONS

Use any and all reasonable approximations. 5% accuracy is fine if the method is correct.

Time function	LaPlace Transform
$\delta(t)$	1
$U(t)$	$1/s$
$e^{-\alpha t}U(t)$	$\frac{1}{s + \alpha}$
$e^{-\alpha t} \cos(\omega_d t)U(t)$	$\frac{s + \alpha}{(s + \alpha)^2 + \omega_d^2}$
$e^{-\alpha t} \sin(\omega_d t)U(t)$	$\frac{\omega_d}{(s + \alpha)^2 + \omega_d^2}$

Problem	Points Received	Points Possible
1a		10
1b		10
1c		20
1d		20
1e		10
2a		10
2b		10
2c		10
total		100

Problem 1, 70 points

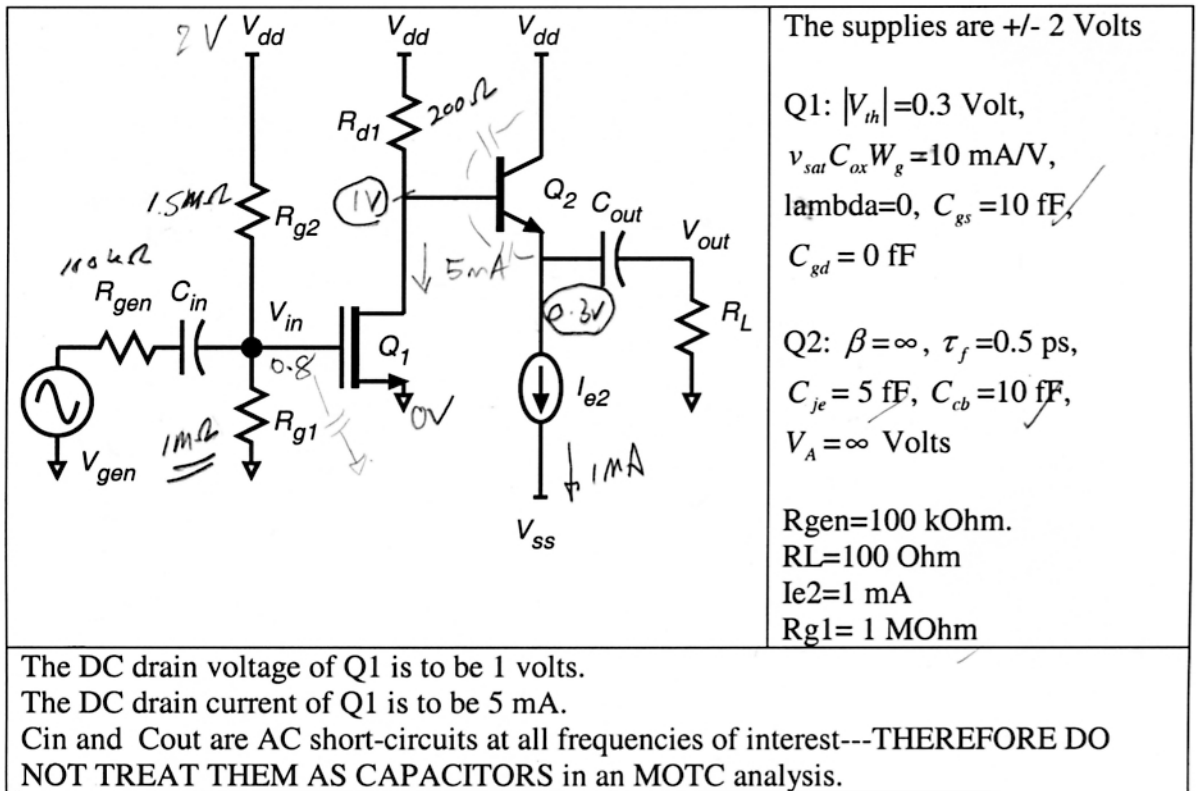

0.6

600

$$V_{dd} \left(\frac{1}{1+x} \right) = 0.8$$

$$\frac{1}{1+x} = 0.8$$

$$1+x = 1.25$$

$$x = 0.25$$

Find the following

$$R_{g2} = \frac{1.5 M\Omega}{(C_{je} + C_{diff}) \text{ of } Q2} = \frac{25 pF}{200\Omega}$$

$$\begin{aligned} I_{DQ1} &= g_{m1} (V_{gsQ1} - V_{thQ1}) \\ I_{DQ1} &= 5mA \text{ (given)} \\ V_{gsQ1} &= \frac{I_{DQ1}}{g_{m1}} + V_{thQ1} = \left(\frac{5mA}{10mA/V} \right) + 0.3V \\ &= \underline{\underline{0.8V}} \end{aligned}$$

$$\begin{aligned} \text{Now, } V_{gsQ1} &= V_{dd} \cdot \frac{R_{g1}}{R_{g1} + R_{g2}} = 0.8V \quad (V_s = 0) \\ V_{dd} &= 2V \\ R_{g1} &= 1M\Omega \rightarrow \text{given} \end{aligned}$$

$$\begin{aligned} \left(\frac{V_{gsQ1}}{V_{DD}} \right) &= \frac{R_{g1}}{R_{g1} + R_{g2}} \Rightarrow R_{g2} = R_{g1} \left[\left(\frac{V_{DD}}{V_{gsQ1}} \right) - 1 \right] \\ R_{g2} &= \underline{\underline{1.5 M\Omega}} \end{aligned}$$

$$\begin{aligned} V_{dd} - (5mA)(R_{D1}) &= 1V \\ \Rightarrow R_{D1} &= \left(\frac{2-1}{5mA} \right) = 200\Omega \end{aligned}$$

$$C_{diff Q2} = g_m \tau_f = \left(\frac{I_L}{V_T} \right) \tau_f = \left(\frac{1mA}{26mV} \right) (0.5ps) = 0.02pF = 20fF$$

Mid Band Analysis:

Find the mid-band small signal voltage gain of Q2 (the small signal voltage at the emitter of Q2 divided by the small signal voltage at the base of Q2)

$$A_{v2} = \underline{0.793}$$

Find the mid-band small signal voltage gain of Q1 (the small signal voltage at the drain of Q1 divided by the small signal voltage at the gate of Q1)

$$A_{v1} = \underline{-2}$$

Find V_{in}/V_{gen}

$$V_{in}/V_{gen} = \underline{0.8571}$$

$$\textcircled{4} \left[A_{v_{Q_2}} = \frac{R_L \textcircled{3}}{R_L + \left(\frac{1}{g_m} \right)_2 \textcircled{3}} = \frac{100 \textcircled{1}}{100 + 26} = \underline{0.793} \right]$$

$$\textcircled{4} \left[A_{v_{Q_1}} = -(g_{m_{Q_1}}) (R_{D1}) \textcircled{3} = - \left(10 \frac{\text{mA}}{\text{V}} \right) (200\Omega) \textcircled{1} = (-2 \text{ V/V}) \textcircled{1} \right]$$

$$\textcircled{2} \left[\frac{V_{in}}{V_{gen}} = \frac{R_{g1} \parallel R_{g2} \textcircled{1}}{R_{g1} \parallel R_{g2} + R_{gen}} = \underline{0.8571} \right]$$

Part c: 20 points

USING MOTC, you will find the two dominant pole frequencies of the transfer function.
Give the frequencies of these in Hz:

Component of a_1 due to C_{gs} of transistor Q1 = 0.857 nsec seconds.

Component of a_1 due to C_{cb} of transistor Q2 = 2 psec seconds.

Component of a_1 due to $(C_{je} + C_{diff})$ of transistor Q2 = 1.55 psec seconds.

$a_1 = \underline{8.6 \times 10^{-10}}$ seconds.

②

$$\begin{aligned} \tau_{C_{gs1}} &= (R_{g1} \parallel R_{g2} \parallel R_{gm}) C_{gs} \quad (5) \\ &= (600 \text{ k} \parallel 100 \text{ k}) (10 \text{ pF}) = 0.86 \text{ ns} \quad (1) \end{aligned} \quad (6)$$

$$\begin{aligned} \tau_{C_{cb2}} &= (R_{D1}) (C_{cb2}) = (200 \text{ k}) (10 \text{ pF}) \quad (5) \quad (1) \\ &= 2 \text{ psec} \quad (6) \end{aligned}$$

$$\begin{aligned} \tau_{C_{je} + C_{diff}} &= (R_{D1} (1 - A_{v2}) + (R_L \parallel \frac{1}{g_{m2}})) C_{be} \quad (5) \quad (6) \\ &= ((200 \text{ k}) (1 - 0.793) + (100 \text{ k} \parallel 26)) C_{be} \\ &= (41.4 + 20.63) C_{be} = 62.6 \Omega \cdot C_{be} \\ &= \underline{1.55 \text{ psec}} \quad (1) \end{aligned}$$

Part d: 20 points

Component of a_2 due to C_{gs1} and $C_{cb2} = \frac{1.71 \cdot 10^{-21}}{\text{seconds}^2}$.

Component of a_2 due to C_{gs1} and $(C_{je} + C_{diff}) = \frac{1.3 \cdot 10^{-21}}{\text{seconds}^2}$.

Component of a_2 due to C_{cb2} and $(C_{je} + C_{diff}) = \frac{1.03 \cdot 10^{-24}}{\text{seconds}^2}$.

$a_2 = \frac{3 \cdot 10^{-24}}{\text{seconds}^2}$

$f_{p1} = 185 \text{ MHz}$, $f_{p2} = 45.6 \text{ GHz}$

C_{gs1} & $C_{cb2} - R_{11}^0 C_1 C_2 R_{22}'$


$R_{22}' \rightarrow$

③ $R_{22}' = R_{D1}$

② $R_{11}^0 C_1 C_2 R_{22}' = (R_{g1} \parallel R_{g2} \parallel R_{gch}) C_{gs1} \cdot C_{cb2} \cdot R_{D1}$

$= (100 \text{ k}\Omega \parallel 1 \text{ M}\Omega \parallel 1.5 \text{ M}\Omega) \cdot 10 \text{ fF} \cdot 10 \text{ fF} \cdot 200 \Omega$

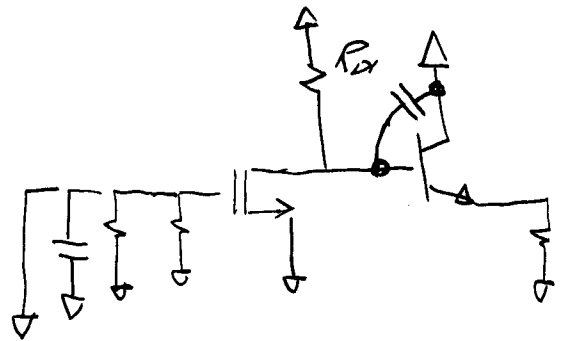① $= 85.7 \text{ k}\Omega \cdot 10 \text{ fF} \cdot 10 \text{ fF} \cdot 200 \Omega = 1.71 \cdot 10^{-21} \text{ Sec}^2$




C_{gs1} & $(C_{je} + C_{diff}) R_{11}^0 C_1 C_3 R_{33}'$

$R_{33}' \rightarrow$

③ $R_{33}' = R_{33}^0 = \text{from part c}$
 $= 62.6 \Omega$

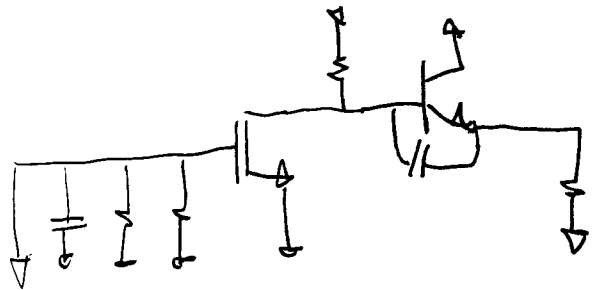② $R_{11}^0 C_1 C_3 R_{33}' = 85.7 \text{ k}\Omega \cdot 10 \text{ fF} \cdot 25 \text{ fF} \cdot 62.6 \Omega = 1.3 \cdot 10^{-21} \text{ Sec}^2$




C_{cb2} & $(C_{je} + C_{diff}) R_{22}^0 C_2 C_3 R_{33}^2$

$R_{33}^2 \rightarrow R$

③ $R_{33}^2 = R_{22} \parallel R_L = 26 \Omega \parallel 100 \Omega = 20.6 \Omega$

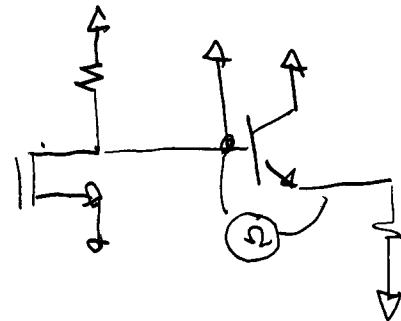$R_{22}^0 C_2 C_3 R_{33}^2 = 200 \Omega \cdot 10 \text{ fF} \cdot 25 \text{ fF} \cdot 20.6 \Omega = 1.03 \cdot 10^{-24} \text{ Sec}^2$



②

①

USE SPN - check for validity

$$\textcircled{1} \left[f_{p1} = \frac{1}{2\pi G_1} = 185 \text{ MHz} \right]$$

$$\textcircled{1} \left[f_{p2} = \frac{1}{2\pi (G_1/G_2)} = 45.6 \text{ GHz} \right]$$

Part e: 10 points

The circuit has 2 zeros its transfer function.

Give the frequencies of these in Hz:

$$f_{z1} = \underline{244 \text{ GHz}}$$

$$f_{z2} = \underline{\hspace{2cm}}$$

← sorry - not true, only one
because $C_{gd1} = 0 \text{ fF}$

Zero due to C_{be2}


$$f_z = \frac{g_{m2}}{2\pi C_{be2}} = \frac{1}{2\pi (26\Omega) \cdot 25\text{fF}} = 244\text{GHz}$$

(5) (4) (1)


- 2 for extra zero

Problem 2, 30 points

Part a 10 points

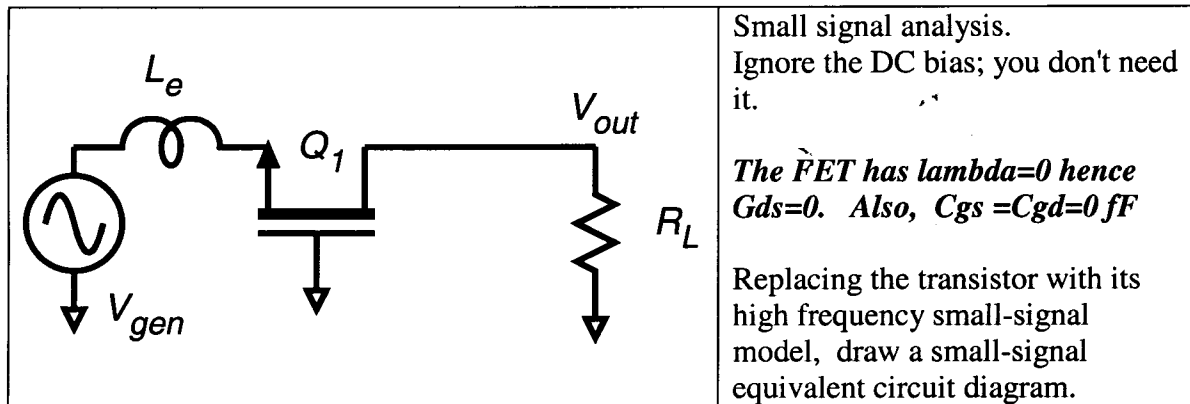


Small-Signal Model

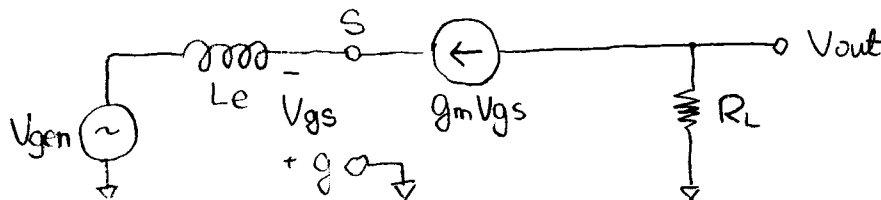

hard to give partial credit.

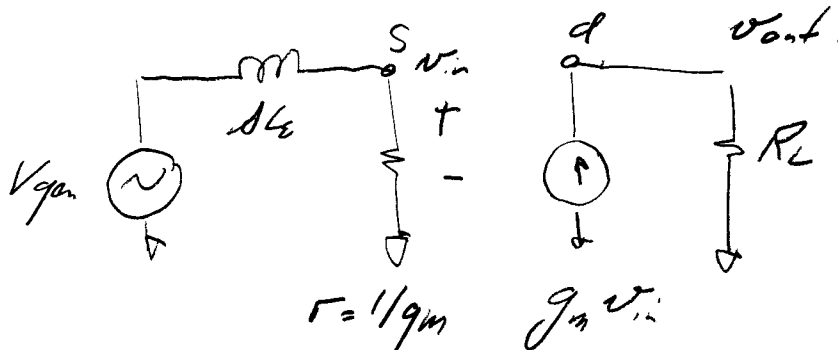- (Grading Rules)
1. No labels for current source -5
 2. wrong voltage expression in current source -5
sign of



3. wrong voltage -5 labels -5
in schematic

USING NODAL ANALYSIS, compute $V_{out}(s)/V_{gen}(s)$ in ratio-of-polynomials form:

$$\frac{V_{out}(s)}{V_{gen}(s)} = \left. \frac{V_{out}}{V_{gen}} \right|_{\text{mid-band}} \times \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots} = \frac{g_m R_L \cdot \frac{1}{1 + g_m L_e S}}{1}$$

① at S node

$$\textcircled{3} \left[\frac{V_{gen} - V_s}{S L_e} + g_m V_{gs} = 0 \right], \text{ where } V_{gs} = V_g - V_s = -V_s$$

$$\Rightarrow \frac{V_s}{V_{gen}} = \frac{1}{1 + S g_m L_e} \quad \text{--- ①}$$

② at output node

$$\textcircled{3} \left[\frac{V_{out}}{R_L} + g_m \cdot V_{gs} = 0 \right]$$

$$\Rightarrow \frac{V_{out}}{V_s} = g_m R_L \quad \text{--- ②}$$

③ From ① and ②

$$\frac{V_{out}(s)}{V_{gen}(s)} = \left. \frac{V_{out}}{V_{gen}} \right|_{\text{mid-band}} \times \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots}$$

$$= \frac{V_{out}}{V_s} \cdot \frac{V_s}{V_{gen}}$$

$$= \frac{g_m R_L \cdot \frac{1}{1 + g_m L_e S}}{1} \quad \text{--- ④}$$

Part c, 10 points

$g_m = 100 \text{ mS}$. $R_L = 1 \text{ k}\Omega$. $L_e = 1 \text{ nH}$

Find the frequencies of any zeros (there may be zero, one or two present) in the transfer function:

$f_{z1} = \text{_____}$, $f_{z2} = \text{_____}$,

There may be either 1 or 2 poles of the transfer function.

If the poles are real, give the 1 or 2 pole frequencies in Hz:

$f_{p1} = 1.59 \text{ GHz}$, $f_{p2} = \text{_____}$

If there are 2 poles, and they are complex, give $f_n = \omega_n / 2\pi$ and the damping factor ζ :

$f_n = \omega_n / 2\pi = \text{_____}$, $\zeta = \text{_____}$

⑩ From part b.

$$\begin{aligned} \frac{V_{out}(s)}{V_{in}(s)} &= g_m R_L \cdot \frac{1}{1 + j \frac{f}{f_p}} \quad \text{where } f_p = \frac{0.159}{g_m L_e} \\ &= \frac{0.159}{100(\text{mS}) \cdot 1(\text{nH})} \\ &= 1.59 \times 10^9 (\text{Hz}) \\ &= 1.59 (\text{GHz}) \end{aligned}$$

⑨ $\left[\begin{aligned} &= 100 \cdot \frac{1}{1 + j \frac{f}{1.59(\text{GHz})}} \\ &g_m R_L = 100(\text{mS}) \cdot 1(\text{k}\Omega) \\ &= 100 \end{aligned} \right.$

① $\left[\begin{aligned} &\text{There is a real pole at } f_p = 1.59 (\text{GHz}) \end{aligned} \right.$

$\left[\begin{aligned} &\text{deduct points 2 each for additional} \\ &\text{poles \& zeros.} \end{aligned} \right.$