

Homework #6 .

(1)

9-16 . (a) . For a short-circuit termination,

$$Z_{is} = Z_0 \tanh(\Gamma L) = Z_0 \cdot \frac{e^{\Gamma L} - e^{-\Gamma L}}{e^{\Gamma L} + e^{-\Gamma L}} = Z_0 \cdot \frac{1 + \Gamma L - (1 - \Gamma L)}{1 + 1 + \Gamma L - \Gamma L}$$

$$= Z_0 \cdot \frac{2\Gamma L}{2} = Z_0 \cdot \Gamma L .$$

Since

$$\Gamma = \sqrt{(R + j\omega L) \cdot (G + j\omega C)} \quad Z_0 = \frac{\sqrt{R + j\omega L}}{\sqrt{G + j\omega C}} .$$

plug into Z_{is} :

$$Z_{is} = Z_0 \cdot \Gamma L = \frac{\sqrt{R + j\omega L}}{\sqrt{G + j\omega C}} \cdot \sqrt{(R + j\omega L)(G + j\omega C)} \cdot L$$

$$= (R + j\omega L) \cdot L$$

(b) . For an open-circuit termination,

$$Z_{io} = Z_0 \coth(\Gamma L) = Z_0 \cdot \frac{e^{\Gamma L} + e^{-\Gamma L}}{e^{\Gamma L} - e^{-\Gamma L}} = Z_0 \cdot \frac{1 + 1}{1 + \Gamma L - (1 - \Gamma L)}$$

$$= Z_0 \cdot \frac{1}{\Gamma L} = \frac{1}{L \cdot (G + j\omega C)}$$

9-21 . For an open-circuit lossy transmission line, the input impedance is

$$Z_{io} = Z_0 \coth(\Gamma L) = Z_0 \cdot \frac{e^{\alpha L + j\beta L} + e^{-\alpha L - j\beta L}}{e^{\alpha L + j\beta L} - e^{-\alpha L - j\beta L}} .$$

$\alpha L \ll 1$ (low-loss) .

$$e^{\alpha L + j\beta L} = (1 + \alpha L) \cdot e^{j\beta L} , \quad e^{-\alpha L - j\beta L} = (1 - \alpha L) \cdot e^{-j\beta L}$$

plug into Z_{io} ,

(2)

$$\begin{aligned}
 Z_{io} &= Z_0 \cdot \frac{(1+\alpha L) \cdot e^{j\beta L} + (1-\alpha L) \cdot e^{-j\beta L}}{(1+\alpha L) \cdot e^{j\beta L} - (1-\alpha L) \cdot e^{-j\beta L}} \\
 &= Z_0 \cdot \frac{2\cos(\beta L) + 2\alpha L \cdot j \sin(\beta L)}{2j \sin(\beta L) + 2\alpha L \cos(\beta L)} \\
 &= Z_0 \cdot \frac{\cos(\beta L) + j \alpha L \sin(\beta L)}{\alpha L \cos(\beta L) + j \sin(\beta L)}
 \end{aligned}$$

$$\text{At } l = \frac{n\lambda}{2}, \quad \beta \cdot L = \frac{2\pi}{\lambda} \cdot \frac{n\lambda}{2} = n\pi.$$

$$Z_{io} = Z_0 \cdot \frac{1}{\alpha L} = Z_{max}.$$

Now consider $f = f_0 + \Delta f$.

$$\beta \cdot L = n\pi \cdot \left(1 + \frac{\Delta f}{f_0}\right).$$

$$Z_{io} = Z_0 \cdot \frac{1}{\alpha L + j \cdot n\pi \cdot \frac{\Delta f}{f_0}}.$$

So that,

$$\frac{|Z_{io}|^2}{|Z_{max}|^2} = \frac{1}{1 + [n\pi \cdot \alpha L \cdot \Delta f / f_0]^2}.$$

To obtain half-power,

$$[n\pi \alpha L \cdot \frac{\Delta f}{f_0}]^2 = 1.$$

$$\Delta f = \pm \frac{\alpha f_0 \cdot L}{n\pi} = \pm \frac{\alpha \cdot f_0 \cdot n\lambda}{2n\pi} = \pm \frac{\alpha}{2\pi \sqrt{LC}}.$$

$$\text{From eq. 55, } \alpha = \frac{1}{2} \left(R \cdot \sqrt{\frac{C}{L}} + G \cdot \sqrt{\frac{L}{C}} \right).$$

$$\Delta f = \pm \frac{1}{4\pi} \cdot \left(\frac{R}{L} + \frac{G}{C} \right).$$

So the half-power bandwidth is

(3)

$$2\Delta f = \frac{1}{2\pi} \left(\frac{R}{L} + \frac{G}{C} \right)$$

$$Q = \frac{f_0}{2\Delta f} = \frac{2\pi f_0}{\frac{R}{L} + \frac{G}{C}}$$

9-24. (a) $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$ for a lossless transmission

line, $Z_0 = R_0$ is real value.

$$\Gamma = \frac{(R_L - R_0) + jX_L}{(R_L + R_0) + jX_L}$$

since $S = \frac{1+|\Gamma|}{1-|\Gamma|}$, to minimize the standing wave ratio is to minimize $|\Gamma|$.

$$|\Gamma|^2 = \frac{(R_L - R_0)^2 + X_L^2}{(R_L + R_0)^2 + X_L^2} \quad \frac{\partial |\Gamma|^2}{\partial R_0} = 0 \Rightarrow R_0 = \sqrt{R_L^2 + X_L^2} = 50(\Omega)$$

(b) $|\Gamma| = \left| \frac{-10 + j30}{90 + j30} \right| = \sqrt{\frac{10000}{90000}} = \frac{1}{3}$

$$S = \frac{1+|\Gamma|}{1-|\Gamma|} = 2$$

(c) The location of minimum voltage is at

$$z' = L, \text{ where } -|\Gamma| = \Gamma \cdot e^{-2\beta L} = \Gamma \cdot e^{-2j\beta L}$$

$$\text{since } \Gamma = \frac{1}{3} e^{j\frac{\pi}{2}},$$

$$\text{we need } -2\beta L + \frac{\pi}{2} = -\pi, \quad -\frac{4\pi}{\lambda} L = -\frac{3\pi}{2}$$

$l = \frac{3}{8} \lambda$. is the nearest minimum voltage point. (4)

9-28. Eq. (9-147) is

$$R_i + jX_i = R_o \frac{R_m + jR_o \tan(\beta l_m)}{R_o + jR_m \tan(\beta l_m)}$$

$$= R_o \frac{R_m(R_o - jR_m \tan(\beta l_m)) + jR_o \tan(\beta l_m)(R_o - jR_m \tan(\beta l_m))}{R_o^2 + R_m^2 \tan^2(\beta l_m)}$$

$$\begin{cases} R_i = \frac{R_o}{R_o^2 + R_m^2 \tan^2(\beta l_m)} [R_m R_o + R_o R_m \tan^2(\beta l_m)] \\ X_i = \frac{R_o}{R_o^2 + R_m^2 \tan^2(\beta l_m)} [R_o^2 \tan(\beta l_m) - R_m^2 \tan(\beta l_m)] \end{cases}$$

Solve these equations :

$$R_m = \frac{R_o^2}{2R_i} \left[\left(1 + \left(\frac{R_i}{R_o} \right)^2 + \left(\frac{X_i}{R_o} \right)^2 \right) \pm \sqrt{\left(1 + \left(\frac{R_i}{R_o} \right)^2 + \left(\frac{X_i}{R_o} \right)^2 \right)^2 - 4 \left(\frac{R_i}{R_o} \right)^2} \right]$$

$$l_m = \frac{1}{\beta} \cdot \tan^{-1} \left\{ \frac{R_o}{2X_i} \cdot \left\{ - \left[1 - \left(\frac{R_i}{R_o} \right)^2 - \left(\frac{X_i}{R_o} \right)^2 \right] \pm \sqrt{\left(1 - \left(\frac{R_i}{R_o} \right)^2 - \left(\frac{X_i}{R_o} \right)^2 \right)^2 + 4 \left(\frac{X_i}{R_o} \right)^2} \right\} \right\}$$

9-29. $Z_L = Z_o \frac{1+\Gamma}{1-\Gamma}$,

$$\Gamma = |\Gamma| e^{j\theta_i}$$

Here $|\Gamma| = \frac{s-1}{s+1}$, $\theta_i = \frac{4\pi}{\lambda} z'_m \pm \pi$.

$$\text{So } \Gamma = \frac{S-1}{S+1} \cdot e^{j\left(\frac{4\pi}{\lambda} z_m' \pm \pi\right)}$$

(5)

$$Z_L = Z_0 \cdot \frac{1+\Gamma}{1-\Gamma} = Z_0 \cdot \frac{S+1 - (S-1) \cdot e^{j\frac{4\pi}{\lambda} z_m'}}{S+1 + (S-1) \cdot e^{j\frac{4\pi}{\lambda} z_m'}}$$

$$= Z_0 \cdot \frac{1 - j S \tan\left(\frac{2\pi z_m'}{\lambda}\right)}{S - j \tan\left(\frac{2\pi z_m'}{\lambda}\right)}$$