

Homework #7.

9-30 (a). $V_g = 0.1 \angle 0^\circ$ (V), $Z_g = R_o = 50(\Omega)$.

$R_L = 25(\Omega)$ $\Gamma = \frac{R_L - Z_o}{R_L + Z_o} = -\frac{1}{3}$.

$V_i = \frac{Z_i}{Z_o + Z_i} \cdot V_g$ $I_i = \frac{V_g}{Z_o + Z_i}$

where $Z_i = Z_o \cdot \frac{R_L + j \cdot Z_o \tan(\beta L)}{Z_o + j \cdot R_L \tan(\beta L)} = Z_o \cdot \frac{1 + j \cdot 2 \tan(\beta L)}{2 + j \cdot \tan(\beta L)}$

$\therefore V_i = \frac{1 + j \cdot 2 \tan(\beta L)}{3(1 + j \cdot \tan(\beta L))} V_g = \frac{1}{30} \left(\frac{1 + j \cdot 2 \tan(\beta L)}{1 + j \cdot \tan(\beta L)} \right)$ (V)

$I_i = \frac{2 + j \cdot \tan(\beta L)}{3 Z_o \cdot (1 + j \cdot \tan(\beta L))} V_g = \frac{2}{3} \left(\frac{2 + j \cdot \tan(\beta L)}{1 + j \cdot \tan(\beta L)} \right)$ (mA)

$V_L = V(z'=0) = \frac{V_g Z_o}{Z_o + Z_g} \cdot e^{-j\beta L} (1 + \Gamma) = \frac{1}{30} e^{-j\beta L}$ (V)

$I_L = \frac{V_g(Z_o)}{Z_o \cdot (Z_o + Z_g)} \cdot e^{-j\beta L} (1 - \Gamma) = \frac{4}{3} e^{-j\beta L}$ (mA)

(b) $S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = 2$

(c) $P_{av} = \frac{1}{2} \text{Re}(V_L \cdot I_L^*) = \frac{1}{2} \left(\frac{1}{30} \right) \cdot \left(\frac{4}{3} \times 10^{-3} \right) = 2.22 \times 10^{-5}$ (W)

if $R_L = 50(\Omega)$ $V_L = \frac{V_g}{2} e^{-j\beta L}$ $I_L = \frac{V_g}{2 Z_o} e^{-j\beta L}$

$P_{av} = 2.50 \times 10^{-5}$ (W)

(matched impedance)

$$9-31. \quad V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$$

$$I(z) = \frac{1}{R_0} (V_0^+ e^{-j\beta z} - V_0^- e^{j\beta z})$$

$$V_0^+ = \frac{V_g}{2} \quad I_0^+ = \frac{V_g}{2R_0}$$

$$(a). \quad P_{inc} = \frac{1}{2} \operatorname{Re} [V_0^+ I_0^{+*}] = \frac{V_g^2}{8R_0}$$

$$(b). \quad P_L = \frac{1}{2} \operatorname{Re} [V(z) \cdot I^*(z)]$$

$$= \frac{1}{2R_0} \cdot (V_0^+)^2 \cdot (1 - |\Gamma|^2) = \frac{V_g^2}{8R_0} (1 - |\Gamma|^2)$$

$$(c). \quad \frac{P_L}{P_{inc}} = 1 - |\Gamma|^2 = 1 - \left(\frac{S-1}{S+1} \right)^2 = \frac{4S}{(S+1)^2}$$

$$(d). \quad P_{inc} = \frac{100^2}{8 \times 50} = 25 \text{ (W)}$$

$$\Gamma = \frac{Z_L - R_0}{Z_L + R_0} = 0.243 \angle -76^\circ$$

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = 1.64 \quad P_L = 25(1 - 0.243^2) = 23.5 \text{ (W)}$$

$$\text{since } P_L = \frac{1}{2} |I_L|^2 R_L$$

$$|I_L| = 0.97 \text{ (A)} \quad |V_L| = |I_L| \cdot |Z_L| = 54.2 \text{ (V)}$$

$$9-42. \quad f = 200 \text{ MHz} = 2 \times 10^8 \text{ Hz} \quad \lambda = \frac{c}{f} = 1.5 \text{ (m)}$$

(a). 1 (m) long open-circuited case,

$$\frac{L}{\lambda} = \frac{2}{3} \quad \text{start from the extreme right}$$

point $P_{oc} (+1, 0)$, rotate clockwise

$$2\beta L = 2 \times \frac{2\pi}{\lambda} \times \frac{2}{3} \lambda = \frac{8}{3} \pi$$

Read $\chi = -0.575$, $r=0$

Thus $Z_L = R_0 (r + j\chi) = 75 \cdot (-j \cdot 0.575) = -j43.1 (\Omega)$

$Y_L = j \cdot 0.0232 (S)$

(b), $l = 0.8 \lambda = 0.533 \lambda$

start from the extreme left point $P_{sc}(-1, 0)$,

rotate clockwise $2 \cdot \frac{2\pi}{\lambda} \cdot l = 2 \cdot \frac{2\pi}{\lambda} \cdot 0.533 \lambda$

read $\chi = 0.21$, $r=0$

$Z_L = R_0 (r + j\chi) = 75 \cdot (j \cdot 0.21) = j \cdot 15.8 (\Omega)$

$Y_L = -j \cdot 0.063 (S)$

9-45 $S = \frac{1+|\Gamma|}{1-|\Gamma|} = 2$, $|\Gamma| = \frac{1}{3}$

$\lambda = \frac{2\pi}{\beta} = 0.5 (m)$, $\beta = 4\pi$

(a) $\Gamma = \frac{Z_L - R_0}{Z_L + R_0}$ where $R_0 = 50 (\Omega)$

$\Gamma = |\Gamma| \cdot e^{j\theta_L}$ since $\theta_L - 2\beta \cdot 0.05 = -\pi$

$\theta_L = -\pi + 2 \times 4\pi \times 0.05 = -\pi + 0.4\pi = -0.6\pi$

$\Gamma = \frac{1}{3} \cdot e^{-j0.6\pi}$

$Z_L = R_0 \cdot \frac{1+\Gamma}{1-\Gamma} = 50 \cdot \frac{1 + \frac{1}{3}e^{-j0.6\pi}}{1 - \frac{1}{3}e^{-j0.6\pi}} = 33.74 - j12.4$
24.07

$$(b). \quad \Gamma = \frac{1}{3} e^{-j0.6\pi}.$$

$$(c). \quad \text{if } z_L = 0, \quad \Gamma = -1.$$

$z' = 0$ is a minimum point.

$z' = \frac{\lambda}{2} = 25 \text{ (cm)}$ is the next one.

$$9-48. \quad (a). \quad z_L = \frac{\hat{z}_L}{R_0} = \frac{25 + j \cdot 25}{50} = 0.5 + j \cdot 0.5.$$

$$y_L = 1 - j.$$

$$P_1: \quad z_L = 0.5 + j \cdot 0.5.$$

$$P_2: \quad y_L = 1 - j \cdot 1 \Rightarrow d_2 = 0$$

$$P_3: \quad y_3 = 1 + j \cdot 1 \Rightarrow d_3 = 0.324 \lambda.$$

$$P_2'': \quad b_2 = j \cdot 1 \Rightarrow l_2 = 0.375 \lambda.$$

$$P_3'': \quad b_3 = -j \cdot 1 \Rightarrow l_3 = 0.125 \lambda.$$

$$(b). \quad \text{for } z'_0 = 75,$$

$$d'_2 = 0, \quad l'_2 = 0.406 \lambda.$$

$$d'_3 = 0.324 \lambda, \quad l'_3 = 0.0936 \lambda.$$