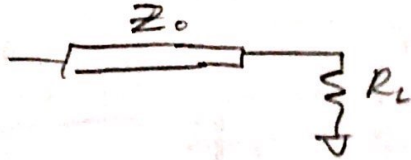


Problem Set #1 SolutionsProblem #1

$$Z_0 = 50\Omega$$



$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

a.) $R_L = 10\Omega$

$$\Gamma_L = -0.667$$

b.) $R_L = 50\Omega$

$$\Gamma_L = 0$$

c.) $R_L = 100\Omega$



$$\Gamma_L = 0.333$$

Problem #2

$$Z_0 = 50\Omega$$



$$l = 10\text{cm}$$

$$V_p = 2 \times 10^8 \text{ m/s}$$

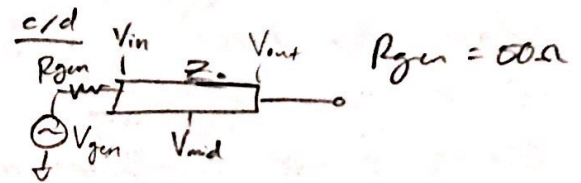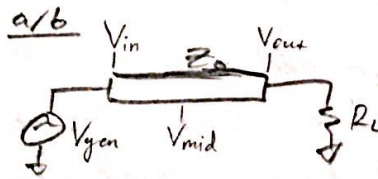Case a/b) $R_L = 50\Omega$, $V_{gen} = 500\text{mV u}(t)$



$$\tau = \frac{l}{V_p} = \frac{10\text{cm}}{2 \times 10^8 \text{ m/s}} = 0.5 \text{ ns}$$
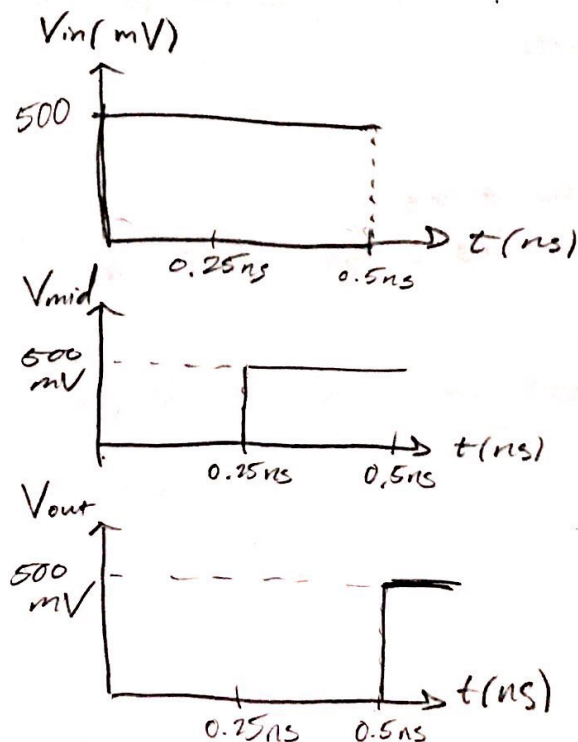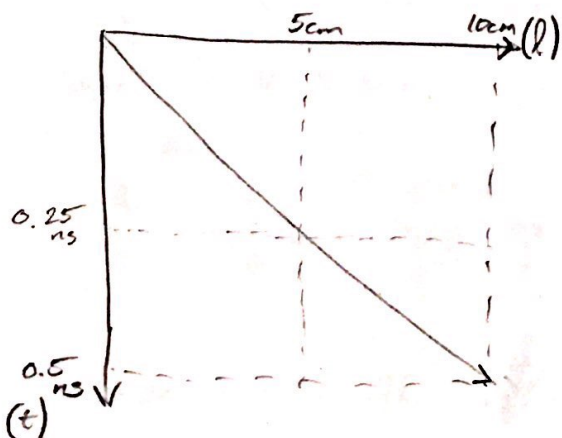
$$R_L = 50\Omega \Rightarrow \Gamma_L = 0$$




Case c/d : $R_L = \infty$ $V_{gen} = 500 \text{ mV (src)}$
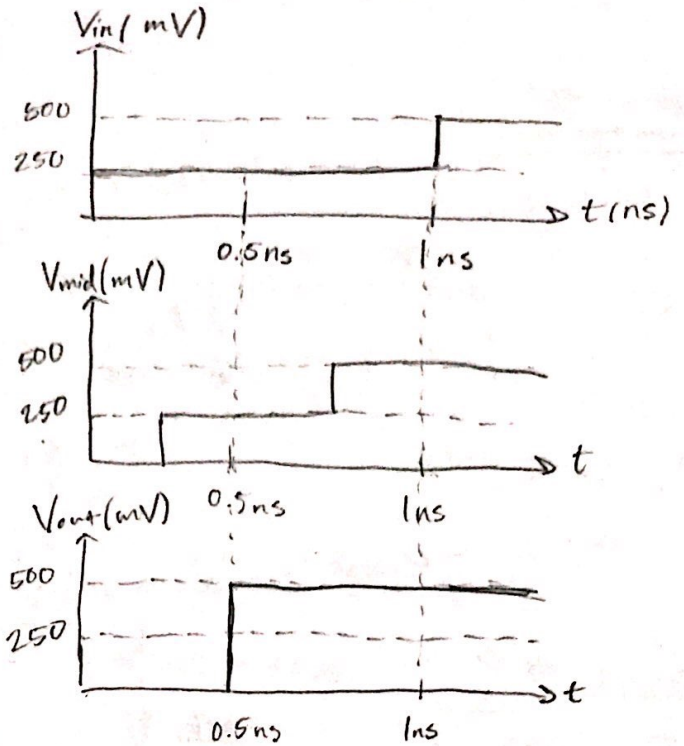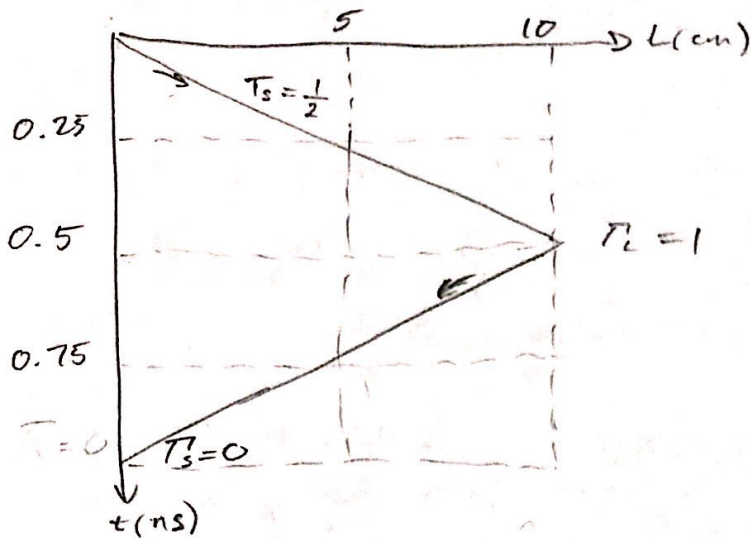
$$\Gamma_L = 1 \quad T_s = \frac{Z_0}{Z_0 + R_{gen}} = \frac{1}{2} \quad T_s' = 0$$



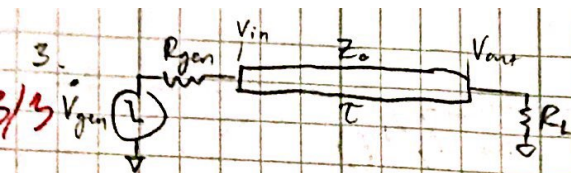Comment : It is generally more desirable to have rising/falling edges that meet the full magnitude as in case a/b. Thus, it is more desirable to have low series source resistance, and have a load termination.



$$Z_0 = 50 \Omega$$

$$\tau = l/v = 300 \text{ ps}$$



$$V_{gen} = 1 \text{ V u(t)}$$

Case a.) $R_L = 200 \Omega, R_{gen} = 200 \Omega$

$$\Gamma_L = \frac{R_L/Z_0 - 1}{R_L/Z_0 + 1} = 0.67$$

$$\Gamma_s = \frac{R_{gen}/Z_0 - 1}{R_{gen}/Z_0 + 1} = 0.67$$
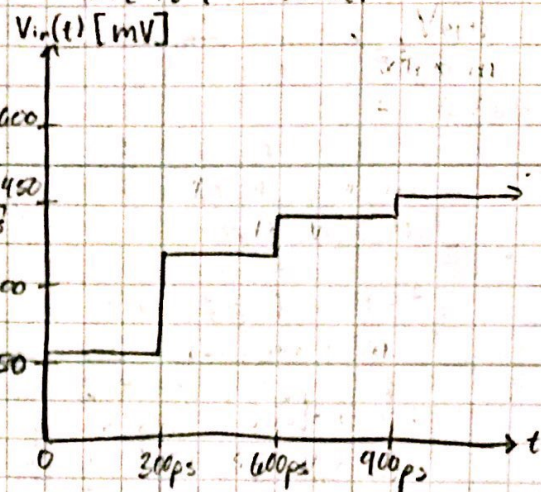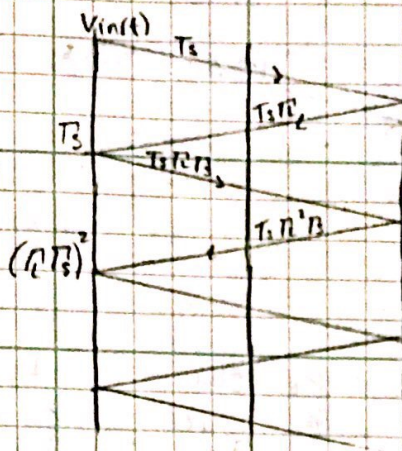
$$\Gamma_s = \frac{Z_0}{Z_0 + R_{gen}} = \frac{1}{6}$$




Case b.) $R_L = 5 \Omega, R_{gen} = 5 \Omega$

$$\Gamma_L = \frac{R_L/Z_0 - 1}{R_L/Z_0 + 1} = -818.2 \text{ mV}$$

$$\Gamma_s = -0.8182$$

$$\Gamma_s = 0.909$$

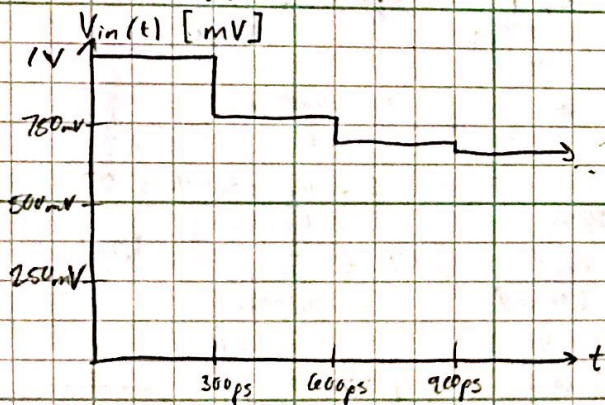

$$\begin{aligned} \Gamma_s \cdot 1 \text{ V u(t)} &= 909.09 \text{ mV} + \\ \Gamma_s \cdot \Gamma_L (1 + \Gamma_s) \text{ u(t)} &= -135.23 \text{ mV} + \\ \Gamma_s \Gamma_L^2 \Gamma_s (1 + \Gamma_s) \text{ u(t)} &= -90.53 \text{ mV} + \\ \Gamma_s \Gamma_L^3 \Gamma_s^2 (1 + \Gamma_s) \text{ u(t)} &= -60.604 \text{ mV} + \\ &\rightarrow -40.57 \text{ mV} \end{aligned}$$

Case c.) $R_L = 250 \Omega, R_{gen} = 5 \Omega$

$$\Gamma_L = 0.67$$

$$\Gamma_s = -0.8182$$

$$\Gamma_s = 0.909$$


$$\Gamma_s \cdot 1 \text{ V u(t)} = 0.909 \text{ V}$$

$$\Rightarrow 110.7 \text{ mV}$$

$$\Rightarrow -60.7 \text{ mV}$$

$$\Rightarrow 33.27 \text{ mV}$$

$$\Rightarrow -18.24 \text{ mV}$$

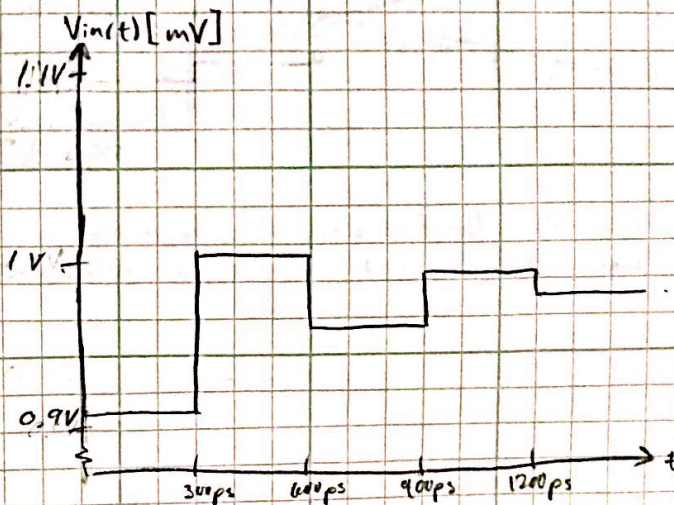

Problem 4

$$Z_0 = 50 \Omega$$


$$\tau = l/v = 300 \text{ ps}$$

$$V_{\text{gen}} = 1 \text{ V (src)}$$

$$L = \tau Z_0 = 15 \text{ nH}$$

$$C = \frac{\tau}{Z_0} = 6 \text{ pF}$$

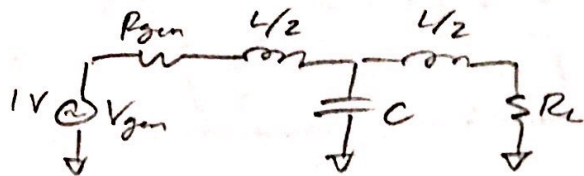
Case a) T-section $R_L = 250 \Omega$, $R_{\text{gen}} = 250 \Omega$




$$\tau_{RC} = C \cdot (R_L \parallel R_{\text{gen}}) = 0.75 \text{ ns}$$

$$\tau_{RL} = \frac{L}{(R_{\text{gen}} + R_L)} = 30 \text{ ps}$$

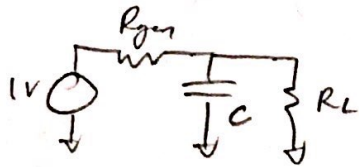$\tau_{RC} > \tau_{RL} \rightarrow$ ignore effects of inductor.




Thevenin
 $\Rightarrow$
Equivalent

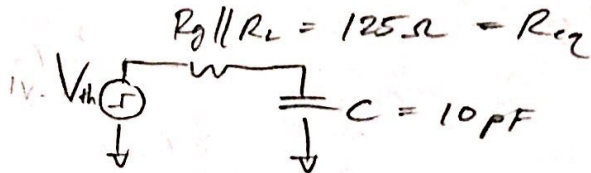


$$V_{th} = 1 \text{ V} \cdot \frac{R_L}{R_L + R_{\text{gen}}} = 0.5 \text{ V}$$
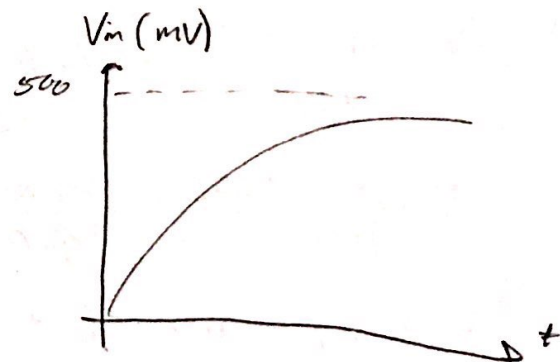
$$\Rightarrow \boxed{V_{in}(t) = 0.5(1 - e^{-t/RC}) = 0.5(1 - e^{-t/1.25 \text{ ns}})}$$




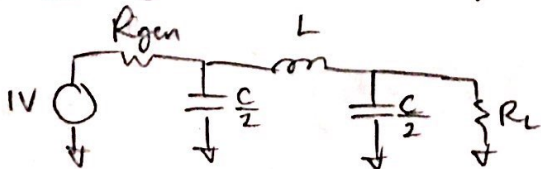Case b) $R_L = 5 \Omega$, $R_{\text{gen}} = 5 \Omega$




$$\tau_{RC} = C(R_{\text{gen}} \parallel R_L) \quad \tau_{RL} = \frac{L}{R_{\text{gen}} + R_L} \Rightarrow \text{ignore capacitor}$$
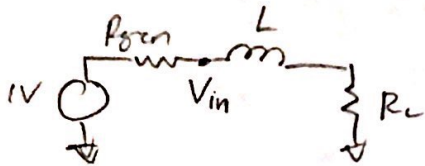
$$= 15 \text{ ps} \quad = 1.5 \text{ ns}$$



$$I(t) = \frac{V_{gen}}{R_{gen} + R_L} (1 - e^{-t/\tau_{RL}})$$
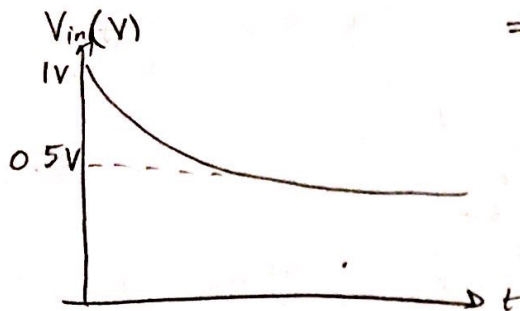
$$= 100 \text{ mA} (1 - e^{-t/1.5 \text{ ns}})$$



$$\Rightarrow V_{in}(t) = V_{gen} - I(t) R_{gen}$$

$$= 1\text{V} - (5\Omega)(100\text{mA})$$


$$= 1 - 0.5\text{V} (1 - e^{-t/1.5 \text{ ns}})$$

$$V_{in}(t) = 0.5\text{V} (1 + e^{-t/1.5 \text{ ns}})$$

Case C: $R_L = 250\Omega$, $R_{gen} = 5\Omega$

$R_L \gg R_{gen} \rightarrow$ neglect time constant associated with R_{gen} .

$\Rightarrow$ neglect first $C/2$

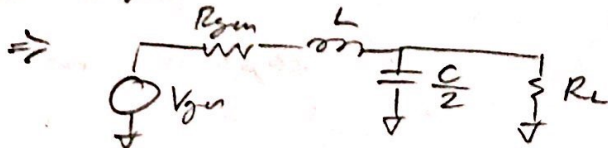

$$\frac{V_{in}(t) - V_{gen}}{R_{gen}} + \frac{V_{in}(t) - V_{out}(t)}{j\omega L} = 0$$

$$\frac{V_{out}(t) - V_{in}(t)}{j\omega L} + \frac{V_{out}(t)}{2/j\omega C} + \frac{V_{out}(t)}{R_L} = 0$$

$$\Rightarrow V_{in}(\omega) = j\omega L \left(\frac{2}{j\omega C} + R_L \right) + \left(\frac{2}{j\omega C} \cdot R_L \right)$$

$$\frac{R_{gen} \left(\frac{2}{j\omega C} + R_L \right) + j\omega L \left(\frac{2}{j\omega C} + R_L \right) + \left(\frac{2}{j\omega C} \cdot R_L \right)}{\left(\frac{2R_{gen}}{j\omega C} + R_L R_{gen} \right) + \left(\frac{2L}{C} + j\omega L R_L \right) + \left(\frac{2R_L}{j\omega C} \right)}$$

$$\Rightarrow V_{in}(s) = \frac{s^2 R_L \cdot L + \frac{2L}{C} \cdot s + \frac{2R_L}{C}}{\frac{2R_{gen}}{C} + s R_L R_{gen} + s \frac{2L}{C} + s^2 R_L \cdot L + \frac{2R_L}{C}}$$

$$= \frac{s^2 + s \cdot \frac{2}{R_L C} + \frac{2}{LC}}{s^2 + s \frac{R_{gen}}{L} + s \frac{2}{R_L C} + \frac{2}{LC} + \frac{2R_{gen}}{C}}$$

$$a = \frac{2}{R_L C} \quad b = \frac{2}{LC} \quad c = \frac{R_{gen}}{L} + \frac{2}{R_L C}$$

$$\frac{s^2 + sa + b}{s^2 + sc + b + \frac{2R_{gen}}{C}} \rightarrow \ll \frac{2}{LC} \dots \text{negligible}$$

Step function $u(t) \rightarrow \frac{1}{s}$ in freq. domain $\Rightarrow$

$$\Rightarrow \frac{s^2 + sa + b}{s^3 + s^2c + bs}$$


$$a = 1.33 \times 10^9$$

$$b = 22.22 \times 10^{18}$$

$$c = 1.667 \times 10^9$$

$\mathcal{L}^{-1}$ inverse Fourier


$$\begin{aligned} \Rightarrow V_{in}(t) &= 1 - \frac{(a-c)(e^{t(-\frac{1}{2}\sqrt{c^2-4b}-\frac{c}{2})} - e^{t(\frac{1}{2}\sqrt{c^2-4b}-\frac{c}{2})})}{\sqrt{c^2-4b}} \\ &= 1 - \frac{(-337 \times 10^6)(e^{t(-833.5 \times 10^6 - 4.64 \times 10^9 j)} - e^{t(833.5 \times 10^6 + 4.64 \times 10^9 j)})}{9.279 \times 10^9 j} \end{aligned}$$

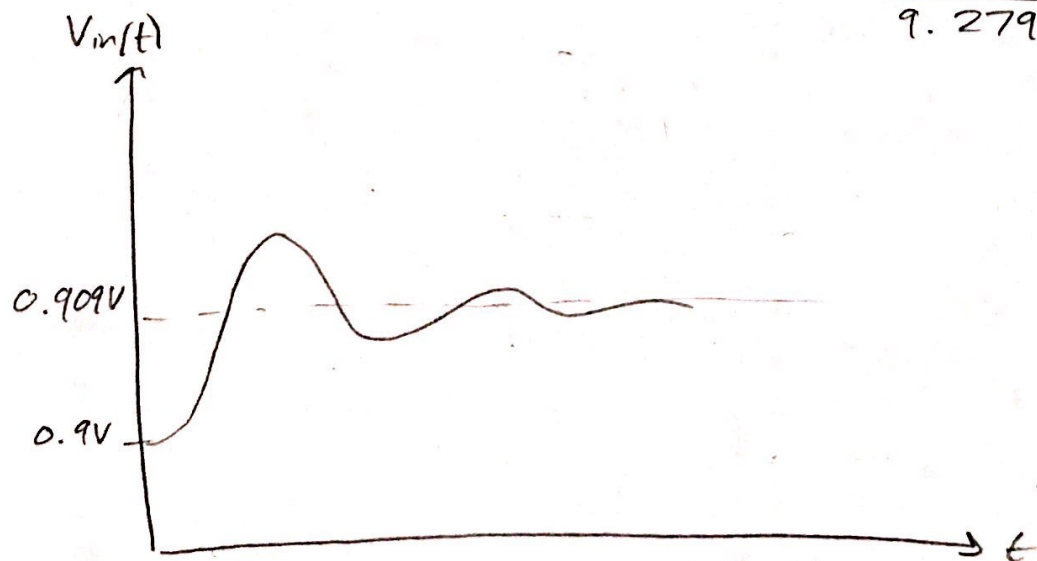

Problem 5

$$l = 300 \mu\text{m}$$

$$Z_0 = 50 \Omega$$

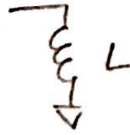

$$Z_0 = \frac{\pi \epsilon_0}{\sqrt{\epsilon_r}} \frac{H}{W+H} \Rightarrow 50 \Omega = \frac{377 \Omega}{\sqrt{2.65}} \frac{10 \mu\text{m}}{W+10 \mu\text{m}}$$

$$\Rightarrow \boxed{W = 36.32 \mu\text{m}}$$

$$V_p = \frac{c}{\sqrt{\mu_r \epsilon_r}} = \frac{c}{\sqrt{2.65}} = 1.84 \times 10^8 \text{ m/s}$$

$$\tau = \frac{l}{V_p} = 1.63 \text{ ps} \Rightarrow \boxed{L = Z_0 \tau = 81.39 \text{ pH}}$$

$$f = 1/\tau = 613.5 \text{ GHz}$$

Smith Chart Attached $\Rightarrow$

Problem 6

$$\tau = 1.63 \text{ ps}$$

$$\boxed{C = \frac{\tau}{Z_0} = 32.6 \text{ fF}}$$