

Problem Set #3 SolutionsProblem #1From smith chart $\rightarrow Z_{in} = 3.423 \cdot j0 \Rightarrow Z_{in} = 171.15 \Omega$

$$\text{@ } \frac{\lambda}{4} \Rightarrow Z_{in} = \frac{Z_0^2}{Z_L} \Rightarrow \boxed{Z_0} = \sqrt{Z_{in} \cdot Z_L} = \boxed{92.5 \Omega}$$

$$\text{Poles @ } f_1 = 105 \text{ GHz} = \frac{1}{4C_1} \Rightarrow \tau_1 = 2.38 \text{ ps} \Rightarrow \boxed{V = \frac{l}{C_1} = 2.1 \times 10^8 \frac{\text{m}}{\text{s}}}$$

Problem #2

$$W_{\max} < \lambda_d / 2$$

$$\text{a.) } \lambda_d = \lambda_0 / \sqrt{\epsilon_r} = \frac{c}{f \sqrt{\epsilon_r}} = \frac{3 \times 10^8 \text{ m/s}}{300 \text{ GHz} \cdot \sqrt{2.7}} = 609 \mu\text{m}$$

$$\Rightarrow \boxed{W_{\max} \approx 304.3 \mu\text{m}}$$

$$\text{DC : } Z_{in} = \infty$$

$$\lambda_d/4 : Z_{in} = 0$$

$$\lambda_d/2 : Z_{in} = \infty$$

$$\left. \begin{array}{l} \text{DC : } Z_{in} = \infty \\ \lambda_d/4 : Z_{in} = 0 \\ \lambda_d/2 : Z_{in} = \infty \end{array} \right\} Z_{in} \text{ goes to } \infty \text{ at } L_{\max} = \frac{\lambda_d}{2} \Rightarrow \boxed{L_{\max} = 304.3 \mu\text{m}}$$

$$C = \frac{\epsilon A}{H} = \frac{\epsilon_0 \cdot \epsilon_r \cdot W_{\max} \cdot L_{\max}}{H} = 0.369 \text{ pF}$$

$H \rightarrow 6 \mu\text{m}$

$$\text{c.) } \begin{array}{c} \triangle \\ \text{A} \\ \text{r=L} \end{array} \quad A = \frac{\pi r^2}{4} \quad \text{where } \epsilon_r \rightarrow \epsilon_{\text{eff}} \approx \frac{\epsilon_r + 1}{2} = 1.85$$

$$L_{\max} = \frac{\lambda_d}{2} = \frac{c}{2f \cdot \sqrt{\epsilon_{\text{eff}}}} = \boxed{367.6 \mu\text{m}}$$

$$C = \frac{\epsilon_r \cdot \epsilon_0 \cdot \pi L^2}{4H} = \boxed{0.423 \text{ pF}}$$

$$C_{\text{radial}} > C_{\text{line}}$$

$$L_{\max, \text{radial}} > L_{\max, \text{line}}$$

Problem 3

0744

Spun 10/2.) From Smith chart $\Rightarrow Z = 3.412 + j0 \Rightarrow Z_{in} = 170.6 \Omega$

$$\Rightarrow \boxed{Z_{\text{eff}}} = \sqrt{Z_{\text{in}} \cdot Z_L} = \boxed{92.36 \Omega}$$

ϵ constant for all other lines
 because it is measured from an open
 line, and is only
 dependent on substrate.

2. @ $f = 653 \text{ GHz} = \frac{1}{4\tau} \Rightarrow \tau = 0.383 \text{ ps} \Rightarrow V = \frac{\ell}{\tau} = 2.11 \times 10^8 \frac{\text{m}}{\text{s}}$

50 μm
Wide

From Smith chart $\Rightarrow y = 0.185 + j0 \Rightarrow Z_{in} = 9.25 \Omega$

$$\Rightarrow \boxed{Z_{\text{load}}} = \sqrt{Z_{\text{in}} \cdot Z_1} = \boxed{21.5 \Omega}$$

Input :

$$\tau_{High} = \frac{L_{High}}{V} = 0.383 \mu s$$

$$\tau_{\text{low}} = \frac{\lambda_{\text{low}}}{v} = \frac{296.04 \mu\text{m}}{2.11 \times 10^8 \text{ s}^{-1}} = 1.4 \text{ ps}$$

$\Rightarrow$ ignore C

$\Rightarrow$ ignore L

$$\Rightarrow L_{\text{high}} = T_{\text{high}} \cdot Z_{\text{high}} = 35.4 \mu\text{H}$$

$$\rightarrow C_{low} = \tau_{low} / Z_{low} = 65.1 \text{ fF}$$


Ques:

$$\tau_{\text{High}} = \frac{452 \mu\text{m}}{V} = 2.14 \text{ ps}$$

$$T_{\text{trav}} = \frac{436.61 \mu\text{m}}{V} = 2.07 \text{ ps}$$

$$L_{H_{24}} = 0.198 \text{ nH}$$

$$C_{low} = 96.3 \text{ fF}$$

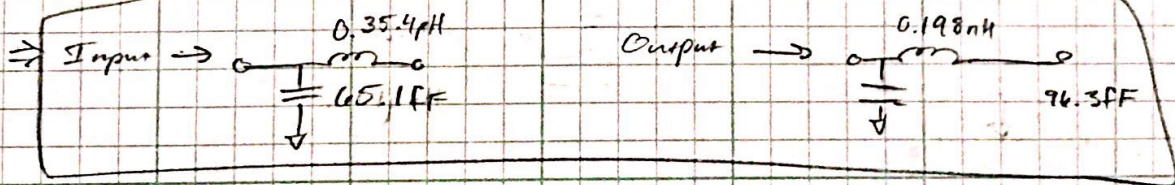

1006Hz

smith chart

Problem 7:



Want: $Z_{line} = 75 \Omega \Rightarrow Z_{in} = \frac{Z_{line}^2}{Z_L} = 112.5 \Rightarrow Y = 2.25 + j0$

From tuning to find $Y = 2.25 + j0 \Rightarrow W = 7.81 \mu m$ Series

Repeat for $Z_{line} = 25 \Omega \Rightarrow Y = 0.25 + j0 \Rightarrow W = 41.54 \mu m$ Shunt

Problem 8

a)

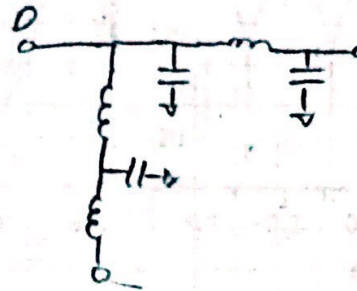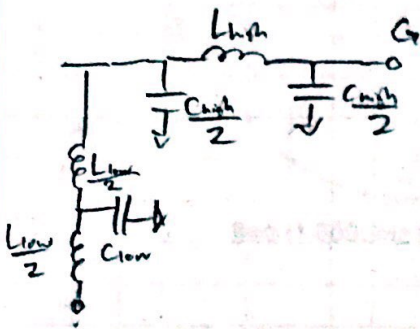

$Z_{High} = 75 \Omega, Z_{Low} = 25 \Omega$

$V = C/\epsilon \epsilon_r = 1.82 \times 10^8 \frac{m}{s}$

Input:

$\tau_{High} = \frac{l_{high}}{V} = \frac{89.5 \mu m}{V} = 0.492 ps \Rightarrow L_{high} = \tau_{high} \cdot Z_{high} = 36.9 pH$


$\tau_{Low} = \frac{l_{low}}{V} = \frac{333.5 \mu m}{V} = 1.83 ps \Rightarrow C_{low} = \tau_{low} / Z_{low} = 73.2 fF$
 $L_{low} = \tau_{low} \cdot Z_{low} = 45.75 pH$

Output:

$\tau_{High} = \frac{135 \mu m}{V} = 0.742 ps \Rightarrow L_{high} = 55.6 pH, C_{high} = 9.89 fF$



$\tau_{Low} = \frac{39 \mu m}{V} = 0.214 ps \Rightarrow C_{low} = 8.56 fF, L_{low} = 5.35 pH$

Problem 1



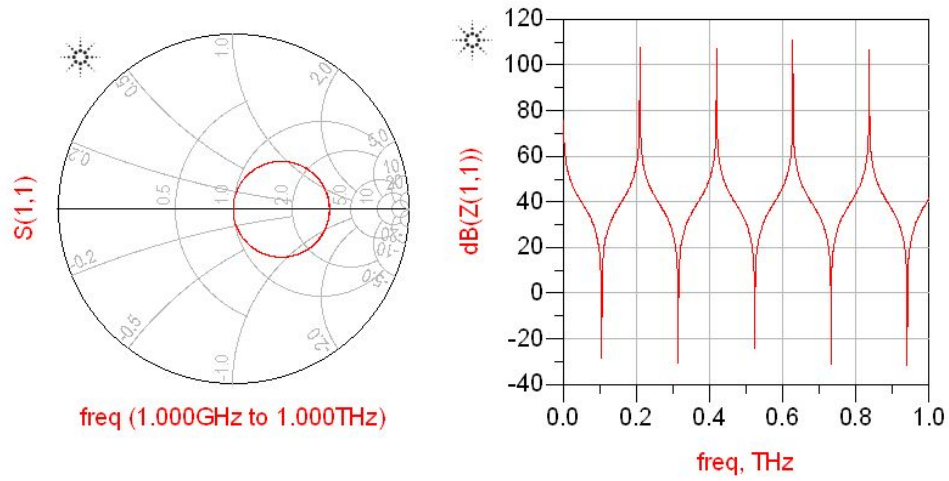


Problem 2

Part B

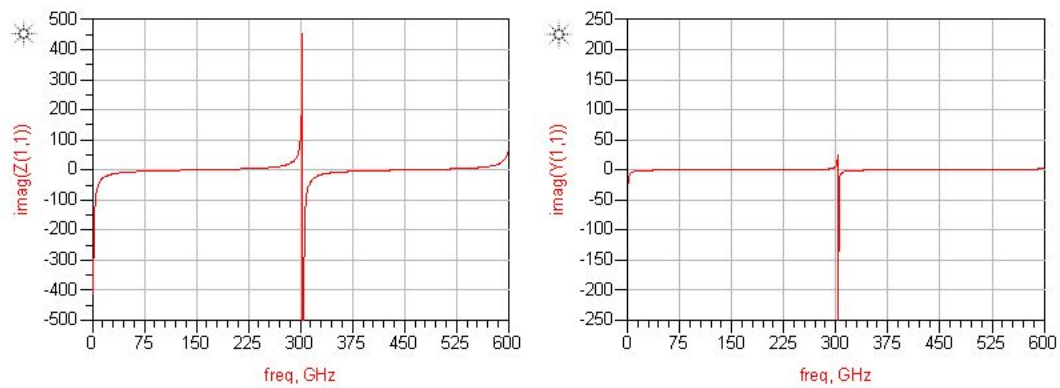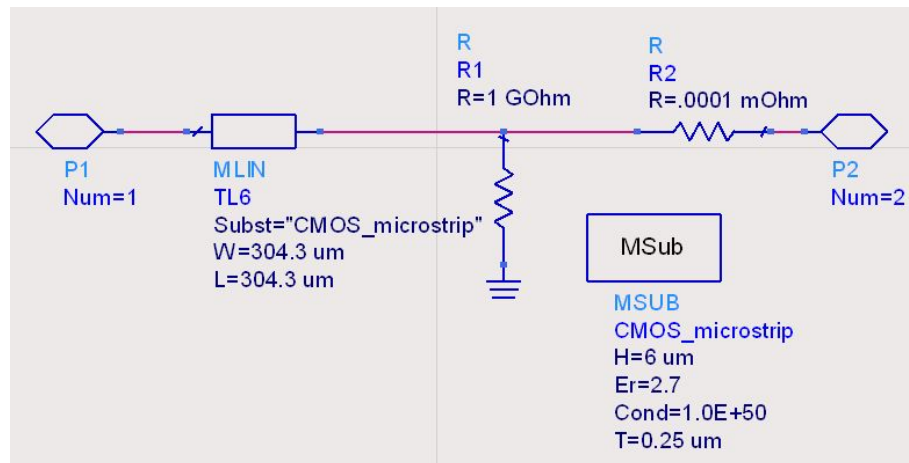


Part D

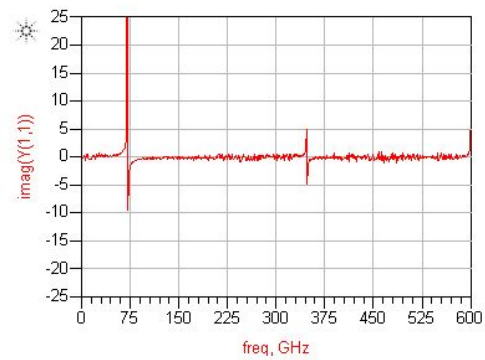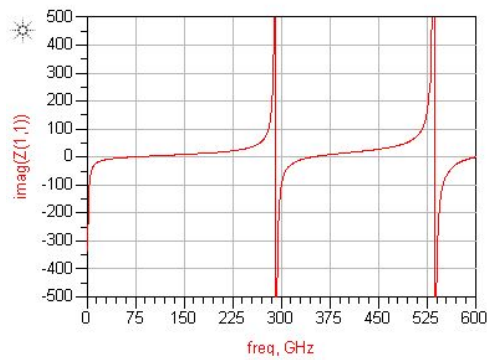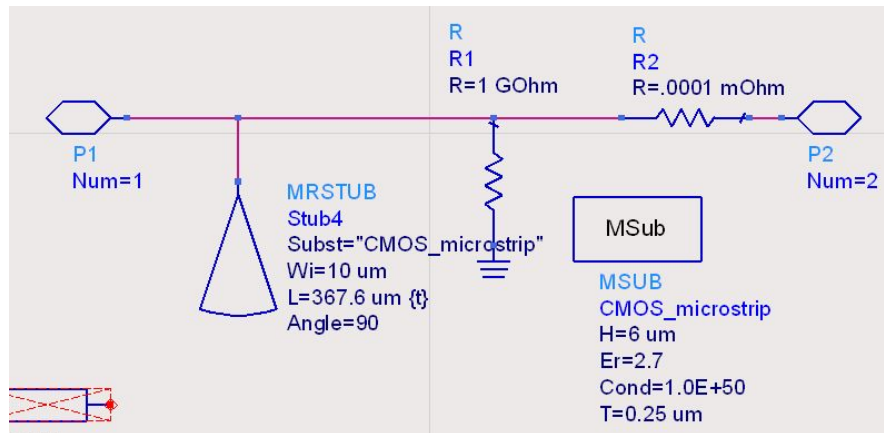

Problem 3


Part A

Before tuning:

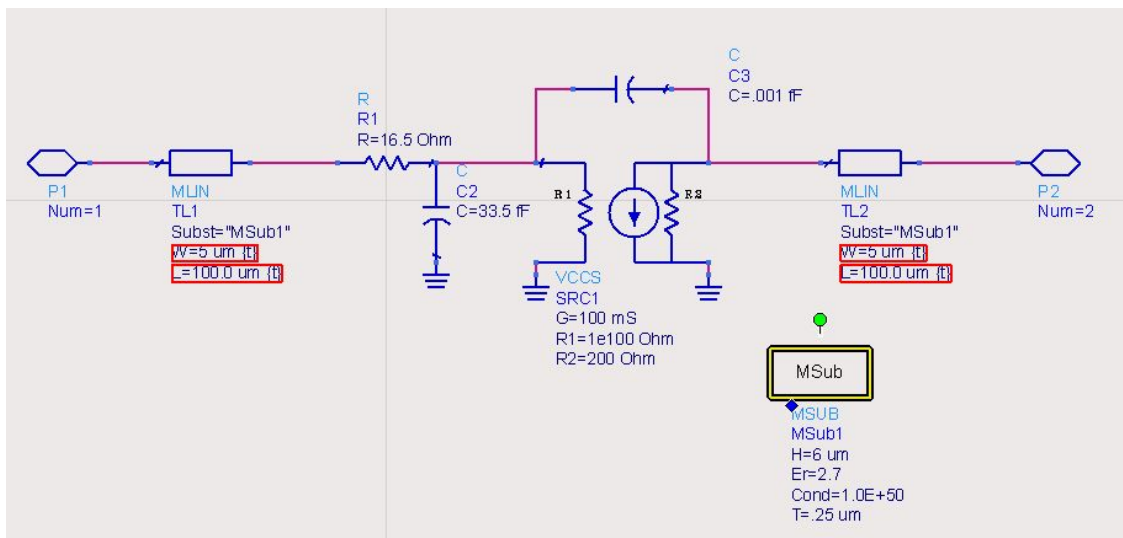

m1
freq=100.0GHz
S(1,1)=0.614 / -140.038
impedance = $Z_0 * (0.269 - j0.340)$

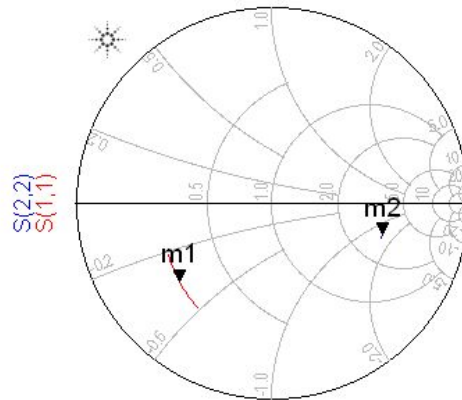
m2
freq=100.0GHz
S(2,2)=0.583 / -15.808
impedance = $Z_0 * (3.026 - j1.453)$



freq (90.00GHz to 110.0GHz)


High-Impedance 5 um-wide line:

Tune to constant conductance:

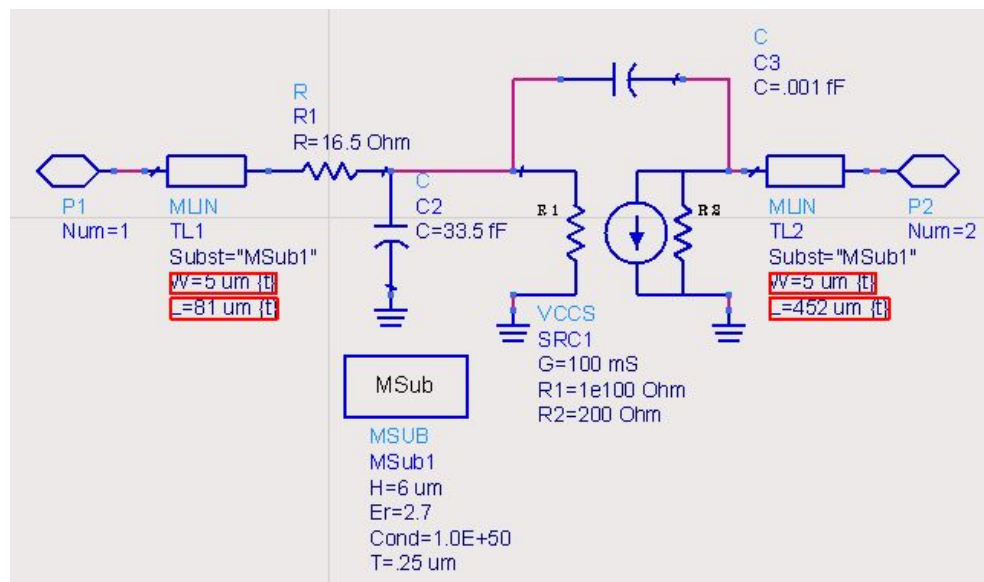


m1
 freq=100.0GHz
 $S(1,1)=0.630 \angle -128.940$
 admittance = $Y_0 * (0.996 + j1.621)$

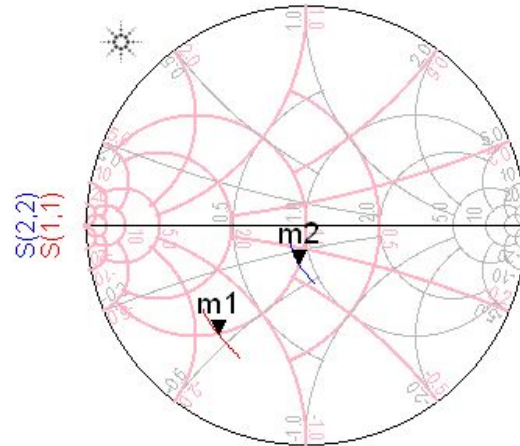m2
 freq=100.0GHz
 $S(2,2)=0.176 \angle -100.354$
 admittance = $Y_0 * (1.001 + j0.358)$




freq (90.00GHz to 110.0GHz)

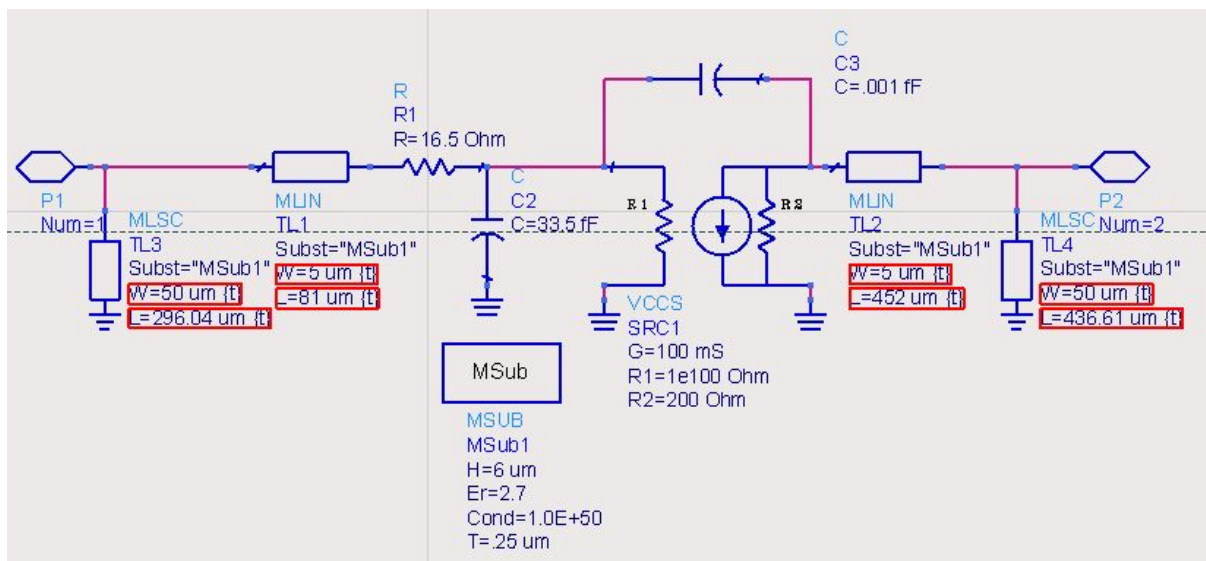Adding shunt inductance to move along constant circle of conductance:



m1
 freq=100.0GHz
 S(1,1)=0.002 / -16.997
 admittance = $Y_0 * (0.996 + j0.001)$

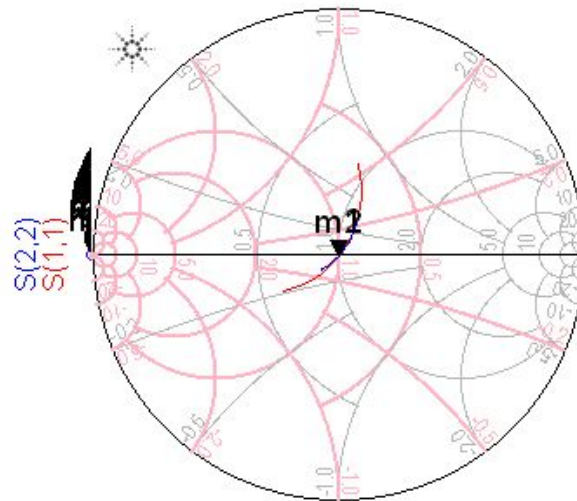
m2
 freq=100.0GHz
 S(2,2)=9.954E-4 / -147.940
 admittance = $Y_0 * (1.002 + j0.001)$



freq (90.00GHz to 110.0GHz)


Low-Impedance 50 um-wide line:

Tune to constant conductance:

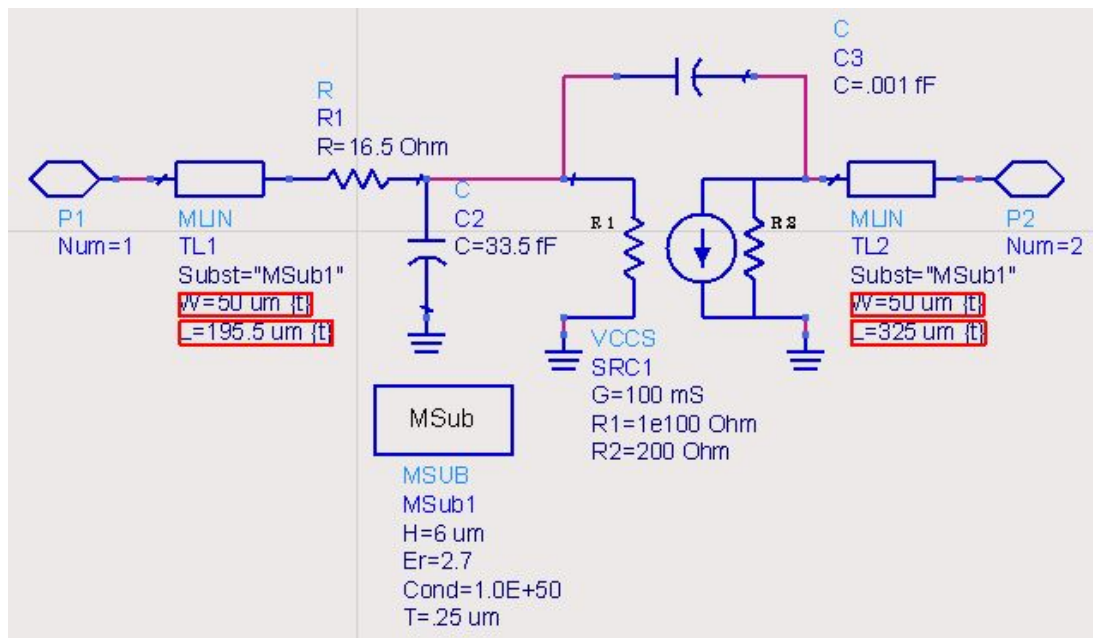


m1
 freq=100.0GHz
 $S(1,1)=0.876 \angle -151.147$
 admittance = $Y_0 * (1.000 + j3.630)$

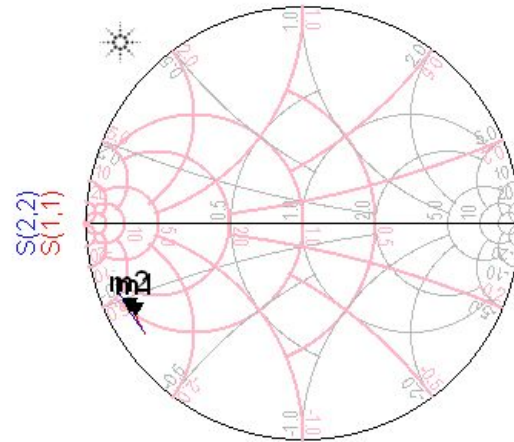m2
 freq=100.0GHz
 $S(2,2)=0.891 \angle -152.944$
 admittance = $Y_0 * (0.996 + j3.918)$




freq (90.00GHz to 110.0GHz)

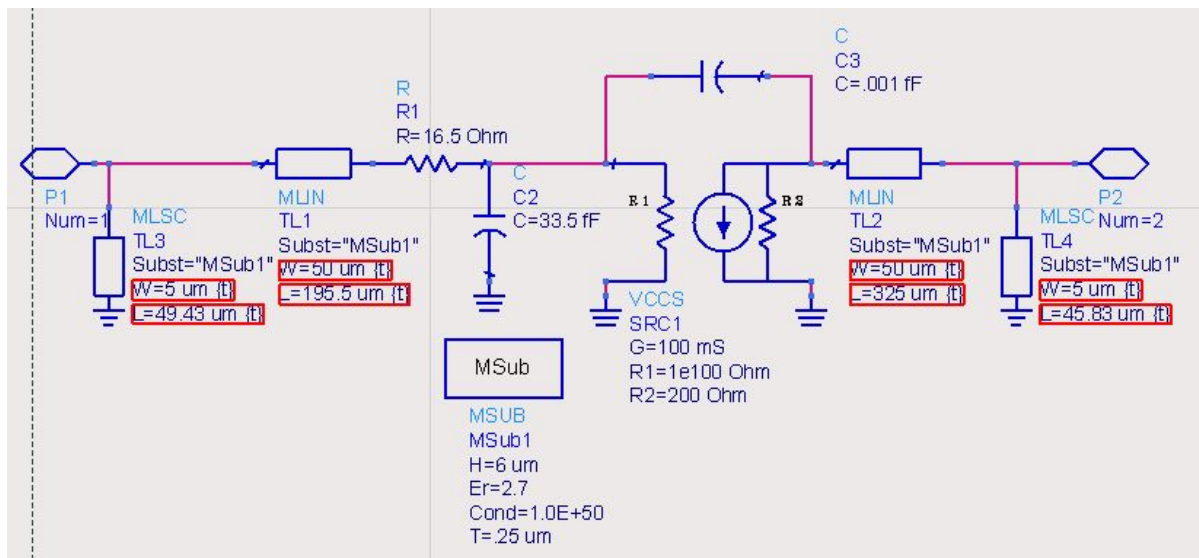Adding shunt inductance to move along constant circle of conductance:




m1
 freq=100.0GHz
 $S(1,1)=7.472\text{E-}4 \angle -113.021$
 admittance = $Y_0 * (1.001 + j0.001)$

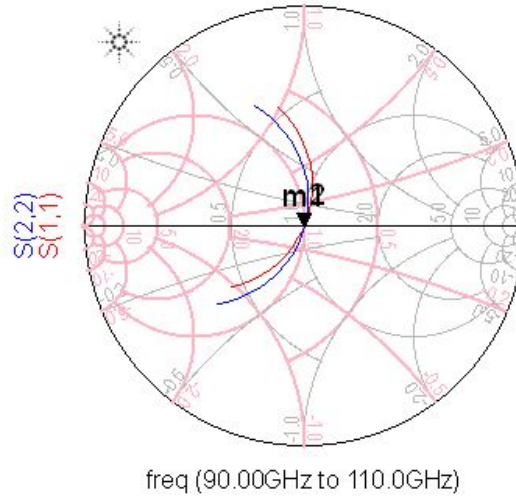m2
 freq=100.0GHz
 $S(2,2)=0.002 \angle -2.284$
 admittance = $Y_0 * (0.996 + j1.497\text{E-}4)$




Part B

Initial Lumped RC Matching Circuit

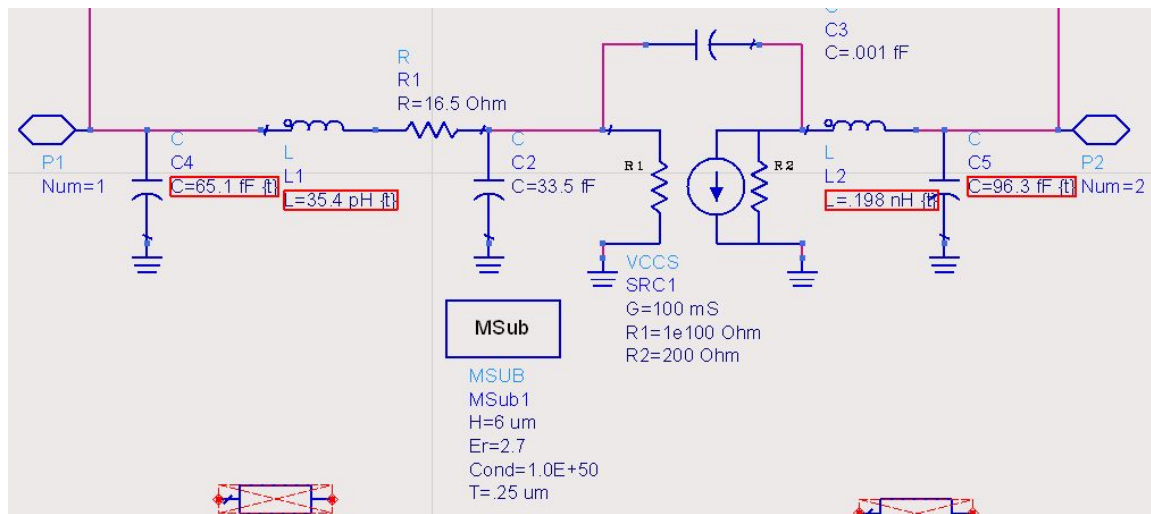


Lumped RC Matching Circuit after tuning

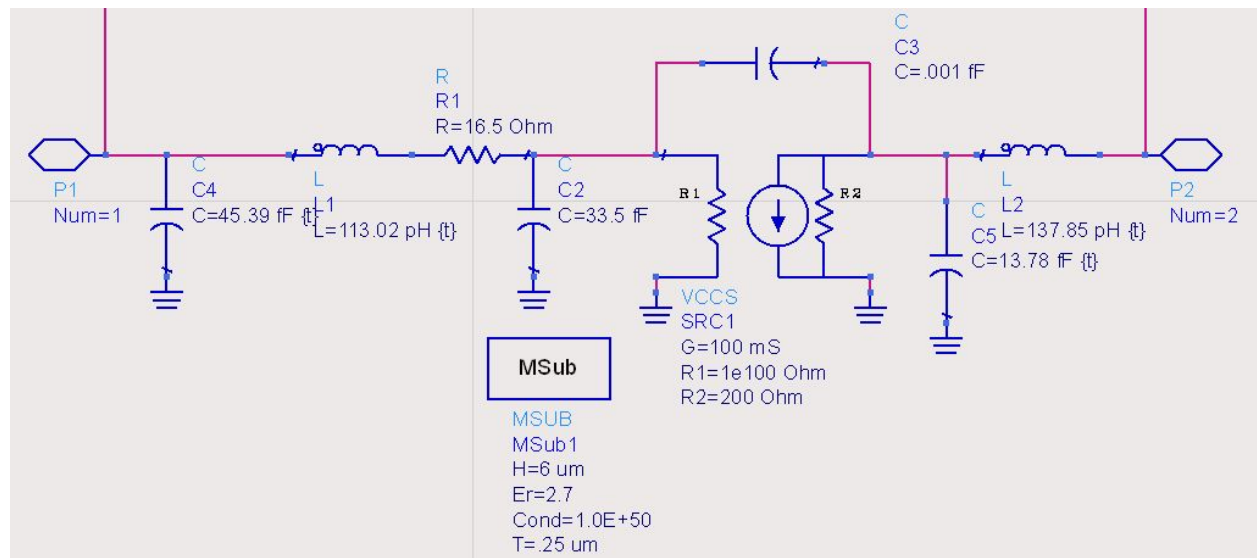




m1
freq= 100.0GHz
S(1,1)=6.754E-4 / -68.804
admittance = $Y_0 * (1.000 + j0.001)$

m2
freq= 100.0GHz
S(2,2)=5.253E-4 / 101.187
impedance = $Z_0 * (1.000 + j0.001)$

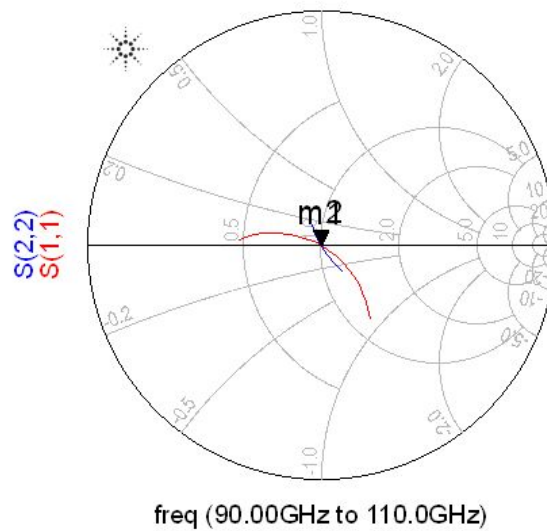



Problem 4

Part A)

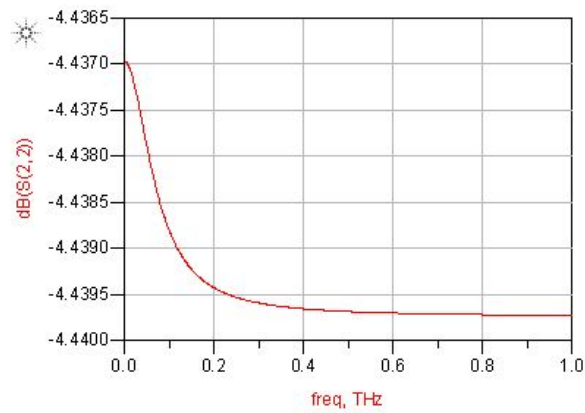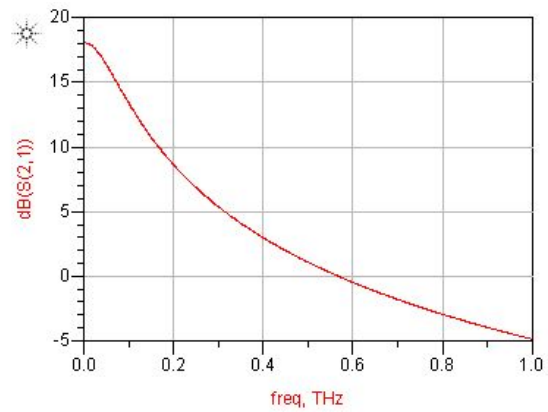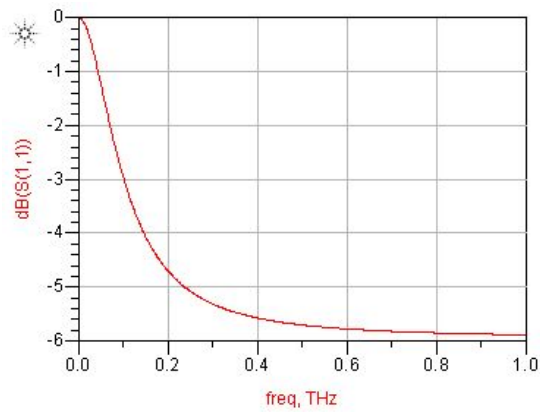



Part B)

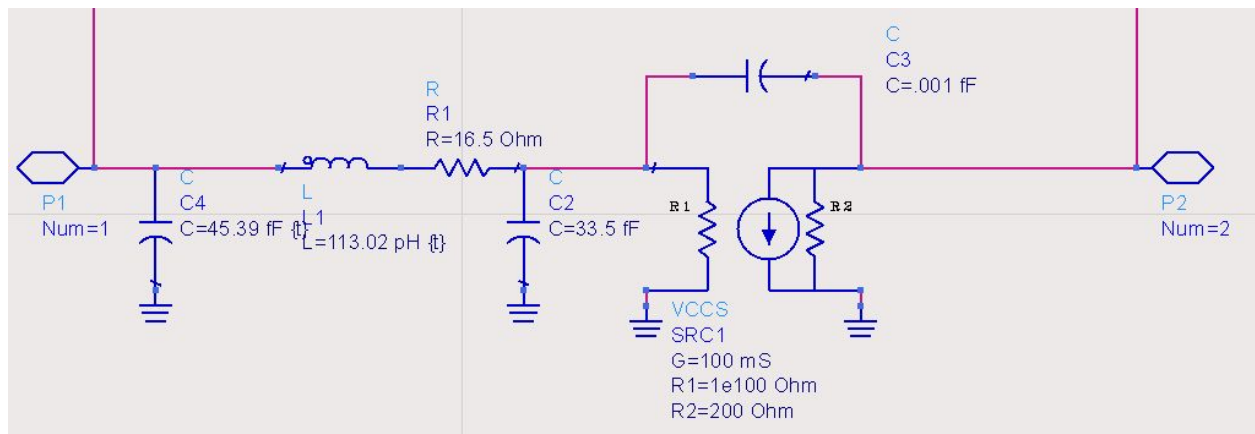

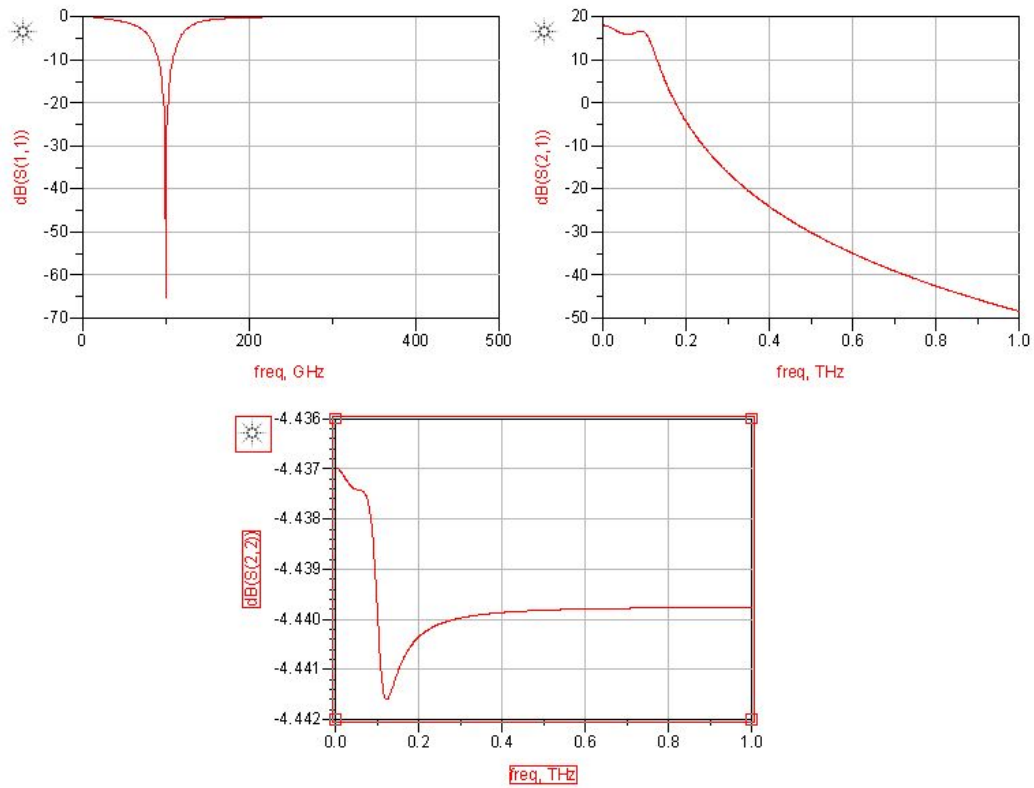


Part C)

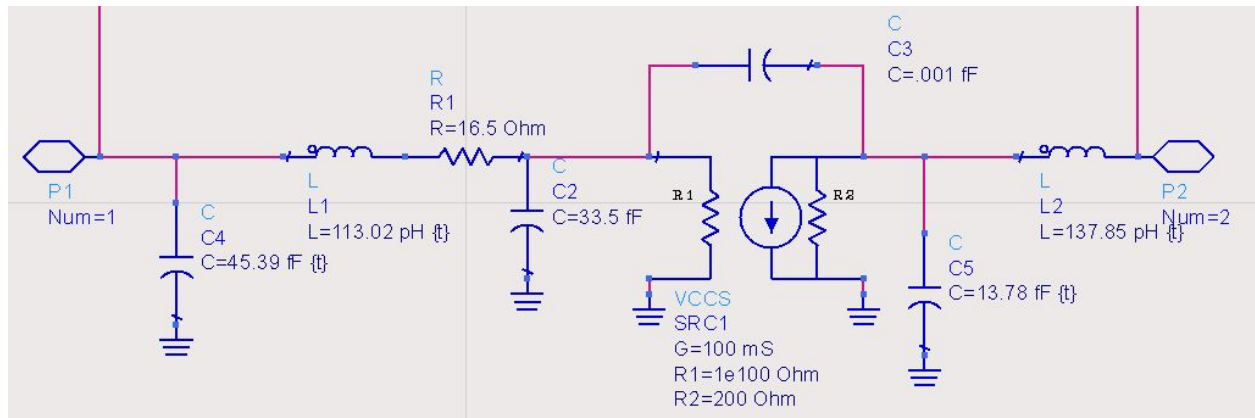

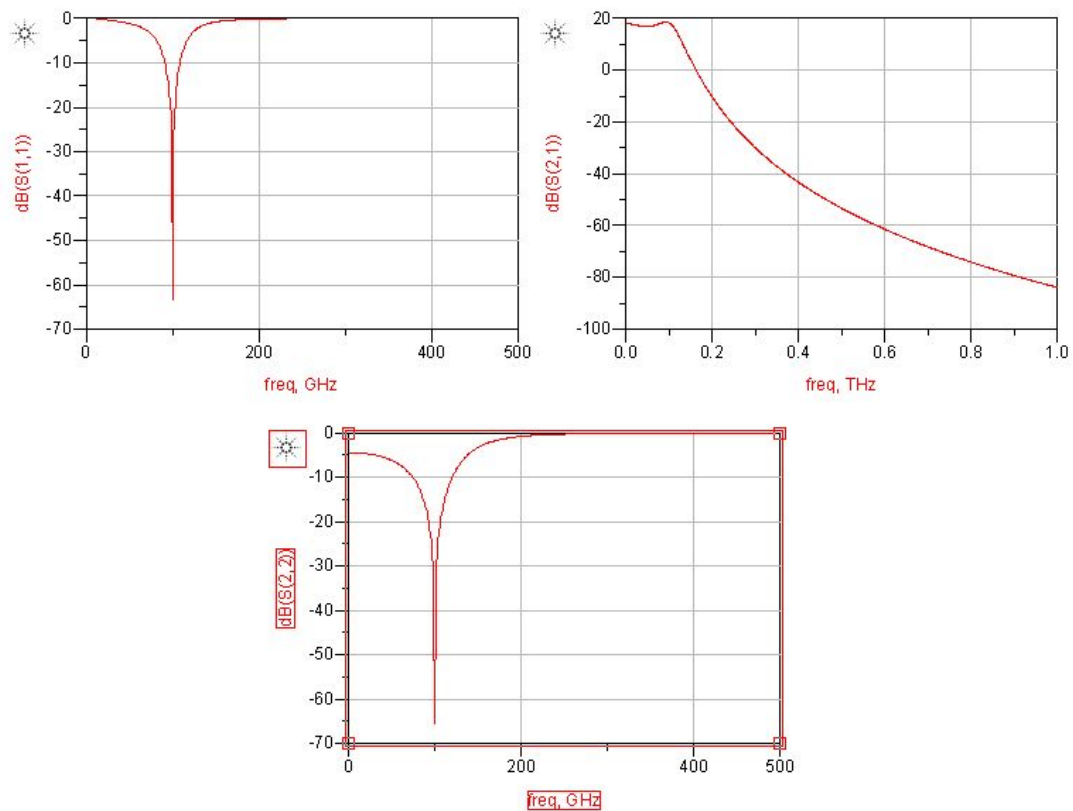

Part D)

m1	m2
freq=100.0GHz	freq=100.0GHz
$S(1,1)=6.840\text{E-}4 / 46.714$	$S(2,2)=5.260\text{E-}4 / 108.216$
admittance = $Y_0 * (0.999 - j9.950\text{E-}4)$	impedance = $Z_0 * (1.000 + j9.989\text{E-}4)$

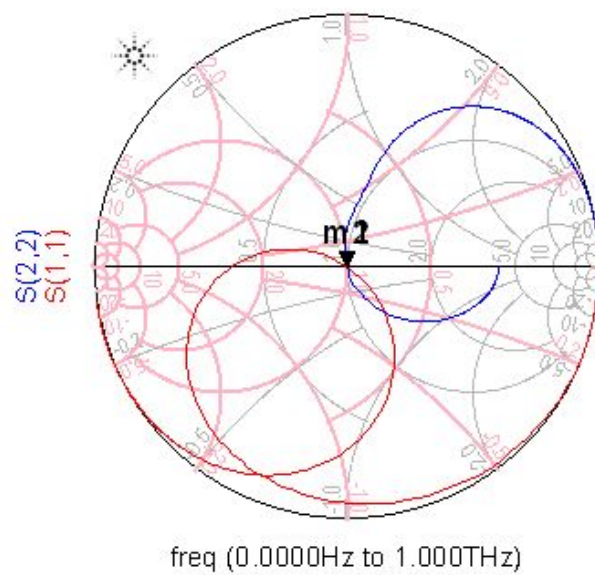


Tuning is more complicated now that S11 and S22 are dependent on each other.


Part E) It is impossible to match the circuits because the connections between the input and the output (Cgd) is too large. In other words, S11 and S22 are too dependent on each other to perfectly match the networks.

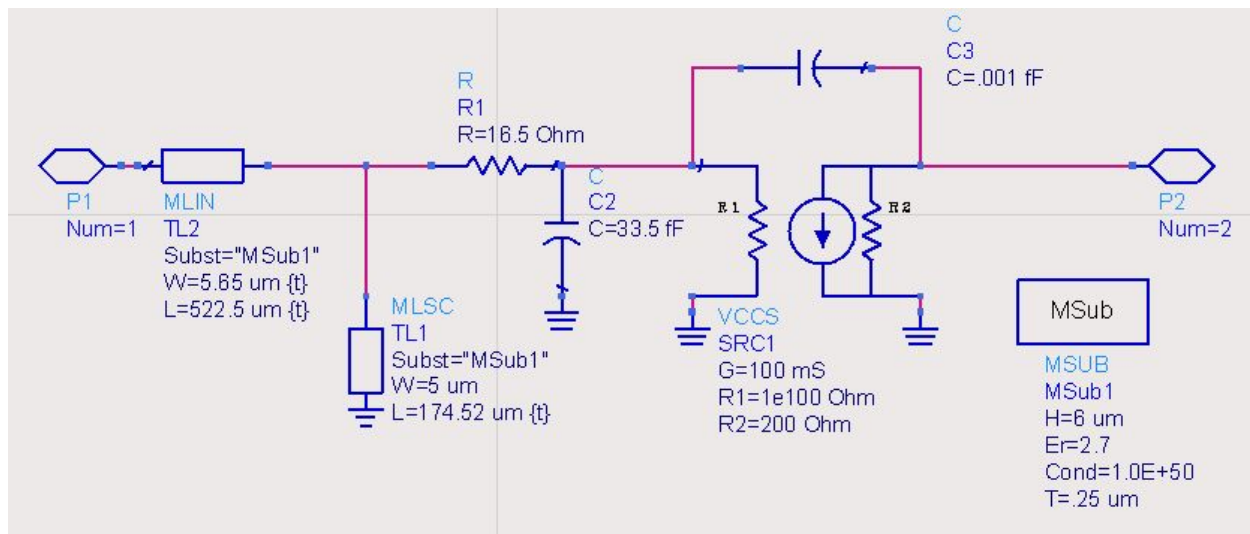Problem 5


SC-High-Impedance-Shunt Stub and Series Line at Input


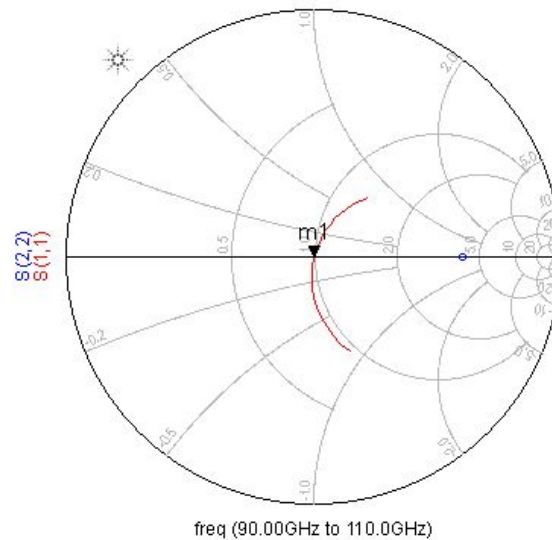
```
m1
freq=100.0GHz
S(1,1)=3.518E-4 / -44.869
impedance = Z0 * (1.000 - j4.966E-4)
```




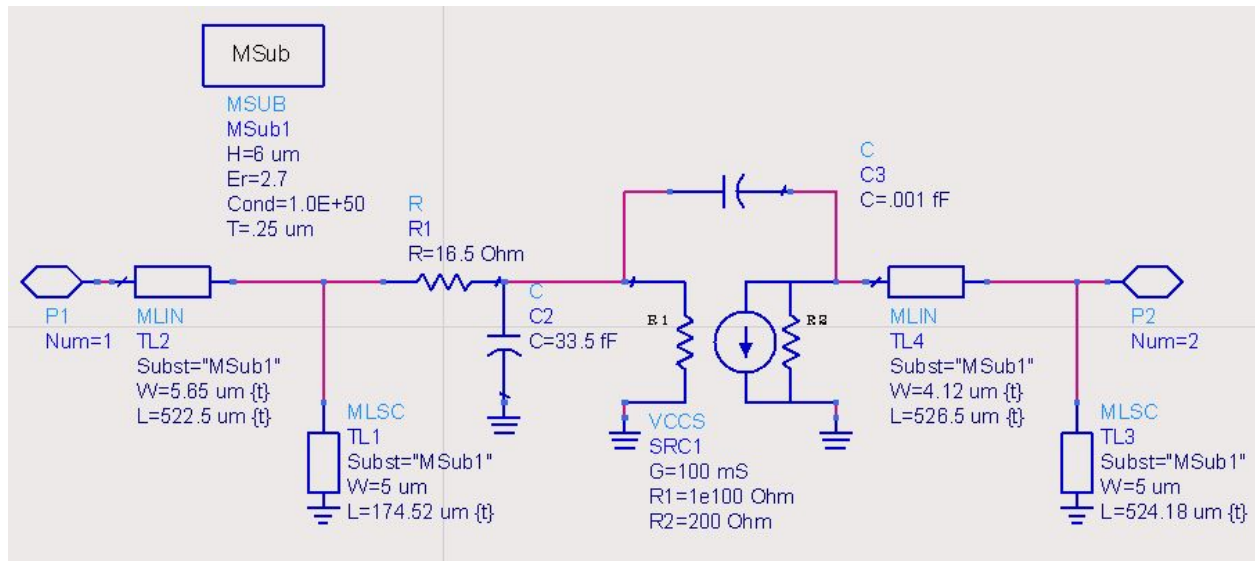SC-High-Impedance-Shunt Stub and Series Line at Output




m1
freq=100.0GHz
S(1,1)=4.112E-4 / -6.367
impedance = Z0 * (1.001 - j9.127E-5)

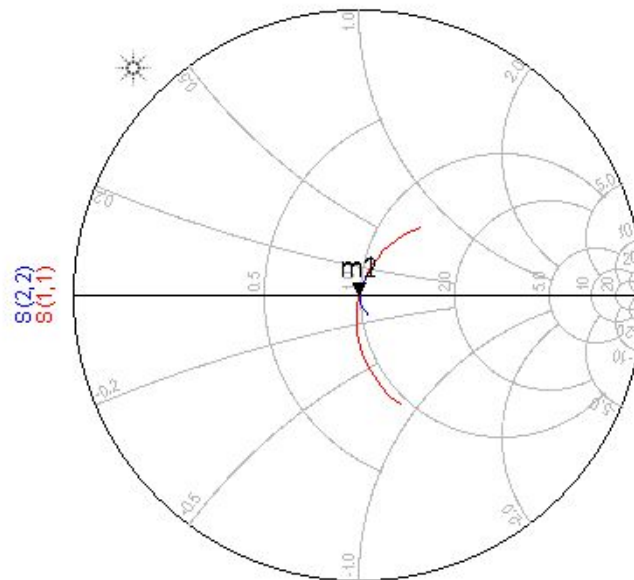m2
freq=100.0GHz
S(2,2)=7.421E-4 / -61.755
impedance = Z0 * (1.001 - j0.001)




freq (90.00GHz to 110.0GHz)

Problem 6

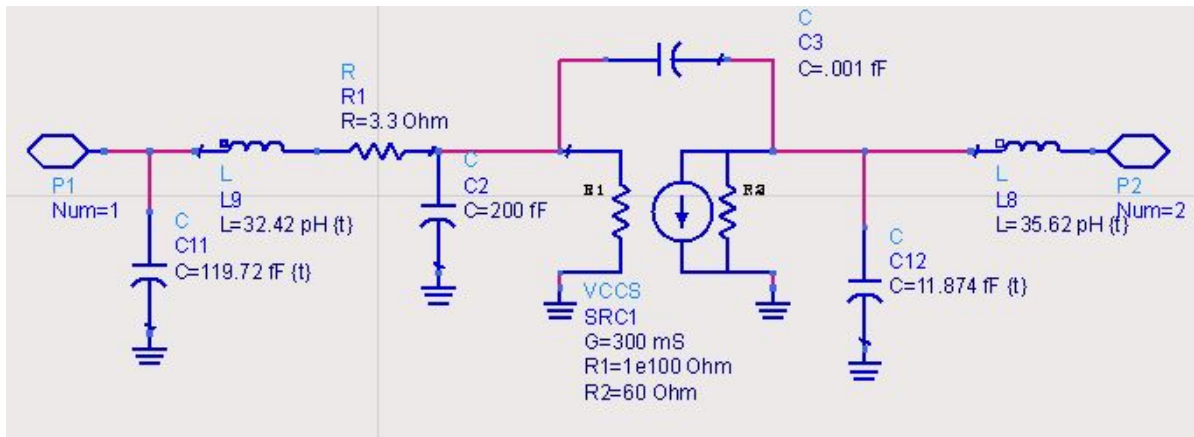



m1
freq=100.0GHz
S(1,1)=5.570E-4 / 100.676
Impedance = $Z_0 * (1.000 + j0.001)$

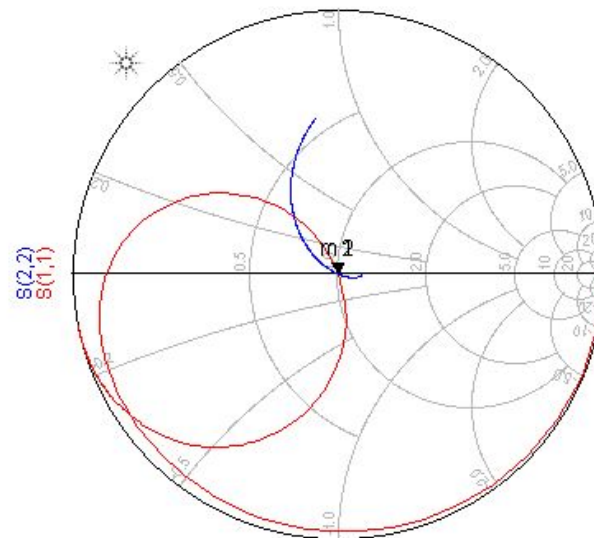m2
freq=100.0GHz
S(2,2)=2.470E-4 / 169.894
Impedance = $Z_0 * (1.000 + j8.663E-5)$




freq (0.0000Hz to 300.0GHz)

Part B

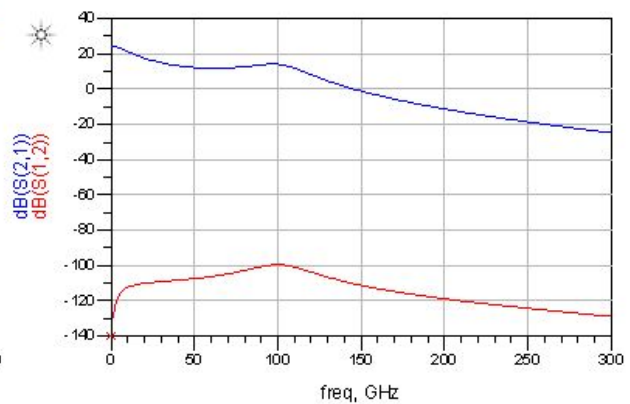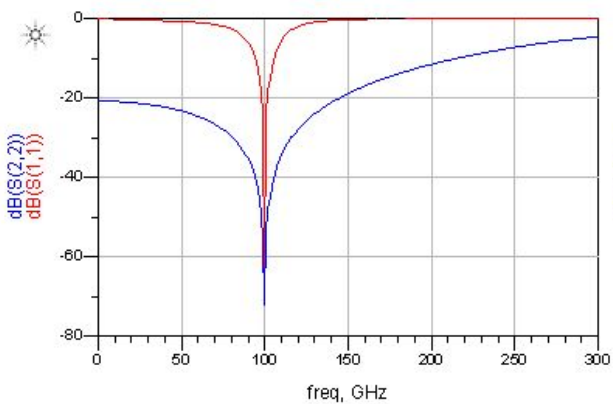


Problem 7

Part A

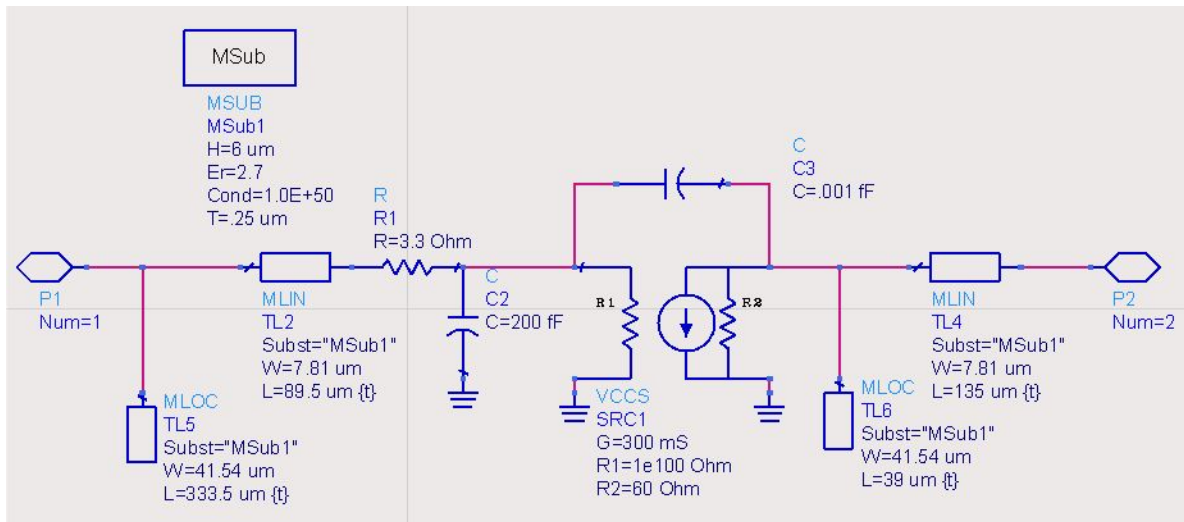


m1
freq=100.0GHz
S(1,1)=0.004 / 59.356
impedance = Z0 * (1.004 + j0.008)

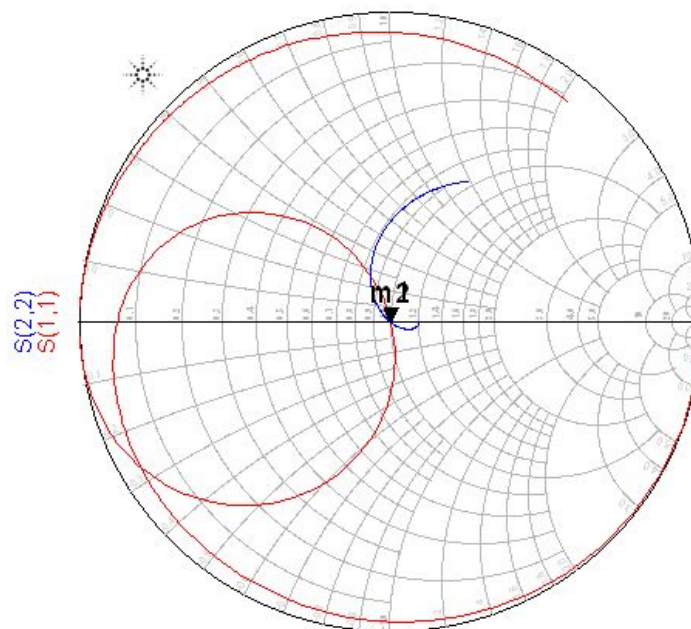m2
freq=100.0GHz
S(2,2)=7.315E-4 / -12.850
impedance = Z0 * (1.001 - j3.258E-4)




freq (0.0000Hz to 300.0GHz)

Part B

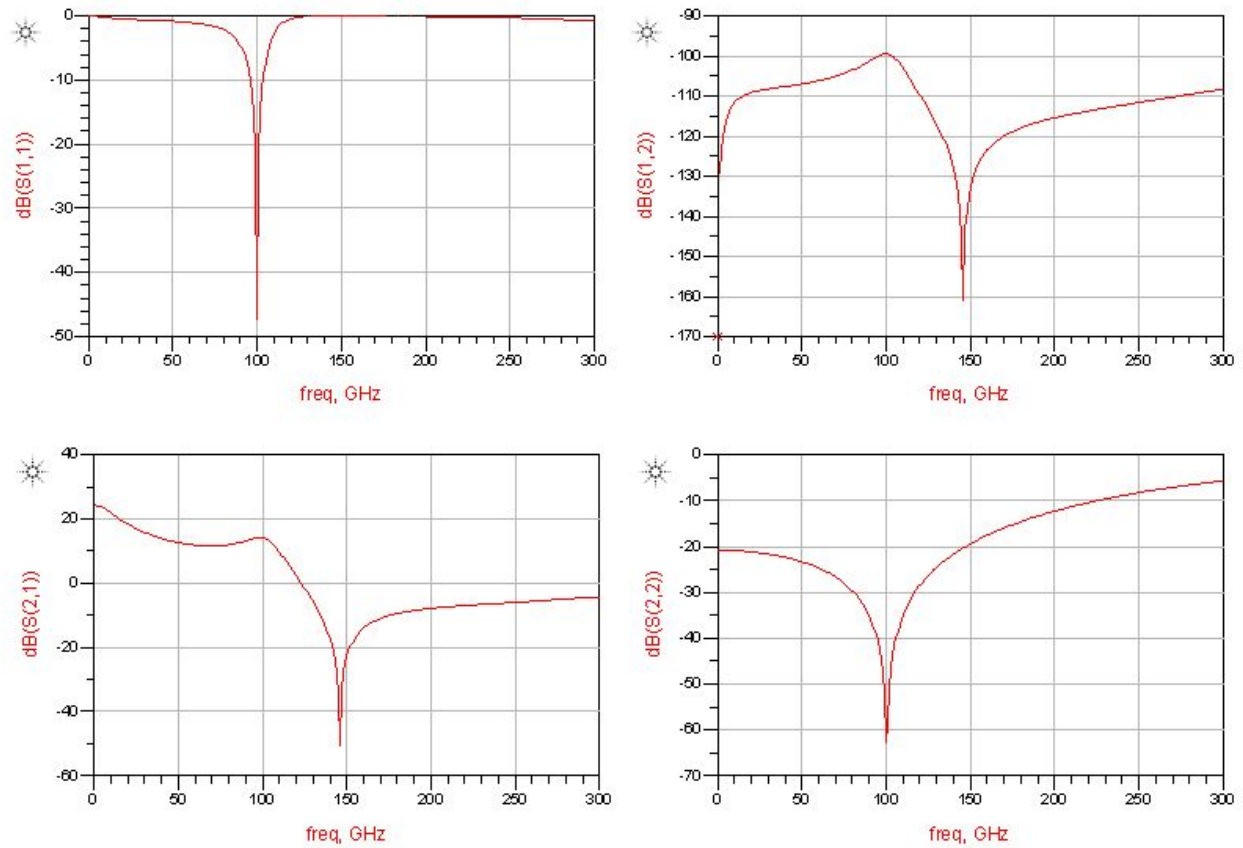


Problem 8

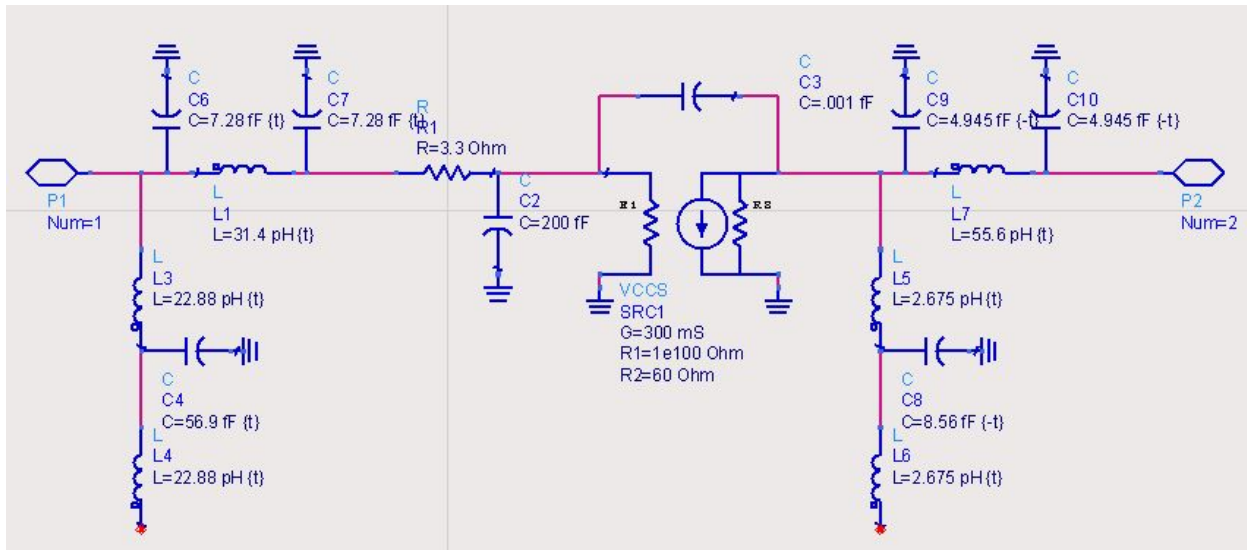



m1
 freq=100.0GHz
 $S(1,1)=0.001 / 87.930$
 impedance = $Z_0 * (1.000 + j0.002)$

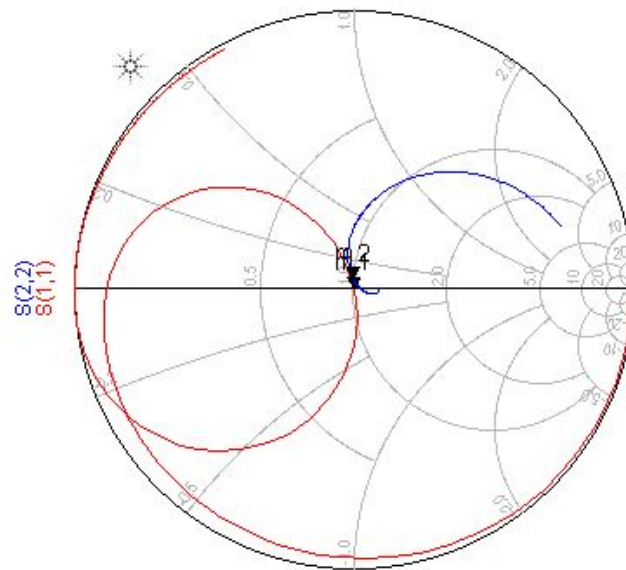m2
 freq=100.0GHz
 $S(2,2)=0.034 / 93.835$
 impedance = $Z_0 * (0.993 + j0.067)$



freq (0.0000Hz to 300.0GHz)

Part B)

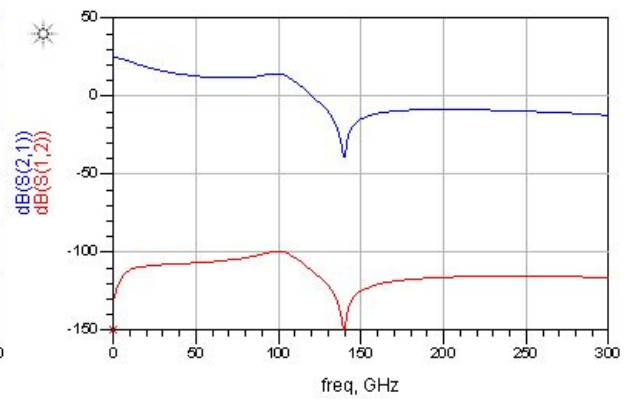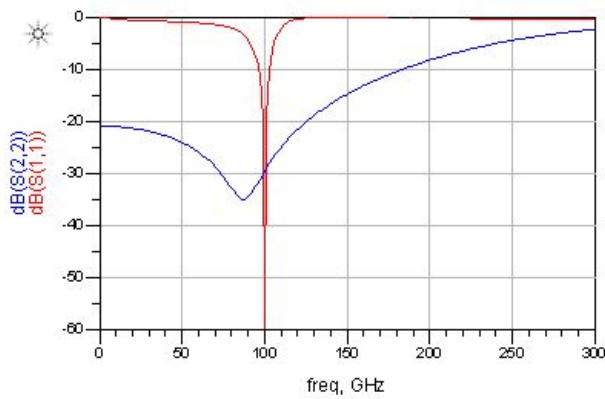

Problem 9

