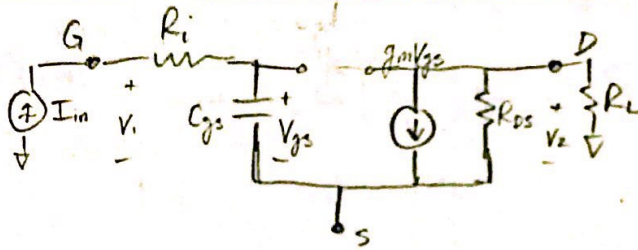


Problem 1



$$\begin{aligned} g_m &= 1.5 \text{ mS}/\mu\text{m}\cdot\text{V} \\ R_i &= 1.5/g_m \\ C_{gd} &= 0 \text{ fF} \\ C_{gs} &= 0.75 \text{ fF}/\mu\text{m}\cdot\text{V} \\ G_{ds} &= 0.1 \text{ mS}/\mu\text{m}\cdot\text{V} \end{aligned}$$

(15/15)

Part a)

$$G_{\text{max}} = \frac{P_{\text{AVA}}}{P_{\text{in}}} = \frac{P_{\text{out}}}{P_{\text{in}}}$$

$$I_{\text{out}} = -\frac{g_m V_{gs}}{2} = \frac{I_{\text{in}}}{j\omega C_{gs}} \cdot \frac{g_m}{2} \rightarrow P_{\text{out}} = \frac{I_{\text{in}}^2 g_m^2}{(\omega^2 C_{gs}^2)} \cdot \frac{R_{DS}}{4}$$

$$P_{\text{in}} = I_{\text{in}}^2 R_i$$

$$\Rightarrow G_{\text{max}}(\omega) = \frac{g_m^2}{\omega^2 C_{gs}^2} \cdot \frac{R_{DS}}{4R_i} = \frac{10 \times 10^{24}}{\omega^2}$$

$$H_{21}(\omega) = \frac{g_m}{j\omega C_{gs}} = \frac{2 \times 10^{12}}{\omega}$$

Part b)

$$G_{\text{max}}\left(\frac{f_{\text{max}}}{3}\right) = \frac{10 \times 10^{24}}{(2\pi f_{\text{max}}/3)^2} = \frac{2.28 \times 10^{24}}{f_{\text{max}}^2}$$


$$f = f_{\text{max}} @ G_{\text{max}} = 1$$

$$G_{\text{max}} = 1 = \frac{10 \times 10^{24}}{(2\pi f_{\text{max}})^2} \Rightarrow f_{\text{max}} = \frac{\sqrt{10 \times 10^{24}}}{2\pi} = 503.3 \text{ GHz}$$

$$\Rightarrow G_{\text{max}}\left(\frac{f_{\text{max}}}{3}\right) = 9$$

$$Z_{\text{gen}} = Z_{\text{in}}^* = R_i - \frac{1}{j\omega C_{gs}} = 10 + j12.65 \Omega$$
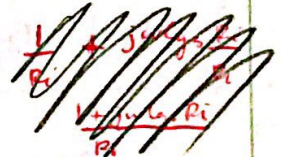
$$Z_L = Z_{\text{out}}^* = R_{DS} = 100 \Omega$$




Part c)

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{I_1}{I_1(R_i + 1/j\omega C_{gs})} = \frac{j\omega C_{gs}}{j\omega C_{gs} R_i + 1}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = \frac{+g_m V_{gs}}{V_1}, \quad V_{gs} = V_1 \left(\frac{1/j\omega C_{gs}}{R_i + 1/j\omega C_{gs}} \right)$$

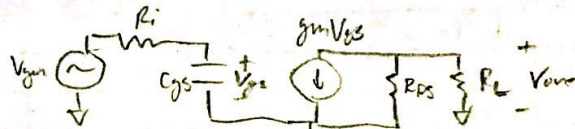
$$= \frac{+g_m}{1 + j\omega C_{gs} R_i}$$



$$S_{21} = \frac{2V_{\text{out}}}{V_{\text{gen}}} \Big|_{Z_L=Z_o} = \frac{-g_m V_{gs} \cdot R_L \parallel Z_o}{V_{gs} (1 + j\omega C_{gs} (R_i + Z_o))}$$

$$V_{gs} = \frac{V_{\text{gen}}}{1 + j\omega C_{gs} (R_i + Z_o)}$$
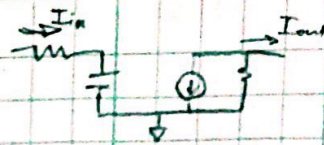
$$= \frac{-2g_m (R_L \parallel Z_o)}{(1 + j\omega C_{gs} (R_i + Z_o))}$$



Part D) Insertion Power Gain:

$$\|S_{21}\|^2 = \left(\frac{2 g_m (R_i \| Z_o)}{1 + j\omega C_{gs} (R_i + Z_o)} \right)^2 = \left(\frac{5}{\sqrt{1^2 + (2.83)^2}} \right)^2 = \frac{25}{1 + 2.83^2} = 11.125$$

$$G_i = 10 \log_{10} (\|S_{21}\|^2) = 10.46 \text{ dB}$$

Operating Power Gain: $Z_L = Z_o$

$$P_{in} = I_{in}^2 R_i = (V_{gs} \cdot j\omega C_{gs})^2 R_i \quad \text{Current Divider}$$

$$P_L = I_{out}^2 Z_L = \left(g_m V_{gs} \left[\frac{R_o}{R_o + Z_o} \right] \right)^2 Z_o$$


$$G_p = \frac{P_L}{P_{in}} = \frac{\left(g_m V_{gs} \left[\frac{R_o}{R_o + Z_o} \right] \right)^2 Z_o}{(V_{gs} \cdot j\omega C_{gs})^2 R_i}$$

$$= \frac{\left((100 \text{ mS}) \left[\frac{100 \Omega}{100 \Omega + 50 \Omega} \right] \right)^2 \cdot 50 \Omega}{(100 \text{ GHz} \cdot 2\pi \cdot 75 \text{ fF})^2 \cdot 10 \Omega}$$

$$= 22.52$$

$$\Rightarrow 13.52 \text{ dB}$$

Available Power Gain

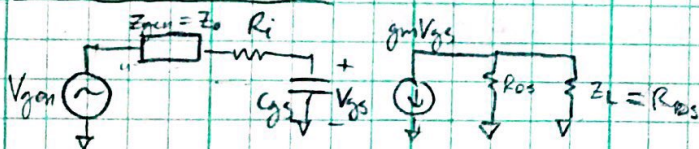

$$V_{gs} = V_{gen} \frac{1/j\omega C_{gs}}{1/j\omega C_{gs} + R_i + Z_o} = V_{gen} \frac{1}{1 + j\omega C_{gs} (R_i + Z_o)}$$

$$P_{out} = (I_{out})^2 R_o = \left(\frac{g_m V_{gs}}{2} \right)^2 R_o$$

$$V_{gs} = \frac{I_{in}}{j\omega C_{gs}} \quad ; \quad I_{in} = \frac{V_{gen}}{R_i + Z_o + 1/j\omega C_{gs}} \Rightarrow V_{gs} = \frac{V_{gen}}{j\omega C_{gs} (R_i + Z_o) + 1}$$

$$\Rightarrow P_{out} = \frac{g_m^2}{4} \left(\frac{V_{gen}}{j\omega C_{gs} (R_i + Z_o) + 1} \right)^2 R_o$$

$$P_{in} = \left(\frac{V_{gen}}{2} \right)^2 \frac{1}{Z_o} =$$


$$G_A = \frac{P_{out}}{P_{in}} = \frac{g_m^2 R_o}{4} \left(\frac{1}{1 + j\omega C_{gs} (R_i + Z_o)} \right)^2 = 12.508 \Rightarrow 10.972 \text{ dB}$$

$$\begin{aligned}
 G_{\max} &= \frac{g_m^2}{\omega^2 C_{gs}^2} \frac{R_{cs}}{4R_i} \quad (\text{from Part a}) \\
 &= 25.33 \\
 &= \boxed{14.04 \text{ dB}}
 \end{aligned}$$

Part c) Wave forms Attached

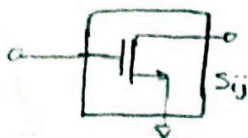Problem 2

$$\begin{aligned}
 S_{11} &= 0.25 & S_{12} &= 0 & Z_0 &= 50 \Omega \\
 S_{22} &= 0.7071 & S_{21} &= 1.0
 \end{aligned}$$



a.) $Z_{gen} = 50 \Omega$ $Z_L = 50 \Omega$
 $P_{avg} = 1 \text{ mW}$

$$G_T = \frac{P_{WR \text{ to } Z_L}}{P_{avg}} = \|S_{21}\|^2 \Rightarrow \boxed{P_L} = \|S_{21}\|^2 P_{avg} = (1.0)^2 (1 \text{ mW}) = \boxed{0.1 \text{ W}}$$

b.) $Z_{gen} = 75 \Omega$ $Z_L = 25 \Omega$
 $P_{avg} = 1 \text{ mW}$

$$G_T = \frac{P_L}{P_{avg}} = \frac{(1 - \| \Gamma_L \|^2)(1 - \| \Gamma_S \|^2) \| S_{21} \|^2}{\| (1 - S_{11} \Gamma_S)(1 - \Gamma_L S_{22}) - \Gamma_S \Gamma_L S_{11} S_{22} \|^2}$$

$$\begin{aligned}
 \Gamma_S &= \frac{75 - 50}{75 + 50} \\
 &= 0.2
 \end{aligned}$$

$$\begin{aligned}
 \Gamma_L &= \frac{25 - 50}{25 + 50} \\
 &= -0.333
 \end{aligned}$$

$$= \frac{(1 - (-0.33)^2)(1 - (0.2)^2)(1.0)^2}{\| (1 - 0.25 \times 0.2)(1 - (-0.33)(0.7071)) - (0.2)(-0.33)(0.25 \times 0.7071) \|^2}$$

$$\Rightarrow \boxed{P_L} = 60.95 \cdot 1 \text{ mW} = \boxed{60.95 \text{ mW}}$$

c.) $Z_{gen} = Z_{in}^*$ $Z_L = 30 \Omega$
 $P_{avg} = 1 \text{ mW}$

$$G_p = \frac{1}{1 - \| \Gamma_{in} \|^2} \cdot \frac{\| S_{21} \|^2}{\| 1 - S_{22} \Gamma_L \|^2} = \frac{P_L}{P_{avg}} \Big|_{\Gamma_S = \Gamma_{in}^*}$$

$$= 72.21$$

$$\Rightarrow \boxed{P_L = 72.21 \text{ mW}}$$

$$\begin{aligned}
 \Gamma_L &= \frac{30 - 50}{30 + 50} = -\frac{1}{4} \\
 \Gamma_{in} &= S_{11} + \Gamma_L \frac{S_{21} S_{12}^*}{1 - S_{22} \Gamma_L} = 0.25
 \end{aligned}$$

d) For transistor (Matched Both ends):

$$G_{MAX} = \frac{1}{1 - \|S_{11}\|^2} \frac{\|S_{21}\|^2}{1 - \|S_{22}\|^2} = 213.33$$

G_{MAX} for transistor equals G_{MAX} for amplifier.

$$G_{MAX} = \frac{1}{1 - \|S_{11}^{amp}\|^2} \frac{\|S_{21}^{amp}\|^2}{1 - \|S_{22}^{amp}\|^2}$$

$S_{11}^{amp} = S_{22}^{amp} = 0$ because input and output are matched.

$$G_{MAX} = \|S_{21}^{amp}\|^2 = 213.33 \Rightarrow S_{21}^{amp} = 14.61$$

For Amplifier:

$$G_T = \frac{P_L}{P_{avg}} = \frac{(1 - \|T_3\|^2)(1 - \|T_4\|^2)\|S_{11}\|^2}{\|(1 - S_{11}T_3)(1 - T_4S_{22}) - T_3T_4S_{11}S_{22}\|^2}$$

$$= 169.4 \text{ mW}$$

$$T_3 = \frac{25 - 50}{25 + 50} = -\frac{1}{3}$$

$$T_4 = \frac{100 - 50}{100 + 50} = \frac{1}{3}$$

$S_{12}^{amp} = 0$ for unilateral amp

Problem 3 $S_{11} = 0.1$ $S_{12} = 1$
 $S_{22} = 0.125$ $S_{21} = 20$




10



$$S_{11} = \frac{Z_{in}/Z_0 - 1}{Z_{in}/Z_0 + 1}, \quad Z_{in} = 50 \parallel Z_0 = 25 \Omega, \Rightarrow S_{11} = -1/3 = S_{22} \text{ by symmetry}$$

$$S_{21} = \frac{2V_{out}}{V_{gen}} \bigg|_{Z_L=Z_0}, \quad V_{out} = \frac{V_{gen} \cdot (Z_0 \parallel 50)}{Z_0 + (Z_0 \parallel 50)} = \frac{V_{gen}}{3}$$
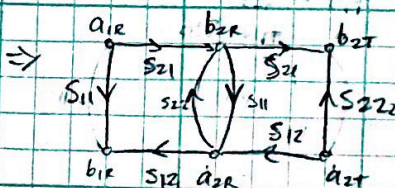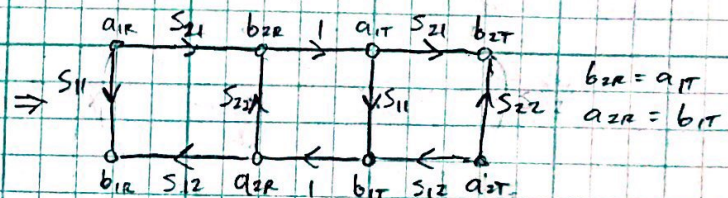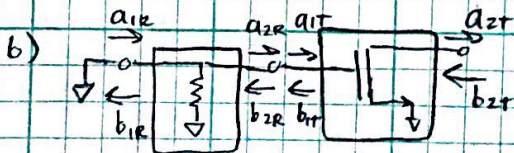
$$= \frac{2}{3} = S_{12} \text{ by symmetry}$$



$$S_{11} = \frac{b_{1R}}{a_{1R}}$$

$$S_{12} = \frac{b_{1R}}{a_{2T}}$$

loops: $S_{11T} S_{22R}$

$$S_{21} = \frac{b_{2T}}{a_{1R}}$$

$$S_{22} = \frac{b_{2T}}{a_{2T}}$$

$$S_{11} = \frac{b_{1R}}{a_{1R}} = \frac{S_{11R}(1 - S_{11T} S_{22R}) + S_{21R} S_{11T} S_{12R}}{1 - S_{11T} S_{22R}} = \boxed{-0.29}$$

$$S_{12} = \frac{b_{1R}}{a_{2T}} = \frac{S_{12R} S_{12T}}{1 - S_{11T} S_{22R}} = \frac{(2/3)(1)}{1 - (0.1)(-1/3)} = \boxed{0.645}$$

$$S_{21} = \frac{b_{2T}}{a_{1R}} = \frac{S_{21T} S_{21R}}{1 - S_{11T} S_{22R}} = \frac{(20)(2/3)}{1 - (0.1)(-1/3)} = \boxed{12.91}$$

$$S_{22} = \frac{b_{2T}}{a_{2T}} = \frac{S_{22T}(1 - S_{11T} S_{22R}) + S_{12T} S_{22R} S_{11T}}{1 - S_{11T} S_{22R}} = \boxed{-6.33}$$



$$S_{in} = \begin{bmatrix} b_{11}/a_{1i} & b_{1i}/a_{2i} \\ b_{2i}/a_{1i} & b_{2i}/a_{2i} \end{bmatrix}$$

Problem 4

$$S_{laser} = \begin{bmatrix} 0.1 & 10 \\ 10 & 0.1 \end{bmatrix}$$

$$S_{isolator} = \begin{bmatrix} 0 & 0.25 \\ 0.5 & 0 \end{bmatrix}$$
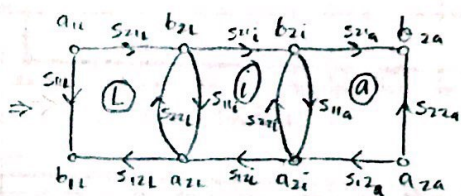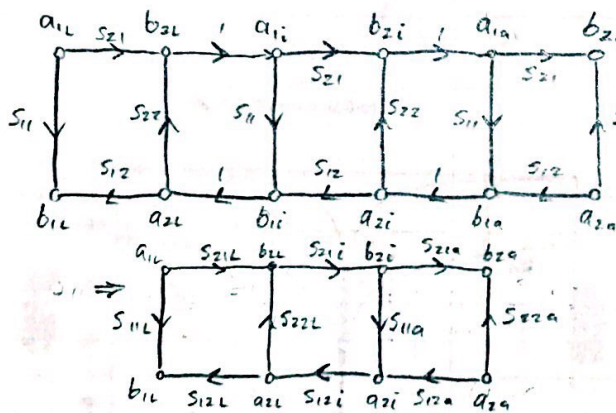
$$S_{attenuator} = \begin{bmatrix} R & T \\ T & R \end{bmatrix} = \begin{bmatrix} b_{1a}/a_{1a} & b_{1a}/a_{2a} \\ b_{2a}/a_{1a} & b_{2a}/a_{2a} \end{bmatrix} = \begin{bmatrix} S_{11a} & S_{12a} \\ S_{21a} & S_{22a} \end{bmatrix}$$



$$b_{2i} = a_{1a}$$

$$a_{2i} = b_{1a}$$

$$S_{11a} = \frac{b_{1a}}{a_{1a}}$$

$$S_{11} = \frac{b_{1L}}{a_{1L}} = \frac{S_{11L}(1 - S_{21i} S_{11a} S_{12i} S_{22L}) + S_{21L} S_{21i} S_{11a} S_{12i} S_{12L}}{1 - S_{21i} S_{11a} S_{12i} S_{22L}} = S_{11L} + \frac{S_{21L} R S_{21i} S_{12i} S_{12L}}{1 - R S_{21i} S_{12i} S_{12L}}$$


$$= 0.1 + \frac{12.5R}{1 - 0.0125R}$$

$$S_{12} = \frac{b_{1L}}{a_{2a}} = \frac{S_{12a} S_{12i} S_{12L}}{1 - S_{21i} S_{11a} S_{12i} S_{22L}} = \boxed{\frac{2.5T}{1 - 0.0125R}}$$

$$S_{21} = \frac{b_{2a}}{a_{1L}} = \frac{S_{21L} S_{21i} S_{21a}}{1 - S_{21i} S_{11a} S_{12i} S_{22L}} = \boxed{\frac{5T}{1 - 0.0125R}}$$

$$S_{22} = \frac{b_{2a}}{a_{2a}} = \frac{S_{22a}(1 - S_{21i} S_{11a} S_{12i} S_{22L}) + S_{12a} S_{12i} S_{22L} S_{21i} S_{21a}}{1 - S_{21i} S_{11a} S_{12i} S_{22L}} = \boxed{\frac{0.125T^2}{1 - 0.0125R}}$$

Problem 1, Part E:

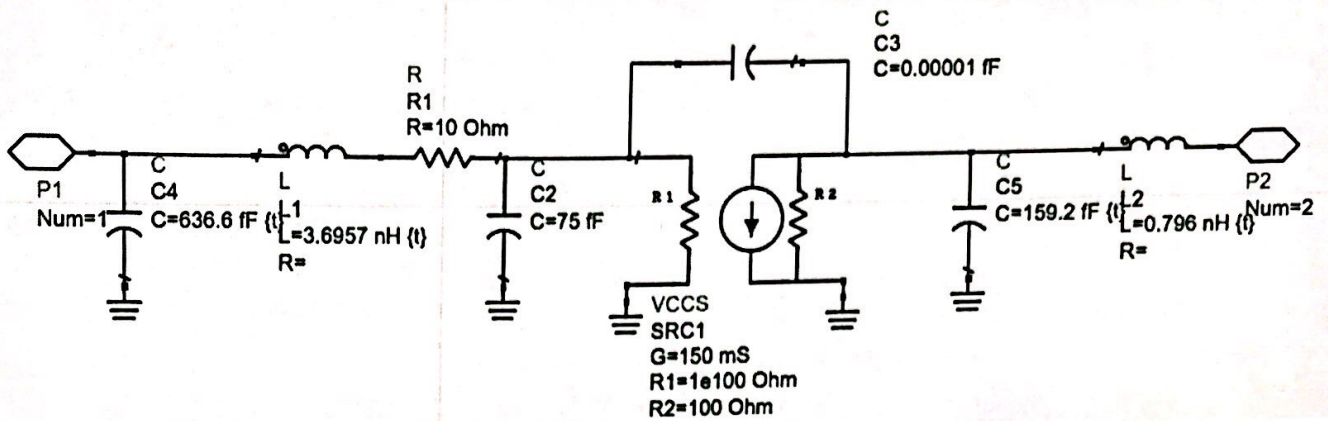

m1
 freq=10.00GHz
 $S(1,1)=5.389E-5 / -9.417$
 impedance = $Z0 * (1.000 - j1.764E-5)$
 m2
 freq=10.00GHz
 $S(2,2)=2.086E-4 / 136.856$
 impedance = $Z0 * (1.000 + j2.851E-4)$

