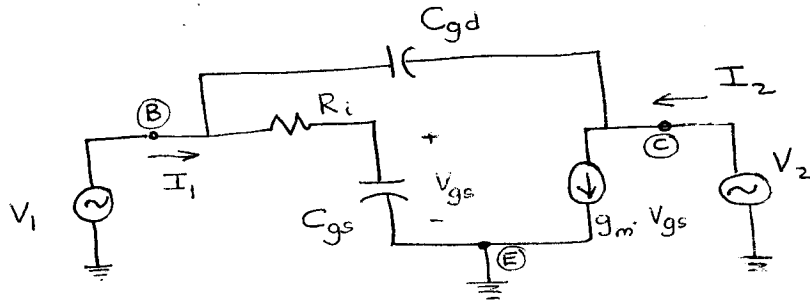


1 a)



$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\frac{1}{1+x} = 1 - x + \dots$$

$$I_1 = \frac{V_1 - V_2}{1/j\omega C_{gd}} + \frac{V_1 - V_{gs}}{R_i}$$

But $\frac{V_1 - V_{gs}}{R_i} = \frac{V_{gs}}{1/j\omega C_{gd}} \Rightarrow V_{gs} = \frac{V_1}{1 + j\omega C_{gs} R_i}$




$$\begin{aligned} \therefore I_1 &= (V_1 - V_2) j\omega C_{gd} + \frac{V_1}{R_i} - \frac{V_1}{R_i (1 + j\omega C_{gs} R_i)} \\ &= V_1 j\omega C_{gd} + \frac{[1 + j\omega C_{gs} R_i] - 1}{R_i (1 + j\omega C_{gs} R_i)} - V_2 j\omega C_{gd} \\ &= V_1 \left[j\omega C_{gd} + \frac{j\omega C_{gs} R_i (1 - j\omega C_{gs} R_i)}{R_i (1 + \omega^2 C_{gs}^2 R_i^2)} \right] - V_2 j\omega C_{gd} \\ &= V_1 \left[\omega^2 C_{gs}^2 R_i + j\omega (C_{gs} + C_{gd}) \right] - V_2 j\omega C_{gd} \end{aligned}$$

Assuming $1 \gg \omega^2 C_{gs}^2 R_i^2$.

$$Y_{11} = \omega^2 C_{gs}^2 R_i + j\omega (C_{gs} + C_{gd})$$

$$Y_{12} = -j\omega C_{gd}$$

(2)

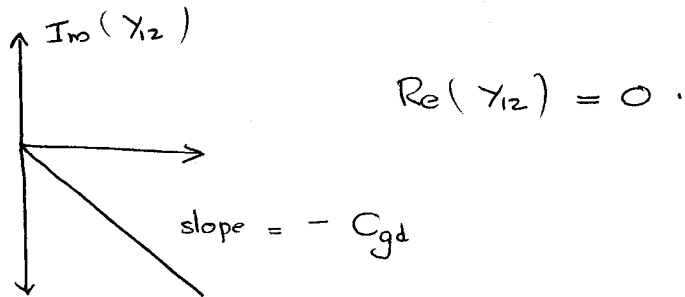
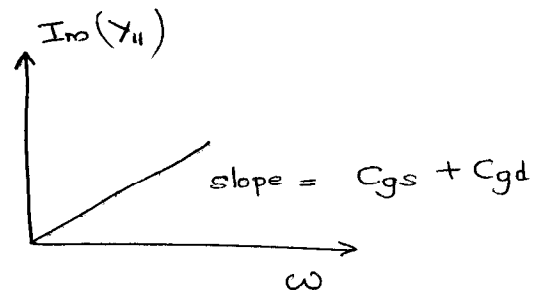
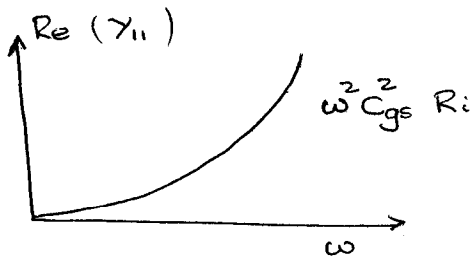


$$I_2 = g_m V_{gs} - j\omega C_{gd} (V_1 - V_2)$$


$$= g_m \frac{V_1}{1 + j\omega C_{gs} R_i} - j\omega C_{gd} (V_1 - V_2) \quad \text{since } V_{gs} = \frac{V_1}{1 + j\omega C_{gs} R_i}$$

$$= V_1 \left(\frac{g_m (1 - j\omega C_{gs} R_i)}{1 + \omega^2 C_{gs}^2 R_i^2} - j\omega C_{gd} \right) + j\omega C_{gd} \cdot V_2$$
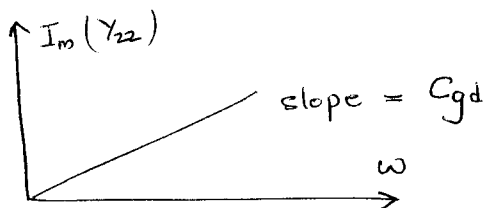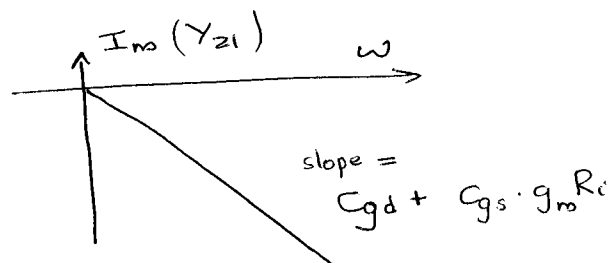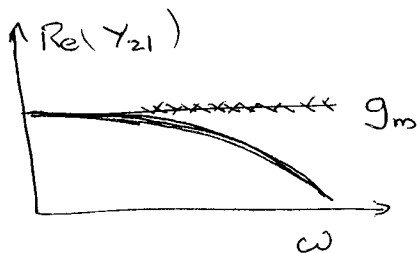
$$\approx V_1 \underbrace{\left[\frac{g_m (1 - \omega^2 C_{gs}^2 R_i^2)}{1 + \omega^2 C_{gs}^2 R_i^2} - j\omega (C_{gs} R_i g_m + C_{gd}) \right]}_{Y_{21}} + V_2 \underbrace{j\omega C_{gd}}_{Y_{22}}$$



b.

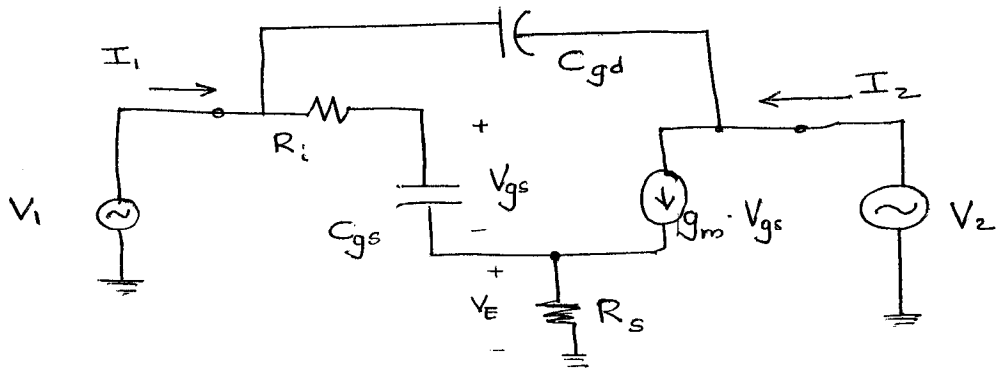

$$I_1 = (V_1 - V_2) j\omega C_{gd} + V_{gs} j\omega C_{gs}$$

$$V_E = [V_{gs} \cdot j\omega C_{gs} + g_m \cdot V_{gs}] \cdot R_s$$

$$\begin{aligned} V_1 &= V_{gs} (g_m R_s + j\omega C_{gs} R_s) + V_{gs} + V_{gs} \cdot j\omega C_{gs} \cdot R_i \\ &= V_{gs} [(1 + g_m R_s) + j\omega C_{gs} (R_s + R_i)] \end{aligned}$$




$$\begin{aligned} \therefore I_1 &= (V_1 - V_2) j\omega C_{gd} + \frac{V_1 \cdot j\omega C_{gs}}{(1 + g_m R_s) + j\omega C_{gs} (R_s + R_i)} \\ &= (V_1 - V_2) j\omega C_{gd} + \frac{V_1 \cdot j\omega C_{gs} [(1 + g_m R_s) - j\omega C_{gs} (R_s + R_i)]}{(1 + g_m R_s)^2 + \omega^2 C_{gs}^2 (R_s + R_i)^2} \end{aligned}$$

$$\text{Assume } \omega^2 C_{gs}^2 (R_s + R_i)^2 \ll 1$$

$$\begin{aligned} \Rightarrow I_1 &= V_1 \left[\frac{\omega^2 C_{gs}^2 (R_s + R_i)}{(1 + g_m R_s)^2} + j \left[\frac{\omega C_{gs}}{1 + g_m R_s} + \omega C_{gd} \right] \right] + \\ &\quad + V_2 (-j\omega C_{gd}) \end{aligned}$$

$\hookrightarrow Y_{11}$
 $\hookrightarrow Y_{12}$




(4)

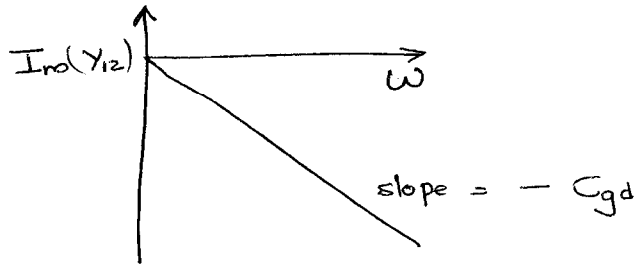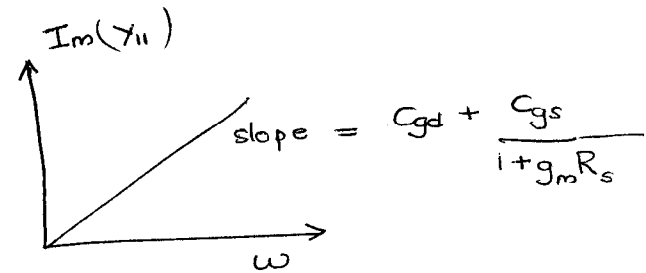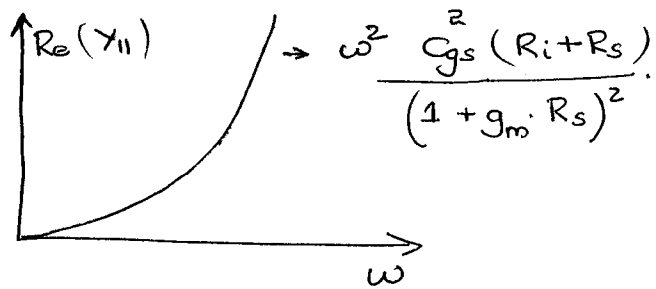

$$I_2 = (V_2 - V_1) j\omega C_{gd} + g_m V_{gs}$$


$$= (V_2 - V_1) \cdot j\omega C_{gd} + g_m V_1 \left[\frac{(1 + g_m R_s) - j\omega C_{gs} (R_i + R_s)}{(1 + g_m R_s)^2 + \omega^2 C_{gs}^2 (R_i + R_s)^2} \right]$$
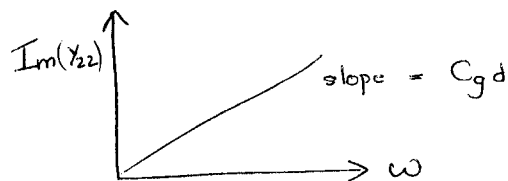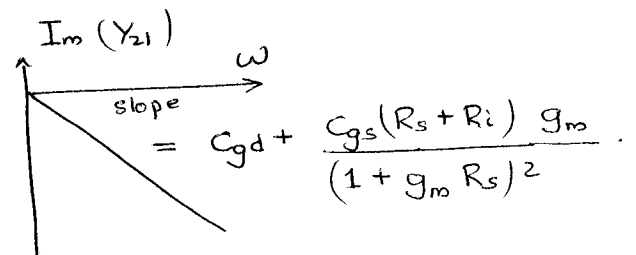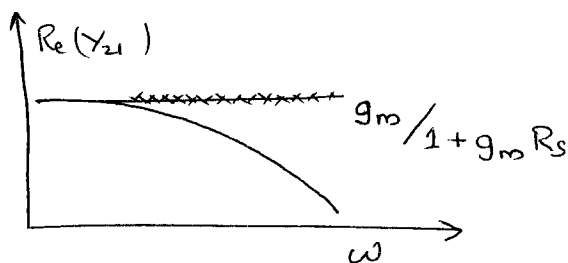
$$= V_1 \left[\underbrace{\frac{g_m}{1 + g_m R_s}}_{\text{Re}(Y_{21})} - j\omega \underbrace{\left[\frac{C_{gs} (R_i + R_s) g_m}{(1 + g_m R_s)^2} + C_{gd} \right]}_{\text{Im}(Y_{21})} \right] + \underbrace{V_2 \cdot j\omega C_{gd}}_{\text{Im}(Y_{22})}$$



(5)

2.

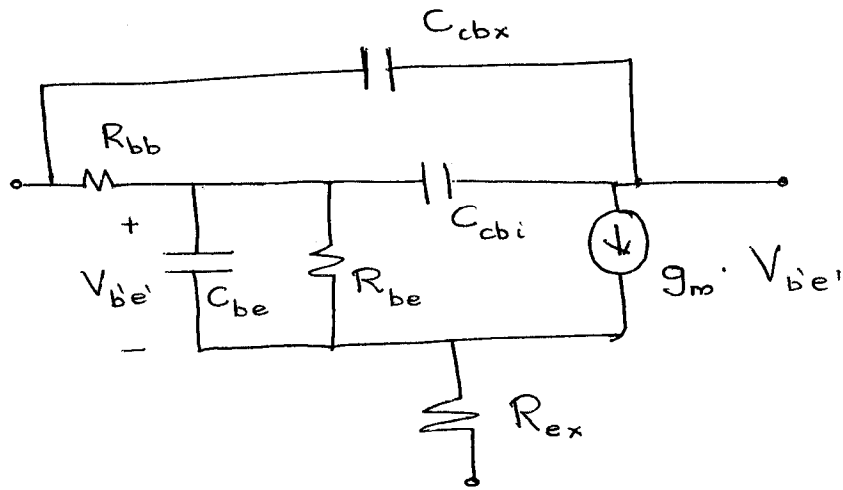

$$I_c = 3 \text{ mA} / 2$$

$$g_m = \frac{I_c}{V_t} = \frac{3 \text{ mA} / 2}{26 \text{ mV}} = 57 \text{ mS}$$

$$\tau_f = 0.44 \text{ ps}, \quad C_{be, \text{depl}} = 17 \text{ fF}$$

$$\therefore C_{be} = g_m \cdot \tau_f + C_{be, \text{depl}} = 57 \times 10^{-3} \times 0.44 \times 10^{-12} + 17 \times 10^{-15} = \underline{\underline{42 \text{ fF}}}$$


$$R_{bb} = 30 \Omega$$

$$R_{be} = \frac{\beta + 1}{g_m} \approx \infty \quad \text{as } \beta \rightarrow \infty$$

$$C_{cbi} \approx 0 \rightarrow C_{cb} = 4.3 \text{ fF}$$


$$R_{ex} = 6.67 \Omega \approx 0$$

$\therefore$ Simplified model

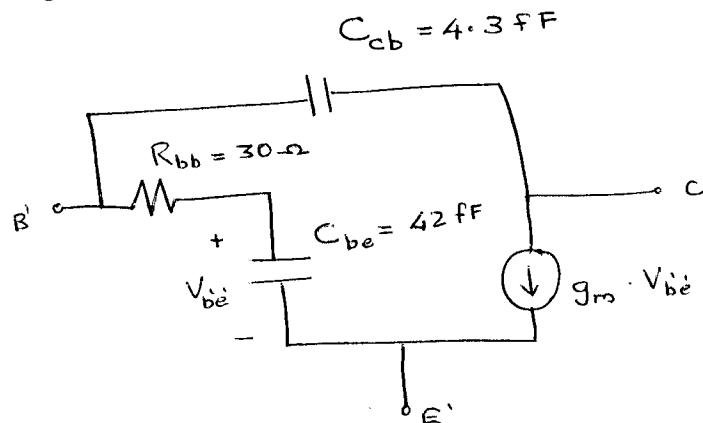


(6)

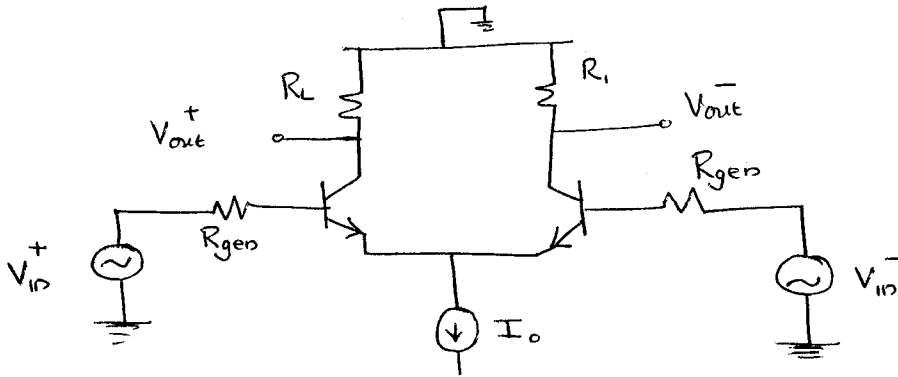A) $I_o = 3 \text{ mA}$, $I_o \cdot R_L = 300 \text{ mV} \Rightarrow R_L = 100 \Omega$.
 $R_{\text{gen}} = R_L = 100 \Omega$.



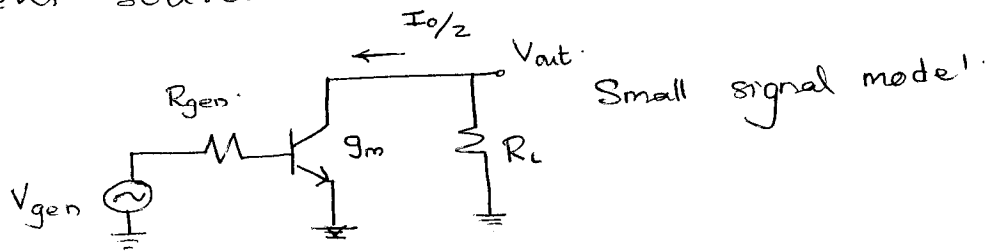Using symmetry split into half circuit.
 The emitter node is at virtual ground assuming ideal current source.



$$g_m = \frac{I_c/2}{V_T} = 57 \text{ mS}.$$

Assuming $\beta \rightarrow \infty$, $Z_{in} \rightarrow \infty \therefore V_{be} \approx V_{in}$

$$V_{out} = g_m V_{be} R_L \Rightarrow \frac{V_{out}}{V_{in}} = A_v = g_m R_L = 57 \times 10^{-3} \times 100 = \underline{\underline{5.7}}$$

Under limiting conditions, full current I_o flows through one transistor.

$$\Rightarrow V_{out} = I_o \cdot R_L = \underline{\underline{-300 \text{ mV}}}.$$

$$\tilde{g}_m = \frac{I_o}{V_T} = 0.12$$


$$V_{in} = \frac{V_{out}}{\tilde{g}_m R_L} \approx 25 \text{ mV}$$

We need differential voltage of 50 mV
 for full switching.

High frequency analysis using MOTC. ⑦

$$\frac{V_o}{V_{gen}} = (A_{V_{midband}}) \cdot \frac{(1 + s \tau_{zero})}{(1 + a_1 \cdot s + a_2 s^2)}$$

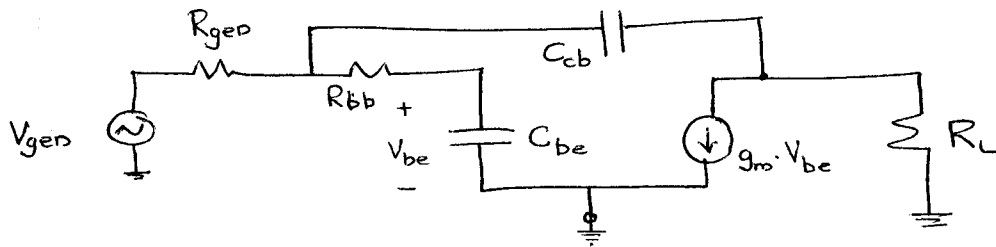Using symmetry we will get half circuit as.



$$\tau_{zero} = -\frac{C_{cb}}{g_m} \approx -74 \cdot f_s$$

$$a_1 = R_{11}^o C_1 + R_{22}^o C_2$$

$$C_1 = C_{be} \Rightarrow R_{11}^o = R_{bb} + R_{gen} = 130 \Omega$$

$$C_2 = C_{cb} \Rightarrow R_{22}^o = R_{gen} (1 + g_m R_L) + R_L = 100 (1 + 5.7) + 100 = 770 \Omega$$

$$\therefore a_1 = (130 \Omega) \cdot (42 \text{ fF}) + (770 \Omega) \cdot (4.3 \text{ fF})$$

$$= \underline{8.9 \text{ ps}}$$

$$a_2 = R_{11}^o C_1 C_2 R_{22}^{\prime} ; R_{22}^{\prime} = (R_{bb} \parallel R_{gen}) (1 - A_v) + R_L \quad \begin{matrix} \nearrow \\ 0 \text{ since } V_{be} = 0 \end{matrix}$$

$$= (30 \parallel 100) \cdot (1 - 0) + 100 = \underline{123 \Omega}$$

$$\therefore a_2 = (130 \Omega) \cdot (42 \text{ fF}) \cdot (4.3 \text{ fF}) \cdot (123 \Omega)$$

$$= 2.9 \times 10^{-24} \cdot \text{sec}^2$$

$$\text{Since } a_2 \ll a_1 \quad f_{3\text{dB}} \approx \frac{1}{2\pi a_1} = \underline{18 \text{ GHz}}$$

$$A(s) = \frac{-5.7 [1 - (74 \times 10^{-15}) s]}{1 + (8.9 \times 10^{-12}) \cdot s + (2.9 \times 10^{-24}) \cdot s^2}$$

b). The given circuit is a differential amplifier which we discussed earlier preceded by an emitter follower [Voltage follower].

$$V_{in} = \frac{V_{gen}}{2} \quad \text{as } R_{gen} = R_{bias}.$$

$$A_{V \text{ emitter follower}} \approx 1 \quad (\text{Assuming infinite } \beta).$$

$$A_{V \text{ diff. amp}} \approx -g_m \cdot R_L = -\frac{I_{cs}}{2V_T} \cdot R_L$$

$$\therefore V_{out} = -V_{in} \cdot A_{V \text{ EF}} \cdot A_{\text{diff amp}} = -\frac{V_{gen}}{2} \cdot 1 \cdot \frac{I_{cs}}{2V_T} \cdot R_L$$

$$\therefore A_V = -\frac{I_{cs} \cdot R_L}{4V_T}$$

Assuming the values used in (a) part

$$A_V = \underline{\underline{-2.85}}$$