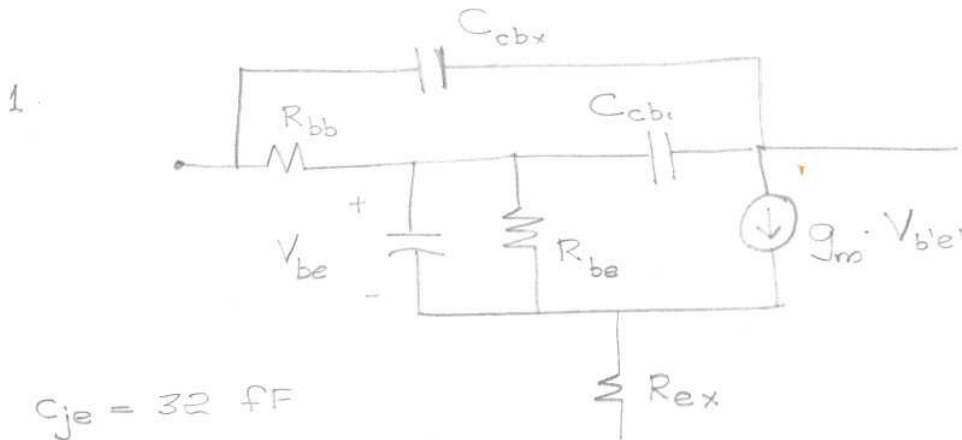


ECE 145C / 218C

HW 4 Solutions



$$C_{je} = 32 \text{ fF}$$

$$\beta = 50$$

$$C_{cbi} = 2.2 \text{ fF}$$

$$C_{cbx} = 6.0 \text{ fF}$$

$$R_{bb} = 38 \Omega$$

$$R_{ex} = 2.8 \Omega$$

$$\tau = 0.28 \text{ ps}$$

$$A_e = 0.6 \times 4.3 = 2.58 \mu\text{m}^2$$

$$V_{ce} = 0.7 \text{ V}$$

$$C_{be} = C_{je} + g_m \tau_f = 14.88 \text{ fF} + (0.1846) \frac{0.28 \text{ ps}}{1} = 66.5 \text{ fF}$$

$$I_c = 4 \text{ mA} / \mu\text{m}^2 \times 1.2 \mu\text{m}^2 = 4.8 \text{ mA}$$

$$R_{be} = \frac{\beta}{g_m} = 270.8 \Omega$$

$$I_c \cdot R_L = 300 \text{ mV} \Rightarrow R_L = \frac{300}{4.8} = 62.5 \Omega$$

$$g_m = \frac{I_c}{V_T} = \frac{4.8}{26} = 0.1846 \text{ S}$$

$$\Rightarrow r_e = \frac{1}{g_m} = 5.417 \Omega$$

$$R_{ee} = \frac{(4.2 - 1) \text{ V}}{4.8 \text{ mA}} = 666.7 \Omega \quad R_{cs} = \frac{1}{2} \frac{(4.2 - 1.7)}{4.8 \text{ mA}} = 260.4 \Omega$$

Assumptions:


$$C_{cbi} \approx 8.2 \text{ fF}, \quad C_{cbx} \approx 0 \text{ fF}$$

$$\text{Voltage rail} = 0 \text{ to } -4.2 \text{ V}$$


$$A_e^1 = 1.2 \mu\text{m}^2$$

$$\Rightarrow C_{je} = 32 \times \frac{1.2}{2.58} = 14.88 \text{ fF}$$
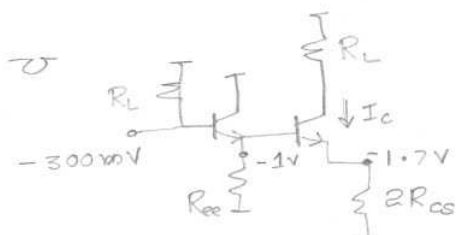
$$\text{Also } R_{ex} = 2.8 \times \frac{2.58}{1.2}$$



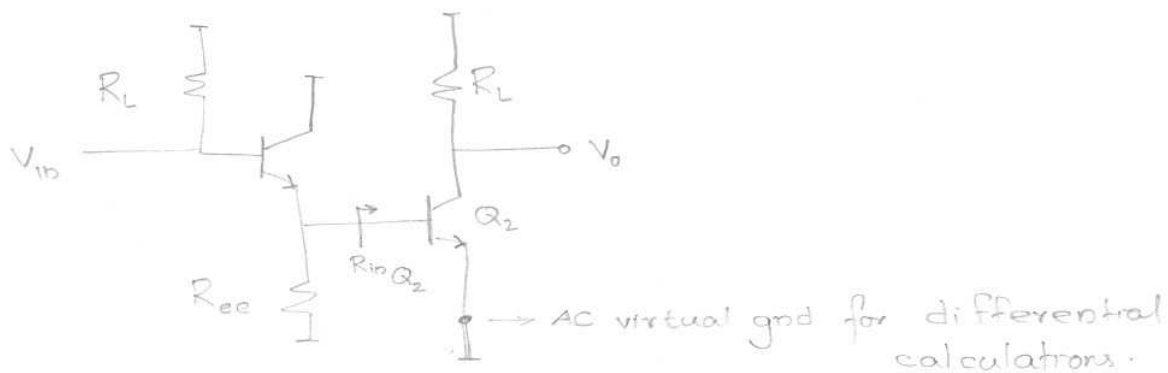a) For AC differential gain, assume half circuit



$$\begin{aligned}
 R_{in Q_2} &= R_{bb} + \beta (r_e + r_{ex}) \\
 &= 38 + 50 (5.4 + 6) \\
 &= 608 \Omega
 \end{aligned}$$


$$\begin{aligned}
 R_{in Q_2} &= R_{bb} + \beta (r_e + r_{ex} + R_{ee} \parallel R_{in Q_2}) \\
 &= 38 + 50 (5.4 + 6 + 666 \parallel 608) \\
 &= 16.5 \text{ k}\Omega
 \end{aligned}$$

$$A_{VMB Q_1} = \frac{R_{ee} \parallel R_{in Q_2}}{R_{ee} \parallel R_{in Q_2} + r_e + r_{ex}} = 0.9654$$

$$A_{VMB Q_2} = \frac{-R_L}{r_{ex} + r_e} = -5.474$$

$$A_{V_{Total}} = -5.285$$

b) High freq, analysis using MOTC.

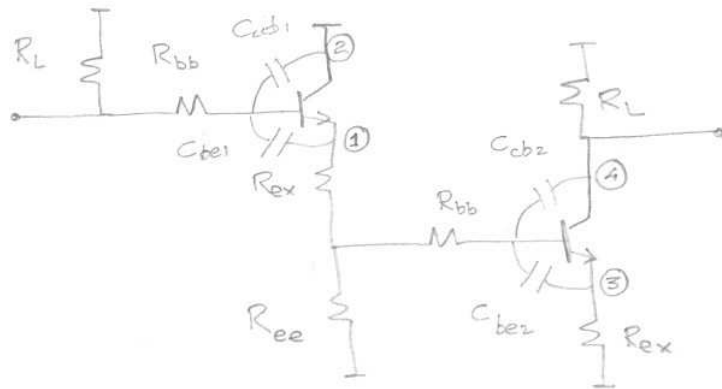

$$C_1 = C_{be1}$$

$$R_{11}^o = \left[(1 - A_{v1}) (R_{bb1} + R_L) + r_{e1} \parallel (R_{ex} + R_{EE} \parallel R_{in Q2}) \right] \parallel R_{BE1}$$

$$= \left[(1 - 0.965) (38 + 62.5) + 5.417 \parallel (6 + 666 \parallel 602) \right] \parallel 271$$

$$= \underline{8.5 \Omega}$$

$$C_2 = C_{cb1}$$

$$R_{22}^o = (R_{bb} + R_L) \parallel R_{in Q1}$$

$$= \underline{100 \Omega}$$

$$C_3 = C_{be2}, \quad R_{33}^o = \left[(1 - A_{2eff}) (R_{bb} + R_{EE} \parallel R_{out Q1}) + R_{ex2} \right] \parallel R_{be2}$$

$$A_{2eff} = \frac{R_{ex2}}{R_{ex2} + r_{e2}} = 0.5255$$

$$R_{out Q1} = R_{ex1} + r_{e1} + \frac{R_{bb} + R_L}{\beta} = 13.42$$

$$R_{33}^o = \underline{27.23 \Omega}$$

$$C_A = C_{b4}, R_{A4}^{\circ} = (1 - A_{v2}) (R_{ee} \parallel R_{in2} \parallel R_{out1}) + R_L$$

$$= \underline{139 \Omega}$$

$$R_{22}' = (R_{bb} + R_L) \parallel (R_{ex} + R_{EE} \parallel R_{inQ_2})$$

$$= 85 \Omega$$

$$R_{33}' = \beta r_e \parallel \left[(1 - A_{ef}) (R_{bb} + R_{EE} \parallel (R_{ex} + R_{bb1} + R_L)) + R_{ex2} \parallel r_{e2} \right]$$

$$= 52 \Omega$$

$$R_{44}^1 = (1 - A_{v2}) \left[R_{inQ_2} \parallel \left\{ R_{bb2} + R_{EE} \parallel (R_{ex} + R_{bb} + R_L) \right\} \right] + R_L$$

$$= 6.5 \times \left[608 \parallel \left\{ 38 + 666 \parallel (6 + 38 + 62.5) \right\} \right] + 62.5$$

$$= \underline{758 \Omega}$$

$$R_{33}^2 = \left[(1 - A_{v2/2}) (R_{bb} + R_{EE} \parallel (R_{ex} + r_e)) + (R_{ex} + r_e) \right] \parallel \beta r_e$$

$$= \underline{22.8 \Omega}$$

$$R_{44}^2 = (1 - A_{v2}) \left[\beta (r_e + r_{ex}) \parallel \left\{ R_{bb} + R_{EE} \parallel (R_{ex} + r_e) \right\} \right] + R_L$$

$$= 350 \Omega$$

$$R_{44}^3 = R_{ex2} \parallel \left[R_{bb} + \left(R_{EE} \parallel R_{ex} + r_e + \frac{R_{bb} + R_L}{\beta} \right) \right] + R_L$$

$$= 70$$

$$a_1 = R_{11}^0 C_1 + R_{22}^0 C_2 + R_{33}^0 C_3 + R_{44}^0 C_4$$

$$= (2.5 \Omega) 66.5 \text{ fF} + (100 \Omega) 8.2 \text{ fF} +$$

$$(27 \Omega) 66.5 \text{ fF} + (139 \Omega) 8.2 \text{ fF}$$

$$= 4 \text{ ps.}$$

$$a_2 = R_{11}^0 C_1 C_2 R_{22}^1 + R_{11}^0 C_1 C_3 R_{33}^1 + R_{11}^0 C_1 C_4 R_{44}^1$$

$$+ R_{22}^0 C_2 C_3 R_{33}^2 + R_{22}^0 C_2 C_4 R_{44}^2 + R_{33}^0 C_3 C_4 R_{44}^3$$

$$= (8.5 \times 66.5 \text{ fF} \times 8.2 \text{ f} \times 25) + (8.5 \times 66.5 \text{ f} \times 66.5 \text{ f} \times 52)$$

$$+ (8.5 \times 66.5 \text{ f} \times 8.2 \text{ f} \times 258) + (100 \times 8.2 \text{ f} \times 66.5 \text{ f} \times 23)$$


$$+ (100 \times 8.2 \text{ f} \times 8.2 \text{ f} \times 350) + (27 \times 66.5 \text{ f} \times 8.2 \text{ f} \times 70)$$

$$= 9 \times 10^{-24} \text{ sec}^2$$

$$\omega_n = \frac{1}{\sqrt{a_2}} = \frac{3.3 \times 10^{11} \text{ rad/s}}{\quad} \quad f_n = \frac{\omega_n}{2\pi}$$

$$\xi = \frac{a_1}{2\sqrt{a_2}} = \underline{0.68}$$

2.

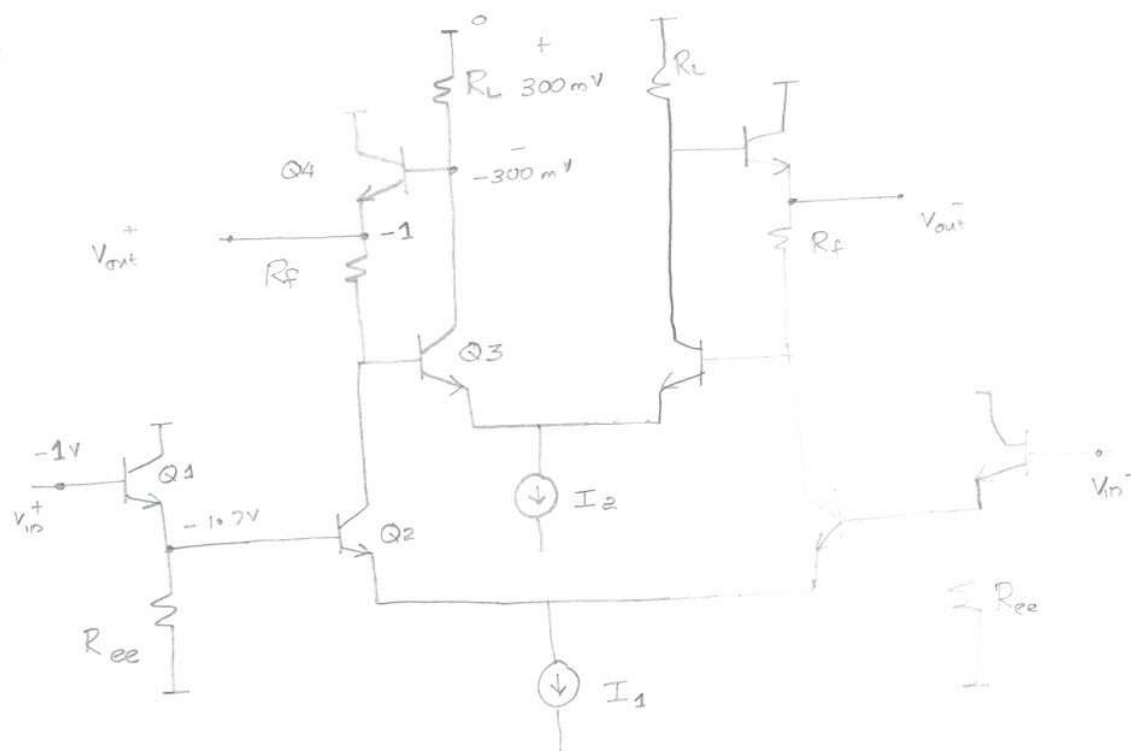

$$V_{ee} = -5.2V$$


$$A_c = 1.2 \mu m^2, I_{den} = 4 mA/\mu m^2, I_c = 4.8 mA$$

$$I_c \cdot R_L = 300 \Rightarrow R_L = \frac{300 mV}{4.8 mA} = 62.5 \Omega$$

$$R_{ee} = \frac{(5.2 - 1.7)V}{4.8 mA} = 729 \Omega$$

Q_1, Q_2 have no parasitic capacitances & have $\beta \rightarrow \infty$.
 Q_3, Q_4 has same parameter values as calculated in problem #1.


Eq. half circuit

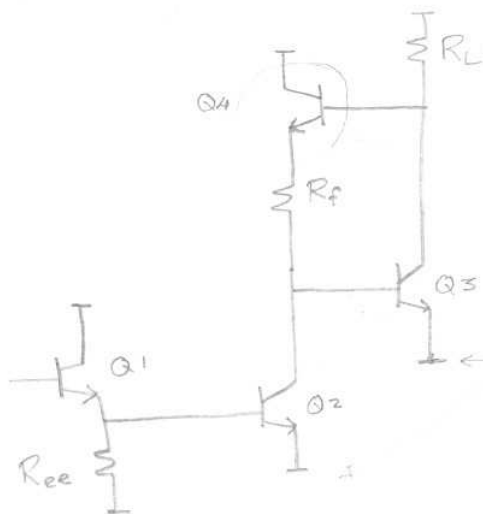

Let's assume to be ideal voltage follower

Virtual gnd for AC diff calc.

L

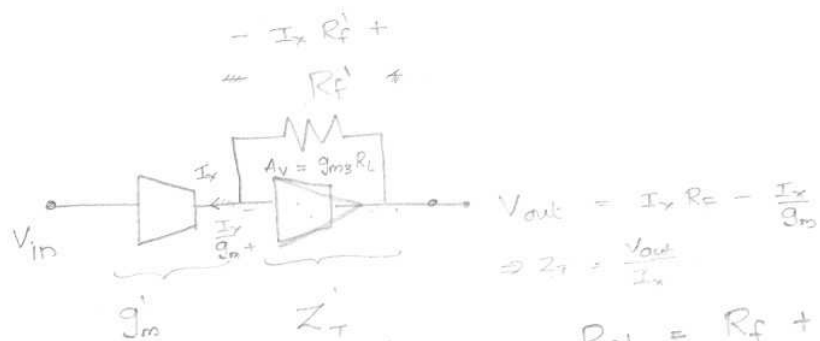

$$R_{f'} = R_f + R_{ex4}$$

$$g_m' = \frac{g_{m2}}{1 + g_{m2} R_{ex}} \quad , \quad Z_T = R_f \cdot \left(1 - \frac{1}{A_v}\right)$$

(since $\beta_1, \beta_2 \gg \infty$)

$$= R_f \left(1 - \frac{1}{g_{m2} R_L}\right)$$

$$\therefore \text{Total gain } A_v = g_m' \cdot Z_T$$

$$= \frac{g_{m2}}{1 + g_{m2} R_{ex}} \cdot \left(R_f \left(1 - \frac{1}{g_{m2} R_L}\right) \right) \quad \times$$


$$\text{Assuming } I_1 = I_2 \Rightarrow g_{m2} = g_{m3} = g_m$$

$$\text{So for } A_v = 3 \quad (\text{stage voltage gain})$$

$$\frac{0.1846}{1 + (0.1846 \times 6)} \cdot \left(R_f - \frac{R_f}{R_L \cdot 0.1846} \right) = 3$$


$$\Rightarrow R_f = R_{f'} - R_{ex} = 33.7 \, \Omega \Rightarrow R_{f'} = 39.7 \, \Omega$$

High Freq Analysis.

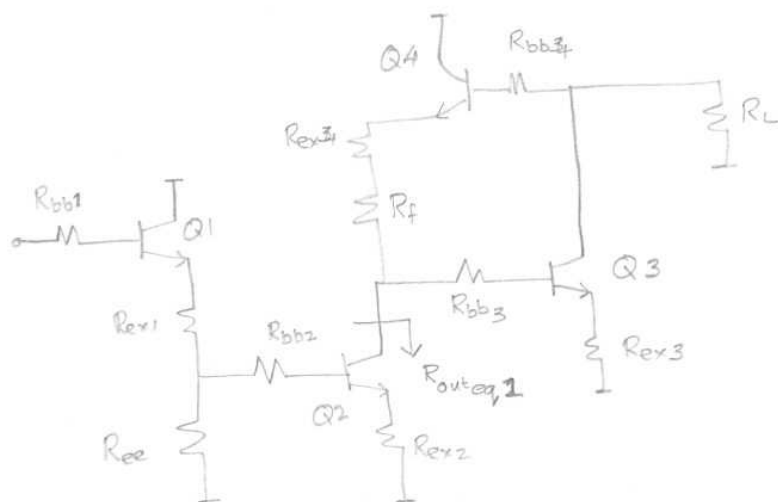

Assuming $\beta \rightarrow \infty$ for $Q1$ & $Q2$, $R_{outeq1} \rightarrow \infty$

So we can reduce the eq. ckt to

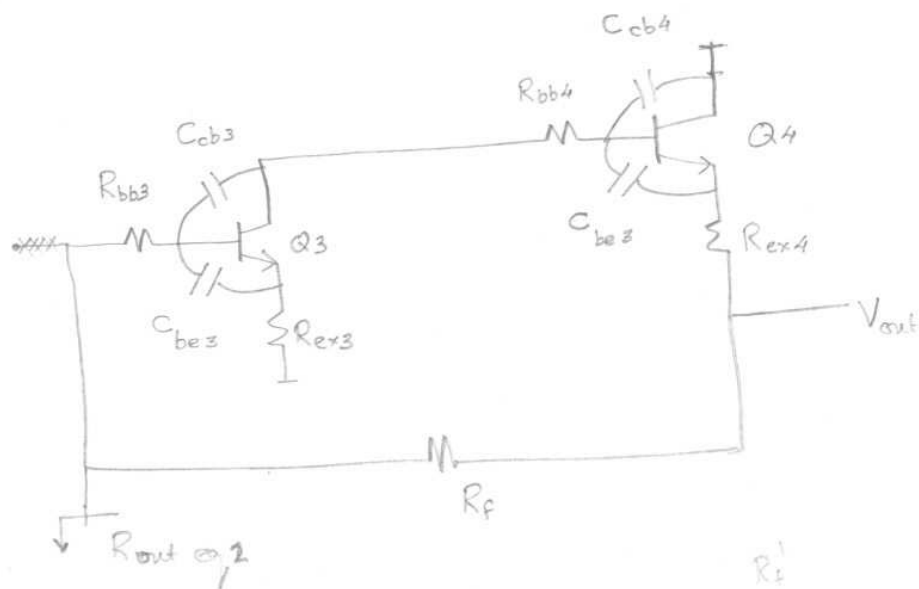

$$A_{v_{LS}} = \frac{R_{ex}}{R_{ex} + \frac{1}{g_m}} \approx 0.52$$


$$C_1 = C_{be3} ; R_{11}^0 = (R_{bb} + R_F + R_{ex4} + r_{e4})(1 - A_{v3}) + R_{ex3}$$

$$= (38 + 40 + 5.42)(1 - 0.522) + 6$$

$$= 46 \Omega$$


$$C_2 = C_{cb3}$$

$$R_{22}^{\circ}$$

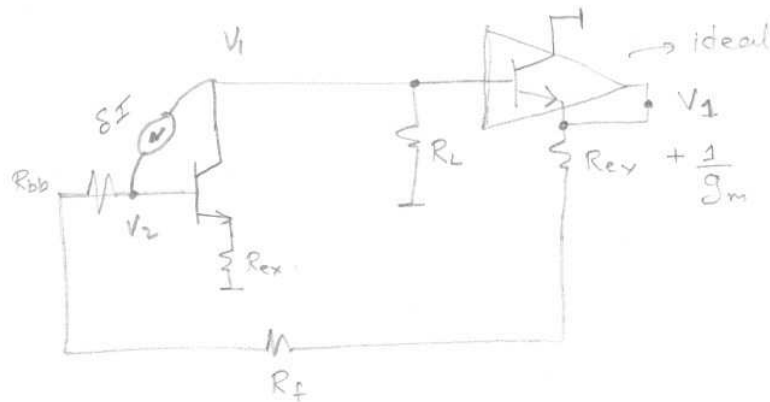

$$\frac{V_2 - V_1}{8I} = R_{bb} + R_f + R_{ex} + \frac{1}{g_m} = R_{22} = 84 \Omega$$

$$C_3 = C_{be4}$$

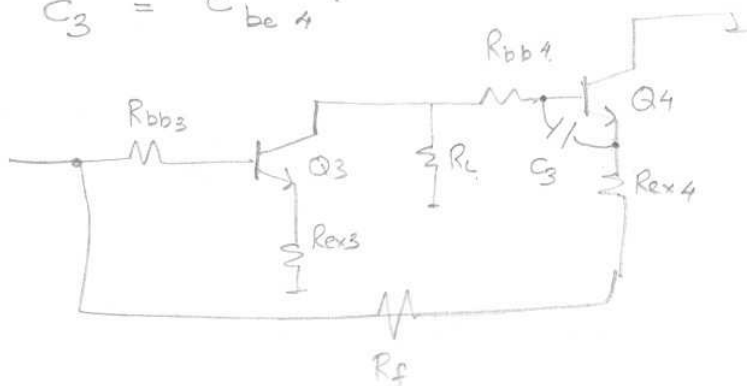

Let's assume Q_4 to be ideal voltage follower

$$A_{vQ4} \approx 1$$

$$R_{33}^{\circ} \approx \left[(1 - A_{vQ4}) (R_{bb4} + R_L) + R_{ex4} + \beta (r_{e3} + R_{ex3}) + R_f + R_{bb3} \right] \parallel \frac{1}{g_{m4}}$$


$$\approx 5 \Omega$$

$$C_4 = C_{cb4}, R_{44}^{\circ} = R_{bb4} + R_L = 100 \Omega$$

$$a_1 = (66.5 \text{ f}) \left[(45.87 + 105) \right] + (8.2 \text{ f}) \left(\frac{5}{530 + 83.5} \right)$$

$$\approx \underline{14 \text{ ps}}$$


$$R_{22}^1$$

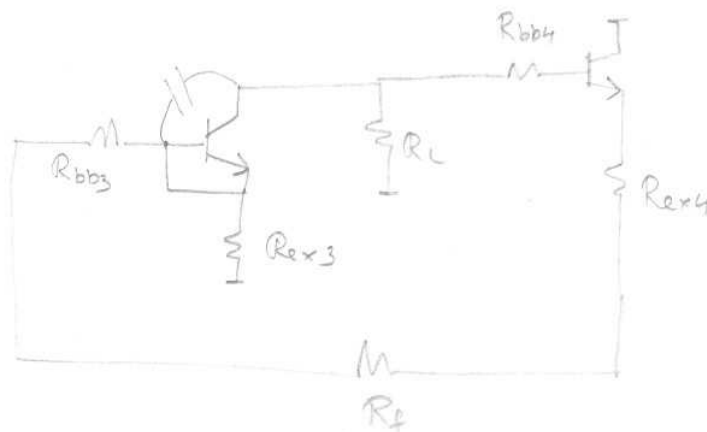

$$R_{22}^1 = R_{ex3} \parallel \left(R_{bb3} + R_f + R_{ex4} + \frac{1}{g_{m4}} \right) + R_L$$

$$\approx 70 \Omega$$


$$R_{33}^1$$

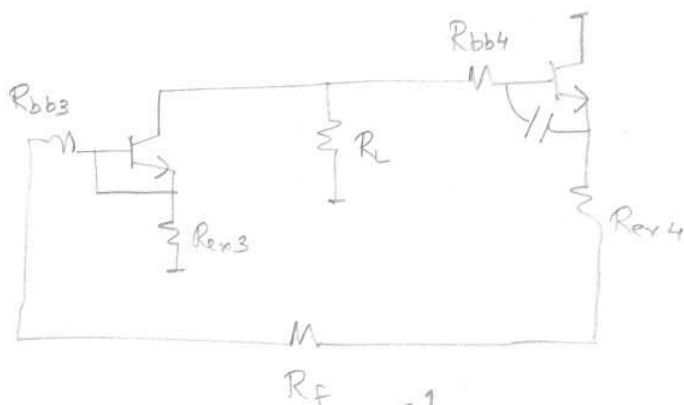


$$R_{33}^1 = \left[(R_L + R_{bb4}) (1 - A_v) \right] + (R_{ex4} + R_f + R_{bb3} + R_{ex3}) \parallel \frac{1}{g_{m4}}$$

$$\approx \frac{1}{g_m} = \underline{5.4}$$
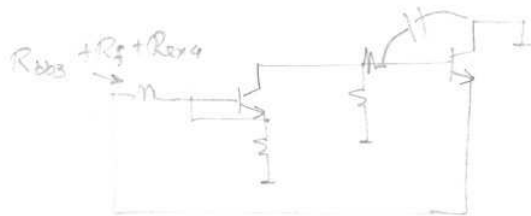
$$R_{44}^1 = R_{bb4} + R_L = 100 \cdot \Omega$$



$$R_{22}^3 \quad \#$$

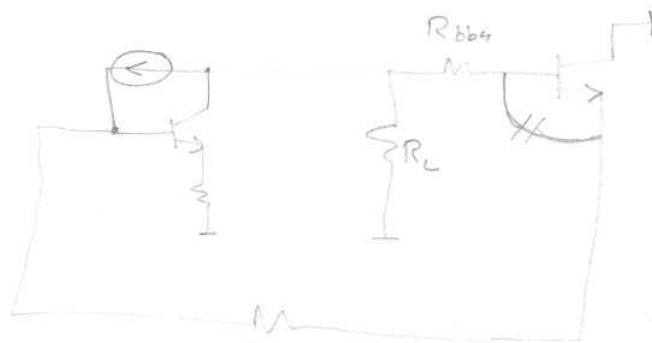

$$R_{feed} = R_{bb3} + R_{ex4} + R_f$$


$$R_{22}^3 = (R_{bb4} + R_{feed}) \parallel \left[\beta (r_{e3} + r_{ex3}) + R_L \right]$$

$$= 120 \parallel (50 \times 11 + 62.5)$$


$$= 120 \parallel 612.5$$

$$\approx 110 \cdot \Omega$$

$$R_{44}^2$$

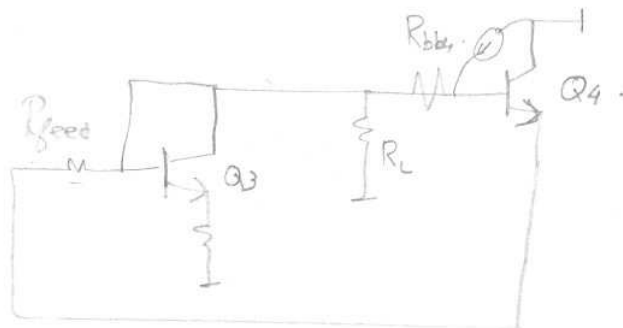
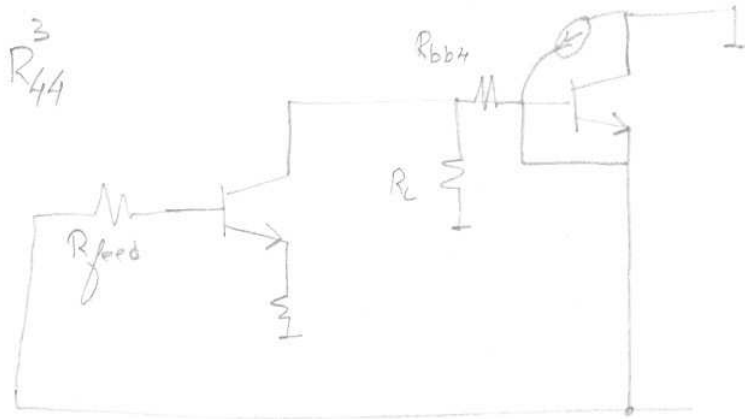
$$R_{44}^2 = R_{bb4} + R_L \parallel \left(R_{feed} + \frac{1}{g_{m3}} \right) = 74 \cdot \Omega$$



$$R_{44}^3 \approx R_L + R_{bb4} = 100 \Omega.$$


$$\begin{aligned} a_2 &= R_{11}^0 C_1 C_2 R_{22}^1 + R_{11}^0 C_1 C_3 R_{33}^1 \\ &\quad R_{11}^0 C_1 C_4 R_{44}^1 + R_{33}^0 C_2 C_3 R_{22}^3 \\ &\quad R_{22}^0 C_2 C_4 R_{44}^2 + R_{33}^0 C_3 C_4 R_{44}^3 \\ &= 21 \times 10^{-24} \text{ sec}^2 \end{aligned}$$

$$\omega_D = \frac{1}{\sqrt{a_2}} \approx 235 \times 10^9 \text{ rad/sec} \rightarrow \frac{f_D}{2} = \frac{60}{2\pi}$$


$$f_D = \frac{\omega_D}{2\pi}$$

$$\xi = \frac{a_1}{2\sqrt{a_2}} \approx 1.3$$

4

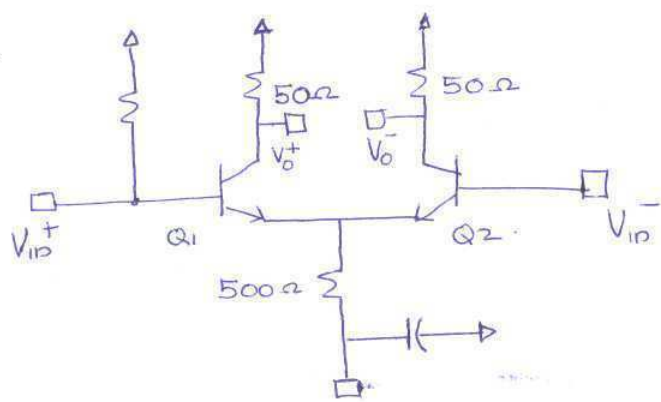

For ease of layout let's redraw it as

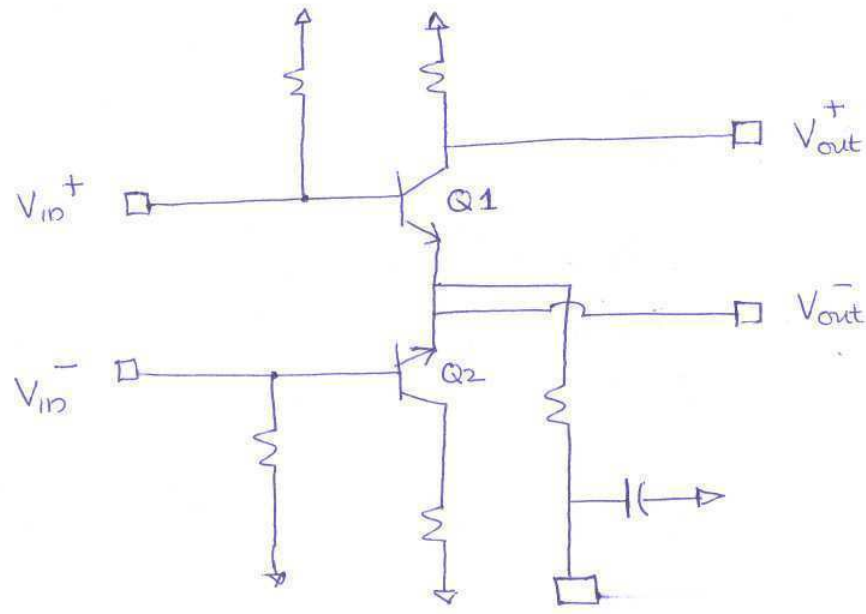

The mask is given in next page:

Concerns:

1. Make sure that all the nodes are well connected.
2. Design the signal carrying interconnect to be 50Ω using LINCALC.
3. Pads with M1-M3 contact is used for signal input & output as well as power.
4. Top metal layer (M3) acts as continuous ground plane.
5. Size the R ~~to~~ assuming $R_{\text{sheet}} = 50\Omega/\square$.
6. C is made using M1-M2 layers.
7. Resistors are grounded on one side by contact to M3.
8. All signal carrying lines (both half circuits) should be symmetric. ~~(same)~~

