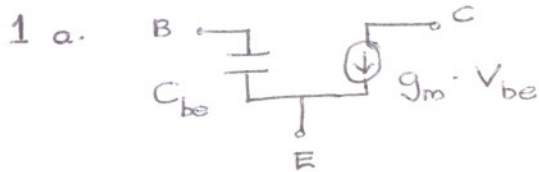



ECE 145C / 218C

HW 3 Solution set *



$$g_m = \frac{q \cdot I_c}{kT} = \underline{0.3846 \text{ S}}$$
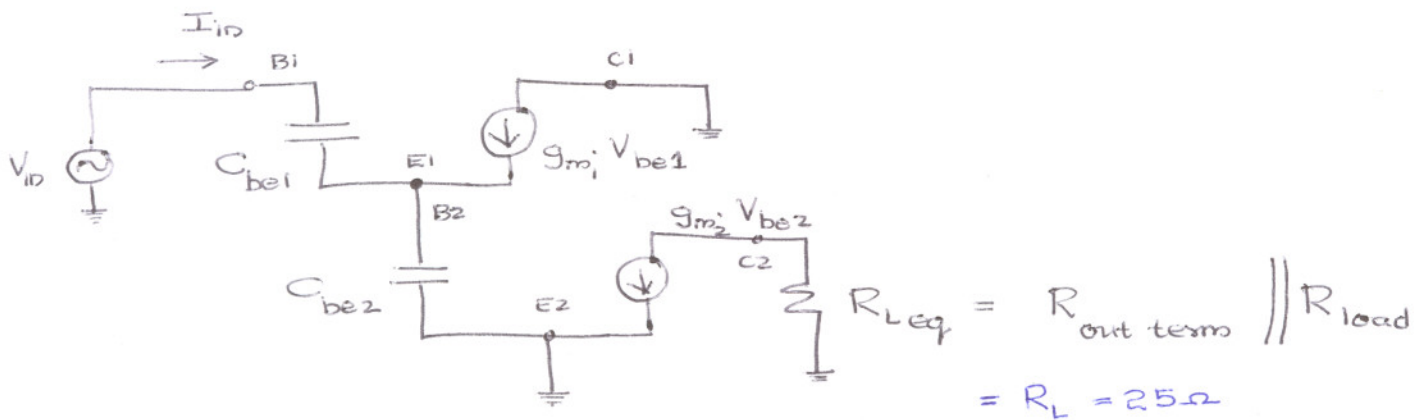
$$\tau_f = 0.32 \text{ ps}; \quad C_{be} = g_m \cdot \tau_f = \underline{0.123 \text{ pF}}$$



$$I_{in} = (V_{in} - V_{be2}) \cdot j\omega C_{be1} \Rightarrow I_{in} + V_{be2} \cdot j\omega C_{be1} =$$

$$V_{be2} = \frac{I_{in} + \frac{I_{in}}{j\omega C_{be1}} \cdot g_{m1}}{j\omega C_{be2}} \cdot V_{in} \cdot j\omega C_{be1}$$

$$I_{in} + \left[I_{in} + \frac{I_{in} \cdot g_{m1}}{j\omega C_{be1}} \right] \frac{C_{be1}}{C_{be2}} = V_{in} \cdot j\omega C_{be1}$$

$$I_{in} \left\{ 1 + \frac{(g_{m1} + j\omega C_{be1})}{j\omega C_{be1}} \cdot \frac{C_{be1}}{C_{be2}} \right\} = V_{in} \cdot j\omega C_{be1}$$

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{-g_{m1}}{\omega^2 C_{be1} C_{be2}} - j \frac{(C_{be1} + C_{be2})}{\omega C_{be1} C_{be2}}$$


Assuming $C_{be1} = C_{be2} = C_{be}$

$g_{m1} = g_m$

$$Z_{in} = \frac{-g_m}{\omega^2 C_{be}^2} - j \frac{2}{\omega C_{be}} \quad \Omega$$

$$\approx -\frac{1}{g_m} \left(\frac{\omega_T}{\omega} \right)^2 - j \frac{2}{g_m} \left(\frac{\omega_T}{\omega} \right) \quad \Omega$$
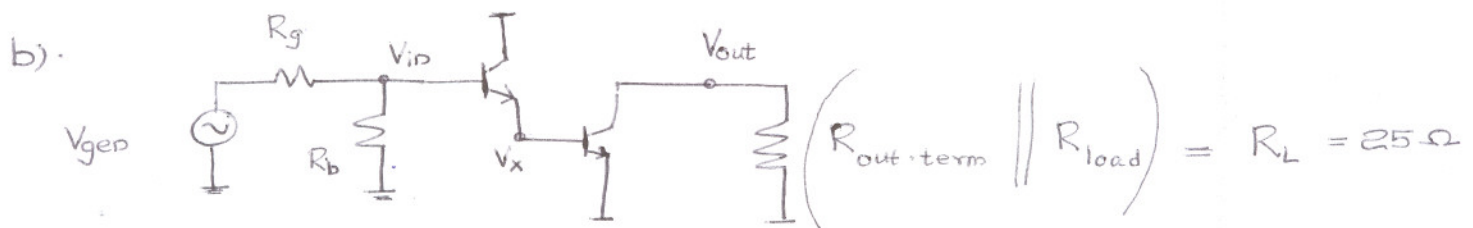
$$S_{11} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$




$$V_{in} = V_{gen} \cdot \frac{R_b}{R_g + R_b} = \frac{V_{gen}}{2}$$

$$V_x = V_{in} \cdot \frac{R_{Leq}}{R_{Leq} + r_e} \approx V_{in}$$

$$V_{out} = -V_x \cdot g_m \cdot R_L$$
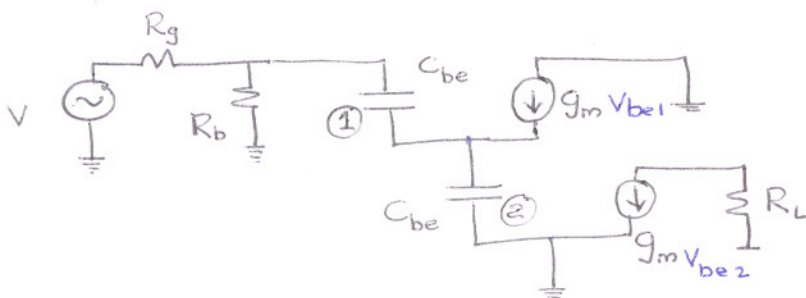
$$\therefore S_{21} = 2 \frac{V_{out}}{V_{gen}} = -g_m \cdot R_L = -9.615$$



$$R_{11}^o = (1 - A_v) (R_g \parallel R_b) + \frac{1}{g_m} \approx 0 \times 25 + 2.6 = 2.6 \quad \Omega$$

$$R_{22}^o = \frac{1}{g_m} = 2.6 \quad \Omega$$

$$a_1 = R_{11}^0 C_1 + R_{22}^0 C_2$$

$$= (21.6 + 2.6) \cdot 0.123 \text{ pF} = \frac{629 \times 10^{-15}}{3.715} \text{ ps}$$

$$R_{22}^1 = R_g \parallel R_b = 25 \Omega$$

$$a_2 = R_{11}^0 \cdot C_1 \cdot C_2 \cdot R_{22}^1 = (21.6) (0.123 \text{ p})^2 (25) = \frac{1.044 \times 10^{-23}}{9.51 \times 10^{-25}} \text{ s}^2$$

$$A(s) = \frac{A_{V \text{ MB}}}{1 + a_1 s + a_2 s^2} = \frac{A_{V \text{ MB}}}{1 + \frac{2\zeta}{\omega_n} s + \frac{s^2}{\omega_n^2}}$$

$$= \frac{-9.6}{1 + \left(\frac{0.629}{3.715 \times 10^{12}} \right) s + \left(\frac{9.51}{1.044 \times 10^{-25}} \right) s^2}$$

$$\therefore \omega_n = \frac{1.02}{3.095 \times 10^{12}} \text{ rad/sec} ; f_n = 162 \text{ GHz}$$

$$\zeta = 0.322$$

$$\text{Pole freq } \omega_d = \omega_n \sqrt{1 - \zeta^2} = \frac{965}{207} \times 10^9 \text{ rad/sec} \quad f_d = 153 \text{ GHz}$$

$$s_{p1,2} = -\zeta \omega_n \pm j \omega_d$$



$$1 + a_1 s + a_2 s^2 = 1 + \frac{2\zeta}{\omega_n} s + \frac{s^2}{\omega_n^2}$$


$$(s - s_{p1})(s - s_{p2}) \quad s_{p1,2} = -\zeta \omega_n \pm j \omega_d$$

draw the root loci


given $\zeta, \omega_n, \phi_d = \frac{\omega_d}{\omega_n}$

2 a)

SS circuit.

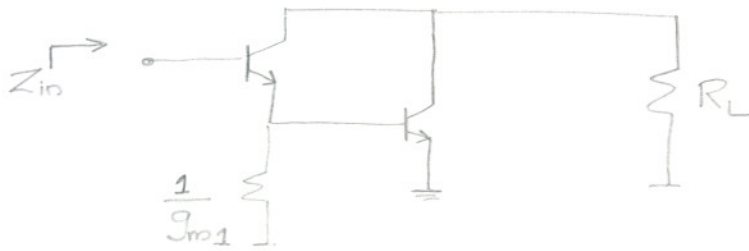

Neglecting $1/g_{m1}$ term R_i ,

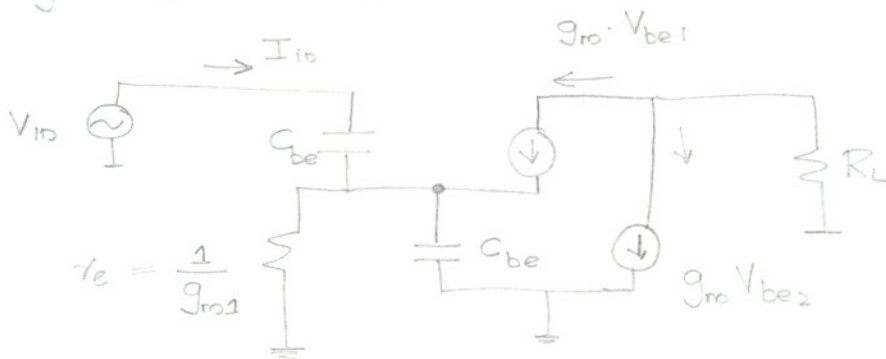

$$g_{m1} = g_{m2} = g_m$$

$$C_{be1} = C_{be2} = C_{be}$$

$$V_{be1} = \frac{I_{in}}{j\omega C_{be}}$$

$$V_{be2} = I_{in} + g_m \cdot V_{be1} = \left(I_{in} + \frac{g_m I_{in}}{j\omega C_{be}} \right) \frac{r_e}{r_e + \frac{1}{j\omega C_{be}}} \cdot \frac{1}{j\omega C_{be}}$$

$$= I_{in} \frac{(g_m + j\omega C_{be}) \cdot r_e}{(1 + j\omega C_{be} \cdot r_e) \cdot (j\omega C_{be})}$$

$$I_{in} = (V_{in} - V_{be2}) j\omega C_{be}$$

$$= \left[V_{in} - \frac{I_{in} (g_m + j\omega C_{be}) r_e}{(1 + j\omega C_{be} \cdot r_e) \cdot (j\omega C_{be})} \right] j\omega C_{be}$$


ERROR: invalid address
OFFENDING COMMAND: /del

$$V_{in} \cdot j\omega C_{be} = I_{in} \left[\frac{1 + (g_{m0} + j\omega C_{be}) r_e \cdot j\omega C_{be}}{(1 + j\omega C_{be} r_e)(j\omega C_{be})} \right]$$

$$\frac{V_{in}}{I_{in}} = Z_{in} = \frac{1 + j\omega C_{be} r_e + g_{m0} r_e + j\omega C_{be} r_e}{j^2 \omega^2 C_{be}^2 r_e + j\omega C_{be}}$$

$$= \frac{1 + (2 + 2j\omega C_{be} r_e)}{(j\omega C_{be} + \omega^2 C_{be}^2 r_e)} = \frac{1 + 2(1 + j\omega C_{be} r_e)}{j\omega C_{be} (1 + j\omega C_{be} r_e)}$$

$$= -\frac{2j}{\omega C_{be}}$$

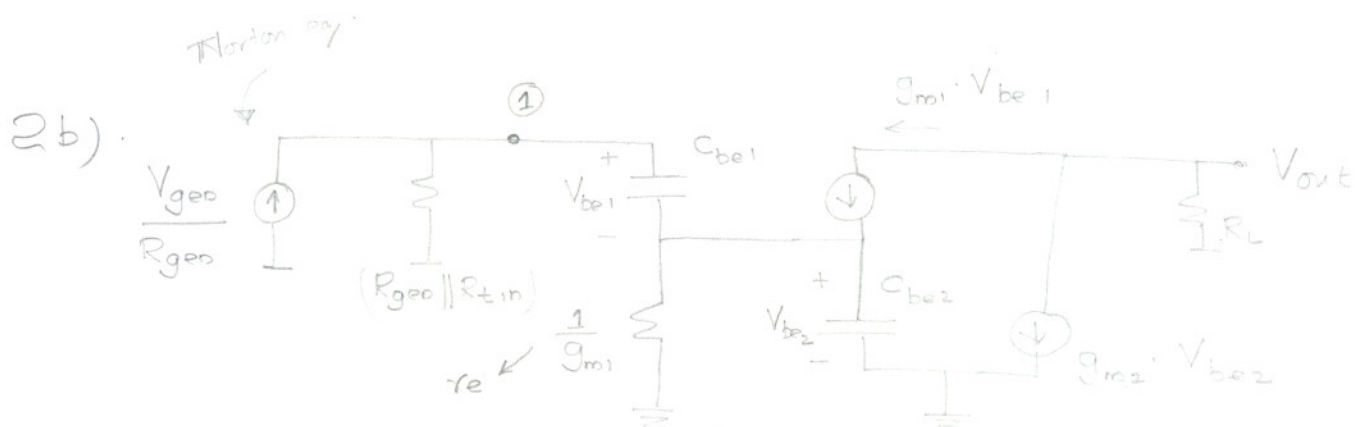

$$\frac{V_{gen}}{R_{gen}} = \frac{(V_{be1} + V_{be2})}{R_{gen} \parallel R_{tin}} + V_{be1} j\omega C_{be1}$$

Kirchoff current eq. @ ①

$$= \frac{(V_{be1} + V_{be2})}{R_g/2} + V_{be1} \cdot j\omega C_{be1} \quad (1)$$

$$(V_{be1} \cdot j\omega C_{be1} + g_{m0} \cdot V_{be1}) \frac{r_e}{r_e + \frac{1}{j\omega C_{be}}} \cdot \frac{1}{j\omega C_{be}} = V_{be2}$$

$$V_{be1} \frac{(g_m + j\omega C_{be}) r_e}{1 + j\omega C_{be} r_e} = V_{be2} = V_{be1}$$

$$V_{out} = (g_{m1} V_{be1} + g_{m2} V_{be2}) R_L$$

$$= g_m R_L (V_{be1} + V_{be2})$$

$$= g_m R_L \left[V_{be1} \right] \cdot 2$$

$$= g_m R_L V_{be1} \cdot 2$$

$$= g_m R_L V_{be1} \cdot 2$$


$$\frac{V_{gen}}{R_{gen}} = \frac{(V_{be1} + V_{be1})}{R_g / 2} + V_{be1} \cdot j\omega C_{be}$$

$$= V_{be1} \left(\frac{4}{R_g} + j\omega C_{be} \right)$$

$$\frac{V_{out}}{V_{gen}} = \frac{g_m R_L V_{be1} \cdot 2}{V_{be1} \cdot R_{gen} \left(4 + j\omega C_{be} \cdot R_{gen} \right)}$$

$$= \frac{-g_m R_L / 2}{\left[1 + j\omega C_{be} \frac{R_{gen}}{4} \right]}$$


3.

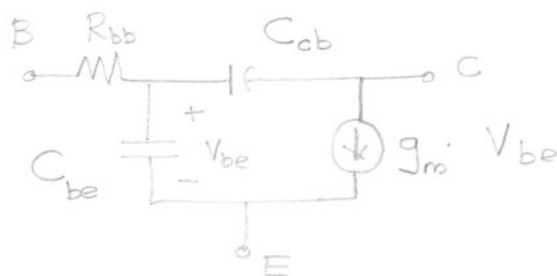

$$R_{bb} \approx \frac{10}{g_m} = 26 \Omega$$

$$C_{cb} \approx \frac{C_{be}}{40} = 0.1 C_{be}$$

$$V_{be} = 2.5 V$$

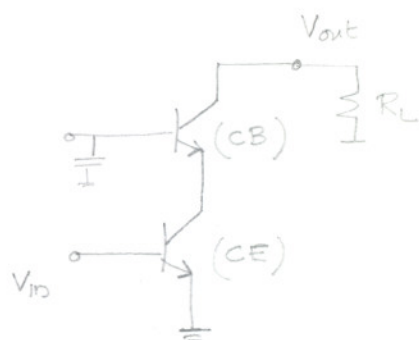

Gain of voltage divider = $\frac{1}{2}$


$$\text{Gain of CE stage} = g_{m1} \cdot \left(\frac{1}{g_{m2}} \right) \approx -1$$

$$\text{Gain of CB stage} = \frac{(R_L)_{-1}}{(1/g_{m2})} = g_m R_L$$

$$\therefore S_{21} = \frac{2 V_{out}}{V_{in}} = g_m R_L = -9.6$$

$$A_{V \text{ Mid band}} = -9.6$$

High freq Analysis

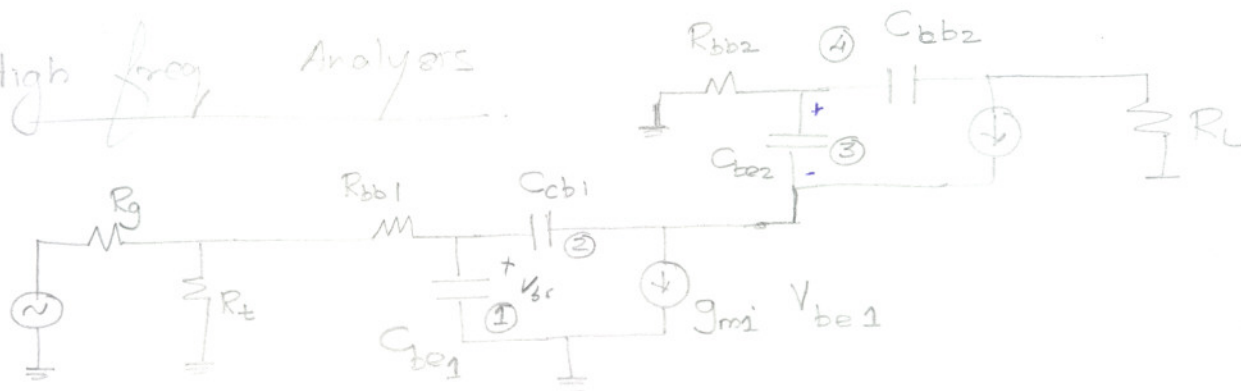

$$R_{bb1} = R_{bb2} = R_{bb}$$

$$C_{be1} = C_{be2} = C_{be}$$

$$C_{cb1} = C_{cb2} = C_{cb}$$

$$g_{m1} = g_{m2} = g_m$$

$$R_{11}^o = R_{bb} + R_g/2 = 26 + 25 = 51 \Omega$$

$$R_{22}^o = (R_{bb} + R_g/2)(1 - A_v) + \frac{1}{g_{m2}}$$

$$= 51 \times 2 + 2.6 = 104.6 \Omega$$

$$R_{23}^o = R_{bb2} + \frac{1}{g_{m2}} = 26 + 2.6 = 28.6 \Omega$$

$$R_{44}^0 = R_{bb} + R_L = 26 + 25 = 51 \Omega.$$

$$\begin{aligned} a_1 &= \sum_{i=1}^4 R_{ii}^0 C_i = (51 + 28.6) \times 0.123 \times 10^{-12} \\ &\quad + (104.6 + 51) \times \frac{0.123}{10} \times 10^{-11} \\ &= 1.17 \times 10^{-11} \text{ sec} \end{aligned}$$

$$\begin{aligned} a_2 &= R_{11}^0 C_1 C_2 R_{22}^1 + R_{11}^0 C_1 C_3 R_{33}^1 + R_{11}^0 C_1 C_4 R_{44}^1 \\ &\quad + R_{22}^0 C_2 C_3 R_{33}^2 + R_{22}^0 C_2 C_4 R_{44}^2 + R_{33}^0 C_3 C_4 R_{44}^3 \end{aligned}$$

$$R_{22}^1 = \frac{1}{g_{m2}} = 2.6 \Omega.$$

$$R_{33}^1 = R_{bb2} + \frac{1}{g_{m2}} = 25 + 2.6 = 27.6 \Omega.$$

$$R_{44}^1 = (1 + g_m R_L) R_{bb} + R_L = 10.6 \times 26 + 25 = \underline{\underline{300.6 \Omega}}$$

$$\begin{aligned} R_{33}^2 &= \left(R_{bb} + \frac{R_0}{2} \right) \parallel \frac{1}{g_m} + R_{bb} = (51 \parallel 2.6) + 26 \\ &= 28 \Omega \end{aligned}$$

$$R_{44}^2 = R_{bb2} (1 + g_m R_L) + R_L = 300.6 \Omega$$

$$R_{44}^3 = R_{bb} + R_L = 51 \Omega$$

$$a_2 = 7.968 \times 10^{-22} \text{ sec}^2.$$

$$A(s) = \frac{-9.6}{1 + 1.17 \times 10^{-11} s + 7.968 \times 10^{-22} s^2}$$

$$\omega_n = 35.4 \times 10^9 \text{ rad/s} ; \quad \xi = 0.2 \quad \omega_d = \omega_n \sqrt{1 - \xi^2}$$

$$s = -\xi \omega_n \pm j \omega_d$$