
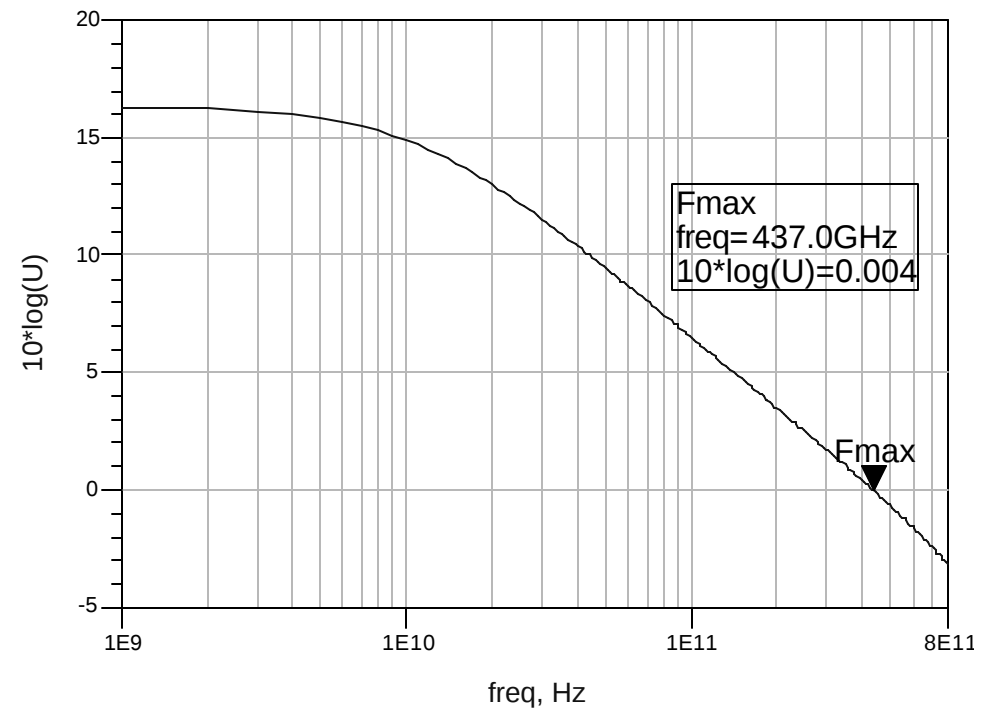



Homework 2: Simulations for problem 2

Ft and Fmax for hbt_gen5

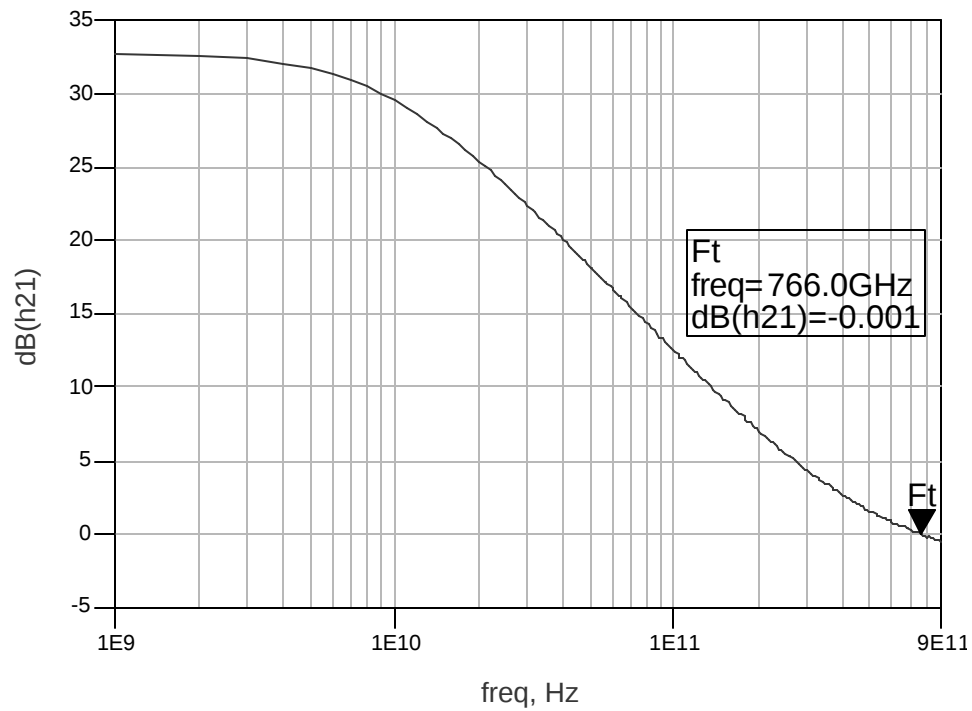





Home work 2: Simulations for problem 3

Differential Amplifier: Schematic

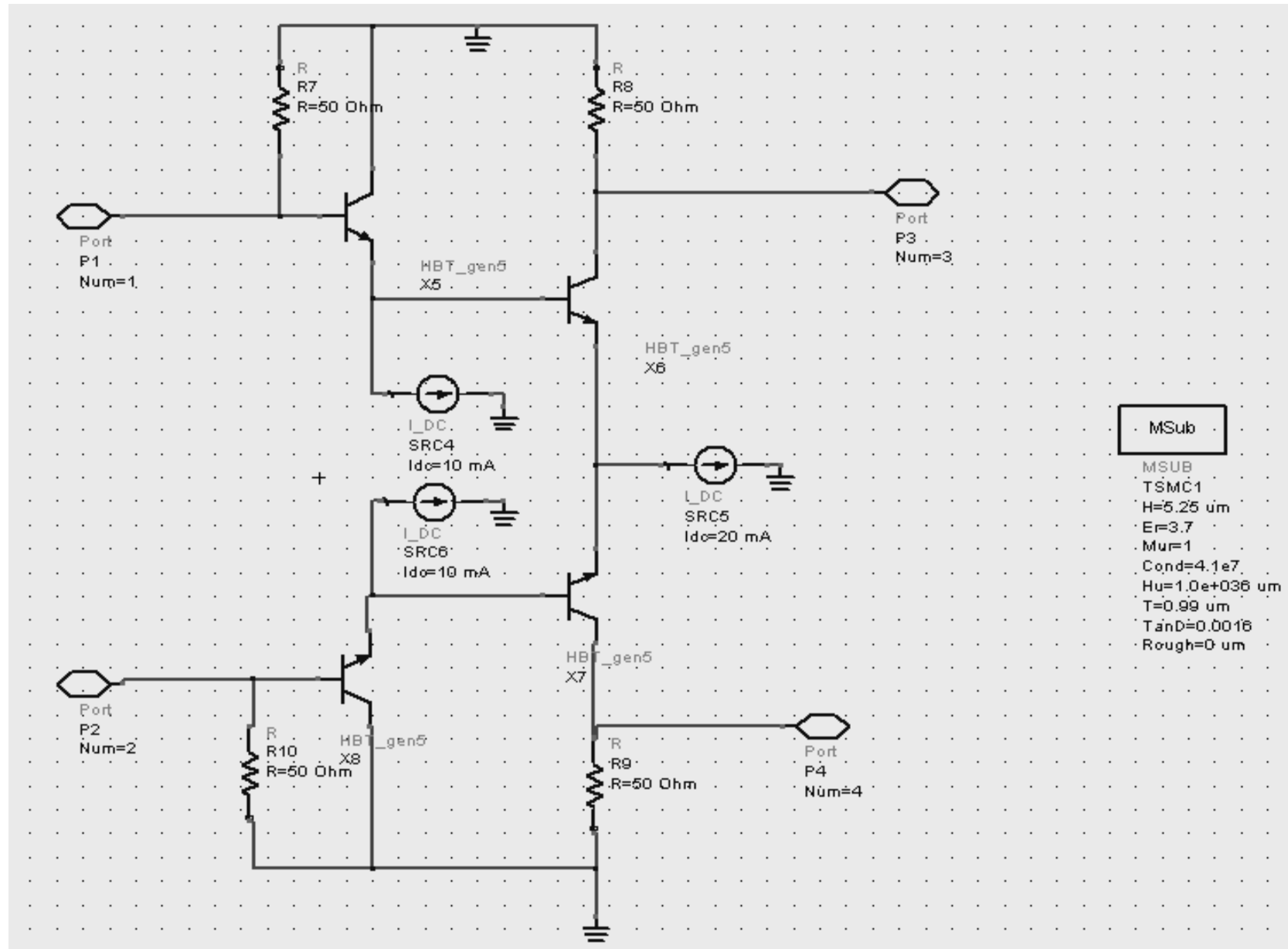

Homework 2: Simulations for problem 3

S Parameters for Differential Amplifier

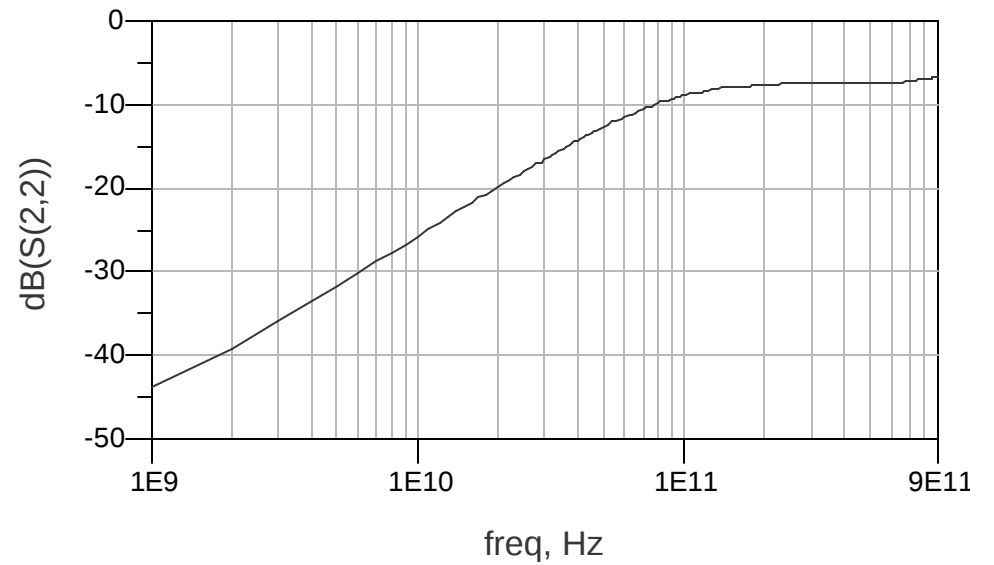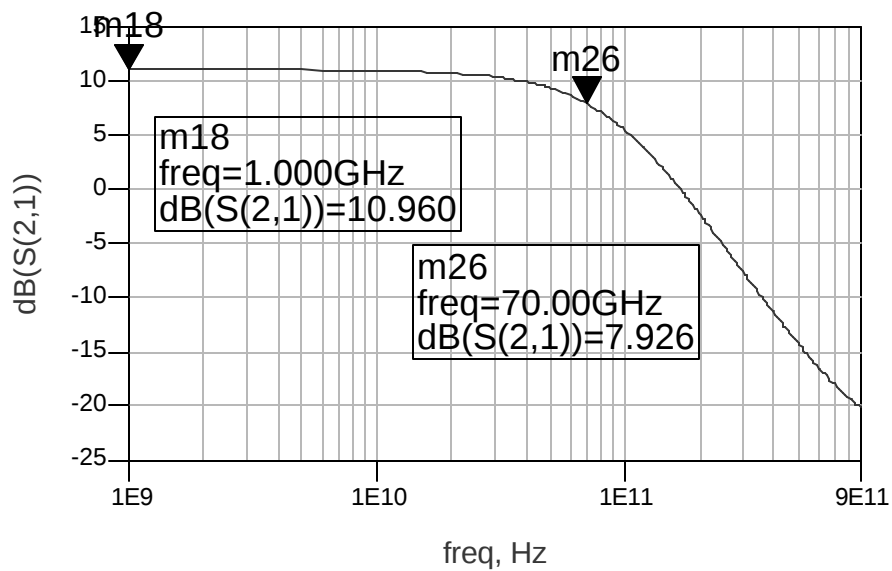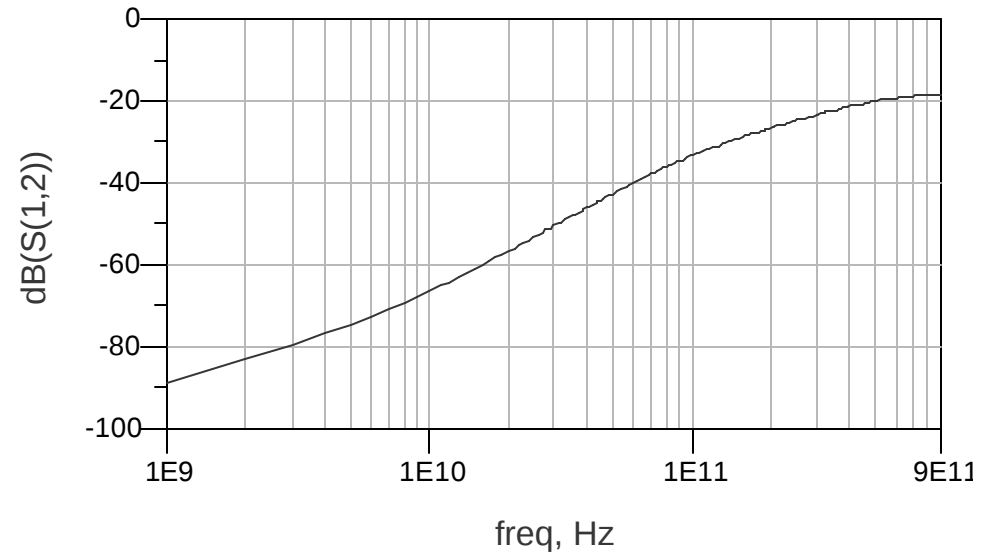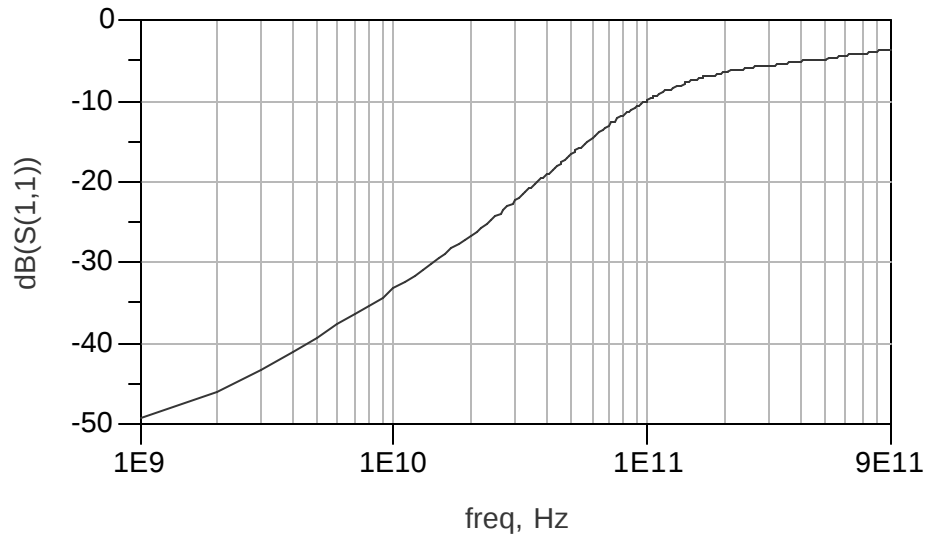

Homework 2: Simulations for Problem 4

Transient Analysis for Differential Amplifier

