

esis

inational circuit. Let
ally, we will design

electronic newspaper

that kind of a price
n!!)

extra money.

d one dime, three
the acceptor does not

approach.

he digital circuit. The
gnal and stays up for

total amount inserted
exactly one clock

assume synchronous

state machine.

time $x10 = 2'b10$.

5 cents

The bubble diagram for the finite state machine is shown in Figure 14-10. Each arc in the FSM is labeled with a label $\langle \text{input} \rangle / \langle \text{output} \rangle$ where input is 2-bit and output is 1-bit. For example, $x5/0$ means transition to the state pointed to by the arc, when input is $x5$ ($2'b01$), and set the output to 0.

State	Money
S0	0 cents
S5	5 cents
S10	10 cents
S15	15 cents

Input	coin[1:0]
$x0$	$2'b00$
$x5$	$2'b01$
$x10$	$2'b10$
-	don't care

 


Figure 14-10 Finite State Machine for Newspaper Vending Machine

14.7.4 Verilog Description

The Verilog RTL description for the finite state machine is shown in Example 14-6.

Example 14-6 RTL Description for Newspaper Vending Machine FSM

```

//Design the newspaper vending machine coin acceptor
//using a FSM approach
module vend( coin, clock, reset, newspaper);

//Input output port declarations
input [1:0] coin;
input clock;
input reset;
output newspaper;
wire newspaper;

//internal FSM state declarations
wire [1:0] NEXT_STATE;

```

Example 14-6 RTL Description for Newspaper Vending Machine FSM (Continued)

```

reg [1:0] PRES_STATE;

//state encodings
parameter s0 = 2'b00;
parameter s5 = 2'b01;
parameter s10 = 2'b10;
parameter s15 = 2'b11;

//Combinational logic
function [2:0] fsm;
input [1:0] fsm_coin;
input [1:0] fsm_PRES_STATE;

reg fsm_newspaper;
reg [1:0] fsm_NEXT_STATE;

begin
case (fsm_PRES_STATE)
s0: //state = s0
begin
if (fsm_coin == 2'b10)
begin
fsm_newspaper = 1'b0;
fsm_NEXT_STATE = s10;
end
else if (fsm_coin == 2'b01)
begin
fsm_newspaper = 1'b0;
fsm_NEXT_STATE = s5;
end
else
begin
fsm_newspaper = 1'b0;
fsm_NEXT_STATE = s0;
end
end
end

s5: //state = s5
begin
if (fsm_coin == 2'b10)
begin
fsm_newspaper = 1'b0;
fsm_NEXT_STATE = s15;

```

Example 14-6 RTL Description for Newspaper Vending Machine FSM (Continued)

```

end
else if (fsm_coin == 2'b01)
begin
fsm_newspaper = 1'b0;
fsm_NEXT_STATE = s5;
end
else
begin
fsm_newspaper = 1'b0;
fsm_NEXT_STATE = s0;
end
end

s10: //state = s10
begin
if (fsm_coin == 2'b10)
begin
fsm_newspaper = 1'b0;
fsm_NEXT_STATE = s10;
end
else if (fsm_coin == 2'b01)
begin
fsm_newspaper = 1'b0;
fsm_NEXT_STATE = s10;
end
else
begin
fsm_newspaper = 1'b0;
fsm_NEXT_STATE = s10;
end
end

s15: //state = s15
begin
fsm_newspaper = 1'b0;
fsm_NEXT_STATE = s15;
end
endcase
fsm = {fsm_newspaper, fsm_NEXT_STATE};
end
endfunction

//Reevaluate combinational logic
//is put or the pre-assign {fsm_newspaper, fsm_NEXT_STATE};
end

```

4 (Continued)

Example 14-6 RTL Description for Newspaper Vending Machine FSM (Continued)

```

end
else if (fsm_coin == 2'b01)
begin
    fsm_newspaper = 1'b0;
    fsm_NEXT_STATE = s10;
end
else
begin
    fsm_newspaper = 1'b0;
    fsm_NEXT_STATE = s5;
end

s10: //state = s10
begin
    if (fsm_coin == 2'b10)
    begin
        fsm_newspaper = 1'b0;
        fsm_NEXT_STATE = s15;
    end
    else if (fsm_coin == 2'b01)
    begin
        fsm_newspaper = 1'b0;
        fsm_NEXT_STATE = s15;
    end
    else
    begin
        fsm_newspaper = 1'b0;
        fsm_NEXT_STATE = s10;
    end
end
s15: //state = s15
begin
    fsm_newspaper = 1'b1;
    fsm_NEXT_STATE = s0;
end
endcase
fsm = {fsm_newspaper, fsm_NEXT_STATE};
end
endfunction

//Reevaluate combinational logic each time a coin
//is put or the present state changes
assign {newspaper, NEXT_STATE} = fsm(coin, PRES_STATE);

```

Example 14-6 RTL Description for Newspaper Vending Machine FSM (Continued)

```
//clock the state flipflops.
//use synchronous reset
always @(posedge clock)
begin
    if (reset == 1'b1)
        PRES_STATE'<= s0;
    else
        PRES_STATE <= NEXT_STATE;
    end
endmodule
```

14.7.5 Technology Library

We defined abc_100 technology in Section 14.4.1, *RTL to Gates*. We will use abc_100 as the target technology library. abc_100 contains the following library cells:

```
//Library cells for abc_100 technology

VNAND//2-input nand gate
VAND//2-input and gate
VNOR//2-input nor gate
VOR//2-input or gate
VNOT//not gate
VBUF//buffer
NDFF//Negative edge triggered D flipflop
PDFF//Positive edge triggered D flipflop
```

14.7.6 Design Constraints

Timing critical is the only design constraint we used in this design. Typically, design constraints are more elaborate.

14.7.7 Logic Synthesis

We synthesize the RTL description by using the specified design constraints and technology library and obtain the optimized gate-level netlist.

14.7.8 Optimized G

We use logic synthesis to optimized gate-level netli

Example 14-7 Optim

```
module vend ( coin,
input [1:0] coin;
input clock, reset;
output newspaper;
    wire \PRES_STATE
        n303, n304
        n295, n296
    PDFF \PRES_STATE

    PDFF \PRES_STATE

    VOR U119 ( .in0(
    VAND U118 ( .in0
        .c
    VNAND U117 ( .in
    VNOR U116 ( .in0
    VNOR U115 ( .in0
    VNOT U128 ( .in(
    VAND U114 ( .in0
    VNOT U127 ( .in(
    VAND U113 ( .in0
    VNOT U126 ( .in(
    VNAND U112 ( .in
    VNAND U125 ( .in
    VNOR U111 ( .in0
    VNAND U124 ( .in
    VAND U110 ( .in0
    VNAND U123 ( .in
    VNAND U122 ( .in
    VNAND U121 ( .in
    VOR U120 ( .in0
endmodule
```

The schematic diagram