

University of California, Santa Barbara
Department of Electrical and Computer Engineering

Homework #5

(Due by 5:00PM on 02/14/03)

Note: Place your homework in the homework-box for ECE 152A located on the fifth floor of Eng. I

1. (a) Find a minimum multiple-output two-level NAND-NAND network to realize
 $f_1 = \Sigma m(3,6,7,11,13,14,15)$ and $f_2 = \Sigma m(3,4,6,11,12,13,14)$. **(20 points)**
 (b) Repeat for a minimum two-level NOR-NOR network.

2. A combinational circuit is specified by the following three Boolean functions:

$$F_1(A, B, C) = \Sigma m(1,5,7)$$

(10 points)

$$F_2(A, B, C) = \Sigma m(2,3,6)$$

$$F_3(A, B, C) = \Sigma m(0,4,7)$$

Implement the circuit with a decoder constructed with NAND gates and external NAND gates.

3. Realize the function of **(20 points)**

$$F(a, b, c, d, e) = \Sigma m(0,1,2,6,7,9,10,15,16,18,20,21,27,30) + \Sigma d(3,4,11,12,19)$$

- (a) Using a 16-to-1 MUX with control inputs a , b , c , and d
- (b) Using an 8-to-1 MUX with control inputs a , b , and c and added gates

4. (a) An adder for excess-3 coded decimal digits is to be designed using a ROM. The adder should add two excess-3 coded digits and give the excess-3 coded sum and a carry. For example, $1010 + 1001 = 0110$ with a carry of 1 ($7 + 6 = 13$). Draw a block diagram showing the required ROM inputs and outputs. What size ROM is required? Indicate how the truth table for the ROM would be specified by giving some typical rows. **(10 points)**
 (b) If the same adder were implemented using a PLA, what size PLA would be required? (Assume that only the 10 legal excess-3 coded digits can occur as inputs.)

5. Braille is a system which allows a blind person to “read” alphanumeric by feeling a pattern of raised dots. Design a network that converts BCD to Braille. The table shows the correspondence between BCD and Braille. **(20 points)**

A	B	C	D		
				W Z	X Y
0	0	0	0		•
0	0	0	1	•	
0	0	1	0	•	
0	0	1	1	•	•
0	1	0	0	•	•
0	1	0	1	•	
0	1	1	0	•	•
0	1	1	1	•	•
1	0	0	0	•	•
1	0	0	1	•	

- (a) Use a multiple-output NAND-gate network and draw the diagram.
- (b) Use a PAL. Specify the PAL type and fuse pattern
6. A binary-coded-decimal priority encoder has nine inputs ($X_1, X_2, \dots, X_9$) and four outputs (A, B, C, D). If only the X_i input is 1, the output $ABCD$ represent a binary number equal to i . For example, if $X_1 = 1$, then $ABCD = 0001$, and if $X_9 = 1$, $ABCD = 1001$. If two or more of the X_i 's are 1, then the largest value of i takes priority. For example, if $X_1 = X_2 = X_5 = X_8 = 1$ (and the other inputs are 0), then $ABCD = 1000$. If all inputs are 0, then $ABCD = 0000$. **(20 points)**
- (a) Derive a PLA table and draw AND-OR array for the priority encoder (10 rows).
- (b) By inspection of the table, find product-of-sums expressions for A, B, C , and D .