

University of California, Santa Barbara
Department of Electrical and Computer Engineering

Homework #6

(Due by 5:00PM on 03/10/03)

Note: Place your homework in the homework-box for ECE 152A located on the fifth floor of Eng. I

1. Using the Fig. 1, trace the signals through the master-slave J-K flip-flop when the following input sequence is applied. Draw the timing diagram. **(10 points)**


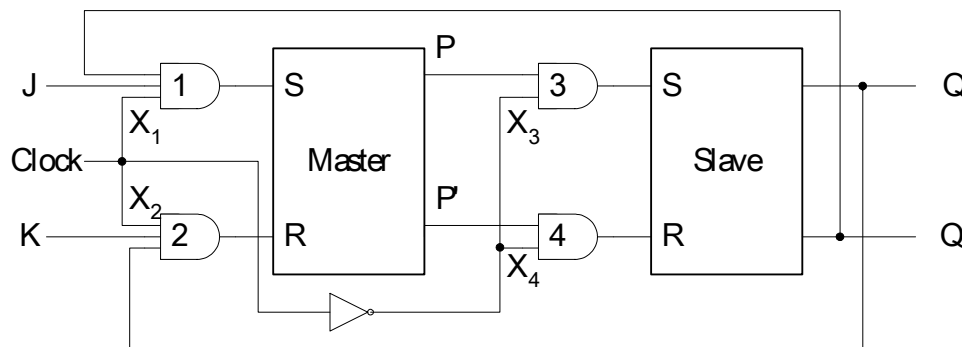


Fig. 1

- (a) Starting with $J = K = P = Q = 0$. JK change to 10, clock pulse, JK change to 01, clock pulse, JK change to 11, clock pulse.
- (b) Starting with $J = K = \text{clock} = P = Q = 0$. Input sequence: $J = 1, K = 1, \text{clock} = 1, J = 0, K = 0, \text{clock} = 0, K = 1, \text{clock} = 1, \text{clock} = 0$.
2. Draw the logic diagram for the following requests. **(20 points)**
- (a) Convert a clocked T flip-flop to a clocked J-K flip-flop by adding external gates.
- (b) Convert a clocked D flip-flop to a clocked T flip-flop by adding external gates.
3. Design a 3-bit counter which counts in the sequence: **(20 points)**
- 001, 100, 101, 111, 110, 010, 011, 001,
- (a) Use clocked D flip-flops
- (b) Use clocked T flip-flops
- (c) What will happen if the counter of (a) is started in state 000?

4. If the cyclic shift register of Fig. 3 is changed so that D is connected to the K input of flip-flop A and D' is connected to J, determine the sequence of register states.

(20 points)

 

- Draw a complete state graph showing all states.
 - Derive a complete state table showing all states.
 - What is the sequence of states starting with ABCD = 0000?
5. A sequential circuit with two D flip-flops A and B, two inputs X and Y, and one output Z is specified by the following input equations: **(30 points)**

$$D_A = \bar{X}Y + XA, \quad D_B = \bar{X}B + XA, \quad Z = B$$

- Draw the logic diagram of the circuit.
- Derive the state table.
- Derive the state diagram (Use the Mealy machine).